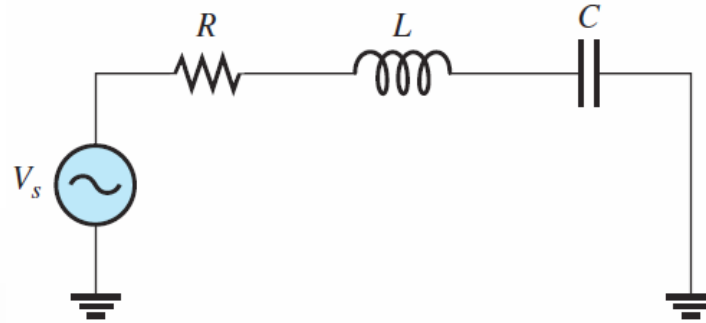


# Chapter 14: RLC Circuits and Resonance

**Instructor:** Jean-François MILLITHALER

[http://faculty.uml.edu/JeanFrancois\\_Millithaler/FunElec/Spring2017](http://faculty.uml.edu/JeanFrancois_Millithaler/FunElec/Spring2017)

# IMPEDANCE AND PHASE ANGLE OF SERIES RLC CIRCUITS



$$Z_{\text{tot}} = Z_R + Z_L + Z_C$$

$$Z_{\text{tot}} = R + j\omega L + \frac{1}{j\omega C}$$

$$Z_{\text{tot}} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$|Z_{\text{tot}}| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\theta = \tan^{-1}\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right)$$

$$X_L = 2\pi fL$$

$$X_C = \frac{1}{2\pi fC}$$


$$X_{\text{tot}} = |X_L - X_C|$$

$$Z_{\text{tot}} = \sqrt{R^2 + X_{\text{tot}}^2}$$

$$\theta = \tan^{-1}\left(\frac{X_{\text{tot}}}{R}\right)$$

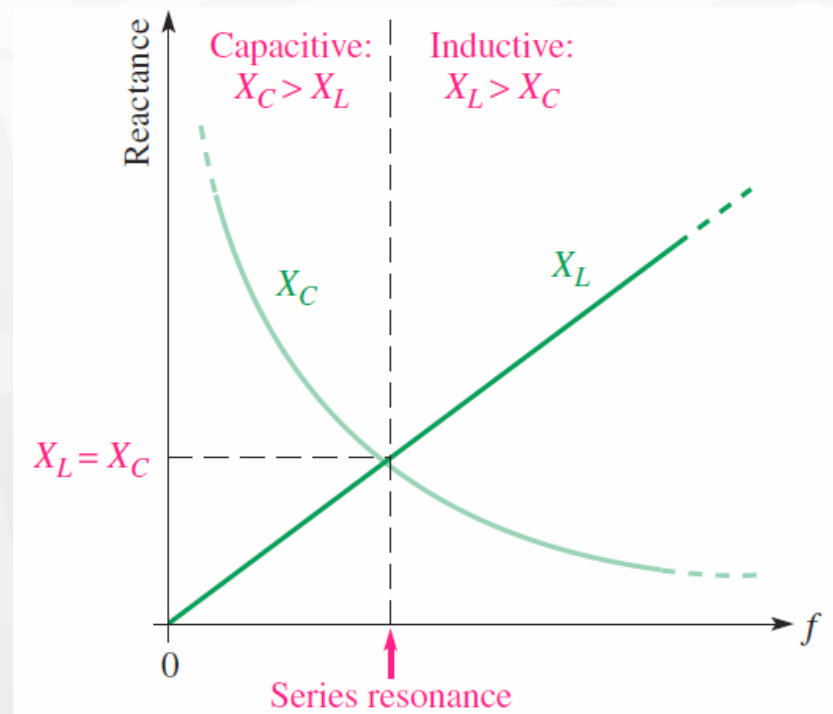
# Variation of $X_L$ and $X_C$ with frequency

- ▶ In a series  $RLC$  circuit, the circuit can be capacitive or inductive, depending on the frequency.
- ▶ At the frequency where  $X_C = X_L$ , the circuit is at series resonance.
- ▶ Below the resonant frequency, the circuit is predominantly **capacitive**.
- ▶ Above the resonant frequency, the circuit is predominantly **inductive**.


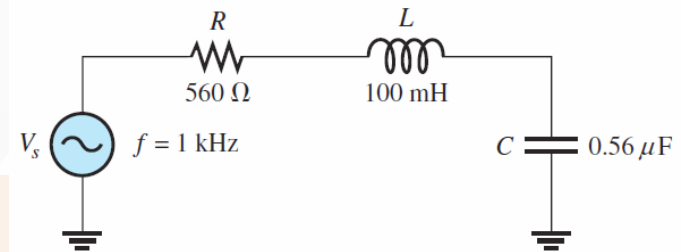
# Exercise

Determine the total impedance and the phase angle for the series *RLC* circuit



First, find  $X_C$  and  $X_L$ .

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(1 \text{ kHz})(0.56 \mu\text{F})} = 284 \Omega$$

$$X_L = 2\pi f L = 2\pi(1 \text{ kHz})(100 \text{ mH}) = 628 \Omega$$

In this case,  $X_L$  is greater than  $X_C$ , so the circuit is more inductive than capacitive. The magnitude of the total reactance is

$$X_{tot} = |X_L - X_C| = |628 \Omega - 284 \Omega| = 344 \Omega \quad (\text{inductive})$$

The total circuit impedance is

$$Z_{tot} = \sqrt{R^2 + X_{tot}^2} = \sqrt{(560 \Omega)^2 + (344 \Omega)^2} = 657 \Omega$$

The phase angle (between  $I$  and  $V_s$ ) is

$$\theta = \tan^{-1}\left(\frac{X_{tot}}{R}\right) = \tan^{-1}\left(\frac{344 \Omega}{560 \Omega}\right) = 31.6^\circ \quad (\text{current lagging } V_s)$$

# Example

At  $f = 1$  kHz, highly capacitive


$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(1 \text{ kHz})(0.022 \mu\text{F})} = 7.23 \text{ k}\Omega$$

$$X_L = 2\pi f L = 2\pi(1 \text{ kHz})(100 \text{ mH}) = 628 \Omega$$

$$X_{tot} = |X_L - X_C| = |628 \Omega - 7.23 \text{ k}\Omega| = 6.6 \text{ k}\Omega$$

$$Z = \sqrt{R^2 + X_{tot}^2} = \sqrt{(3.3 \text{ k}\Omega)^2 + (6.6 \text{ k}\Omega)^2} = 7.38 \text{ k}\Omega$$
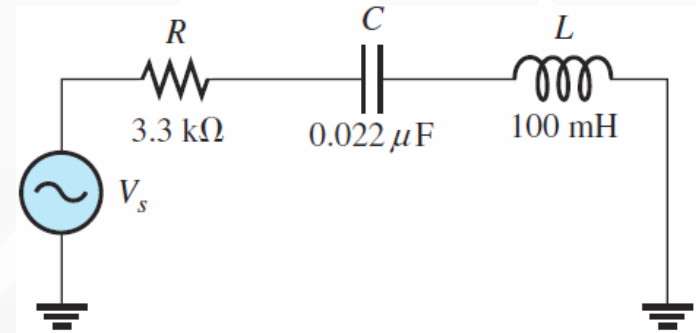
$$\theta = \tan^{-1}\left(\frac{X_{tot}}{R}\right) = \tan^{-1}\left(\frac{6.60 \text{ k}\Omega}{3.3 \text{ k}\Omega}\right) = 63.4^\circ$$



At  $f = 3.5$  kHz,

purely resistive but is slightly inductive

$$X_C = \frac{1}{2\pi(3.5 \text{ kHz})(0.022 \mu\text{F})} = 2.07 \text{ k}\Omega$$

$$X_L = 2\pi(3.5 \text{ kHz})(100 \text{ mH}) = 2.20 \text{ k}\Omega$$

$$X_{tot} = |2.20 \text{ k}\Omega - 2.07 \text{ k}\Omega| = 130 \Omega$$

$$Z = \sqrt{(3.3 \text{ k}\Omega)^2 + (130 \Omega)^2} = 3.30 \text{ k}\Omega$$

$$\theta = \tan^{-1}\left(\frac{130 \Omega}{3.3 \text{ k}\Omega}\right) = 2.26^\circ$$

At  $f = 5$  kHz,

predominantly inductive

$$X_C = \frac{1}{2\pi(5 \text{ kHz})(0.022 \mu\text{F})} = 1.45 \text{ k}\Omega$$

$$X_L = 2\pi(5 \text{ kHz})(100 \text{ mH}) = 3.14 \text{ k}\Omega$$

$$X_{tot} = |3.14 \text{ k}\Omega - 1.45 \text{ k}\Omega| = 1.69 \text{ k}\Omega$$


$$Z = \sqrt{(3.3 \text{ k}\Omega)^2 + (1.69 \text{ k}\Omega)^2} = 3.71 \text{ k}\Omega$$

$$\theta = \tan^{-1}\left(\frac{1.69 \text{ k}\Omega}{3.3 \text{ k}\Omega}\right) = 27.1^\circ$$
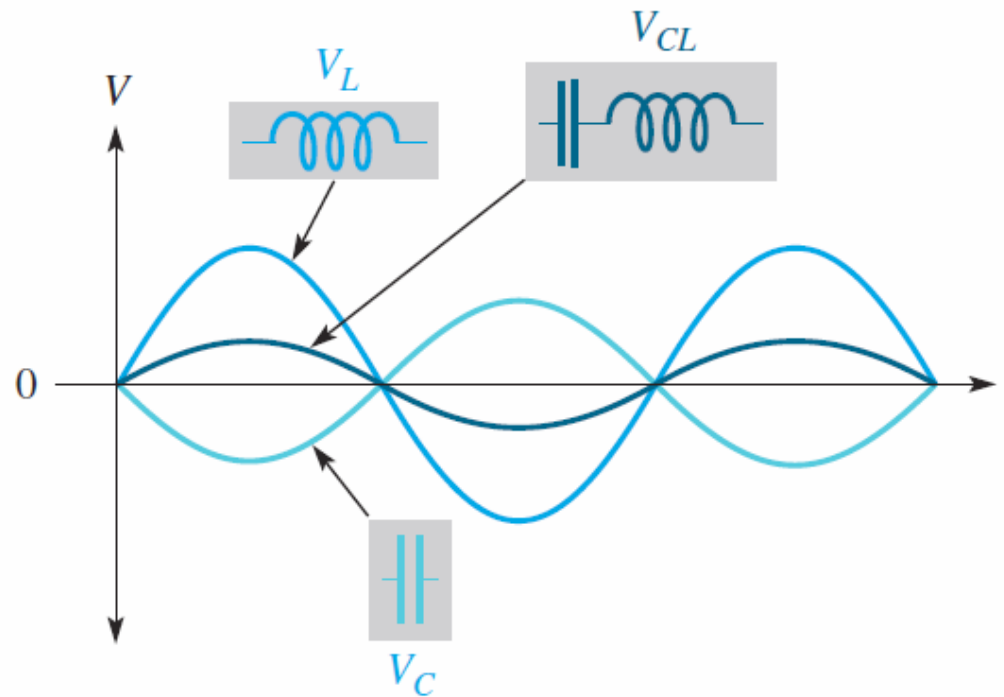
# Voltages in a series *RLC* circuits


The voltages across the *RLC* components must add to the source voltage in accordance with KVL. Because of the opposite phase shift due to *L* and *C*,  $V_L$  and  $V_C$  effectively subtract.

Notice that  $V_C$  is out of phase with  $V_L$ . When they are algebraically added, the result is...



# Exercice

Find the voltage across each component

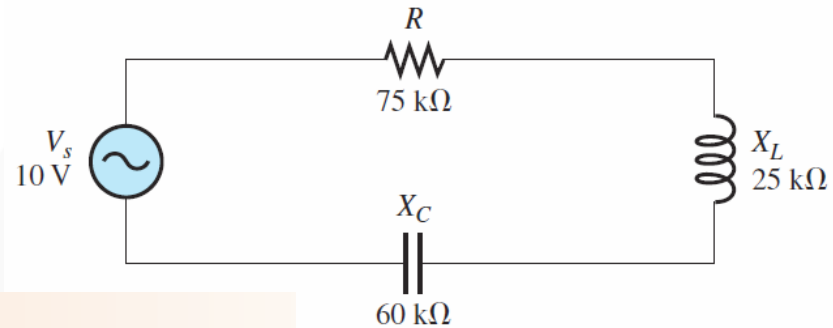

First, find the total reactance.

$$X_{tot} = |X_L - X_C| = |25 \text{ k}\Omega - 60 \text{ k}\Omega| = 35 \text{ k}\Omega$$

The total impedance is

$$Z_{tot} = \sqrt{R^2 + X_{tot}^2} = \sqrt{(75 \text{ k}\Omega)^2 + (35 \text{ k}\Omega)^2} = 82.8 \text{ k}\Omega$$

Apply Ohm's law to find the current.

$$I = \frac{V_s}{Z_{tot}} = \frac{10 \text{ V}}{82.8 \text{ k}\Omega} = 121 \mu\text{A}$$

Now, apply Ohm's law to find the voltages across  $R$ ,  $L$ , and  $C$ .

$$V_R = IR = (121 \mu\text{A})(75 \text{ k}\Omega) = \mathbf{9.08 \text{ V}}$$

$$V_L = IX_L = (121 \mu\text{A})(25 \text{ k}\Omega) = \mathbf{3.03 \text{ V}}$$


$$V_C = IX_C = (121 \mu\text{A})(60 \text{ k}\Omega) = \mathbf{7.26 \text{ V}}$$

# Series Resonance

- ▶ At series resonance,  $X_C$  and  $X_L$  cancel.  $V_C$  and  $V_L$  also cancel because the voltages are equal and opposite. The circuit is purely resistive at resonance.

$$X_L = X_C$$




$$Z_r = R$$

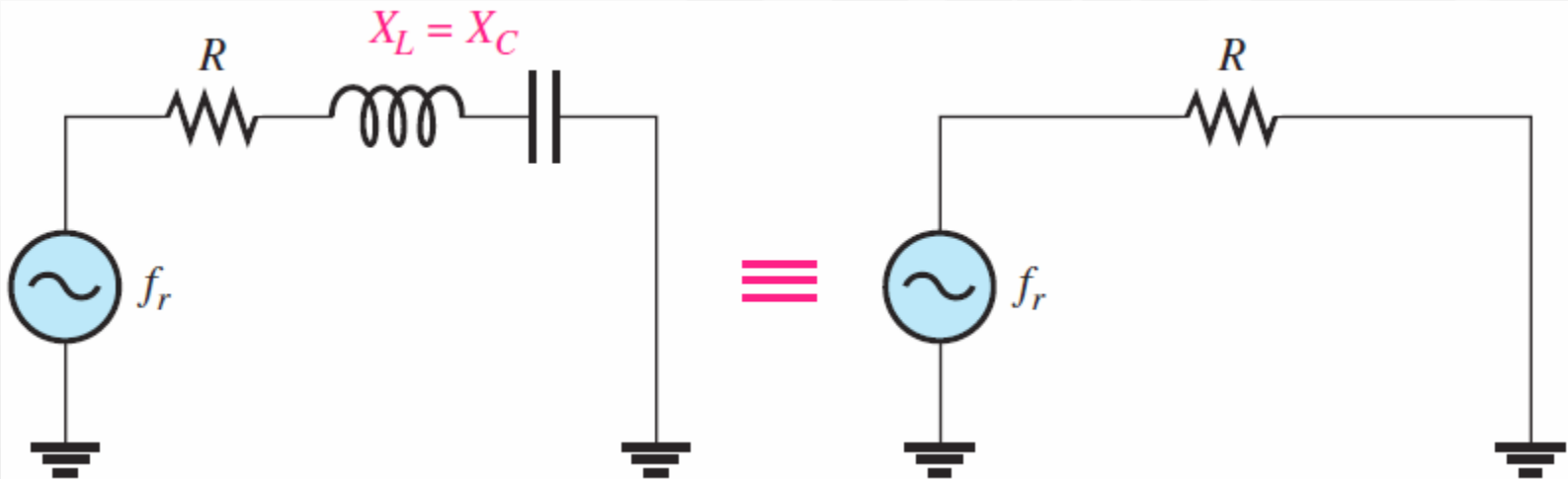


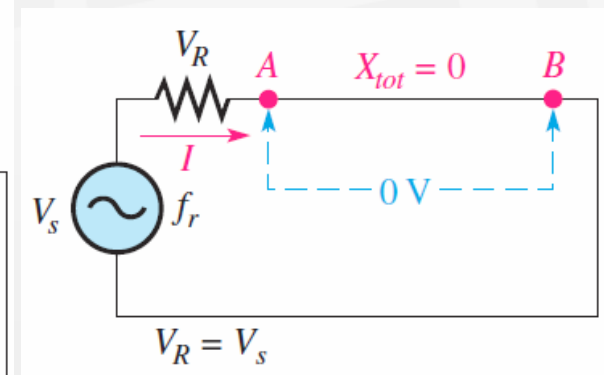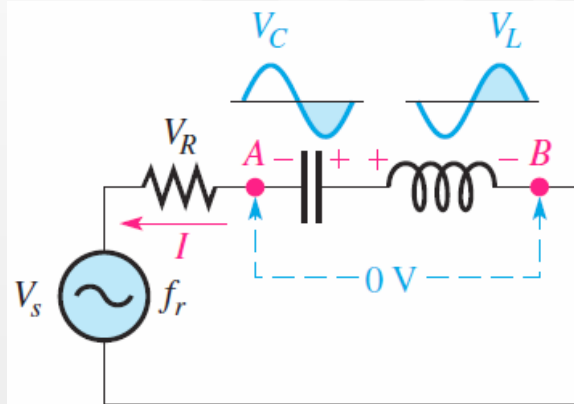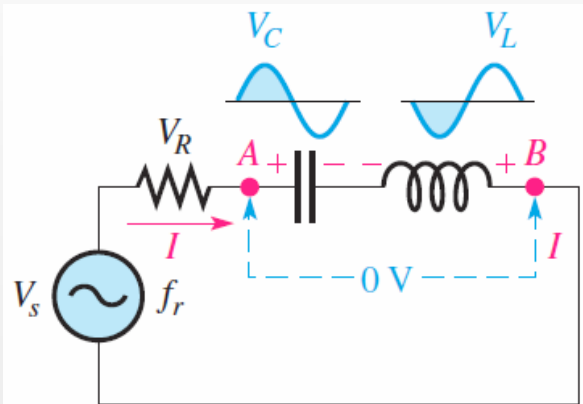
# Series Resonance

- ▶ At the resonant frequency,  $f_r$ , the voltages across  $C$  and  $L$  are equal in magnitude.
- ▶ Since they are  $180^\circ$  out of phase with each other, they cancel, leaving  $0\text{ V}$  across the  $CL$  combination (point  $A$  to point  $B$ ).
- ▶ The section of the circuit from  $A$  to  $B$  effectively looks like a short at resonance (neglecting winding resistance).



# Series Resonance

- ▶ For a given series  $RLC$  circuit, resonance occurs at only one specific frequency. A formula for this resonant frequency is developed as follows:

$$X_L = X_C$$


- ▶ Substitute the reactance formulas, and solve for the resonant frequency,  $f_r$

$$\begin{aligned}2\pi f_r L &= \frac{1}{2\pi f_r C} \\(2\pi f_r L)(2\pi f_r C) &= 4\pi^2 f_r^2 LC = 1 \\f_r^2 &= \frac{1}{4\pi^2 LC}\end{aligned}$$

- ▶ Take the square root of both sides. The formula for resonant frequency is

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

# Exercise

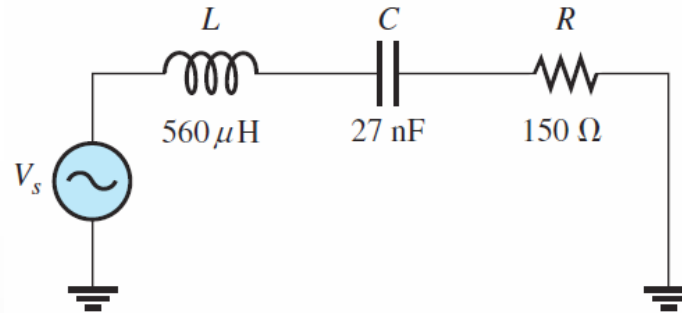


Find the series resonant frequency for the circuit


The resonant frequency is

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(560 \mu\text{H})(27 \text{ nF})}} = \mathbf{40.9 \text{ kHz}}$$


# Frequency Response

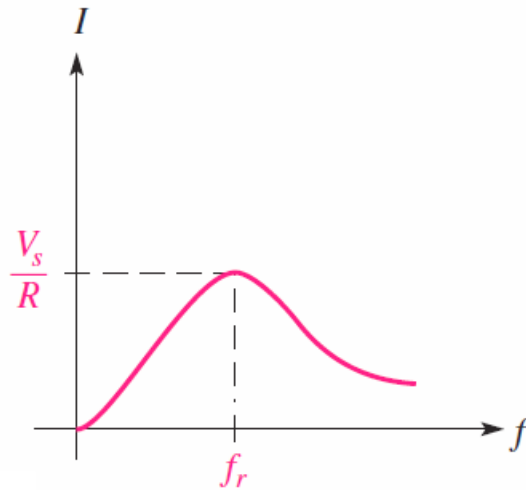


Current

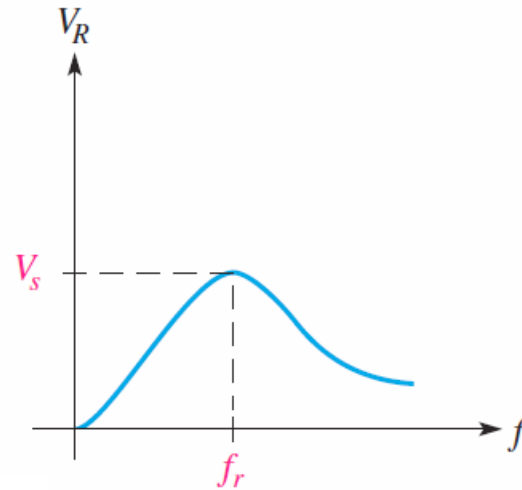


Resistor voltage

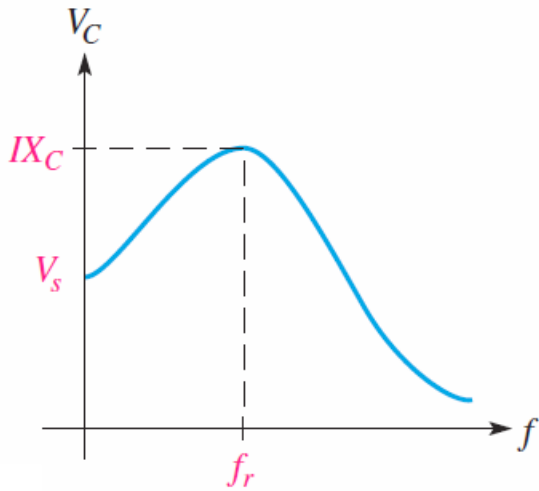

Capacitor voltage

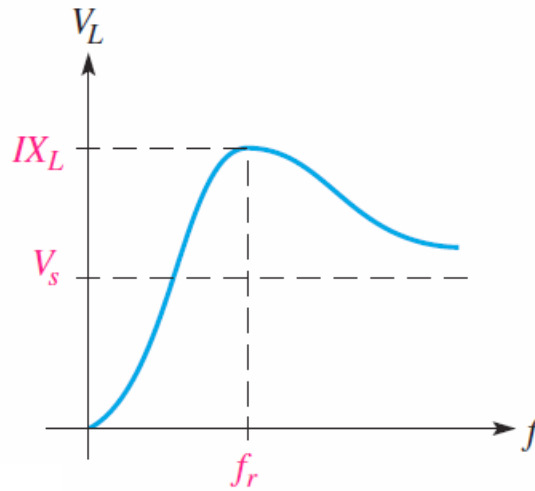


Inductor voltage

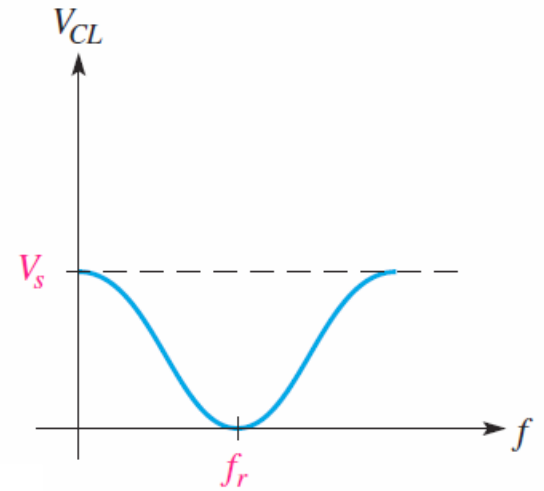

Voltage across C and L combined
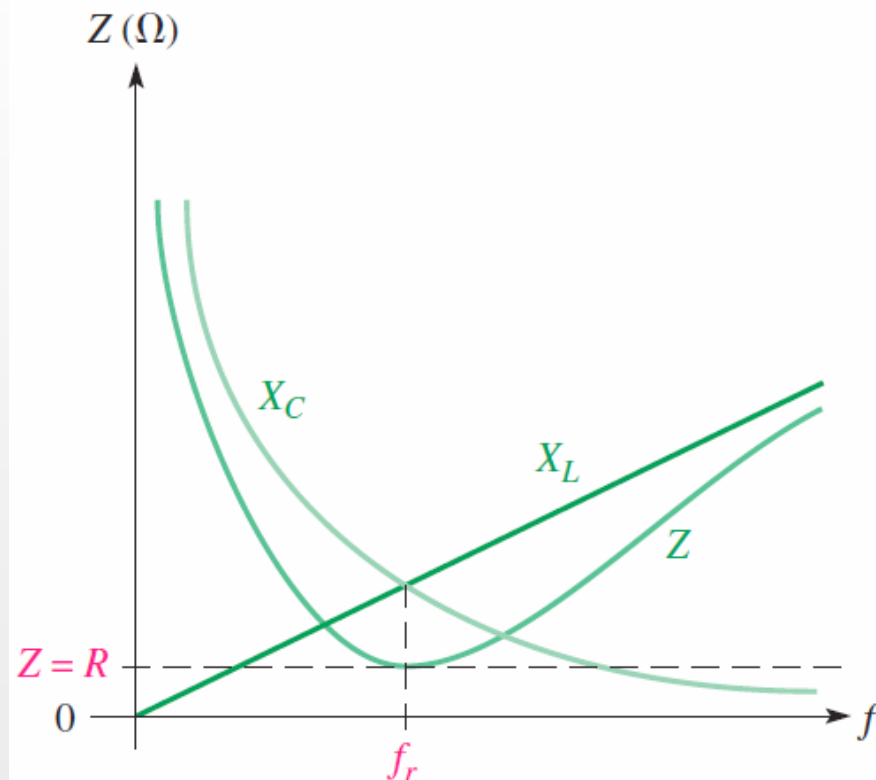
# Impedance of series *RLC* circuits

- ▶ The general shape of the impedance versus frequency for a series *RLC* circuit is superimposed on the curves for  $X_L$  and  $X_C$ . Notice that at the resonant frequency, the circuit is resistive, and  $Z = R$



# Series Resonance

## Summary

- ▶ Summary of important concepts for series resonance:
  - Capacitive and inductive reactances are equal.
  - Total impedance is a minimum and is resistive.
  - The current is maximum.
  - The phase angle between  $V_s$  and  $I_s$  is zero.
  - $f_r$  is given by  $f_r = \frac{1}{2\pi\sqrt{LC}}$