

Fundamentals of Electricity


Fall 2016

Assignment #7

You have to provide the **detailed solution** for each problem
AND fill the **answer table** on last page

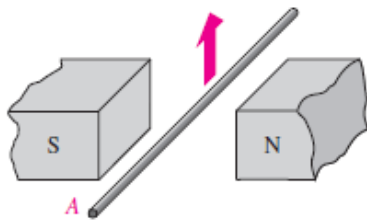Problem 1:

A 20 cm long conductor is moving upward between the poles of a magnet as shown in the following Figure. The pole faces are 8.5 cm^2 on each side and the flux is 1.24 mWb . The motion produces an induced voltage across the conductor of 44 mV . What is the speed of the conductor?



When a conductor is moved in a magnetic field, the induced voltage is given by the formula,

$$v_{\text{ind}} = B_{\perp} l v$$

Where,

$B_{\perp}$ is the magnetic flux density that is perpendicular to the moving conductor in teslas, and v is the velocity or speed of the conductor in m/s.

The flux density is given by,

$$\begin{aligned} B_{\perp} &= \frac{\phi}{A} \\ &= \frac{1.24 \times 10^{-3} \text{ Wb}}{(8.5 \times 10^{-2} \text{ m}^2)^2} \\ &= 0.172 \text{ Wb/m}^2 \text{ or tesla} \end{aligned}$$

Although the conductor is 20 cm long, only 8.5 cm is in the magnetic field. Thus the value of $l = 8.5$ cm .

By substituting the known values in the induced voltage formula, we obtain the following:

$$(44 \times 10^{-3} \text{ V}) = (0.172)(8.5 \times 10^{-2} \text{ m})v$$

$$v = \frac{44 \times 10^{-3} \text{ V}}{(0.172)(8.5 \times 10^{-2} \text{ m})}$$


$$v = 3.01 \text{ m/s}$$

Thus the speed of the conductor is,

$$\boxed{v = 3.01 \text{ m/s}}$$

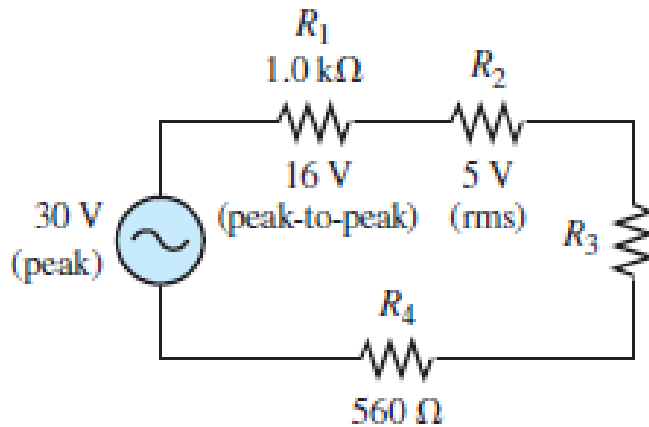Problem 2:

Determine the rms voltage across R_3 in the following figure.



We can find the rms current going through the loop by finding the current through one of the resistors since it is a series circuit. So by applying Ohm's Law on R_1 ,

$$\begin{aligned} I &= \frac{V_1}{R_1} \\ &= \frac{5.66 \text{ V}}{1.0 \text{ k}\Omega} \\ I &= 5.66 \text{ mA} \end{aligned}$$

Again by applying Ohm's Law on R_4 , we get

$$\begin{aligned} V_4 &= IR_4 \\ &= (5.66 \text{ mA})(560 \Omega) \\ V_4 &= 3.17 \text{ V} \end{aligned}$$

By applying Kirchhoff's voltage law to the above circuit, we get


$$\begin{aligned} V_3 &= V_s - V_1 - V_2 - V_4 \\ &= 21.21 \text{ V} - 5.66 \text{ V} - 5 \text{ V} - 3.17 \text{ V} \\ V_3 &= 7.38 \text{ V} \end{aligned}$$

Therefore rms voltage across R_3 is given by

$$\boxed{V_3 = 7.38 \text{ V}}$$

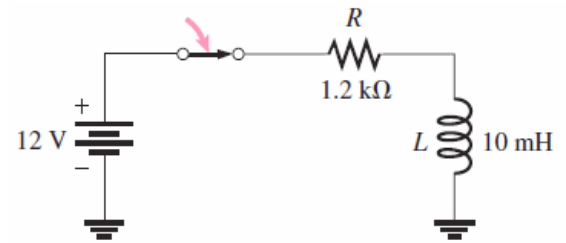Problem 3:

From this figure and given the following general formula $i = I_F + (I_i - I_F)e^{-\frac{t}{\tau}}$, define I_i , I_F , τ , and i at $20 \mu s$.



$$I_i = 0 A \quad (\tau = 0 s)$$

$$I_F = \frac{V_s}{R} \quad (\tau = \infty) \rightarrow \text{the inductance is considered as a conducting wire, no resistance} \\ \rightarrow \text{then Ohm's Law.}$$

$$I_F = \frac{12}{1,2 \cdot 10^3} = 0,01 = \underline{10 mA}$$

$$i(t) = I_F + (0 - I_F)e^{-\frac{t}{\tau}}$$

$$i(t) = I_F - I_F e^{-\frac{t}{\tau}} = I_F (1 - e^{-\frac{t}{\tau}})$$

$$\text{with } \tau = \frac{L}{R} = \frac{10 \cdot 10^{-3}}{1,2 \cdot 10^3} = 8,3 \cdot 10^{-6} s. = \underline{8,3 \mu s}$$


at $t = 20 \mu s$

$$i(20 \mu s) = 0,01 (1 - e^{-\frac{20}{8,3}}) = 0,08 = \underline{8 mA}$$

We have an increase of current over time with a maximum of I_F . $i(20 \mu s) < I_F$ is correct.

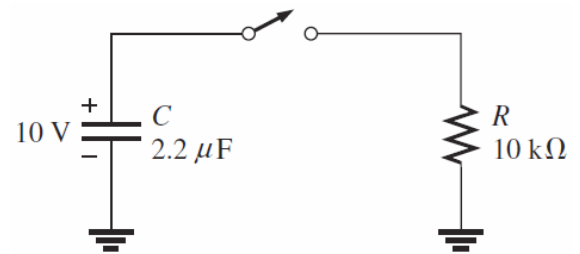Problem 4:

From this figure and given the following general formula $v = V_F + (V_i - V_F)e^{-\frac{t}{\tau}}$, define V_i , V_F , τ , and v at 45 ms.



$$V_I = 10V \quad (t=0s)$$

$$V_F = 0V \quad (t=\infty) \rightarrow \text{the capacitor is completely discharged.}$$

$$\tau = RC = 10 \cdot 10^3 \times 2.2 \cdot 10^{-6} = 22 \cdot 10^{-3} s = \underline{22ms}.$$

$$v(t) = 0 + (V_I - 0)e^{-\frac{t}{\tau}}$$
$$= V_I e^{-\frac{t}{\tau}}$$

$$v(45ms) = 10 e^{-\frac{45}{22}} = 1.3V$$

We have a discharge of the voltage from the capacitor.



with 0V at ∞ . $v(45ms) < V_I$ is correct.

$v(45ms) > V_F$ is correct.


Problem 5:

Using Thevenin's theorem, find the voltage across R_4

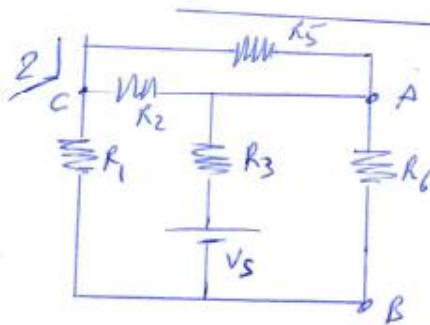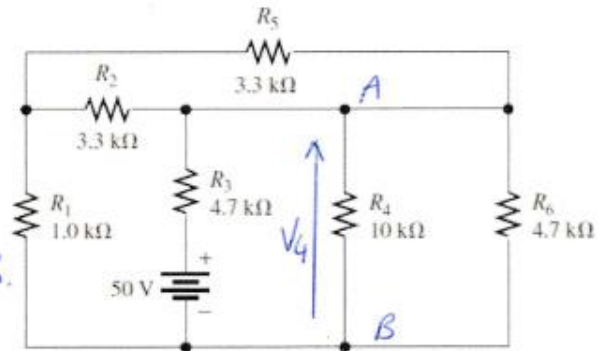
1. Removing R_4
2. Find the Voltage between A & B.
3. Find the Thevenin Resistance
4. Find V_4 .



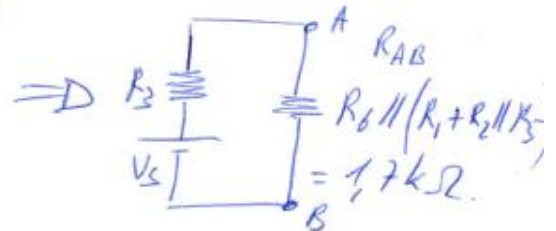R_5 is // to R_2 .
They share same nodes
Then they are in
Series with R_1
 $\Rightarrow$ all // to R_6 .



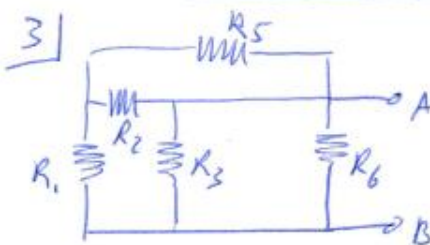
$$\Rightarrow V_{AB} = V_{TH} = \frac{R_{AB}}{R_3 + R_{AB}} \times V_s = \frac{1.7}{6.4} \times 50 = 13.3 \text{ V}$$



R_{TH} can be found when we shortcircuiting V_s

$$R_{TH} = R_6 // R_3 // [R_1 + R_2 // R_5]$$
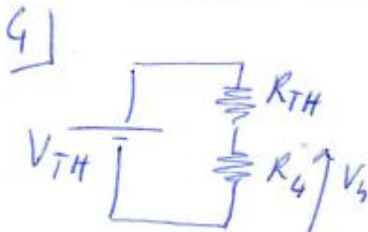
$$R_{TH} = 2.35 // 2.65 = 1.2455 \text{ k}\Omega$$



$$V_4 = \frac{R_4}{R_4 + R_{TH}} \times V_{TH} = \frac{10}{10 + 1.25} \times 13.3 \text{ V} = 11.8 \text{ V}$$

ANSWERS

Problem 1	<i>Speed</i>	3.01 m/s
Problem 2	V_{rms}	7.38 V
Problem 3	$I_i =$ $I_F =$ $\tau =$ $i(20\mu s) =$	0 A 10 mA 8.3 μs 9 mA
Problem 4	$V_i =$ $V_F =$ $\tau =$ $v(45ms) =$	10 V 0 V 22 ms 1.3 V
Problem 5	$V_4 =$	11.7 or 11.8 V