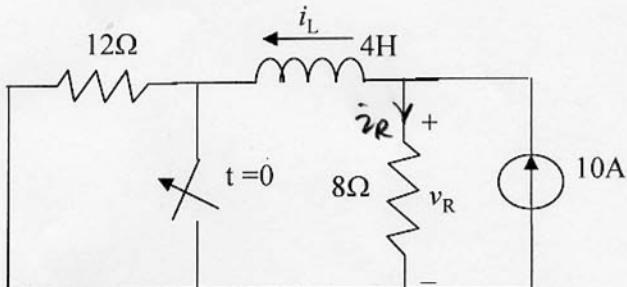


Name: _____


Circuit Theory I (16.201): Final Exam Practice B solution

Total 25 pts

1. (5) The switch in the circuit has been closed for a long time before opening at $t = 0$.
Find $i_L(t)$, and $v_R(t)$ for $t \geq 0$.




Before switch, $t < 0$

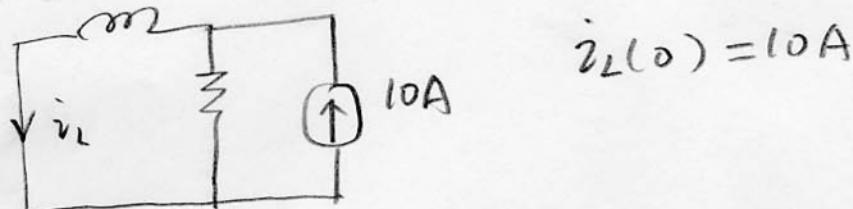

$$i_L(0) = 10A$$

After switch $t > 0$, By current division
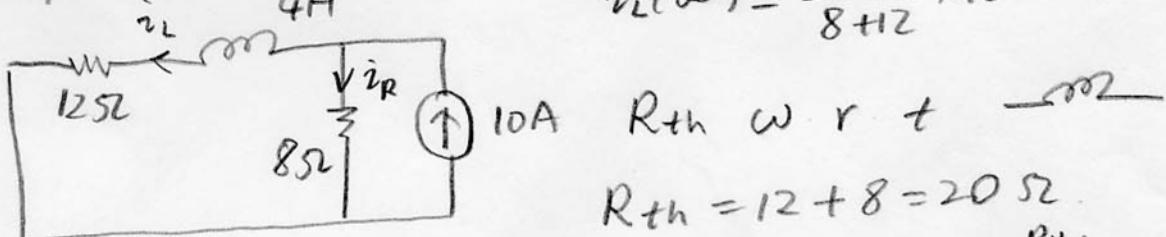
$$i_L(\infty) = \frac{8}{8+12} \times 10 = 4A$$



$$R_{th} = 12 + 8 = 20 \Omega$$


$$-\frac{R_{th}}{L}t$$

$$\begin{aligned} i_L(t) &= i_L(\infty) + (i_L(0) - i_L(\infty)) e^{-\frac{R_{th}}{L}t} \\ &= 4 + (10 - 4) e^{-\frac{20}{4}t} \\ &= 4 + 6 e^{-5t} A \end{aligned}$$


$$v_R(t) = 8i_R = 8(10 - i_L(t)) = 8(6 - 6e^{-5t})$$

$$v_R(t) = 48(1 - e^{-5t}) V$$

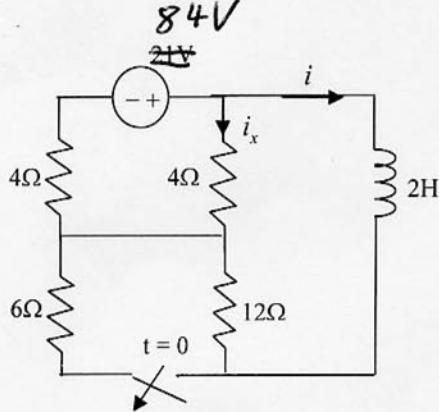2 (5pts) The switch has been closed for a long time before it is open at $t = 0$. Find $i(t)$ and $i_x(t)$ for $t \geq 0$.




For $t < 0$

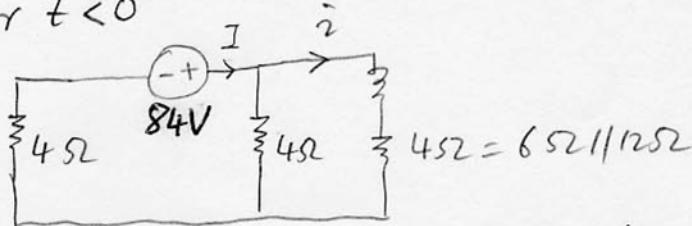

$$R_{eq} \text{ w.r.t } t \quad R_{eq} = 4 + 4/14 = 6.52$$

$$I = \frac{84}{6.52} = 14A, \quad \bar{i} = \frac{14}{2} = 7A, \quad \bar{i}(0) = 7A$$

For $t > 0$

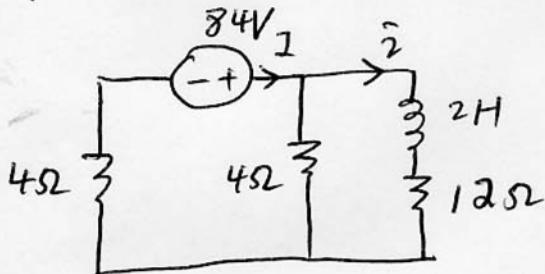


under DC condition

$$I = \frac{84}{4 + 4/12} = \frac{84}{7} = 12A$$

$$\bar{i}(\infty) = \frac{84}{4+12} \times 12 = \frac{4}{16} \times 12 = 3A$$

$$R_{th} \text{ w.r.t } -\infty \quad R_{th} = 12 + 4/14 = 14.52$$
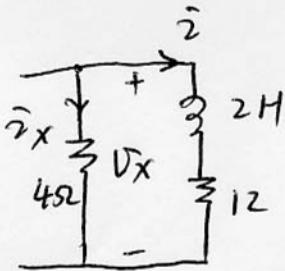
$$\bar{i}(t) = 3 + (7-3)e^{-\frac{14}{2}t} = 3 + 4e^{-7t} A$$




$$V_x = L \frac{di}{dt} + 12i$$

$$\bar{i}_x = \frac{V_x}{4} = \frac{2}{4} \frac{di}{dt} + \frac{12}{4} i$$


$$\bar{i}_x(t) = \frac{1}{2} \frac{di}{dt} + 3i = -14e^{-7t} + 9 + 12e^{-7t}$$

$$= 9 - 2e^{-7t} A$$

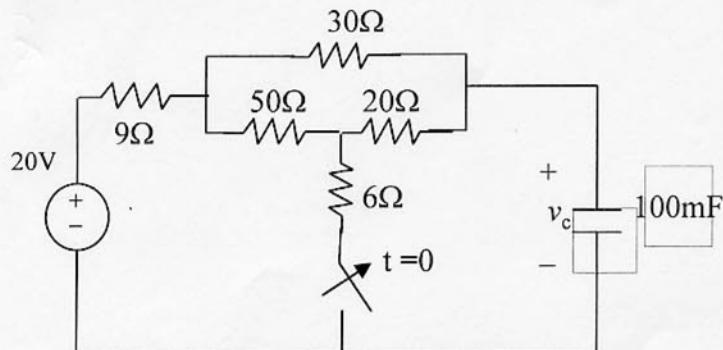3. The switch has been closed for a long time before open at $t = 0$. Find $v_c(t)$ for $t > 0$.



Before switch, at $t = 0^-$

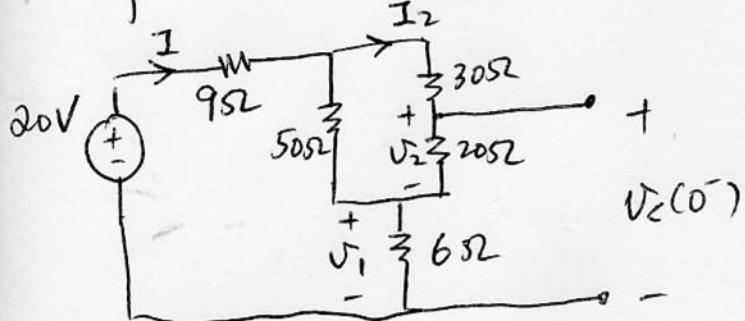

Req w.r.t 20V

$$\text{Req} = 9 + 50 \parallel (30 + 20) + 6\Omega$$

$$= 9 + 25 + 6 = 40\Omega.$$


$$I = \frac{20}{\text{Req}} = 0.5A, I_2 = 0.5 \times \frac{1}{3} = 0.25A$$

$$V_1 = 6I = 6 \times 0.5 = 3V,$$

$$V_2 = 20I_2 = 20 \times 0.25 = 5V$$

$$V_c(0^-) = V_1 + V_2 = 3 + 5 = 8V$$

After switch

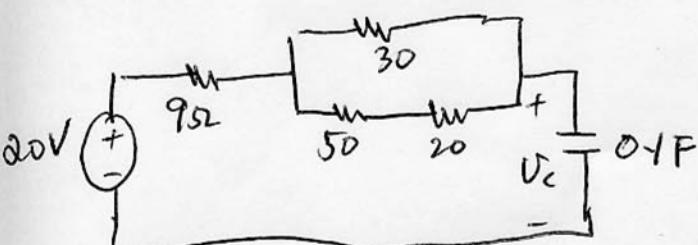

$$R_{th} = 9 + 30 \parallel (50 + 20)$$

$$= 9 + \frac{30 \times 70}{100} = 30\Omega$$



$$V_c(\infty) = 20V, R_{th}C = 30 \times 0.1 = 3$$

$$V_c(t) = V_c(\infty) + (V_c(0^-) - V_c(\infty)) e^{-\frac{1}{R_{th}C}t}$$

$$= 20 + (8 - 20) e^{-\frac{1}{3}t}$$

$$= 20 - 12 e^{-\frac{1}{3}t} V.$$

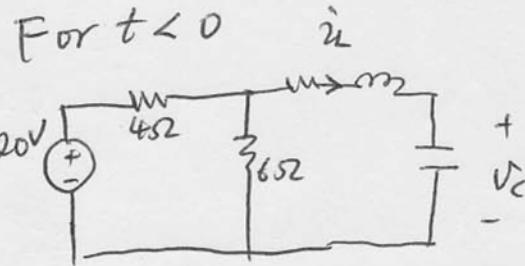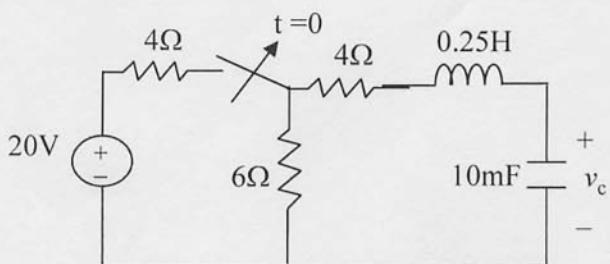4. (5pts) For $t < 0$, the switch is closed. Assume that a steady state has been reached by $t = 0$. At $t = 0$, the switch is open. Find $v_c(t)$ for $t > 0$.



$$V_c(0) = \frac{6}{6+4} \times 20 = 12V, i_L(0) = 0$$

For $t > 0$, R_{th} w.r.t $-m_1$ is $R_{th} = 4 + 6 = 10\Omega$

$$\text{At } t=0^+, i_c(0^+) = i_L(0^+) = 0, \frac{dV_c(0)}{dt} = \frac{1}{C} i_c(0^+) = 0$$

$$\alpha = \frac{R_{th}}{2L} = \frac{10}{2 \times 0.25} = 20, \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.25 \times 0.01}} = 20$$

$\alpha = \omega_0$, \Rightarrow case 2.

Since $V_c(\infty) = 0$, the general solution is

$$V_c(t) = (A_1 + A_2 t) e^{-20t}$$

$$\dot{V}_c(t) = (A_1 + A_2 t)(-20)e^{-20t} + A_2 e^{-20t}$$



By initial condition, $V_c(0) = A_1 = 12$

$$\dot{V}_c(0) = -20A_1 + A_2 = 0.$$

$$\Rightarrow A_1 = 12, A_2 = 240.$$

$$\text{Finally } V_c(t) = (12 + 240t)e^{-20t} \text{ V}$$

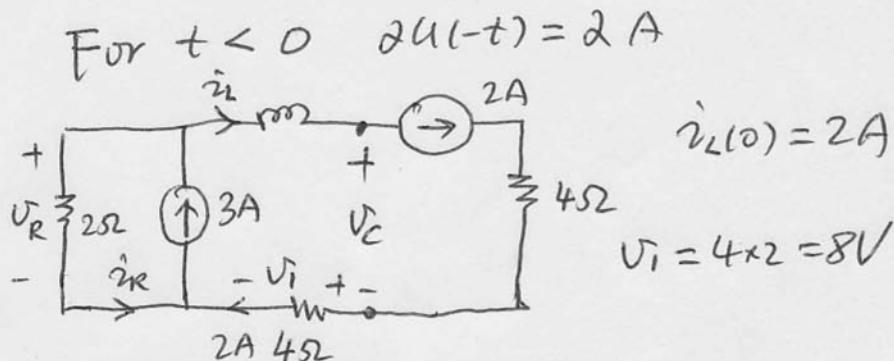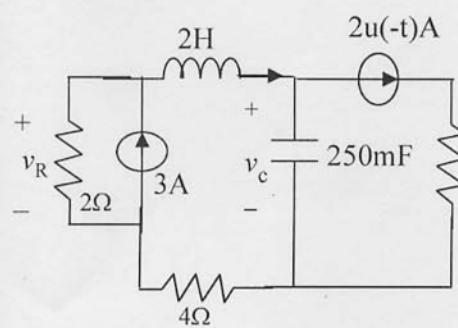5. (5pts) Find $v_c(t)$ and $v_R(t)$ for $t > 0$. Recall that $u(-t)=1$ for $t < 0$ and $u(-t)=0$ for $t > 0$.




$$\text{By KCL, } i_R = 3 - 2 = 1 \text{ A}, \quad V_R = 2 \text{ V}$$

$$\text{By KVL, } V_C = V_R - V_I = 2 - 8 = -6 \text{ V}, \quad \underline{V_{c(0)} = -6 \text{ V}}$$

For $t > 0$,
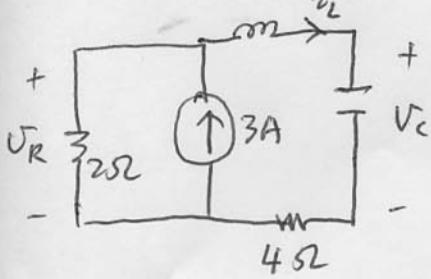
$$\text{At } t=0^+, i_{c(0^+)} = i_{L(0^+)} = 2 \text{ A}.$$



$$\frac{dV_{c(0^+)}}{dt} = \frac{1}{C} i_{L(0^+)} = \frac{1}{0.25} \times 2 = 8 \text{ V/s}$$

$$\text{At } t=\infty, \quad \underline{V_{c(\infty)} = 3 \times 2 = 6 \text{ V}.}$$

$$R_{th} = 4 + 2 = 6 \Omega, \quad \alpha = \frac{R_{th}}{2L} = \frac{6}{2 \times 2} = 1.5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{2}$$

$\alpha > \omega_0$, Case 1.


$$s_1, s_2 = -1.5 \pm \sqrt{1.5^2 - 2} = -1.5 \pm 0.5,$$

$$s_1 = -1, \quad s_2 = -2, \quad V_{c(t)} = 6 + A_1 e^{-t} + A_2 e^{-2t}$$

$$\text{By initial condition, } V_{c(0)} = 6 + A_1 + A_2 = -6 \Rightarrow \begin{cases} A_1 = -16 \\ A_2 = 4 \end{cases}$$

$$V_{c(t)} = 6 - 16e^{-t} + 4e^{-2t} \text{ V}$$
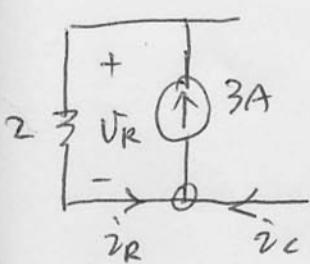
$$V_R = 2i_R = 2(3 - i_c) = 2(3 - C \frac{dV_c}{dt})$$



$$\begin{aligned} V_R(t) &= 2(3 - 0.25 \times (16e^{-t} - 8e^{-2t})) \\ &= 6 - 8e^{-t} + 4e^{-2t} \text{ V} \end{aligned}$$