

L5


Today, we learn some tools derived from the 3 basic laws:

- Equivalent resistance
- Voltage division
- Current division

They help you develop intuition about circuits:

- To see relationship between variables
- To see several steps ahead
- To plan a solution to a circuit

Two terminal circuit
with all resistors

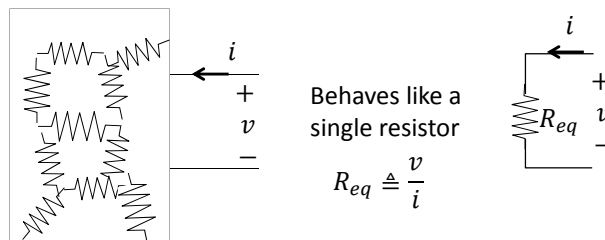


1


L5

Ways of connection

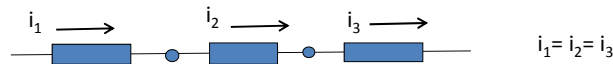
Series connection: Two or more elements are in series if every connected pair exclusively share a single node, i.e., one node connects only two elements.



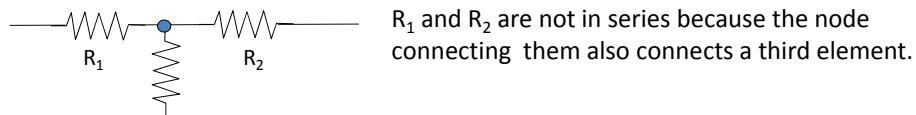By KCL, same current flows through elements in series



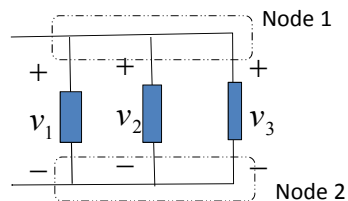Parallel connection: Two or more elements are in parallel if they are connected between the same two nodes.




By KVL, same voltage across parallel elements:

$$v_1 = v_2 = v_3$$

2

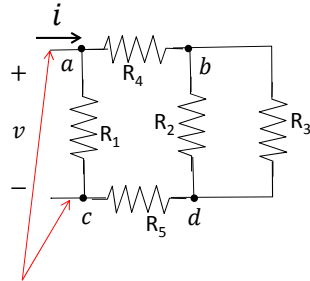Determine series and parallel connection:




R_2 and R_3 are in parallel,
 How about R_1 and R_2 ?
 R_1 and R_2 are not in parallel.
 R_1 is between "a" and "c", R_2 between "b" and "d"
 Any series connection?
 R_1 and R_5 are not in series
 R_1 and R_4 are not in series
 No series connection between any two elements.


These wires cannot be thrown away.
 They must be connected to somewhere to draw power

3

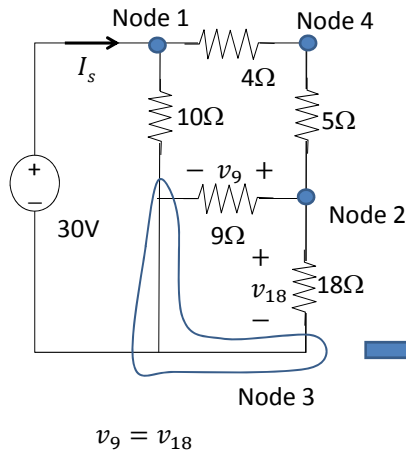Which pair of resistors are in series? Which pair in parallel?



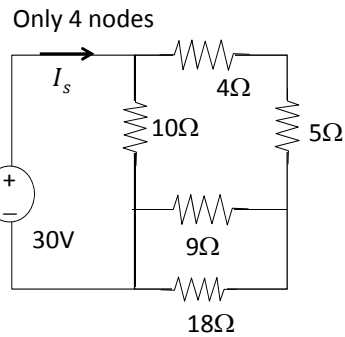
10Ω and 5Ω ? Not parallel, Not series
 4Ω and 9Ω ? Not parallel, Not series
 4Ω and 5Ω ? In Series
 9Ω and 18Ω ? In parallel
 How many nodes in the circuit?



4

§ 2.5 Series resistors and voltage division

L5

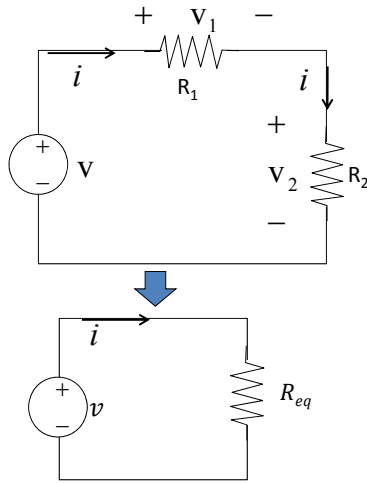

Given R_1, R_2 .
What is v/i ?

By KCL, same current in R_1, R_2

By Ohm's law, $v_1 = R_1 i, v_2 = R_2 i$

By KVL, $v = v_1 + v_2$.

Putting together:

$$v = v_1 + v_2 = R_1 i + R_2 i = (R_1 + R_2) i$$

$$\Rightarrow v = (R_1 + R_2) i \quad (1)$$


$$v = R_{eq} i \quad (2) \quad R_{eq} = ?$$

Compare (1) and (2):

$$R_{eq} = R_1 + R_2$$

5

In general:

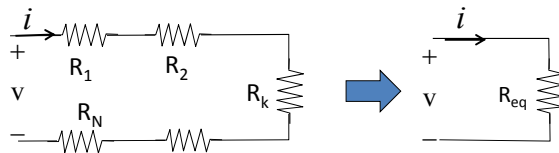

If $R_{eq} = R_1 + R_2 + \dots + R_N$, same $v \sim i$ relationship.
 R_{eq} is called the equivalent resistance.


$$R_{eq} = R_1 + R_2 + \dots + R_N$$

L5

6


Voltage division

L5

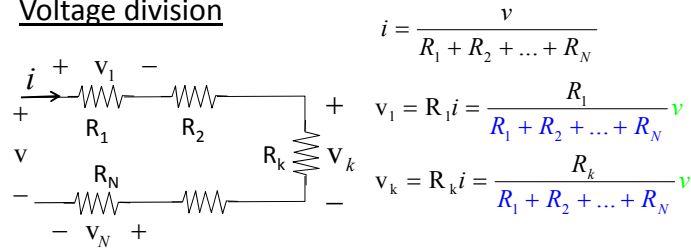

Voltage division: Total voltage v is divided among the resistors in direct proportion to the resistances. Larger resistance takes more voltage.


Special case with two resistors:

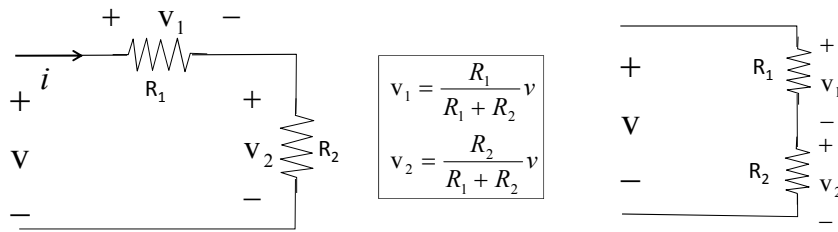

7

§ 2.6 parallel resistors and current division


L5

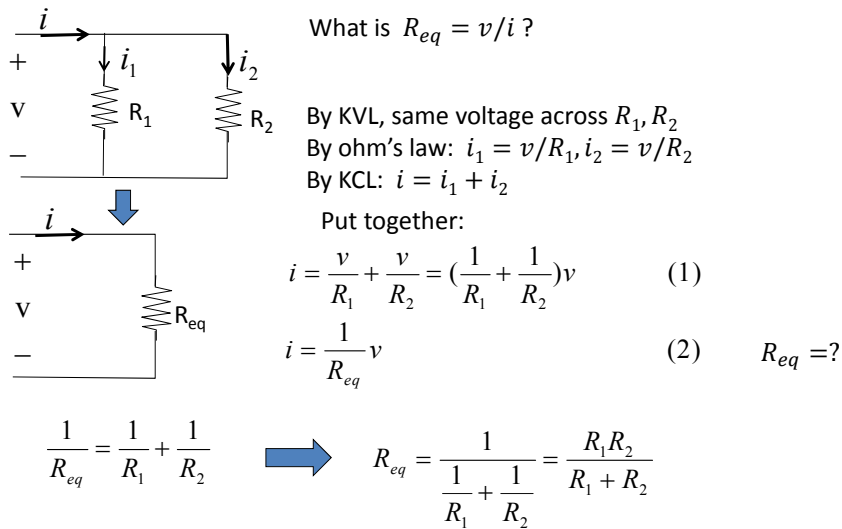

8

L5

In general

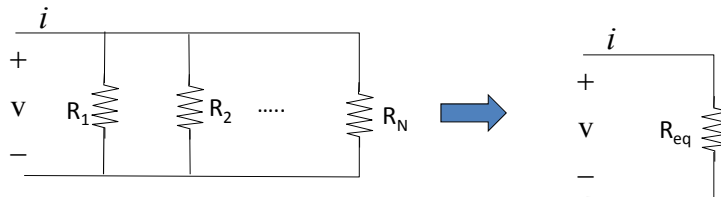

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$

9

Equivalent resistance for parallel resistors:

L5

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}} \quad \text{Notation: } R_{eq} = R_1 // R_2 // \dots // R_N$$

Special cases:

$$N=2: R_1 // R_2 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_1=R_2=\dots=R_N=R: R_{eq} = \frac{1}{\frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R}} = \frac{R}{N}$$

Simple combinations:

$$\begin{aligned} 3//6 &= 2 \\ 12//6 &= 4 \\ 15//10 &= 6 \\ 20//5 &= 4 \end{aligned}$$

Simple rule:

$$\alpha R_1 // \alpha R_2 = \frac{\alpha R_1 \times \alpha R_2}{\alpha R_1 + \alpha R_2} = \frac{\alpha R_1 R_2}{R_1 + R_2} = \alpha (R_1 // R_2)$$

$$27//54 = 9(3//6) = 9 \times 2 = 18$$

10

L5

Common sense:

Adding more resistor to existing parallel ones reduces R_{eq} :

$$\frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} + \frac{1}{R_{N+1}}} < \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$


$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}} < \frac{1}{\frac{1}{R_k}} = R_k, \quad \text{for any } k = 1, 2, \dots, N$$

Equivalent resistance for parallel connection is less than any individual resistance

Equivalent conductance:

$$G_{eq} = \frac{i}{v} = \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} = G_1 + G_2 + \dots + G_N$$

11

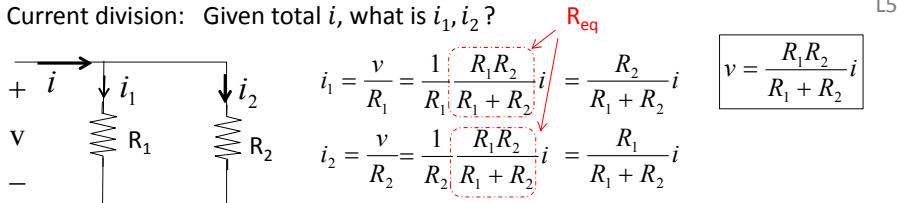Current division: Given total i , what is i_1, i_2 ?

$$i_1 = \frac{R_2}{R_1 + R_2} i$$

$$i_2 = \frac{R_1}{R_1 + R_2} i$$

The other resistance on top


The current is shared by resistors in inverse proportion to resistance.
Larger resistor takes less current.

12


L5

Two extreme cases:

Case 1: A resistor in parallel with a short circuit

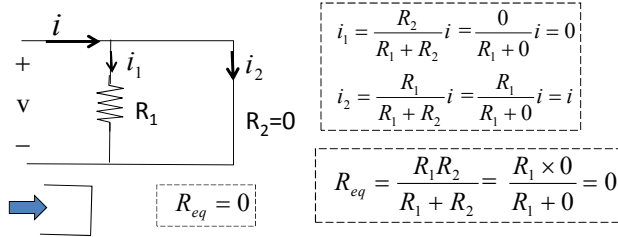

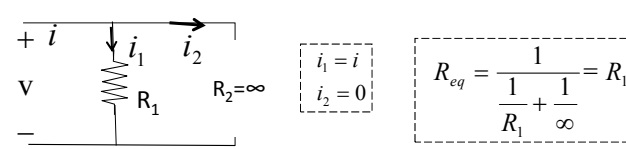
Case 2: A resistor in parallel with an open circuit



13

Equivalent resistance Examples




L5

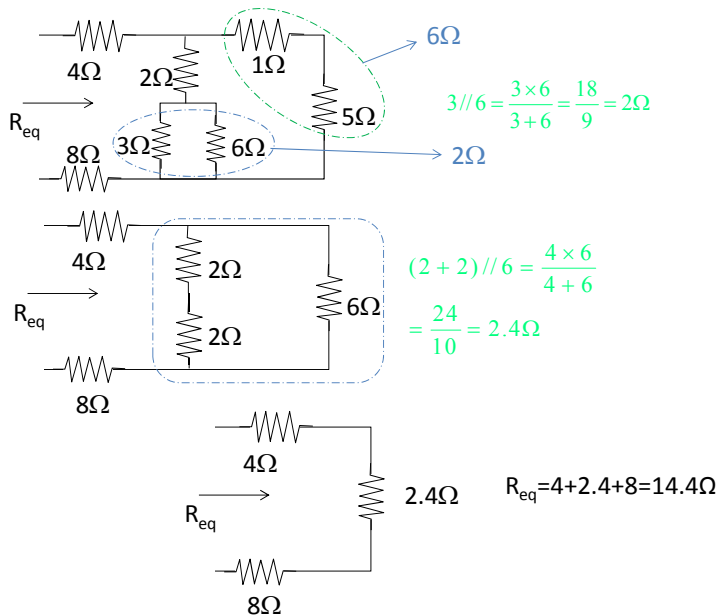

14

Equivalent resistance Examples


L5

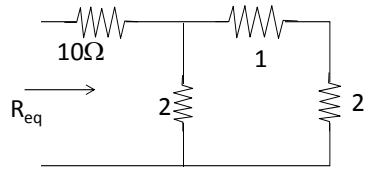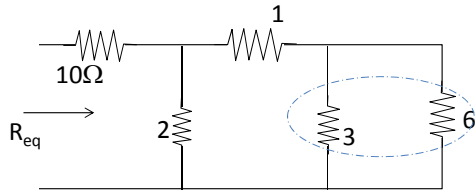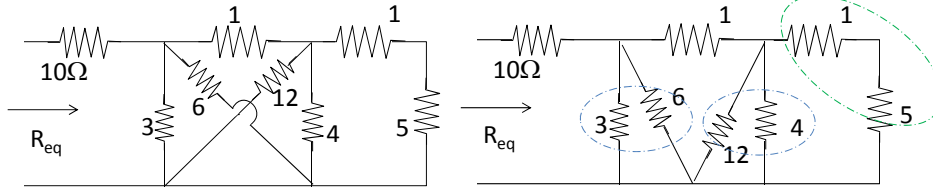

$$\begin{aligned}
 R_{eq} &= 10 + 2 // (1 + 2) \\
 &= 10 + 2 // 3 \\
 &= 10 + 1.2 \\
 &= 11.2 \Omega
 \end{aligned}$$

15


Example: Compute I_s

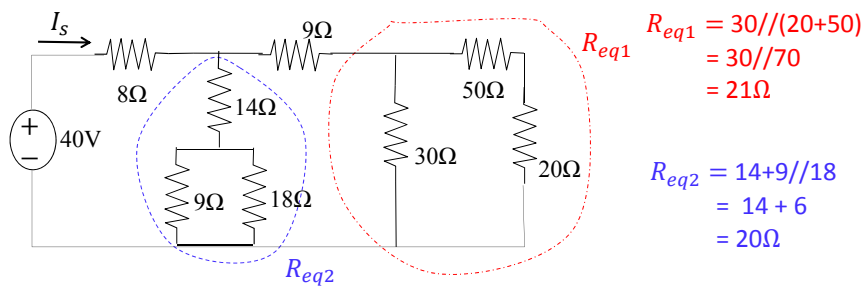

$$\begin{aligned}
 R_{eq1} &= 30 // (20 + 50) \\
 &= 30 // 70 \\
 &= 21 \Omega
 \end{aligned}$$

$$\begin{aligned}
 R_{eq2} &= 14 + 9 // 18 \\
 &= 14 + 6 \\
 &= 20 \Omega
 \end{aligned}$$

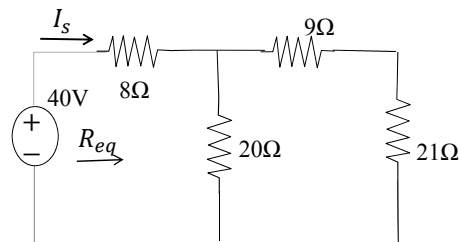Need to find the equivalent resistance with respect to 40V




$$\begin{aligned}
 R_{eq} &= 8 + 20 // (21 + 9) \\
 &= 8 + 12 = 20 \Omega
 \end{aligned}$$

$$I_s = \frac{40}{20} = 2A$$


16

Example: Compute R_{eq}

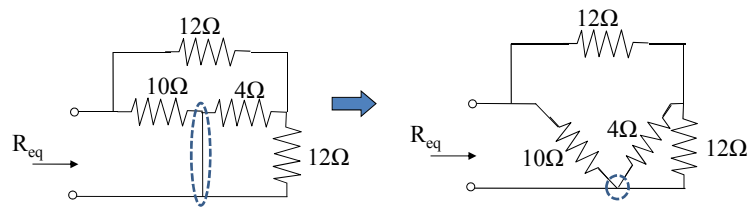



$$R_{eq} = 10 // (12 + 4 // 12)$$

$$= 10 // 15 = 6 \Omega$$

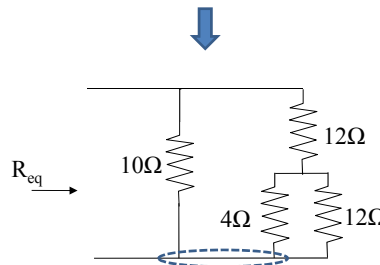


17

Practice 6: Find R_{eq}

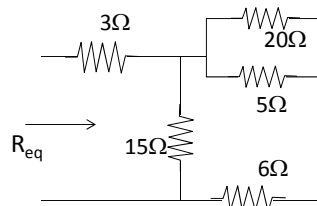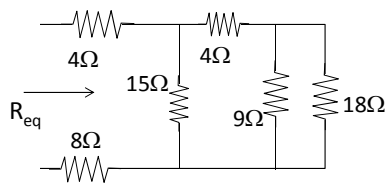

R5


Practice 7: Find I_s

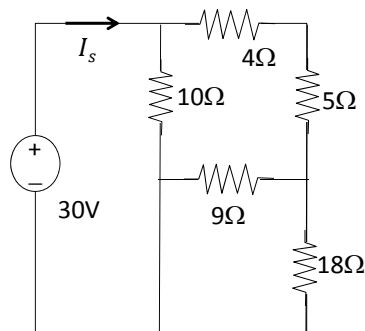


18

Practice 8: Find v_s


R5

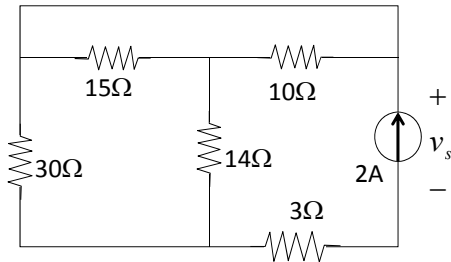

Practice 9: Find v_1, v_2

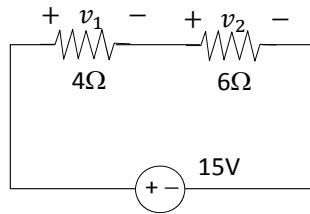

Practice 10: Find i_1, i_2

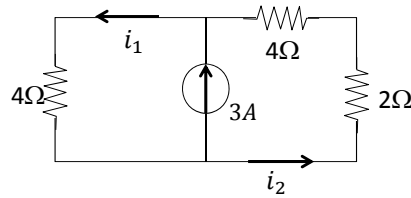

19


Three useful tools derived from basic laws:

L6

- Equivalent resistance
- Voltage division
- Current division





Used together to solve circuit problems

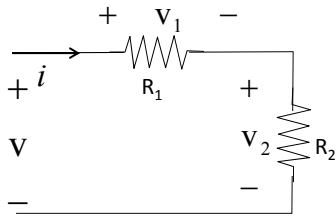

Voltage division:

$$v_1 = \frac{R_1}{R_1 + R_2} v$$


$$v_2 = \frac{R_2}{R_1 + R_2} v$$

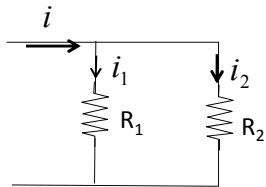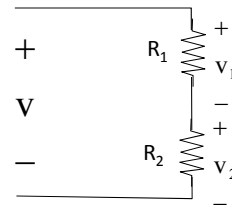

Current Division:

$$i_1 = \frac{R_2}{R_1 + R_2} i$$


$$i_2 = \frac{R_1}{R_1 + R_2} i$$

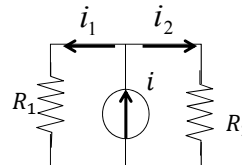

20


L6

Example: Find i_0 and v_1 .

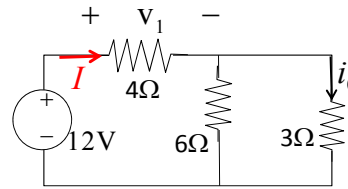

Approach 1: Assign auxiliary variable I .

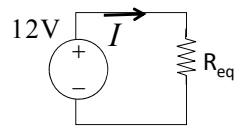Use equivalent resistance with respect to 12V to find I , then $v_1=4I$, and i_0 can be computed by current division.



$$R_{eq} = 4 + 6//3 = 4 + 2 = 6\Omega$$

$$\text{By Ohm's Law, } I = 12/R_{eq} = 12/6 = 2A$$


$$\text{Thus } v_1 = 4I = 8V.$$

$$\text{By current division: } i_0 = \frac{6}{3+6} I = \frac{6}{3+6} \times 2 = \frac{4}{3} A$$


Be Careful: In this equivalent circuit, only I is the same as in the original circuit. Neither v_1 nor i_0 , can be found in it. You need to go back to the original circuit to find v_1 and i_0 .

21

L6

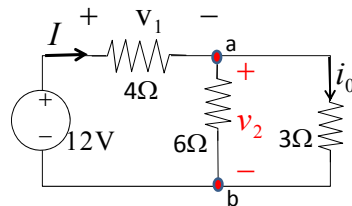

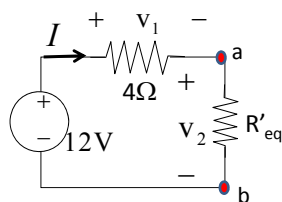Approach 2: Use equivalent resistance of $6//3$, denoted as R'_{eq} .



$$R'_{eq} = 3//6 = 2\Omega. \text{ By voltage division,}$$

$$v_1 = \frac{4}{4+2} \times 12 = 8V, v_2 = \frac{2}{4+2} \times 12 = 4V$$

Be careful, i_0 cannot be found in the equivalent circuit. $i_0 \neq I$. You have to use the original circuit to find i_0 .



Where is v_2 in the original circuit?

Since the voltage across 3Ω is v_2 , by Ohm's Law, $i_0 = v_2/3 = 4/3A$

22


22

Example: Find v_1, v_2 ,

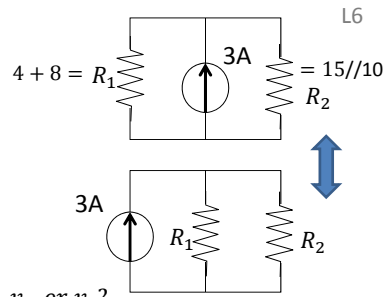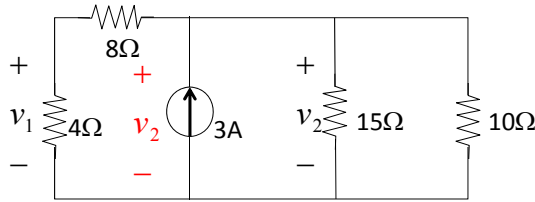

Approach 1: Which is the voltage across 3A? v_1 or v_2 ?

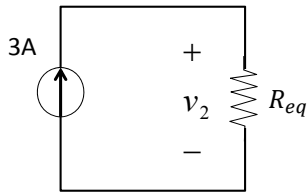It is v_2 . If you know the R_{eq} w.r.t 3A, you can obtain v_2 by ohm's law.



$$R_{eq} = R_1 // R_2$$

$$R_{eq} = (4+8) // 15 // 10 = 12 // 6 = 4\Omega$$


$$v_2 = R_{eq} \times 3 = 4 \times 3 = 12V$$

How to find v_1 ?
Need the original circuit.

By voltage division,


$$v_1 = \frac{4}{4+8} \times v_2 = \frac{4}{12} \times 12 = 4V$$

23

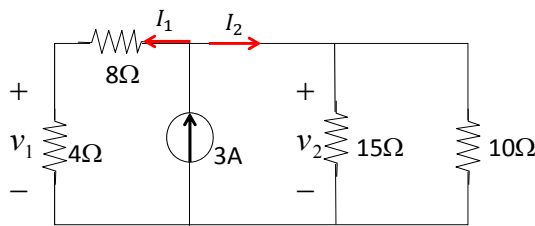

Be careful, you cannot find v_1 in the simplified circuit. Have to use the original circuit to find v_1

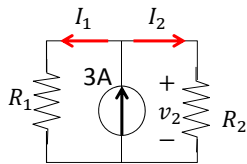Approach 2: Use current division. Assign I_1, I_2 .



$$R_1 = 4 + 8 = 12\Omega$$

$$R_2 = 15 // 10 = 6\Omega$$

By current division,


$$I_1 = \frac{R_2}{R_1 + R_2} \times 3 = \frac{6}{18} \times 3 = 1A$$

$$I_2 = \frac{R_1}{R_1 + R_2} \times 3 = \frac{12}{18} \times 3 = 2A$$

By ohm's law, $v_1 = 4I_1 = 4V$; $v_2 = R_2 I_2 = 6 \times 2 = 12V$.

24

Example: Find I_s , I_1 , v_{ab}

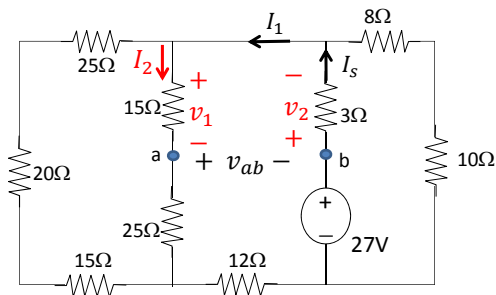

Outline of the solution:

Find I_s first, then use current division to find I_1 .

To find v_{ab} , need to find v_1, v_2 , then use KVL


$$v_2 + v_{ab} + v_1 = 0 \Rightarrow v_{ab} = -v_2 - v_1$$

To find v_1 , need the current through 15Ω .

Assign I_2 ,


I_2 can be computed by current division on I_1

25

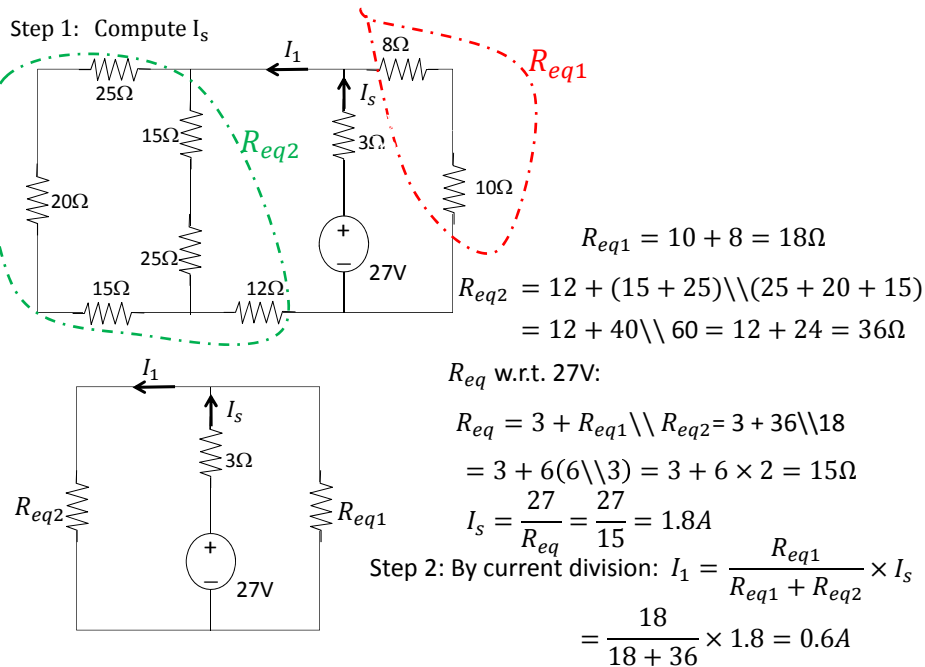

26

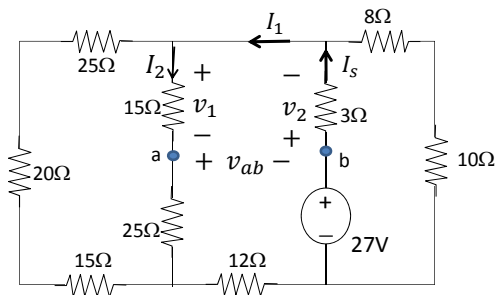Step 3: Go back to the original circuit to find v_{ab} :



$$I_s = 1.8A;$$

$$I_1 = 0.6A$$

I_1 is divided by $15\Omega + 25\Omega = 40\Omega$ and $25\Omega + 20\Omega + 15\Omega = 60\Omega$

$$I_2 = \frac{60}{60 + 40} \times 0.6 = 0.36A$$

$$v_1 = 15I_2 = 15 \times 0.36 = 5.4V$$


$$v_2 = 3I_s = 3 \times 1.8 = 5.4V$$

$$v_{ab} + v_1 + v_2 = 0$$

$$v_{ab} = -v_1 - v_2 = -5.4 - 5.4 = -10.8V$$


27

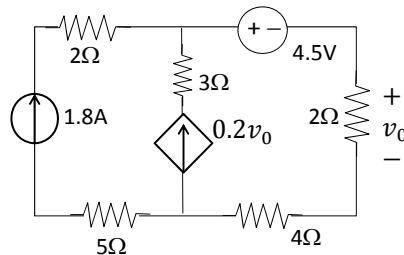Example: Find v_0 and the power absorbed by the dependent current source.



Hint: Use KCL to make an equation for v_0

Solution: Assign current I_1

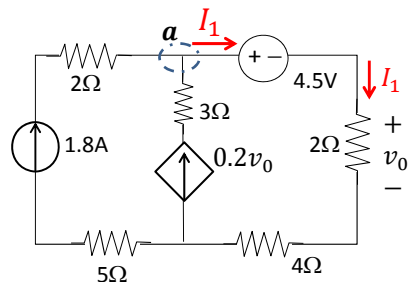

I_1 is the same current through 2Ω

By Ohm's Law, $I_1 = \frac{v_0}{2} = 0.5v_0$

KCL at node **a**:


$$1.8 + 0.2v_0 = I_1 = 0.5v_0$$

$$\Rightarrow 1.8 = 0.3v_0$$

$$\Rightarrow v_0 = 6V$$

28

We have : $v_0 = 6V$

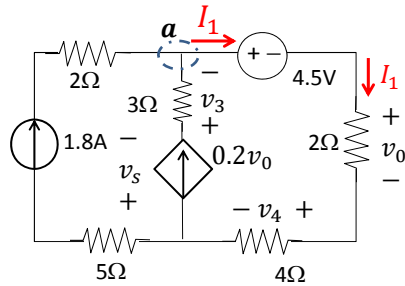

$$v_3 = ? \quad v_3 = 3 \times 0.2v_0 = 3 \times 0.2 \times 6 = 3.6V$$

$$v_4 = ? \quad v_4 = 4I_1, \quad I_1 = \frac{v_0}{2} = \frac{6}{2} = 3A$$

$$v_4 = 4 \times 3 = 12V$$

Power absorbed by the dependent current source?

Need voltage across $0.2v_0$

Assign v_s

To apply KVL correctly, Assign v_3, v_4



KVL around right side loop:

$$v_s + v_3 + 4.5 + v_0 + v_4 = 0$$


$$v_s = -v_3 - 4.5 - v_0 - v_4 = -3.6 - 4.5 - 6 - 12 = -26.1V$$

$$p_{0.2v_0} = v_s \times 0.2v_0 = -26.1 \times 0.2 \times 6 = -31.32W$$

29

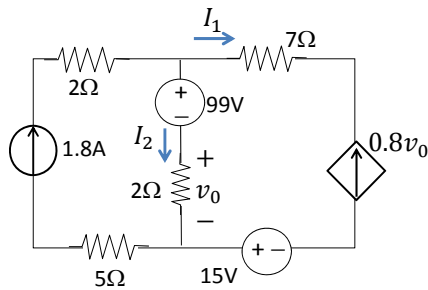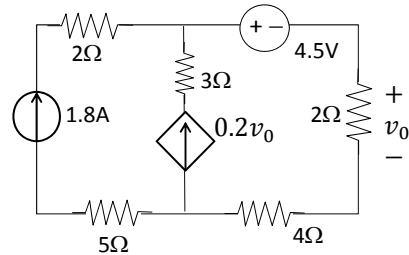

Variations of the circuit

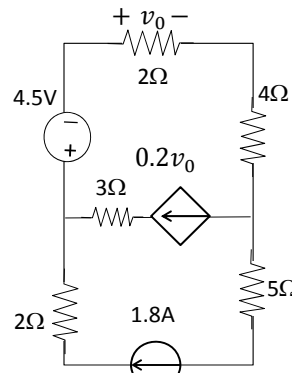


Same idea!
Express Branch current I_1, I_2
In terms of v_0 ,
Then apply KCL

If power by a current source is needed, compute its voltage by using KVL

30

Example: Find v_1 and v_2 .

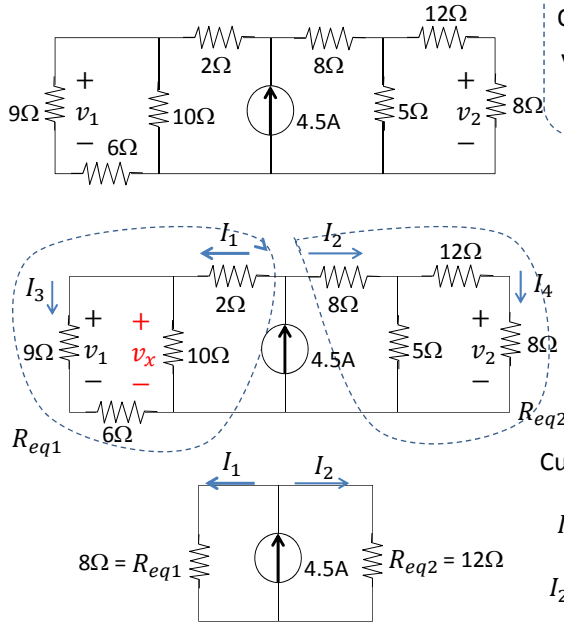

Alternatively:
Ohms Law: $v_x = 6I_1 = 16.2V$
Voltage division:
 $v_1 = \frac{9}{9+6} \times v_x = 9.72V$


More current division:
 $I_3 = \frac{10}{10+15} \times I_1 = 1.08A$
 $v_1 = 9I_3 = 9.72V$
 $I_4 = \frac{5}{5+20} \times I_2 = 0.36A$
 $v_2 = 8I_4 = 2.88V$

Current division:
 $I_1 = \frac{12}{8+12} \times 4.5 = 2.7A$
 $I_2 = \frac{8}{8+12} \times 4.5 = 1.8A$



31

Example: Find the currents i_1, \dots, i_5

L6

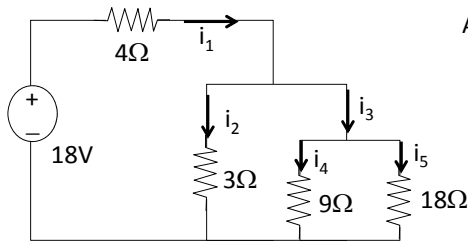

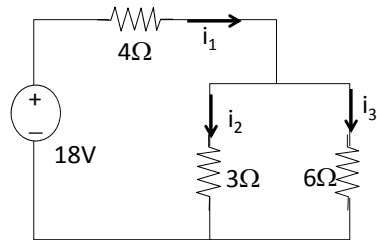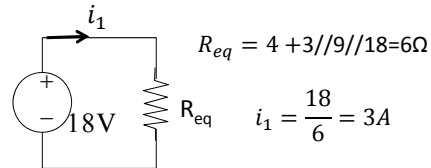Approach1: Use equivalence resistance and current division.



$$R_{eq} = 4 + 3//9//18 = 6\Omega$$

$$i_1 = \frac{18}{6} = 3A$$

$$i_2 = \frac{6}{3+6} \times i_1 = \frac{6}{9} \times 3 = 2A$$

$$i_3 = \frac{3}{3+6} \times i_1 = \frac{3}{9} \times 3 = 1A$$


$$i_4 = \frac{18}{9+18} \times i_3 = \frac{18}{27} \times 1 = \frac{2}{3}A$$

$$i_5 = \frac{9}{9+18} \times i_3 = \frac{9}{27} \times 1 = \frac{1}{3}A$$


32

Example: Find the currents i_1, \dots, i_5

L6

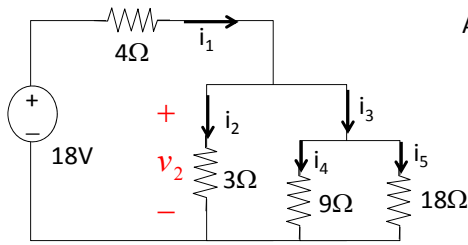

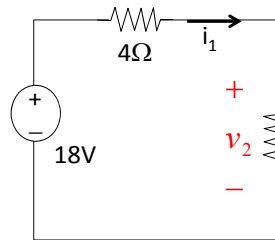Approach2: Use voltage division and Ohm's law. Assign v_2 .



By voltage division $v_2 = \frac{2}{4+2} \times 18 = 6V$

By Ohm's law, $i_1 = \frac{v_2}{2} = \frac{6}{2} = 3A$


$i_2 = \frac{v_2}{3} = \frac{6}{3} = 2A$

$i_4 = \frac{v_2}{9} = \frac{6}{9} = \frac{2}{3}A$ $i_5 = \frac{v_2}{18} = \frac{6}{18} = \frac{1}{3}A$

$i_3 = i_4 + i_5 = \frac{2}{3} + \frac{1}{3} = 1A$

33

Example: Find i_1, i_2, i_3, i_4, I_x

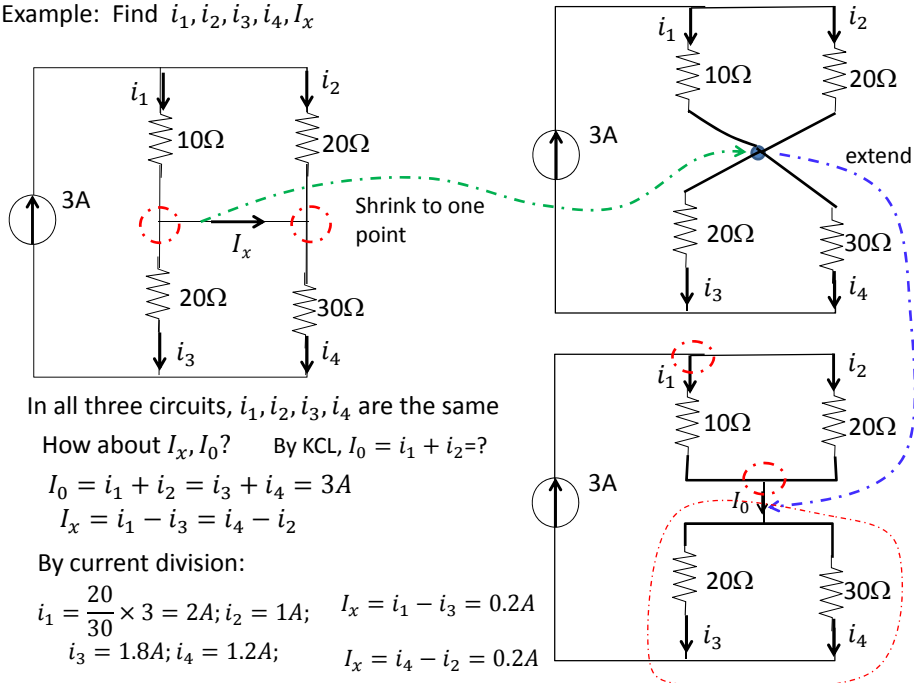

In all three circuits, i_1, i_2, i_3, i_4 are the same

How about I_x, I_0 ? By KCL, $I_0 = i_1 + i_2 = ?$

$I_0 = i_1 + i_2 = i_3 + i_4 = 3A$

$I_x = i_1 - i_3 = i_4 - i_2$

By current division:

$i_1 = \frac{20}{30} \times 3 = 2A; i_2 = 1A; I_x = i_1 - i_3 = 0.2A$

$i_3 = 1.8A; i_4 = 1.2A; I_x = i_4 - i_2 = 0.2A$

34

- Test 1 will be given on Sept 30 (Monday), 11-11:50am.
In Ball Hall 210 There will be two versions in different colors.


Please arrive 5-10 minutes earlier

- A practice exam will be given on 9/25/2019(Wednesday), 11-11:50am
in Ball Hall 210

Solution to practice exams will be posted at website


Solution to all practice problems in lecture note will be posted.

35

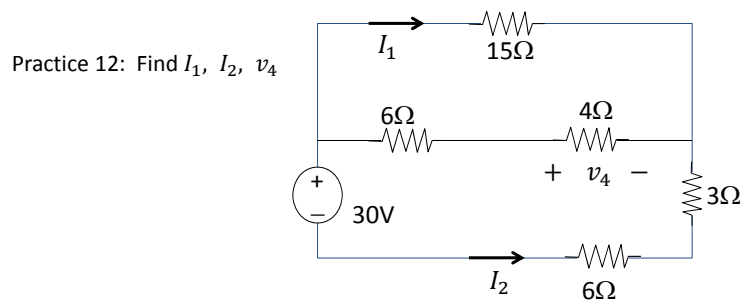

R6


Practice 13: Find I_0 , v_4

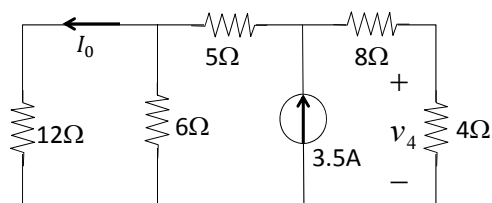

36

Practice 14: Find I_0, v_2



R6

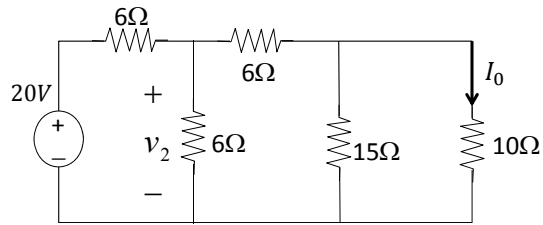

37


Practice 15: Find the voltage v_x

R6

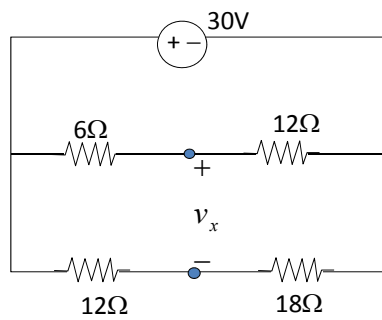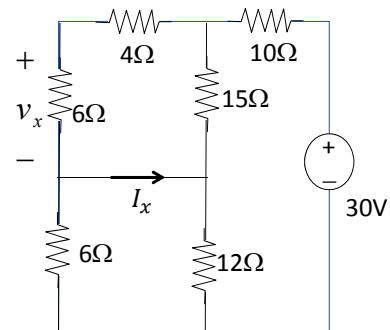Practice 16: Find v_0, I_x 


38

R6

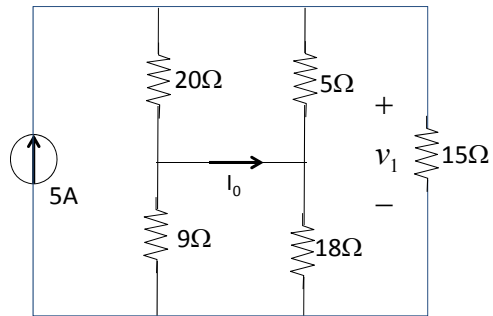Practice 16a: Find v_1 , I_0 ,


39

R7

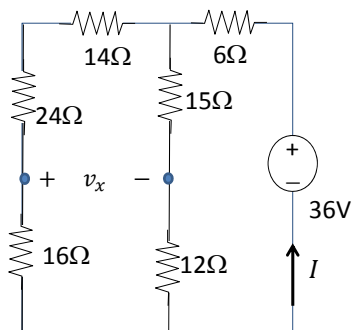Practice 17: Find v_x , I ,


40

Practice 18: Find i_0

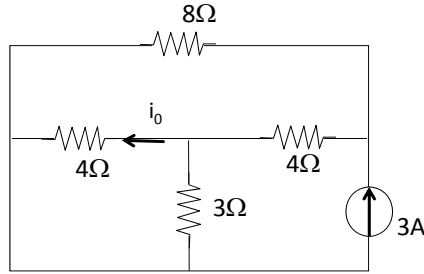


R7

Practice 19: Find i_0

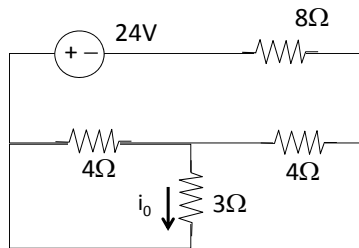


41

Practice 20: Find R for the circuit

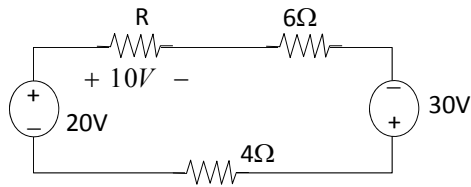


R7

Practice 21: Find V_s for the circuit

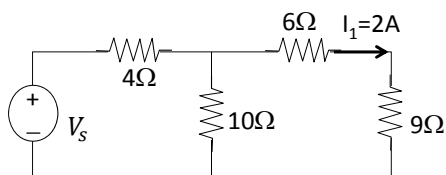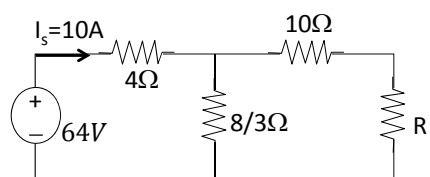

42

R7

Practice 22: Find R so that I_s is 10A

43