

Chapter 3 Methods of Analysis: Nodal analysis and Mesh analysis


L8

Basic concepts for nodal analysis:


Node voltage and ground

Symbols for the ground:

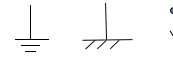
Definition: The ground for a circuit is defined as the point (or node), where the voltage = 0.



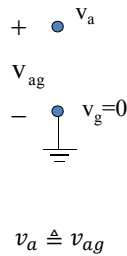Node voltage at any other point is defined as the voltage drop from this point to the ground.




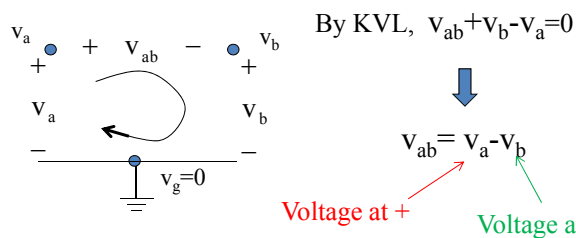With node voltage defined this way, the voltage drop between any two points is simply the difference of two node voltages.



KVL automatically satisfied:

L8

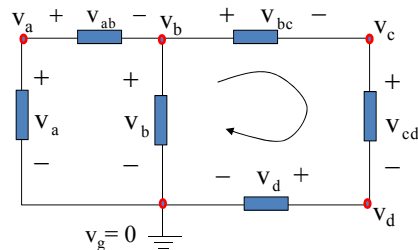

$$\begin{aligned} v_{ab} &= v_a - v_b \\ v_{bc} &= v_b - v_c \\ v_{cd} &= v_c - v_d \end{aligned}$$

Along right loop: $v_{bc} + v_{cd} + v_d - v_b = v_b - v_c + v_c - v_d + v_d - v_b = 0$

All items cancelled. KVL automatically satisfied. This is due to the assignment of node voltage and that the voltage between any two points is the difference of two node voltages.

Main Idea of nodal analysis:


L8

Pick node voltages as key variables.

Express everything else in terms of node voltages,
such as branch voltage, currents.

Then apply KCL at the nodes to form equations for node voltages.

A typical node:

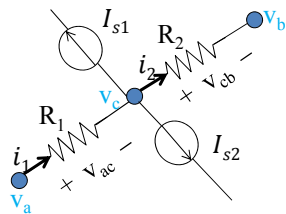

Express resistor currents in terms of node voltages

$$i_1 = \frac{v_{ac}}{R_1} = \frac{v_a - v_c}{R_1}; \quad i_2 = \frac{v_{cb}}{R_2} = \frac{v_c - v_b}{R_2}$$

KCL at center node:

$$i_1 - i_2 - I_{s1} - I_{s2} = 0$$


$$\frac{v_a - v_c}{R_1} - \frac{v_c - v_b}{R_2} - I_{s1} - I_{s2} = 0$$

An equation for node voltages

One key step in nodal analysis:

L8

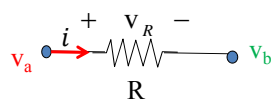Express the current through a resistor in terms of node voltages.



Assign v_R so that passive sign convention is satisfied. Then

$$i = \frac{v_R}{R} = \frac{v_a - v_b}{R}$$

Observation:


The current i enters at v_a and exits at v_b .

In the future, v_R will not be assigned.

<p>General rule: $i = \frac{v_{at\ entrance} - v_{at\ exit}}{R}$</p>

L8

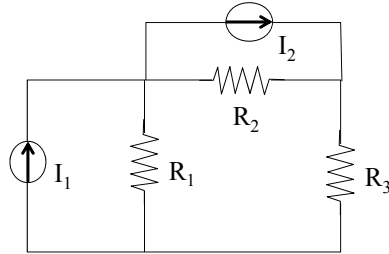Example: A circuit with only current sources. We need to find the current through each resistor.



Solution: Additional variables need to be assigned.

L8


How many nodes? only three nodes.

Step 1: pick the ground.

Assign node voltages, v_1, v_2 .

Step 2: Assign resistor current

with reference direction, i_1, i_2, i_3

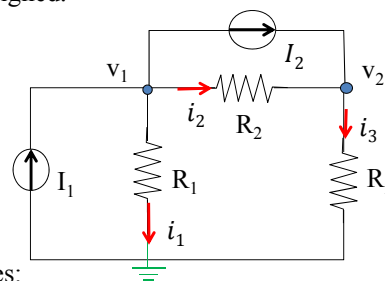

Express the currents in terms of node voltages:

$$i_1 = \frac{v_1 - 0}{R_1} = \frac{v_1}{R_1}; i_2 = \frac{v_1 - v_2}{R_2}; i_3 = \frac{v_2}{R_3} \quad (*)$$

Plug (*) into (1), (2), respectively,

$$-\frac{v_1}{R_1} - \frac{v_1 - v_2}{R_2} = I_2 - I_1;$$

$$\frac{v_1 - v_2}{R_2} - \frac{v_2}{R_3} = -I_2$$

Step 3: Apply KCL at each node

$$\begin{aligned} \text{At } v_1: \quad & -i_1 - i_2 + I_1 - I_2 = 0 \\ & \Rightarrow -i_1 - i_2 = I_2 - I_1 \quad (1) \end{aligned}$$


$$\begin{aligned} \text{At } v_2: \quad & i_2 - i_3 + I_2 = 0 \\ & \Rightarrow i_2 - i_3 = -I_2 \quad (2) \end{aligned}$$

$$\begin{bmatrix} \frac{1}{R_1} & \frac{1}{R_2} & \frac{1}{R_2} \\ \frac{1}{R_2} & \frac{1}{R_2} & \frac{1}{R_3} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} I_2 - I_1 \\ -I_2 \end{bmatrix}$$

The reference direction of currents can be arbitrarily assigned.

Reversing the direction does not change the equations for node voltages.

Let us reverse i_1 and i_2

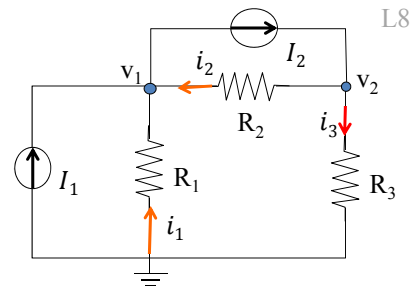

Then the signs of i_1 and i_2 are reversed:

$$i_1 = \frac{0 - v_1}{R_1} = -\frac{v_1}{R_1}; \quad i_2 = \frac{+v_2 - v_1}{R_2} = -\frac{v_1 - v_2}{R_2}; \quad i_3 = \frac{v_2}{R_3} \quad (*)$$

When apply KCL at each node, the sign for i_1, i_2 also reversed

$$\text{At } v_1: +i_1 + i_2 + I_1 - I_2 \Rightarrow i_1 + i_2 = I_2 - I_1 \quad (1)$$

$$\text{At } v_2: -i_2 - i_3 + I_2 = 0 \Rightarrow -i_2 - i_3 = -I_2 \quad (2)$$

Plug (*) into (1), (2), respectively, we obtain the same equations

$$-\frac{v_1}{R_1} - \frac{v_1 - v_2}{R_2} = I_2 - I_1;$$

$$\frac{v_1 - v_2}{R_2} - \frac{v_2}{R_3} = -I_2$$

Summary of steps in nodal analysis.

Suppose that the circuit has $n+1$ nodes and has only current sources.

- Step 1: pick the ground. Assign node voltages for the remaining n nodes: v_1, v_2, \dots, v_n
- Step 2: Assign resistor currents with reference direction, i_1, i_2, \dots , Express them in terms of node voltages.
- Step 3: Apply KCL at each of the node to obtain n equations for all branch currents. Then plug in the expressions from step 2, to obtain n equations for the n node voltages.
- Step 4: clean up the equations, solve for the voltages v_1, v_2, \dots, v_n and compute whatever is asked. Since all variables can be expressed in terms of these node voltages.

For circuit with only current sources, every branch current is either given, or, can be expressed in terms of node voltages.

L8

L8

Example: Find i_1, i_2, i_3 using nodal analysis

The ground and node voltages already assigned.

Express resistor currents:

$$i_1 = \frac{v_1}{2}; \quad i_2 = \frac{v_1 - v_2}{4}; \quad i_3 = \frac{v_2}{6} \quad (*)$$


Apply KCL at the nodes:

$$\text{At } v_1: \quad -i_1 - i_2 + 5 = 0 \quad (1)$$

$$\text{At } v_2: \quad i_2 - i_3 + 10 - 5 = 0 \quad (2)$$

Plug (*) into (1), (2)
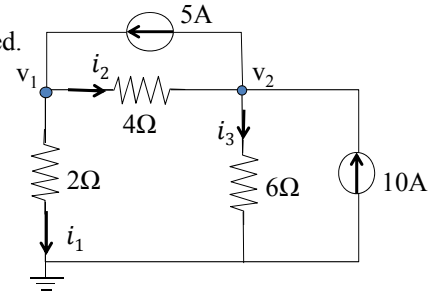
$$\begin{aligned} -\frac{v_1}{2} - \frac{v_1 - v_2}{4} + 5 &= 0 & \times 4 \\ \frac{v_1 - v_2}{4} - \frac{v_2}{6} + 5 &= 0 & \times 12 \end{aligned}$$



$$-2v_1 - v_1 + v_2 + 20 = 0$$

$$3v_1 - 3v_2 - 2v_2 + 60 = 0$$

$$3v_1 - v_2 = 20 \quad (1a)$$

$$3v_1 - 5v_2 = -60 \quad (2a)$$

$$v_1 = \frac{40}{3}V; \quad v_2 = 20V$$

$$i_1 = 6.667A; \quad i_2 = -1.667A; \quad i_3 = 6.667A$$

Example: A circuit with dependent current source. Form 3 equations for v_1, v_2, v_3 .^{L8}

i_x has been assigned. Assign other resistor currents, i_1, i_2, i_3

$$i_x = \frac{v_1 - v_2}{2}; \quad i_1 = \frac{v_1 - v_3}{4}$$

$$i_2 = \frac{v_2}{4}; \quad i_3 = \frac{v_2 - v_3}{8};$$

$$\text{KCL at } v_1: \quad i_1 + i_x = 3$$

$$\text{KCL at } v_2: \quad i_x - i_2 - i_3 = 0$$


$$\text{KCL at } v_3: \quad i_1 + i_3 - 2i_x = 0$$

Plug in current expression:

$$\frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{2} = 3$$

$$\frac{v_1 - v_2}{2} - \frac{v_2}{4} - \frac{v_2 - v_3}{8} = 0$$
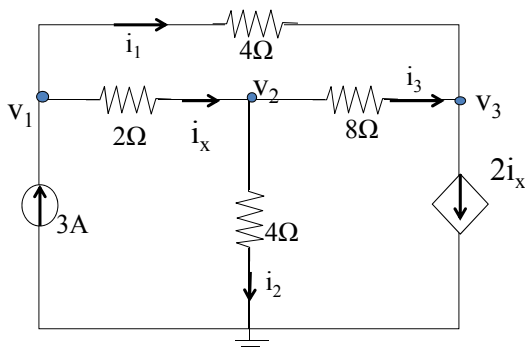
$$\frac{v_1 - v_3}{4} + \frac{v_2 - v_3}{8} - 2 \frac{v_1 - v_2}{2} = 0$$




$$3v_1 - 2v_2 - v_3 = 12 \quad (1)$$

$$4v_1 - 7v_2 + v_3 = 0 \quad (2)$$

$$-6v_1 + 9v_2 - 3v_3 = 0 \quad (3)$$

R8

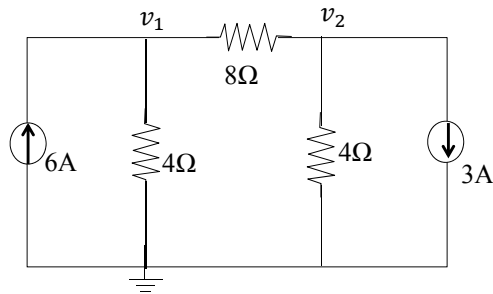
Practice problem 1:
Find v_1 and v_2 by using nodal analysis method




Practice problem 2:
Find i_1 by using nodal analysis method.

How many node voltages?

R8

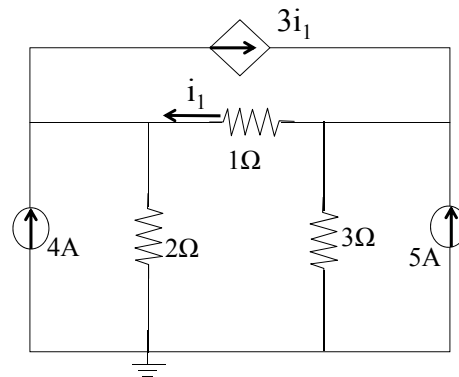

R8

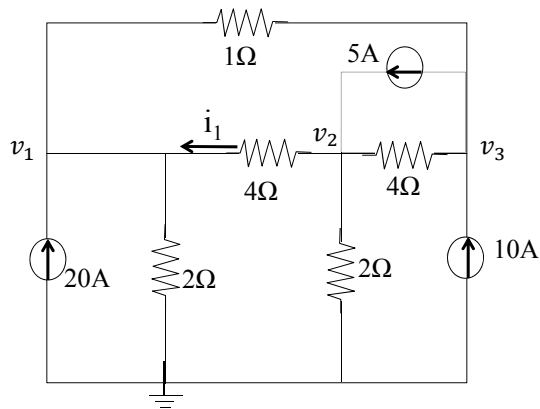Practice problem 3: Form 3 equations for v_1, v_2, v_3 

Nodal analysis

L9

- Basic concepts: node voltage and ground
 - Voltage between any two points is the difference of two node voltages

$$\begin{array}{ccc}
 \bullet & + & v & - & \bullet \\
 v_a & & & & v_b
 \end{array}
 \quad
 \begin{array}{l}
 v = v_a - v_b; \\
 v_a: \text{voltage at } + \\
 v_b: \text{voltage at } -
 \end{array}$$

- Basic step: Express resistor current in terms of node voltages:


$$\begin{array}{c}
 i \\
 \bullet \xrightarrow{\quad} \text{---} \text{---} \text{---} \bullet \\
 v_a \quad \quad \quad R \quad \quad \quad v_b
 \end{array}
 \quad
 i = \frac{v_{\text{at the entrance}} - v_{\text{at the exit}}}{R}$$

$$= \frac{v_a - v_b}{R}$$

- Basic idea: use KCL to form equations for node voltages

L9

What if we have a voltage source?

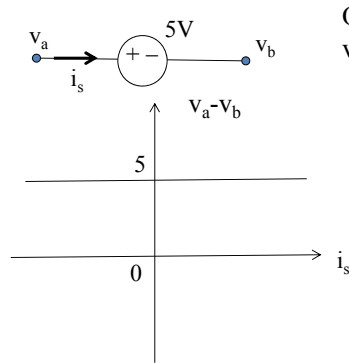

Q: How to express i_s in terms of v_a and v_b ?

A: i_s can not be expressed in terms of only v_a and v_b

i_s can be anything.

§ 3.3 Nodal Analysis with voltage sources

L9

Case 1: The voltage source is connected to the ground

Three non-reference nodes: v_1, v_2, v_3

$$i_1 = \frac{v_1 - v_2}{4}; i_2 = \frac{v_2}{2}; i_3 = \frac{v_2 - v_3}{4}; i_4 = \frac{v_1 - v_3}{6}$$

At v_2 , $i_1 - i_2 - i_3 = 0$

$$\frac{v_1 - v_2}{4} - \frac{v_2}{2} - \frac{v_2 - v_3}{4} = 0 \quad (1)$$


At v_3 , $i_3 + i_4 = -2$

$$\frac{v_2}{4} + \frac{v_1 - v_3}{6} = -2 \quad (2)$$

At v_1 , $i_s - i_1 - i_4 = 0$

But i_s can't be expressed in terms of v_1

Get stuck here

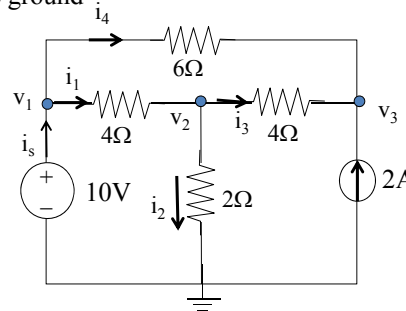

Do we really need a third KCL equation at v_1 ?

How many unknown node voltages?

$$v_1 = ? \quad v_1 = 10V$$

So we only have two unknowns, v_2 and v_3

(1) and (2) are sufficient to solve for v_2 and v_3

Case 2: One voltage source is not connected to the ground
 -- A floating voltage source

L9

Now we know $v_1=10V$

Only two equations are needed for v_2 and v_3

$$\text{KCL at } v_2: i_1 - i_2 - i_s = 0 \quad (1)$$

$$\text{KCL at } v_3: i_4 - i_3 + i_s = 0 \quad (2)$$

Same trouble with i_s ,
 can't be expressed in terms of v_2, v_3

Neither (1) nor (2) would yield an equation for v_2, v_3


➤ Approach:

Add up (1) and (2): $i_1 - i_2 + i_4 - i_3 = 0 \quad (3)$


What is this equation (3)?

❖ (3) is obtained by applying KCL
 at the closed boundary

It includes both nodes v_2 and v_3

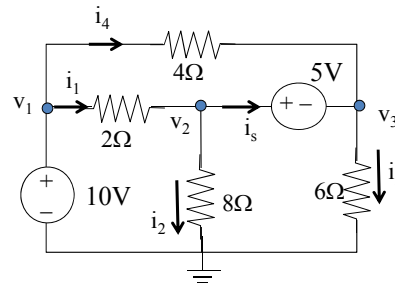

A supernode

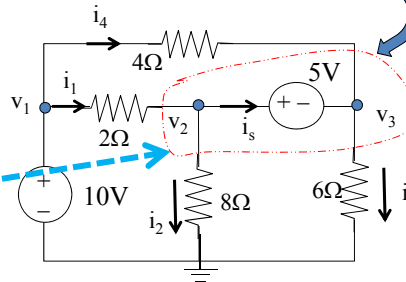

In the future, we don't apply KCL at each node connected
 to a voltage source (such as (1), (2)), then add them up.

L9

We directly make a supernode and apply KCL at the supernode

The currents:

$$i_1 = \frac{10 - v_2}{2}; \quad i_2 = \frac{v_2}{8}; \quad i_3 = \frac{v_3}{6}; \quad i_4 = \frac{10 - v_3}{4}$$


KCL at the super node: $i_1 - i_2 + i_4 - i_3 = 0$

Plug in current expressions

$$\frac{10 - v_2}{2} - \frac{v_2}{8} + \frac{10 - v_3}{4} - \frac{v_3}{6} = 0$$

$$\Rightarrow 15v_2 + 10v_3 = 180 \quad (\text{Eq1})$$

Need a second equation for v_2 and v_3

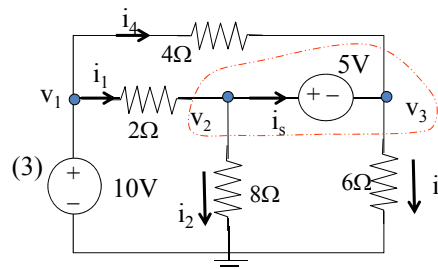

It comes from the 5V voltage source:

$$v_2 - v_3 = 5 \quad (\text{Eq2})$$


Combining (Eq1) and (Eq2),
 v_2 and v_3 can be solved.

$$v_2 = 9.2V; \quad v_3 = 4.2V$$

General steps for nodal analysis with floating voltage sources:

L9

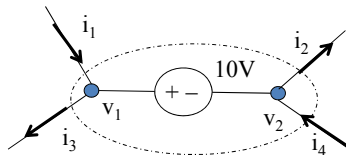- Step 1: Choose ground and assign node voltages
 Step 2: Assign resistor currents with reference direction, express them in terms of node voltages
 Step 3: Form super node to combine two or more nodes. The purpose is to avoid the current of a voltage source in a KCL equation. The super node is made such that the closed boundary does not intersect a voltage source.




KCL at super node:

$$i_1 - i_2 - i_3 + i_4 = 0$$

Additional equation:

$$v_1 - v_2 = 10$$

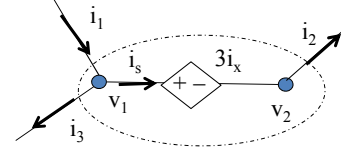

KCL at super node: $i_1 - i_2 - i_3 = 0$

Additional equation: $v_1 - v_2 = 3i_x$

Be careful: $i_s \neq 3i_x$
 Never make equation like: $i_1 - 3i_x - i_3 = 0$

$3i_x$ is a voltage,
not current

Step 4: clean up and solve equations

Example: Find i_0 using nodal analysis. What is the power supplied by the 10V voltage source?

L9

Solution:

Express resistor currents:

$$i_0 = 6v_1; \quad \text{Note that the conductance is given, not resistance}$$

$$i_1 = 5v_2$$

$$i_2 = 3(v_2 - v_3)$$

Need to combine nodes at v_1, v_2 to form a super node

KCL at super node v_1, v_2


$$i_0 + i_1 + i_2 + 2 = 0$$

$$6v_1 + 5v_2 + 3(v_2 - v_3) = -2$$

$$6v_1 + 8v_2 - 3v_3 = -2 \quad (1)$$

At v_3 : $i_2 + 6 = 0$

$$3v_2 - 3v_3 = -6 \quad (2)$$

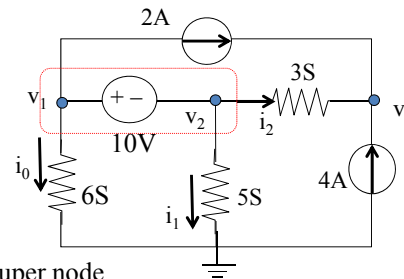

The 3rd equation comes from the 10V voltage source:

$$v_1 - v_2 = 10 \quad (3)$$

$$\begin{bmatrix} 6 & 8 & -3 \\ 0 & 3 & -3 \\ 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -2 \\ -6 \\ 10 \end{bmatrix}$$

$$v_1 = 4.909V; v_2 = -5.091V; v_3 = -3.091V$$

How to find the power supplied by the 10V voltage source?

L9

We have obtained

$$v_1 = 4.909V; v_2 = -5.091V; v_3 = -3.091V$$

With these node voltage, everything can be solved


To find the power by the voltage source, We need the current coming out of the positive terminal

How to find I_s ?

$$\text{By KCL at } v_1: I_s = i_0 + 2 \quad i_0 = 6v_1 = 6 \times 4.909 = 29.454A$$

$$I_s = 31.454A,$$
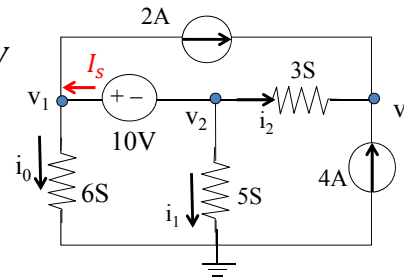
$$\text{Power supplied by } 10V = 10I_s = 314.54W$$



Example: Form 3 equations for the 3 node voltages

L9

Assign resistor currents:

$$i_1 = 2(4 - v_1)$$


$$i_2 = v_1$$

$$i_3 = 2v_2$$

$$i_4 = 2v_3$$

$$i_5 = v_2 - v_3$$

$$i_x = 4(v_1 - v_3)$$

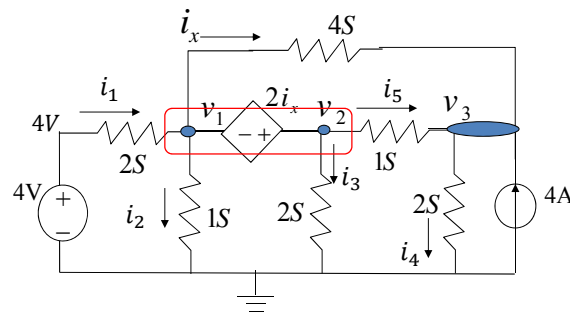

KCL at supernode v_1, v_2 :

$$i_1 - i_2 - i_3 - i_5 - i_x = 0$$

$$2(4 - v_1) - v_1 - 2v_2 - (v_2 - v_3) - 4(v_1 - v_3) = 0$$

$$\boxed{-7v_1 - 3v_2 + 5v_3 = -8} \quad (1)$$

KCL at v_3 : $i_5 - i_4 + i_x + 4 = 0$

$$v_2 - v_3 - 2v_3 + 4(v_1 - v_3) = -4$$

$$\boxed{4v_1 + v_2 - 7v_3 = -4} \quad (2)$$

$$\text{By } \begin{array}{|c|} \hline \diamond \\ \hline \end{array} \begin{array}{c} 2i_x \\ - \\ + \end{array}$$


$$v_2 - v_1 = 2i_x$$

$$v_2 - v_1 = 2(4(v_1 - v_3))$$

$$\boxed{9v_1 - v_2 - 8v_3 = 0} \quad (3)$$


Practice 4: Form 3 equations for the three node voltages

R9

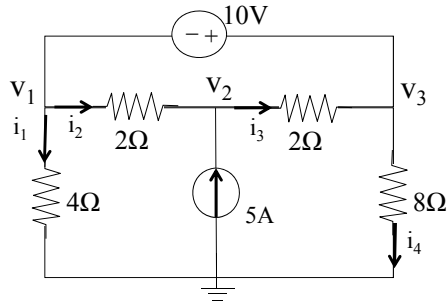

Practice 5: Form 4 equations for the four node voltages

R9

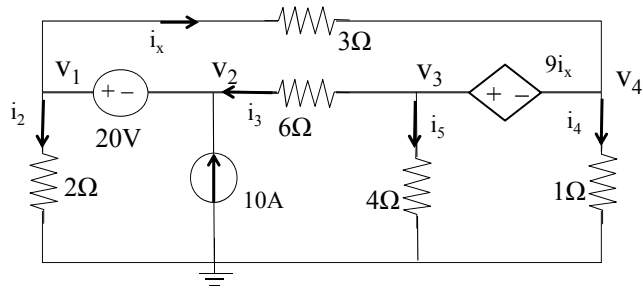

R9

Practice 6: Find v_1 , v_2 , v_3 and i_{dep} 