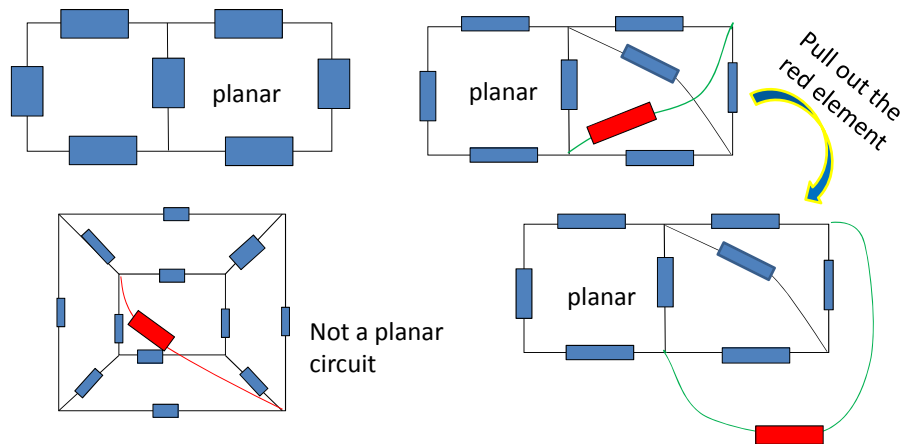


§ 3.4 Mesh analysis - for circuits without current sources

L10

Planar circuit: A circuit that can be drawn in a plane with no branches crossing each other




Mesh analysis can only be applied to planar circuits

Nodal analysis can be applied to any circuit.

Basic concepts: Mesh and mesh current

L10

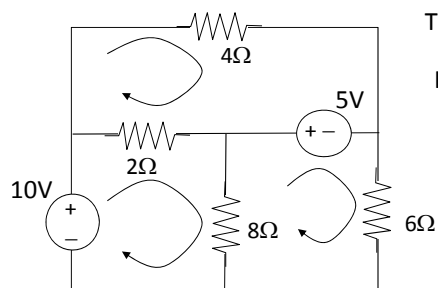Mesh: a loop that does not contain any other loop in it




This circuit has 3 meshes

How many loops?

L10


Mesh Current: Mesh currents are variables assigned to all meshes in a certain direction, so that the current through each element is the algebraic sum of two mesh currents.

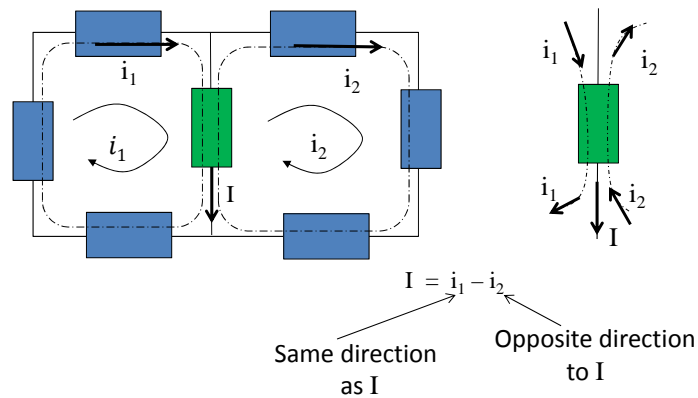For convenience, choose clockwise direction



L10

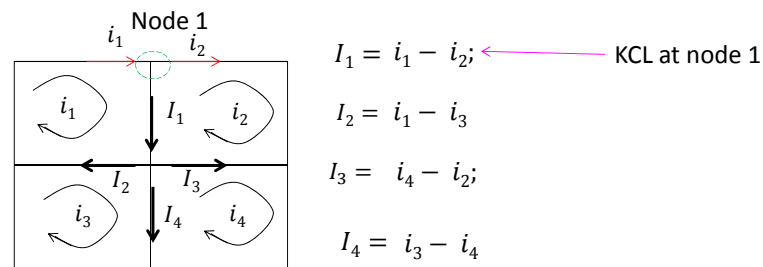In a planar circuit, an element is involved in at most two meshes



Sum of current entering the center node:

$$\begin{aligned} & I_1 - I_2 - I_3 - I_4 \\ &= i_1 - i_2 - i_1 + i_3 - i_4 + i_2 - i_3 + i_4 \\ &= 0 \end{aligned}$$

KCL automatically satisfied


Basic Idea of mesh analysis:

L10

Express branch voltages in terms of mesh currents.
Form equations by applying KVL along the meshes.


Basic step:

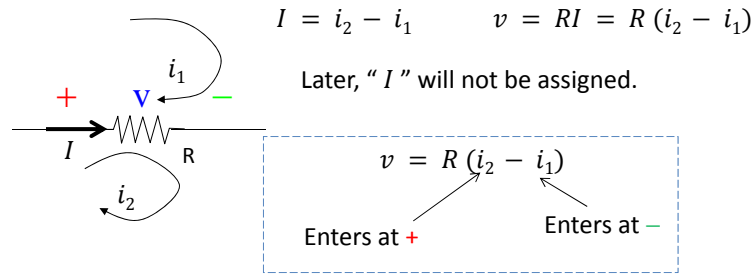Express resistor voltages in terms of mesh currents



Example: Find the mesh currents i_1, i_2


L10

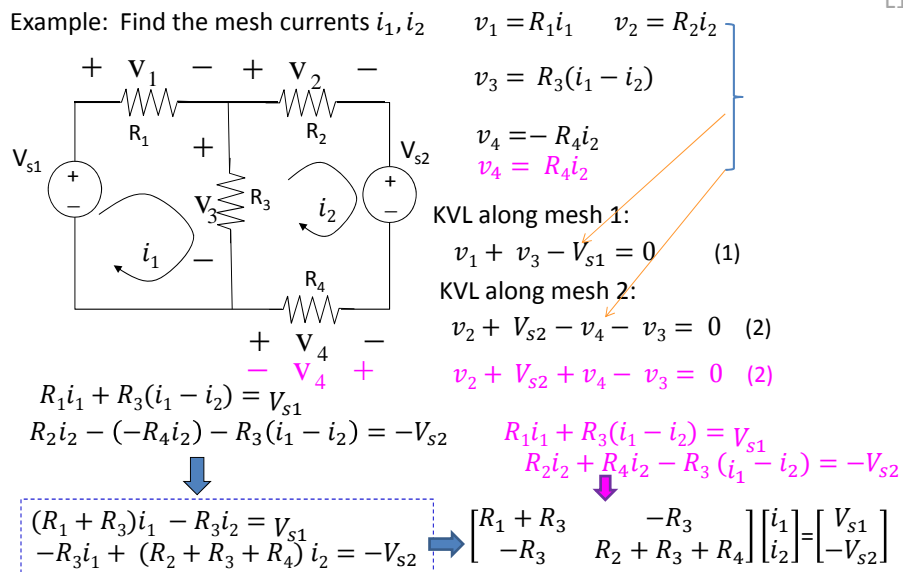

L10

Summary of general steps for circuit without current sources

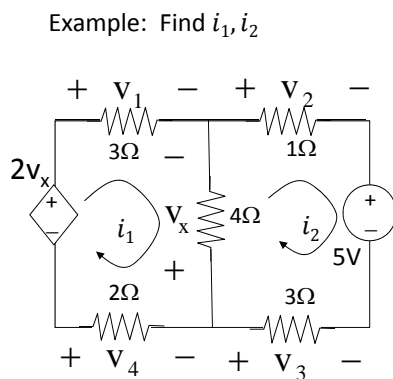- Step 1: Assign mesh currents, i_1, i_2, \dots, i_n
- Step 2: Assign resistor voltages with polarity, and express these voltages in terms of mesh currents
- Step 3: Apply KVL along each mesh to obtain n equations with respect to mesh currents (first in terms of voltages, then plug in the expressions from step 2)
- Step 4: Solve equations for mesh currents. Obtain everything else asked



Express resistor voltages

$$v_1 = 3i_1; \quad v_2 = i_2;$$

$$v_3 = -3i_2; \quad v_4 = -2i_1$$

Why "-"?

$$v_x = 4(i_2 - i_1)$$

KVL along mesh 1:

$$v_1 - v_x - v_4 - 2v_x = 0$$

$$3i_1 - 4(i_2 - i_1) - (-2i_1) - 2 \times 4(i_2 - i_1) = 0$$

$$17i_1 - 12i_2 = 0 \quad (1)$$

KVL along mesh 2:

$$v_2 + 5 - v_3 + v_x = 0$$

$$i_2 + 5 - (-3i_2) + 4(i_2 - i_1) = 0$$

$$-4i_1 + 8i_2 = -5 \quad (2)$$

Solving (1) and (2):


$$i_1 = -0.682A$$

$$i_2 = -0.966A$$

L10

A short-cut for making KVL equation along one mesh:

L10

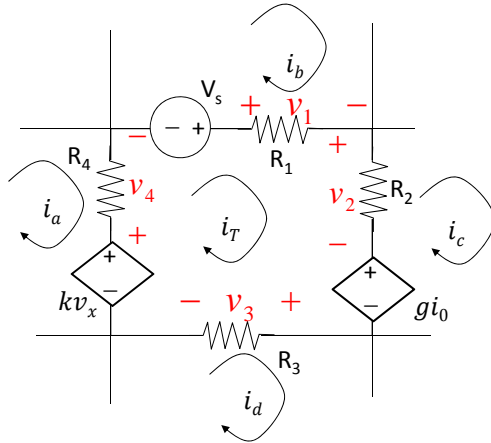

Consider the center mesh
We call it "This mesh"
All resistor voltages are assigned as voltage drop along clockwise direction.

$$\begin{aligned} v_1 &= R_1(i_T - i_b) \\ v_2 &= R_2(i_T - i_c) \\ v_3 &= R_3(i_T - i_d) \\ v_4 &= R_4(i_T - i_a) \end{aligned}$$

The current of "This mesh", i_T has positive sign,
Other mesh currents all have negative sign.

KVL along "This mesh": $-V_s + v_1 + v_2 + gi_0 + v_3 - kv_x + v_4 = 0$

All resistor voltages have positive signs. Plug in the expression:


$$-V_s + R_1(i_T - i_b) + R_2(i_T - i_c) + gi_0 + R_3(i_T - i_d) - kv_x + R_4(i_T - i_a) = 0$$

In the future, you don't need to assign resistor voltages.

You can directly write the equation. The simple rule is that

voltage drop of $R_k = R_k$ (current of This mesh - current of other mesh)

Previous example:

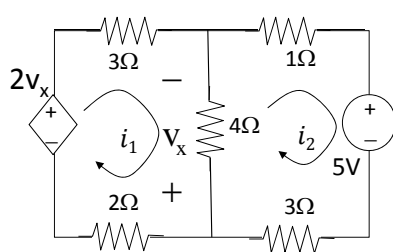

You must express controlling voltage or current: $v_x = 4(i_2 - i_1)$

Clockwise along mesh 1:

Voltage drop across 3Ω : $3i_1$
Voltage drop across 4Ω : $4(i_1 - i_2)$
Voltage drop across 2Ω : $2i_1$

KVL along mesh 1:

$$3i_1 + 4(i_1 - i_2) + 2i_1 - 2v_x = 0$$

Clockwise along mesh 2:

Voltage drop across 1Ω : i_2
Voltage drop across 3Ω : $3i_2$
Voltage drop across 4Ω : $4(i_2 - i_1)$

KVL along mesh 2:

$$i_2 + 5 + 3i_2 + 4(i_2 - i_1) = 0$$


Plug in v_x and simplify:

$$\begin{aligned} 17i_1 - 12i_2 &= 0 \\ -4i_1 + 8i_2 &= -5 \end{aligned}$$

L10


Practice 1: Form 3 mesh equations for i_1, i_2, i_3

R10

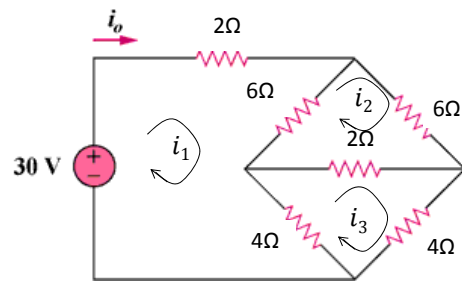


Practice 2: Form 3 mesh equations for i_1, i_2, i_3

R10

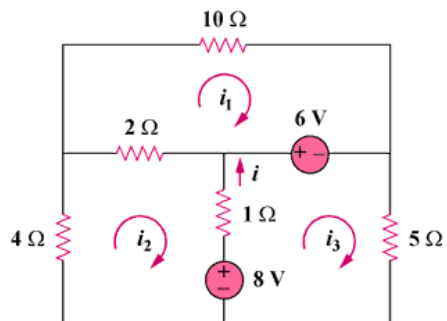


Practice 3: Form 3 mesh equations for i_1, i_2, i_3

R10

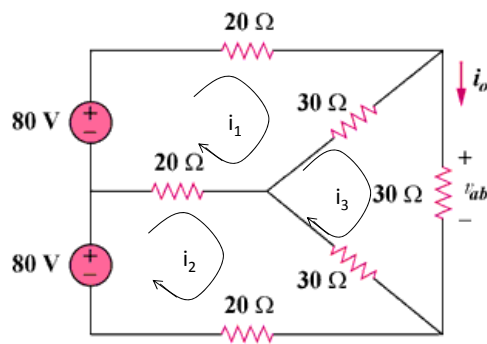

Practice 4: Find i_1, i_2 and v_0

R10

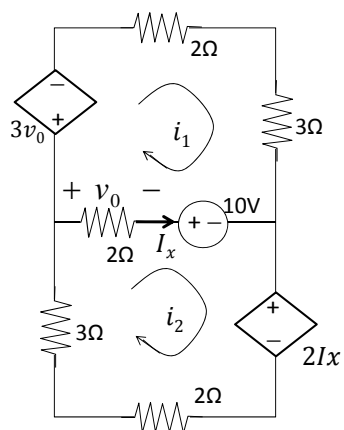

§ 3.5 Mesh analysis with current source


L11

What is the trouble with current source?

Its voltage cannot be expressed in terms of mesh currents

Posing problems for making equations by KVL

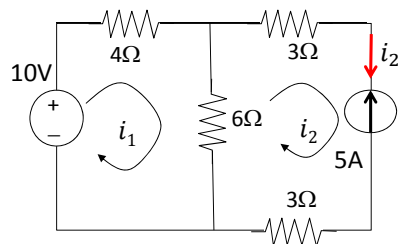Case 1: The current source exists only in one mesh
-- at the boundary of the circuit



What is i_2 ? $i_2 = -5A$

We have only one unknown mesh current i_1

One equation is enough

$$\text{KVL along mesh 1} \quad 4i_1 + 6(i_1 - i_2) = 10 \quad \leftarrow i_2 = -5A$$

$$4i_1 + 6(i_1 + 5) = 10, \quad 10i_1 = -20; \quad i_1 = -2A$$

Case 2: The current source exists as a common branch
of two meshes

L11

All resistor voltages

$$v_1 = 6i_1; \quad v_2 = 2(i_1 - i_2)$$

$$v_3 = 10i_2; \quad v_4 = 4i_2$$

How to express v_{6A} ? Cannot be expressed directly in terms of i_1, i_2

KVL along mesh 1:

$$v_1 + v_2 + v_{6A} = 20 \quad (1)$$

KVL along mesh 2:

$$v_3 + v_4 - v_{6A} - v_2 = 0 \quad (2)$$


Both equations has v_{6A} (and v_2) but with different signs.

$$\text{Adding up (1) and (2):} \quad v_1 + v_3 + v_4 = 20 \quad (3)$$

What is (3)? It is the KVL along the outer loop. Called a super mesh

In the future, we don't make KVL along individual meshes (with current sources) and add them up.

We make KVL along a super mesh directly.

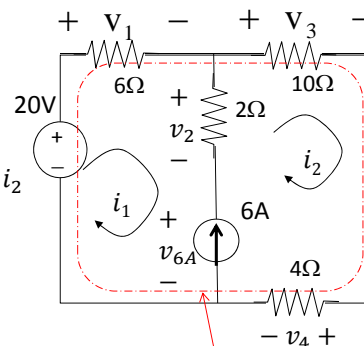

Super mesh: is formed by combining two or more meshes

L11

All resistor voltages

$$v_1 = 6i_1; \quad v_2 = 2(i_1 - i_2)$$

$$v_3 = 10i_2; \quad v_4 = 4i_2$$

KVL along super mesh:

$$v_1 + v_3 + v_4 = 20 \quad (3)$$

Plug in voltage expressions:

$$6i_1 + 10i_2 + 4i_2 = 20 \quad (\text{Eq1})$$

Need another equation for i_1 and i_2 .


It comes from the 6A current source:

$$i_2 - i_1 = 6 \quad (\text{Eq2})$$

You can also consider (Eq2) as KCL at node a.

Solving (Eq1) and (Eq2) to obtain:


$$i_1 = -3.2A; \quad i_2 = 2.8A$$

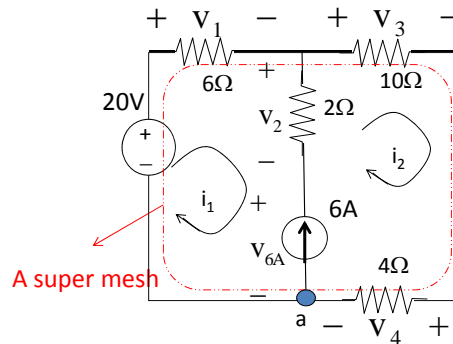

The purpose of making a super mesh is to avoid the voltage of a current source in a KVL equation.

A short-cut for making KVL equation along super mesh:

L11

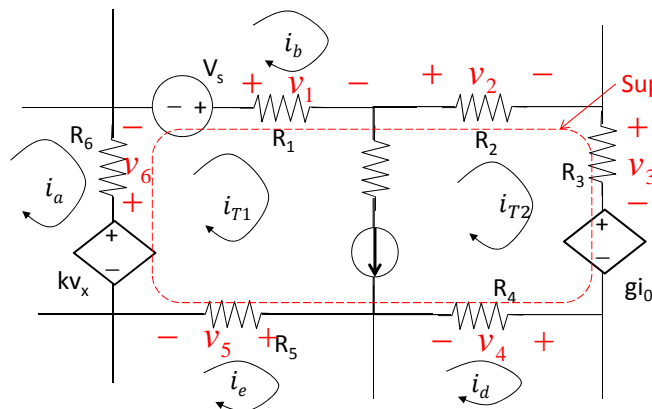

$$v_1 = R_1(i_{T1} - i_b)$$

$$v_2 = R_2(i_{T2} - i_b)$$

$$v_3 = R_3i_{T2}$$

$$v_4 = R_4(i_{T2} - i_d)$$

$$v_5 = R_5(i_{T1} - i_e)$$

$$v_6 = R_6(i_{T1} - i_a)$$

Let $i_{T1}, i_{T2}, i_{T3}, \dots$ be the mesh currents inside the super mesh. Voltage drop of a resistor along clockwise direction: $v = R(i_{Tk} - \text{other mesh current})$,

i_{Tk} is one of i_{T1}, i_{T2}, \dots . For example, across R_1 : $v_1 = R_1(i_{T1} - i_b)$

$$\text{KVL along super mesh: } -V_s + V_1 + V_2 + V_3 + gi_0 + V_4 + V_5 - kv_x + V_6 = 0$$

$$-V_s + R_1(i_{T1} - i_b) + R_2(i_{T2} - i_b) + R_3i_{T2} + gi_0 + R_4(i_{T2} - i_d) + R_5(i_{T1} - i_e) - kv_x + R_6(i_{T1} - i_a) = 0 \quad (1)$$

Example: Use mesh analysis to find i_0 and v_0 :

L11

Solution 1:

Assign mesh currents, i_1, i_2, i_3

Assign resistor voltages: v_1, v_2, v_3, v_4

Express resistor voltages:

$$v_1 = -4i_1 \quad v_2 = 2(i_1 - i_3)$$

$$v_3 = 8i_3 \quad v_4 = 10(i_2 - i_1)$$

KVL along mesh 1:

$$-v_1 + v_2 - v_4 = 0$$

$$-(-4i_1) + 2(i_1 - i_3) - 10(i_2 - i_1) = 0$$

$$16i_1 - 10i_2 - 2i_3 = 0 \quad (1)$$

Due to the current source $3i_0$, need to combine mesh 2 and mesh 3 into a super mesh KVL along super mesh:

$$v_4 - v_2 + v_3 = 60$$

$$10(i_2 - i_1) - 2(i_1 - i_3) + 8i_3 = 60$$

$$-12i_1 + 10i_2 + 10i_3 = 60 \quad (2)$$

By the $3i_0$ current source:


$$i_3 - i_2 = 3i_0 \quad \leftarrow i_0 = i_1$$

$$i_3 - i_2 = 3i_1$$

$$3i_1 + i_2 - i_3 = 0 \quad (3)$$

$$\text{Solving (1),(2),(3)} \quad i_0 = i_1 = 1.731A,$$
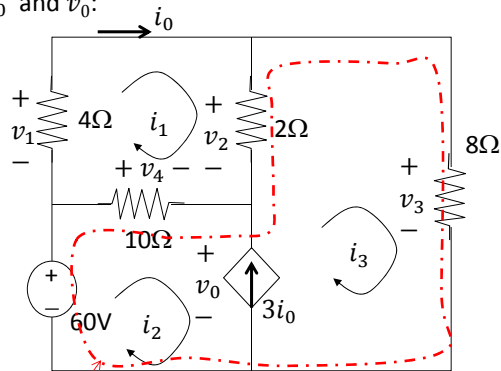
$$i_1 = 1.731A, i_2 = 1.442A; i_3 = 6.635A$$



We have found

$$\begin{aligned} i_1 &= 1.731A, \\ i_2 &= 1.442A \\ i_3 &= 6.635A \end{aligned}$$

You can use these currents to find all resistor voltages.

Question: How to compute v_0 ?


Answer: By KVL

KVL along mesh 2,

$$v_4 + v_0 - 60 = 0$$

$$v_0 = 60 - v_4 \quad v_4 = 10(i_2 - i_1) = -2.89V$$

$$v_0 = 62.89V$$

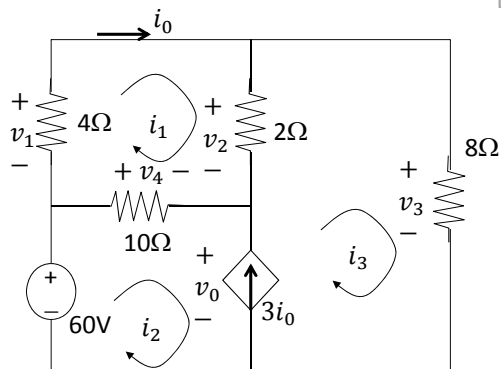

L11

Solution 2:

Using shortcut to make KVL equations:

KVL along mesh 1


$$+4i_1 + 2(i_1 - i_3) + 10(i_1 - i_2) = 0$$

$$16i_1 - 10i_2 - 2i_3 = 0 \quad (1)$$

KVL along super mesh:

$$+10(i_2 - i_1) + 2(i_3 - i_1) + 8i_3 = 60$$
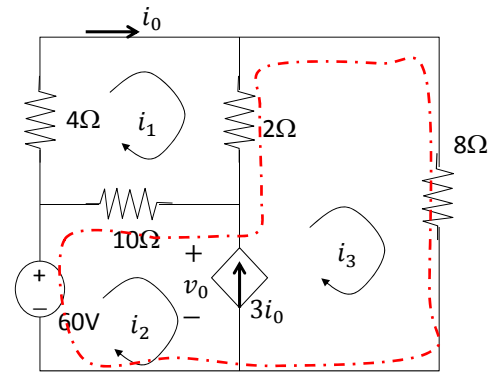
$$-12i_1 + 10i_2 + 10i_3 = 60 \quad (2)$$



Same as solution 1, the 3rd equation comes from the $3i_0$ current source:

$$i_3 - i_2 = 3i_0 = 3i_1$$

$$3i_1 + i_2 - i_3 = 0 \quad (3)$$

Example: Find i_0 using mesh analysis

An overview:

Need 3 equations for i_1, i_2, i_3


One from mesh 2; (1)

One from Mesh 3; (2)

One from the dependent current source:

$$i_1 = 0.5i_0 = -0.5i_2$$

$$i_1 + 0.5i_2 = 0 \quad (3)$$

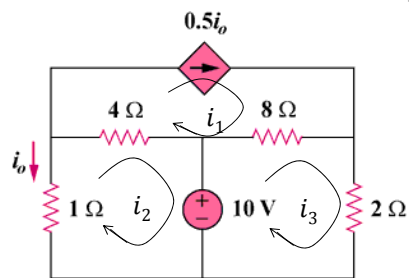

$$\begin{aligned} \text{KVL along mesh 2: } i_2 + 4(i_2 - i_1) + 10 &= 0 \\ -4i_1 + 5i_2 &= -10 \quad (1) \end{aligned}$$

$$\begin{aligned} \text{KVL along mesh 3: } 8(i_3 - i_1) + 2i_3 - 10 &= 0 \\ -8i_1 + 10i_3 &= 10 \quad (2) \end{aligned}$$


All 3 equations together:

$$\begin{bmatrix} -4 & 5 & 0 \\ -8 & 0 & 10 \\ 1 & 0.5 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -10 \\ 10 \\ 0 \end{bmatrix}$$

$$\begin{aligned} i_1 &= 0.7143A = 5/7A \\ i_2 &= -1.4286A = -10/7A \\ i_3 &= 1.5714A = 11/7A \\ i_0 &= -i_2 = 1.4286A \end{aligned}$$


Practice 5: Find the mesh currents and v_x

R11

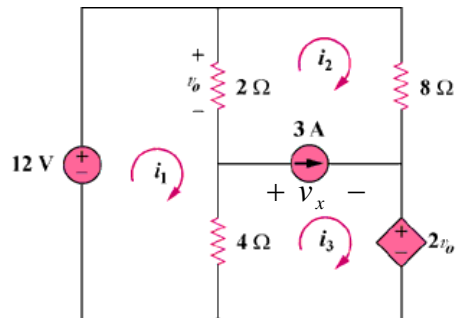

Practice 6: Find i_o and v_o :

L11

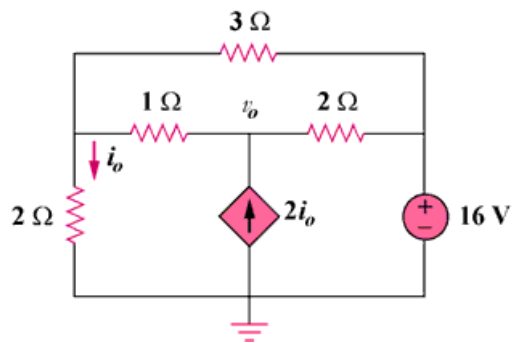

Practice 7: Use mesh analysis to find i_x and v_0 :

R11

