

L12

Chapter 4 Circuit Theorems

From Chapter 2: Basic laws -- Foundations.

From Chapter 3: Mesh analysis, Nodal analysis.

Systematic tools, can be used for complex circuits.

More useful tools to be learned in Chapter 4:

1. Linearity
2. Superposition
3. Source transformation
4. Thevenin's Theorem
5. Norton's Theorem
6. Maximum power transfer

Could be more tricky than Chapters 2,3.


- There may exist several solutions to one problem
- Need to develop insight to plan solutions ahead and identify the simplest solution

L12


§4.2 Linearity

Basic concepts: Input, output


Input: the cause, or excitation,

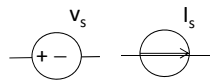

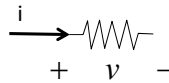Output: voltage or current of any element



Example:

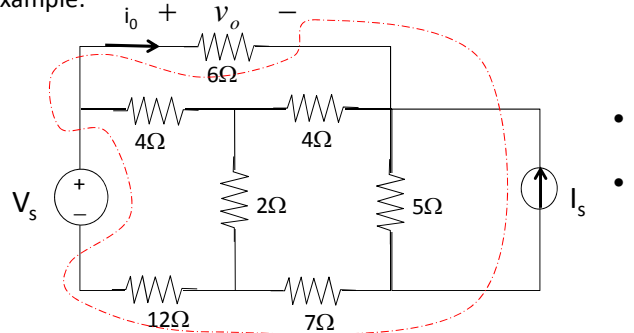


- Two inputs
 V_s, I_s
- Two outputs:
 i_0, v_0


You can imagine pulling out the inputs, outputs and put the rest inside a box

L12

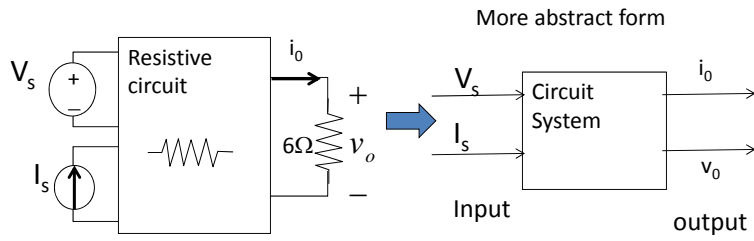Pull out the inputs, outputs and put the rest inside a box




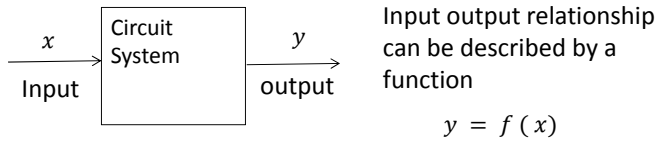First consider a circuit with one input, one output:



L12

Input output relationship: $y = f(x)$:

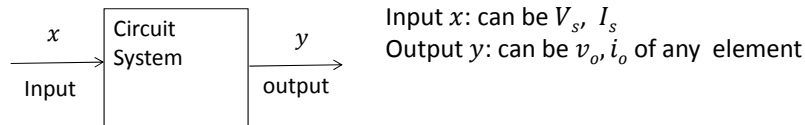

Linearity: The input output relationship is said to be linear if $y = kx$ for a certain constant k .


Two implications: Linearity = homogeneity + additivity

Homogeneity: If $x_1 \Rightarrow y_1$, then $\alpha x_1 \Rightarrow \alpha y_1$

Additivity: If $x_1 \Rightarrow y_1$,
 $x_2 \Rightarrow y_2$, } then $x_1 + x_2 \Rightarrow y_1 + y_2$

L12

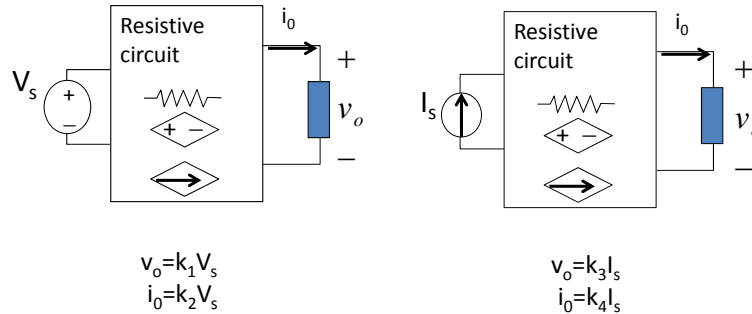Linear circuit: the input-output relationship of a resistive circuit is linear.



Linearity is the simplest relationship between input and output
It is predictable: double efforts → double results

If $V_s = 5V \rightarrow v_o = 3V$

Then $V_s = 10V \rightarrow v_o = 6V$


$V_s = 2.5V \rightarrow v_o = 1.5V$

We first use one example to demonstrate linearity

Later on, we use this linear property to analyze circuits

L12

Example:

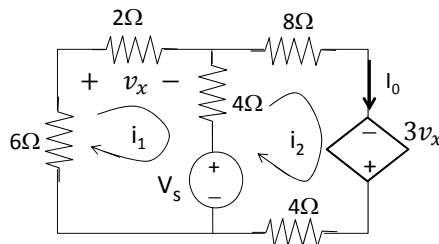

Input: V_s (x)
Output: I_o (y)

A resistive circuit.

There exists a k such that

$I_o = kV_s$ ($y = kx$)

What is k ?

- Use mesh analysis to find k .

Assign mesh currents i_1, i_2 .

$v_x = 2i_1 \Rightarrow 3v_x = 6i_1 \quad I_o = i_2$

KVL along mesh 1: $2i_1 + 4(i_1 - i_2) + V_s + 6i_1 = 0$
 $\Rightarrow 12i_1 - 4i_2 = -V_s \quad (1)$

KVL along mesh 2: $8i_2 - 3v_x + 4i_2 - V_s + 4(i_2 - i_1) = 0$
 $8i_2 - 6i_1 + 4i_2 - V_s + 4(i_2 - i_1) = 0$
 $\Rightarrow -10i_1 + 16i_2 = V_s \quad (2)$

$(1) \cdot 5 + (2) \cdot 6 \rightarrow 76i_2 = V_s$

$I_o = i_2 = \frac{1}{76} V_s$ Compare with $I_o = kV_s$

$k = \frac{1}{76}$

$V_s = 1V \rightarrow I_o = \frac{1}{76} A$

$V_s = 4V \rightarrow I_o = \frac{4}{76} A$

L12


For this circuit, the input output relationship is derived by solving the output from the input

Given input \Rightarrow find output, The direct approach

For some circuit, it is more convenient to find the input from the output.

Given output \Rightarrow find input, The backward approach

In general,

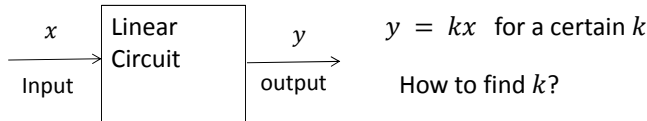

If you know any pair of input and output, $(x, y) = (x_0, y_0)$

Then $y_0 = kx_0 \Rightarrow k = \frac{y_0}{x_0}$

Just need one pair (x_0, y_0) to determine k

Direct approach:

Assume $x = x_0$, find $y = y_0$


Backward approach:

Assume $y = y_0$, find $x = x_0$

R7


A practice problem from Chapter 2:

Practice 20: Find V_s for the circuit

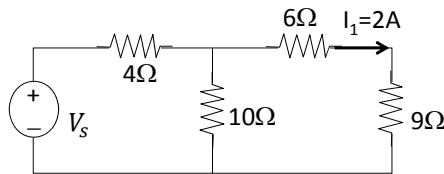


V_s is the input, the cause
 I_1 is the output, the result

Assume $I_1 = 2A$, $V_s = ?$

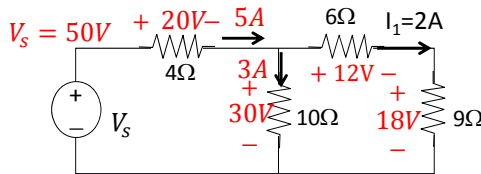

L12

Example:

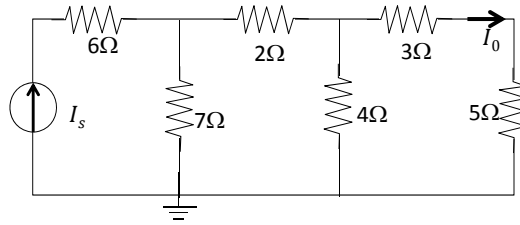


Input: $x = I_s$
 Output: $y = I_0$
 Find k such that
 $I_0 = kI_s$
 Use backward
 method

Assume $I_0 = 1A$, $I_s = ?$ You may assume I_0 to be any number.


With I_s solved, you have $k = \frac{y}{x} = \frac{I_0}{I_s}$

L12

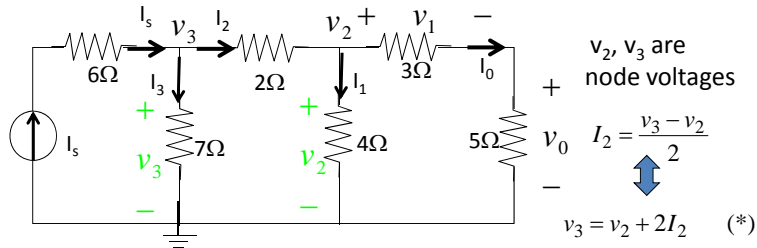Solution: Assign additional variables as in the following circuit:



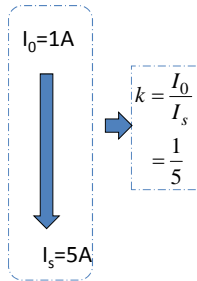Starting with $I_0=1A$
 By Ohm's law: $v_0=5I_0=5V$; $v_1=3I_0=3V$
 By KVL: $v_2=v_0+v_1=5+3=8V$
 By Ohms Law: $I_1=v_2/4=2A$
 By KCL at v_2 : $I_2=I_0+I_1=1+2=3A$
 By (*): $v_3=v_2+2I_2=8+2*3=14V$
 By Ohms Law: $I_3=v_3/7=14/7=2A$
 By KCL at v_3 : $I_s=I_2+I_3=3+2=5A$




Conclusion:
 The input-output relationship is
 $I_0 = kI_s = 0.2I_s$
 If $I_s=15A$, then
 $I_0=0.2*15=3A$
 If $I_s=10A$, then
 $I_0=0.2*10=2A$

With $I_0=0.2I_s$, you can find output I_0 for any input I_s
 You can also find the input I_s for any output I_0

L12


A simple demonstration:

Suppose $I_0 = 1A$, $I_s = ?$

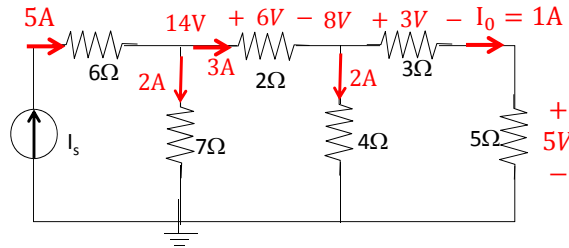

For $I_0 = 1A$,
 $I_s = 5A$,
 $k = \frac{I_0}{I_s} = 0.2$

What if I_s is replaced by V_s ?

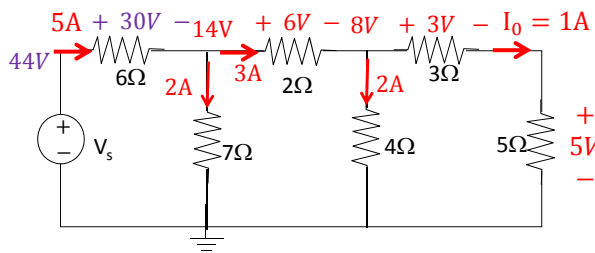


For $I_0 = 1A$,
 $V_s = 44V$,
 $k = \frac{I_0}{V_s} = \frac{1}{44}$


L12

§4.3 Superposition -- About the relationship between one output and several inputs

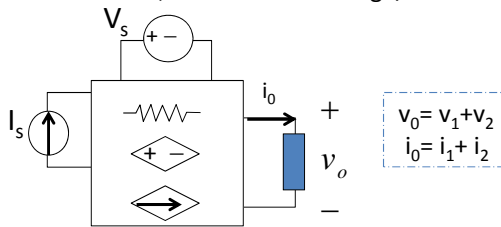
Superposition principle: the voltage across (or current through) an element in a linear circuit, is the sum of voltage/current due to each independent source alone.



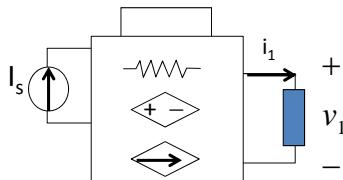Due to I_s alone: turn off V_s
 Set $V_s = 0 \Leftrightarrow$ replace voltage source with short circuit



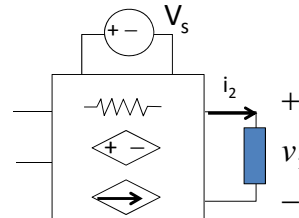Due to V_s alone: turn off I_s
 Set $I_s = 0 \Leftrightarrow$ replace current source with open circuit




Key points: when you examine the effect due to one source, turn off the other sources

L12


- Turn off voltage source with short circuit
- Turn of current source with open circuit

Example : Find the output v .

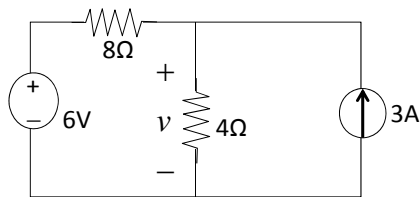


$$v = v_1 + v_2 = 2 + 8 = 10V$$

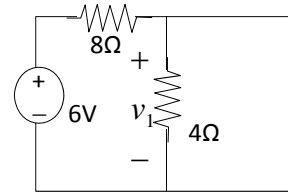Step 1: Due to 6V alone
– turn off 3A with open circuit



By voltage division: $v_1 = \frac{4}{4+8} \times 6 = 2V$

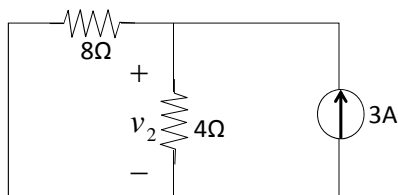Step 2: Due to 3A – turn off 6V with short circuit



By equivalent resistance and ohm's law


$$\begin{aligned} v_2 &= (8 // 4) \times 3 \\ &= \frac{4 \times 8}{4+8} \times 3 = 8V \end{aligned}$$

Superposition breaks down a circuit into several circuits with only one independent source – typically can be solved with simple methods in Chapter 2.

L12

R12

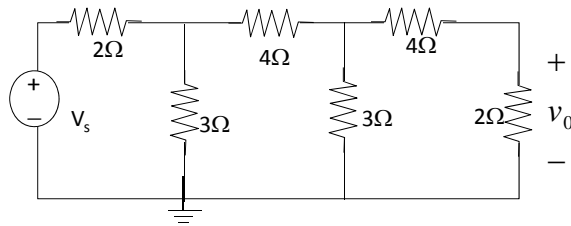Practice 1: Find v_0 for $V_s=27V$ by linearity




Step 1: Find k such that $v_0=kV_s$ by assuming $v_0=$ some value

Step 2: For $V_s=27V$, $v_0= k V_s$


R12

Practice 2: Find i using linearity

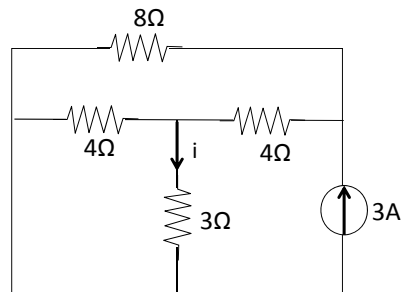


R12

Practice 3: Find i using superposition.

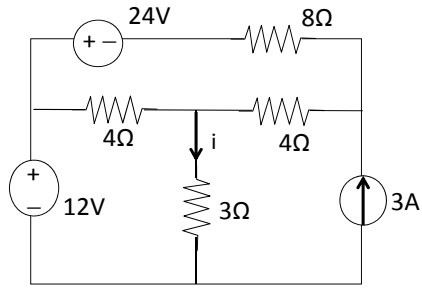


R12

Practice 4: Find i using superposition.

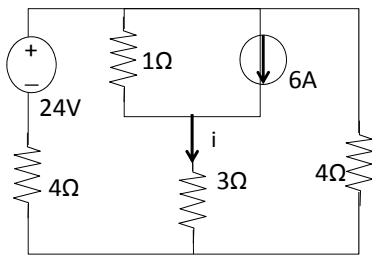


Example: Find I_0 using superposition.


L13

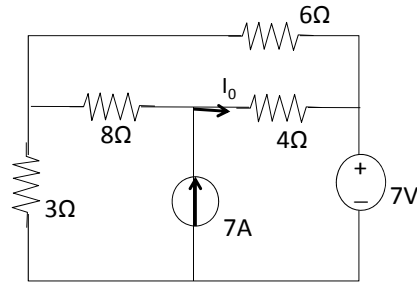

Due to 7V:

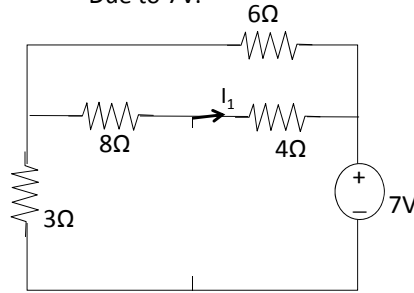

Due to 7A:





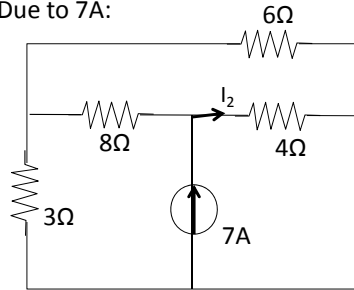


Due to 7V: replace 7A with open circuit
Due to 7A: replace 7V with short circuit

$$I_0 = I_1 + I_2$$


Due to 7A:

L13

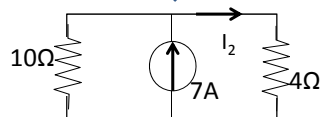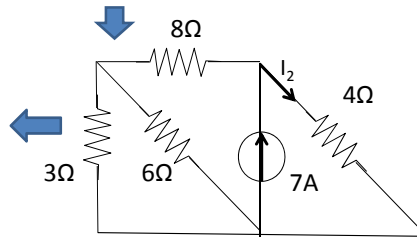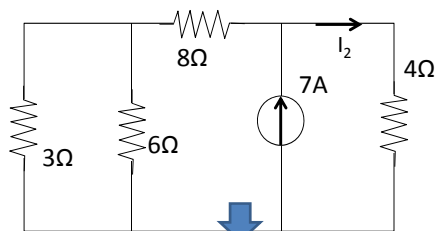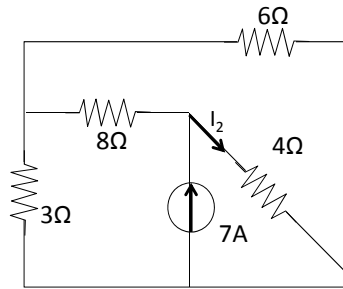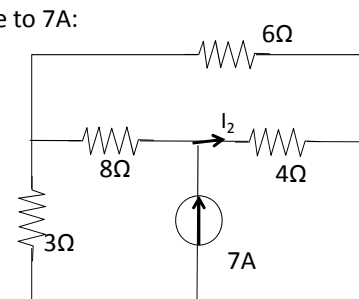

$$I_2 = \frac{10}{10 + 4} \times 7 = 5A$$

L13

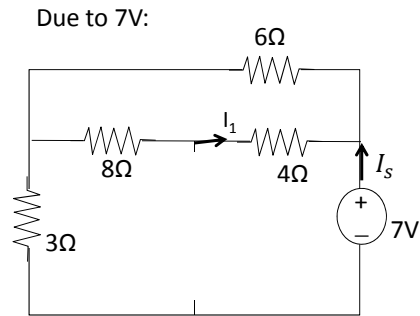

R_{eq} with respect to 7A:

$$R_{eq} = 3 + 6 // (8 + 4) = 7\Omega$$

$$I_s = 1A$$

By current division:

$$I_1 = -\frac{6}{8 + 4 + 6} I_s = -0.333A$$


Going back to the original circuit: $I_0 = I_1 + I_2 = 5 - 0.333 = 4.667A$

L13


Superposition with dependent sources:

For circuit with dependent sources, keep the dependent sources. They cannot be turned off. They are not input

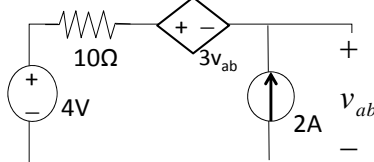Example: Find v_{ab} using superposition:




$$v_{ab} = v_1 + v_2 = 1 + 5 = 6V$$

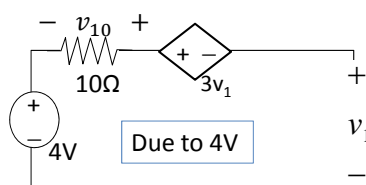

By KVL: $3v_1 + v_1 = 4 + v_{10}$,

$$v_{10} = 0,$$

$$v_1 = 1V$$

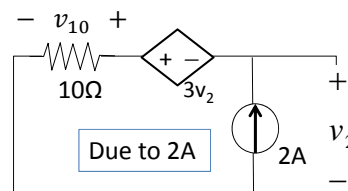


$$3v_2 + v_2 = v_{10} = 2 \times 10 = 20V$$

$$v_2 = 5V$$

§ 4.4: Source transformation


L13

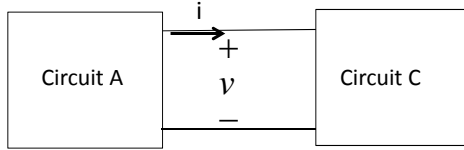A general situation: you can separate a circuit as the connection of two parts.



You may need to make change to one part,
But want to ensure this change does not affect the other part

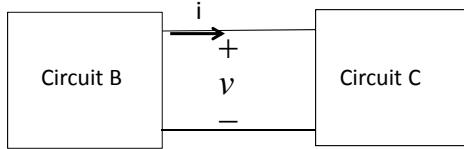For circuit A, you can obtain a function $v = f(i)$
If there is another circuit B, with the same $v \sim i$ relationship,
You can replace Circuit A with Circuit B without affecting Circuit C




All variables in Circuit C are unchanged,
But the variables in Circuit A may not exist in Circuit B.


Sometimes you need to replace a complex circuit with a simpler one; as with Thevenin's equivalent
Sometimes with one which is more convenient for analysis as with source transformation

L13

Compare the two connections:

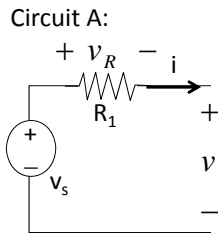

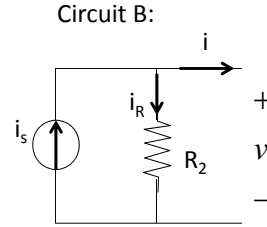What is the $v \sim i$ relationship for each circuit?
How to express v in terms of i ?



By KVL,

$$v = v_s - v_R = v_s - R_1 i$$

$$v = v_s - R_1 i$$

By KCL, $i_R = i_s - i$

$$v = R_2 i_R = R_2 i_s - R_2 i$$


$$v = R_2 i_s - R_2 i$$

To have the same $v \sim i$ relationship: $R_1 = R_2, v_s = R_2 i_s$

L13

Conclusion:

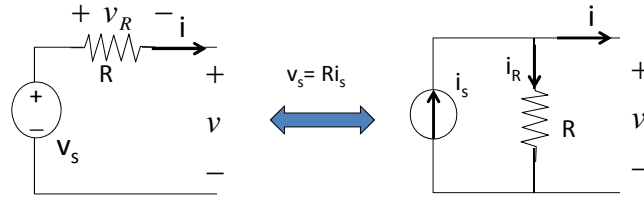The following two connections are equivalent



If you replace one with another, the rest of the circuit will not be affected.

However, be careful:


The voltages across resistor R in the two circuits are different;

The currents through R in the two circuits also differ.

L13

Extension to dependent sources:

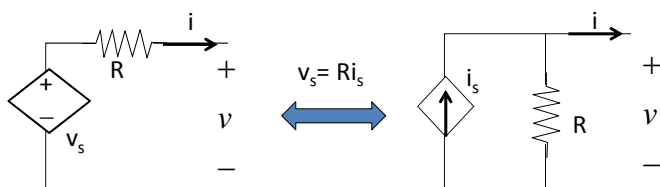The following two connections are equivalent





For example, if $i_s = kv_x$, then $v_s = Ri_s = Rkv_x$

If $v_s = ki_0$, then $i_s = ki_0/R$

The rule: if you put the two sources side by side, the arrow of the current source points from $-$ to $+$ of the voltage source

L13

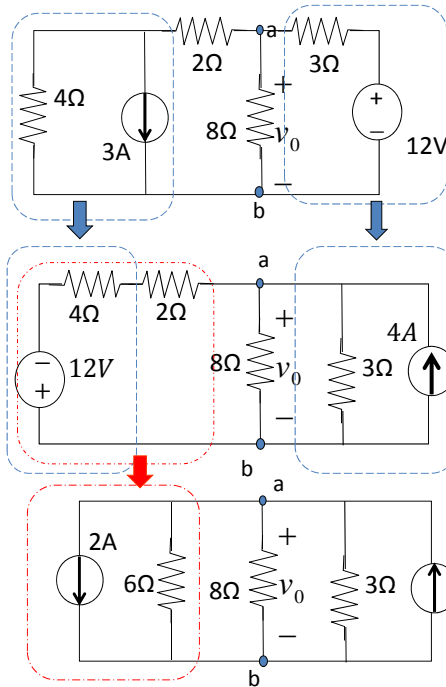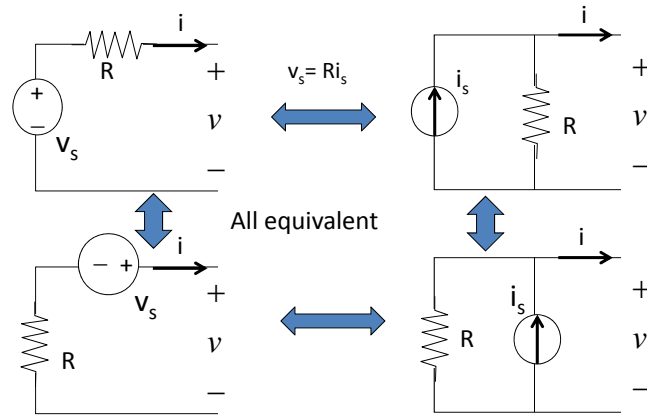

Example: Find the voltage v_0 using source transformation


L13

Caution:
Need to keep the two nodes "a" and "b" so that v_0 is kept after every change


After these transformations, 4Ω and 2Ω can be combined, 3Ω and 8Ω can be combined. Reducing the number of elements

When everything in parallel, you can rearrange the elements without changing the voltage and branch current.

L13

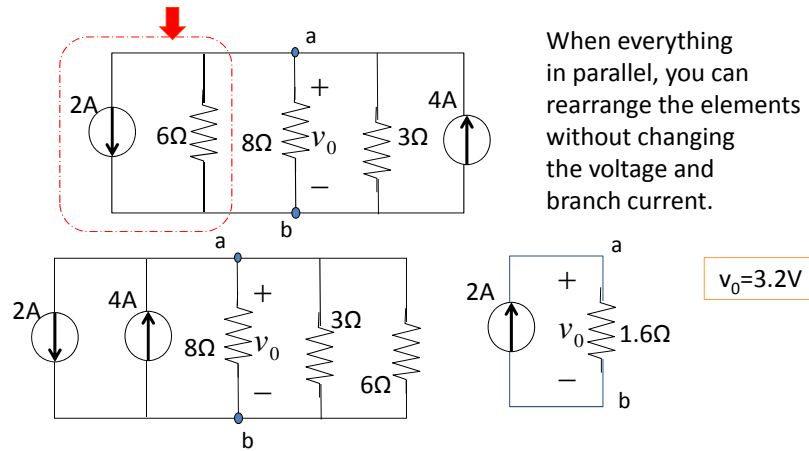

L13

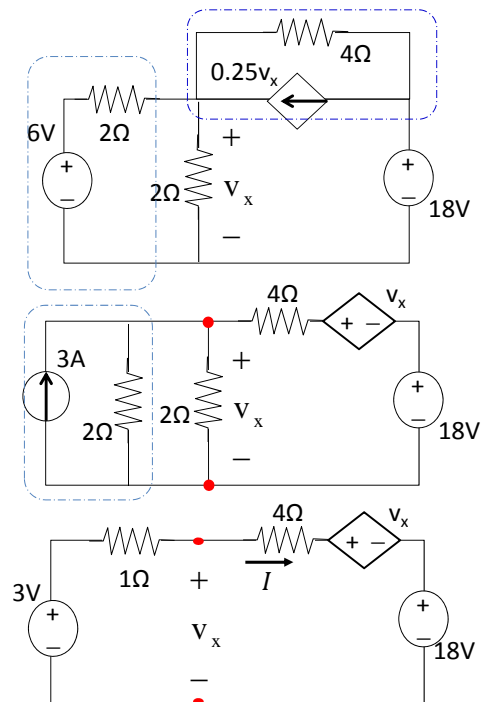Example: Find v_x

Approach 1:

Convert to a circuit with one loop.

$$\text{Express } v_x: \quad v_x = 3 - I$$

KVL around loop:


$$I + 4I + v_x + 18 - 3 = 0$$

Plug in $v_x = 3 - I$



$$I + 4I + 3 - I + 18 - 3 = 0$$

$$4I = -18 \quad I = -4.5A$$

$$v_x = 3 - I = 3 - (-4.5) = 7.5V$$

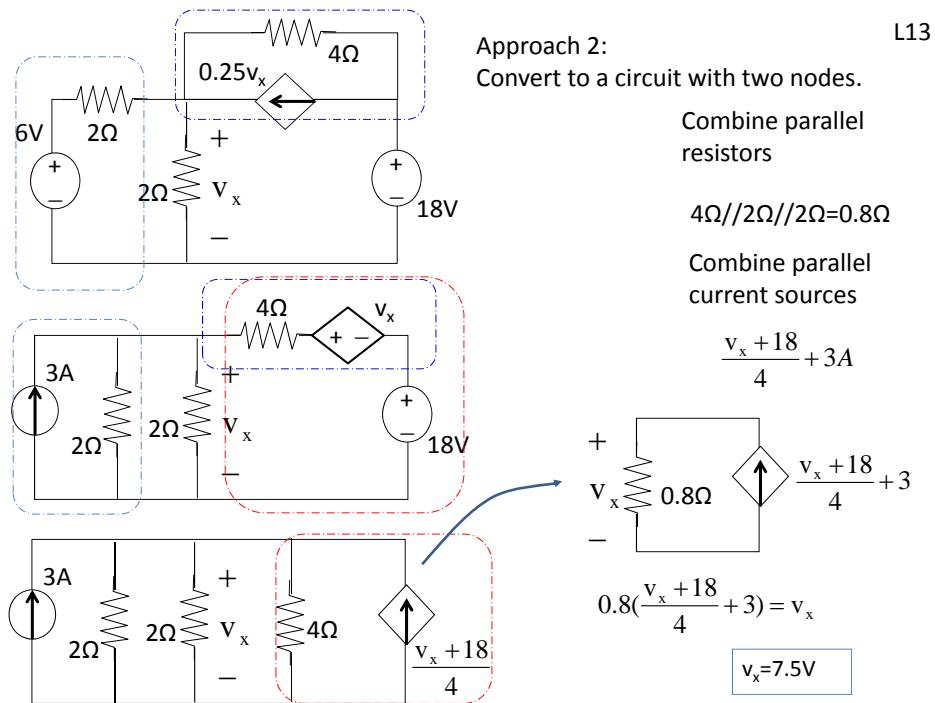


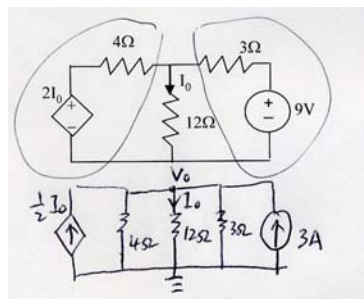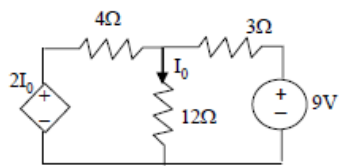2. (4pts) Use source transformation to determine I_0




KCL at V_0 $\frac{V_0}{4} + \frac{V_0}{12} + \frac{V_0}{3} = 3 + I_0/2$
 $I_0 = \frac{V_0}{12}$
 multiply both sides with 24.
 $6V_0 + 2V_0 + 8V_0 = 3 \times 24 + V_0$
 $15V_0 = 3 \times 24, V_0 = \frac{3 \times 24}{15}$
 $I_0 = \frac{V_0}{12} = \frac{3 \times 24}{15 \times 12} = \frac{1}{5} \times \frac{2}{1} = 0.4A$

R13

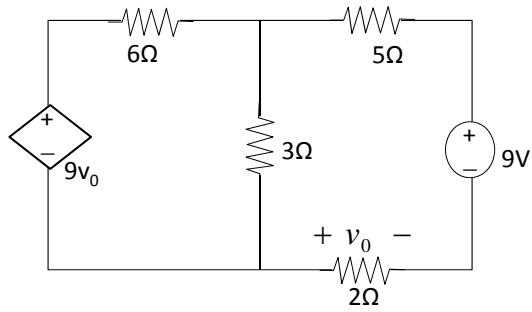Practice 5: Find v_0 using source transformation

R13

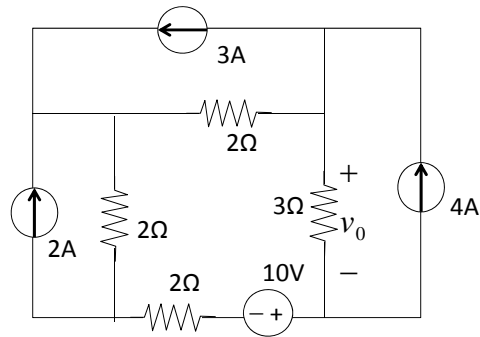Practice 6: Find v_0 using source transformation

R13

Practice 7: Find I_0 using source transformation