
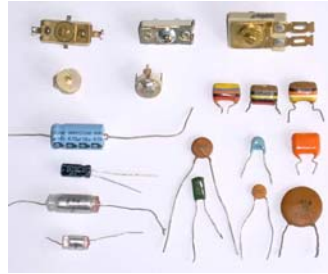


L16

Chapter 6 Capacitors and Inductors


Making preparation for dynamic circuits, which have far more applications than the static circuits we have learned so far.

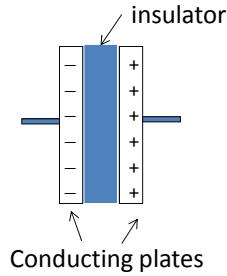§6.2 Capacitors – Store energy in electric field



A capacitor consists of two conducting plates, separated by an insulator.

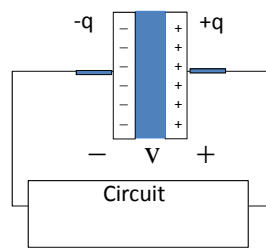- Conduction plates: e.g., Aluminum foil
- Insulator: air, mica, ceramic, etc



L16


- No direct exchange of charge between the plates
- Electrons move from one plate to another via the rest of circuit
- Same amount of positive charge and negative charge: q

Basic Property:

The voltage v is proportional to the charge q .

The capacitance: $C \triangleq \frac{q}{v}$ Measured in Farads (F) \Rightarrow $q = Cv$
 $v = q/C$

Circuit Symbol

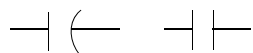


Fixed capacitors



Variable capacitor

L16

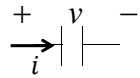Capacitors are passive elements, v and i assigned by passive sign convention



$$\text{Basic property: } q = Cv$$

What is the relationship between v and i ?

Take derivative on both side of $q = Cv$,

$$\frac{dq}{dt} = C \frac{dv}{dt} \quad \Rightarrow \quad i = C \frac{dv}{dt} \quad \Leftarrow \quad \frac{dq}{dt} = i$$

➤ Current is proportional to the time derivative of voltage

If current $i(t)$ is given, $dv = \frac{1}{C} i dt$ $\int_{t_0}^t dv = \int_{t_0}^t \frac{1}{C} i dt$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i dt$$

$$\text{Assume } v(-\infty) = 0, \quad v(t) = \frac{1}{C} \int_{-\infty}^t i dt$$

L16

$$i = C \frac{dv}{dt}$$

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i dt$$

Power delivered:

$$p = v i = Cv \frac{dv}{dt}$$

Energy stored:

$$w(t) = \int_{-\infty}^t p dt = \int_{-\infty}^t Cv \frac{dv}{dt} dt$$

$$= C \int_{-\infty}^t v dv = \frac{1}{2} C (v^2(t) - v^2(-\infty)) = \frac{1}{2} C v^2(t)$$

$$w = \frac{1}{2} C v^2$$

Since $v = q/C$,

$$w = \frac{q^2}{2C}$$

L16

Important things to remember:

1. A capacitor is an open circuit under DC condition

Under DC condition $v(t) = const,$

$$i = C \frac{dv}{dt} = 0 \quad \text{No current through}$$

2. The voltage on a capacitor cannot change abruptly.


As a function of time, $v(t)$ must be continuous

$$v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i dt$$

$i(t)$ is finite, integration must be continuous

3. An ideal capacitor does not dissipate energy

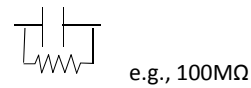4. A real, non-ideal capacitor has a large leakage resistance



L16

In summary:

$$\begin{array}{c} + \\ \xrightarrow{i} | \frac{v}{C} - \end{array} \quad i = C \frac{dv}{dt}; \quad v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i dt$$

Example: Given $C = 2\mu\text{F}$, $i(t) = 6e^{-3000t}\text{mA}$, $v(0) = 2\text{V}$, $v(t) = ?$


In computation, everything should be in standard unit.

$$C = 2\mu\text{F} = 2 \times 10^{-6}\text{F}, \quad i(t) = 6e^{-3000t} \times 10^{-3}\text{A},$$

$$\begin{aligned} v(t) &= v(t_0) + \frac{1}{C} \int_0^t i dt = 2 + \frac{1}{2 \times 10^{-6}} \int_0^t 6e^{-3000t} \times 10^{-3} dt \\ &= 2 + \int_0^t 3e^{-3000t} \times 10^3 dt \\ &= 2 - e^{-3000t} \bigg|_0^t \\ &= 2 - e^{-3000t} - (-1) = 3 - e^{-3000t} \text{V} \end{aligned}$$

L16

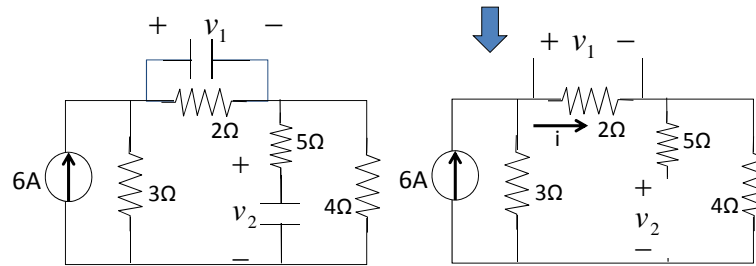Example: Find v_1 and v_2 under DC condition



Under DC condition, capacitors are open circuit.

No current through 5Ω , no voltage drop.

v_2 same as voltage across 4Ω .

Also, 2Ω and 4Ω are in series.


By current division, $i = 6 \cdot (3/9) = 2\text{A}$, $v_1 = 4\text{V}$, $v_2 = 8\text{V}$

L16

§ 6.3 Series and parallel capacitors

– Find equivalent capacitance

Parallel connection:

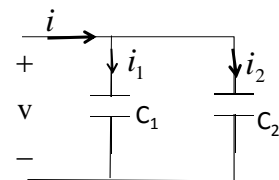

What is the relationship between v and i ?

By KVL, same voltage across C_1, C_2


By property of capacitor:

$$i_1 = C_1 \frac{dv}{dt}; \quad i_2 = C_2 \frac{dv}{dt}$$



By KCL:

$$i = i_1 + i_2 = (C_1 + C_2) \frac{dv}{dt}$$

$$\Rightarrow C_{eq} = C_1 + C_2$$

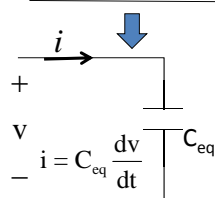

Series connection:

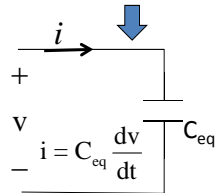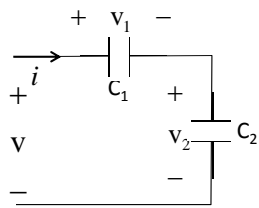

By KCL, same current through C_1, C_2

By property of capacitor:

$$v_1(t) = v_1(t_0) + \frac{1}{C_1} \int_{t_0}^t i \, dt$$

$$v_2(t) = v_2(t_0) + \frac{1}{C_2} \int_{t_0}^t i \, dt$$


By KVL:

$$v(t) = v_1(t) + v_2(t) = v_1(t_0) + v_2(t_0) + \left(\frac{1}{C_1} + \frac{1}{C_2}\right) \int_{t_0}^t i \, dt$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \quad C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

L16

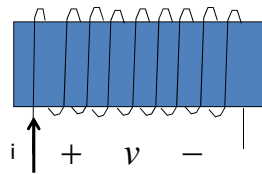6.4 Inductors – store energy in magnetic field




Inductors are usually constructed as a cylindrical coil with many turns of conducting wire around a core

e.g., ferromagnetic core

Also a passive element: current i and voltage v assigned according to passive sign convention.

L16

L16

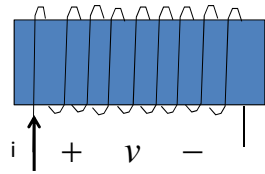

Basic property:



$$v = L \frac{di}{dt}$$

Voltage proportional to the time derivative of current

L : Inductance, measured in Henry (H)
a constant depending on the structure and material

It can be derived:

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v dt \quad \text{Assume } i(-\infty) = 0$$

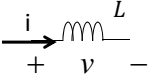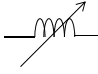Circuit Symbol:   Variable inductor

Energy stored:
$$w = \frac{1}{2} Li^2$$

L16

Important things to remember:

1. An inductor is a short circuit under DC condition

Under DC condition $i(t) = \text{const}$,

$$v = L \frac{di}{dt} = 0 \quad \text{No voltage drop}$$

2. The current on an inductor cannot change abruptly.

As a function of time, $i(t)$ must be continuous

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v dt \quad v(t) \text{ is finite, integration must be continuous}$$

3. An ideal inductor does not dissipate energy


4. A real, non-ideal inductor



L16

§6.5 Series and parallel Inductors

Series connection:

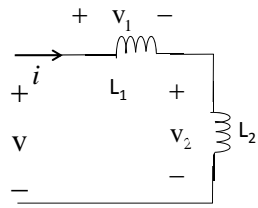

By KCL, same current through \$L_1, L_2\$

By property of inductor:

$$v_1(t) = L_1 \frac{di}{dt}; \quad v_2(t) = L_2 \frac{di}{dt};$$


By KVL:

$$v(t) = v_1(t) + v_2(t) = (L_1 + L_2) \frac{di}{dt}$$

$$\text{Equivalent inductance:} \quad L_{eq} = L_1 + L_2$$

L16

Parallel inductors:

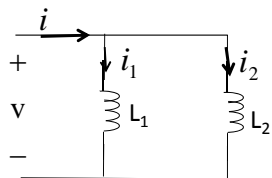

By KVL, same voltage across \$L_1, L_2\$

By property of inductor:

$$i_1(t) = i_1(t_0) + \frac{1}{L_1} \int_{t_0}^t v dt$$

$$i_2(t) = i_2(t_0) + \frac{1}{L_2} \int_{t_0}^t v dt$$

By KCL:



$$i(t) = i_1(t) + i_2(t)$$

$$= i_1(t_0) + i_2(t_0) + \left(\frac{1}{L_1} + \frac{1}{L_2} \right) \int_{t_0}^t v dt$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} \quad L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$$

L16

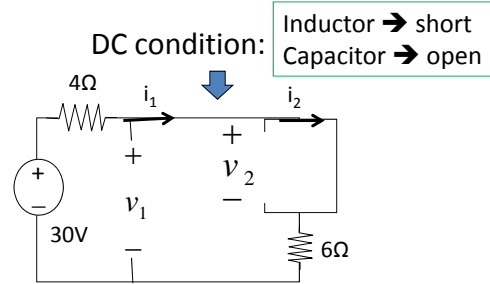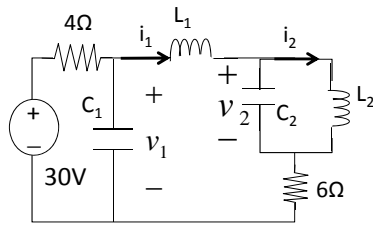Example: Find capacitor voltage and inductor current under DC condition




$$v_2 = 0$$


$$i_1 = i_2 = 30 / (4 + 6) = 3A$$

$$v_1 = 6i_2 = 18V$$

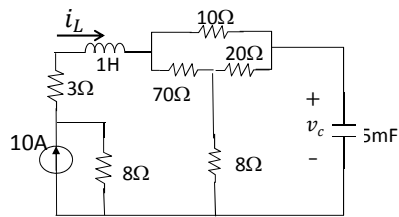
Example: Find v_c and i_L under DC condition.



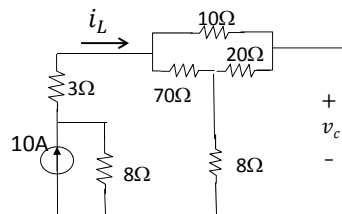Under DC condition,
Inductor = short, capacitor = open



Use source transformation:

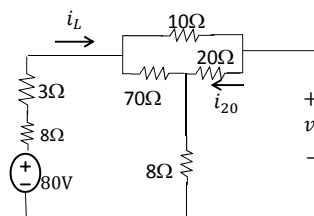



$$i_L = \frac{80}{11 + 70 // 30 + 8} = 2A$$

$$i_{20} = \frac{70}{100} \times 2 = 1.4A$$

$$v_c = 8i_L + 20i_{20} = 16 + 28 = 44V$$


Applications:

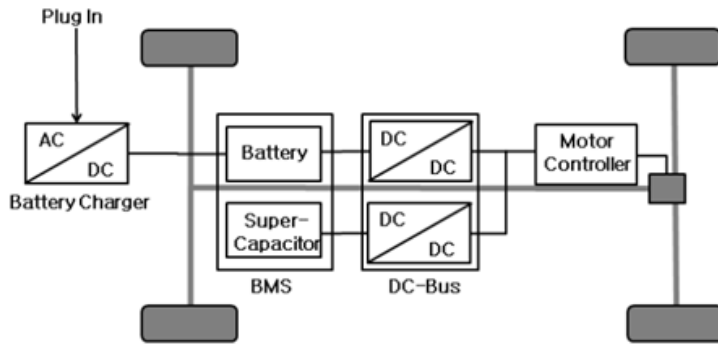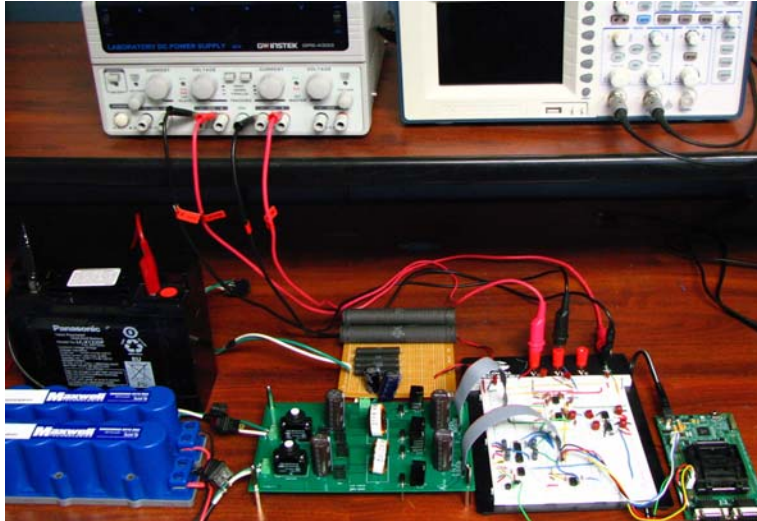Power systems driven by battery/supercapacitor hybrid energy storage devices, by Hoeguk Jung (Ph.D student)







Architecture of Electric Vehicle

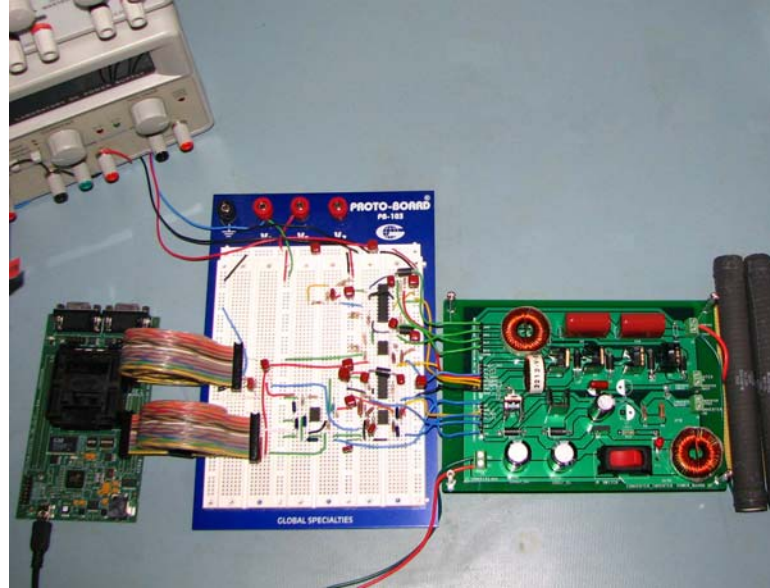Ripple reduction in two stage inverter: experiment setup



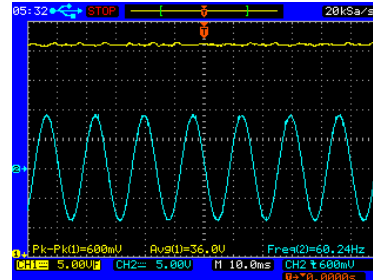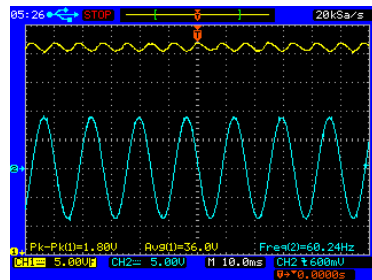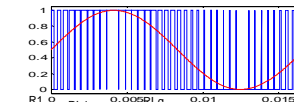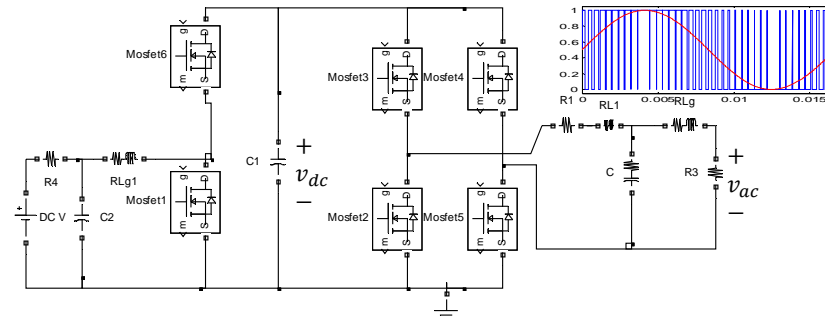Ripple-reduction in boost-converter-inverter



L16

Practice 1: For a capacitor with $C=2F$, given $i(t) = 6\sin 4t$ A, $v(0)=1V$. Find $v(t)$ for $t \geq 0$.

Practice 2: For an inductor with $L=0.1H$, given $i(t) = 10t e^{-5t}$ A. Find $v(t)$, $w(t)$.


Practice 3: Given $C= 4mF$, $i(0)=2A$, and

$$v(t) = \begin{cases} 50V, & t < 0 \\ Ae^{-100t} + Be^{-600t}, & t \geq 0 \end{cases}$$

Find A and B.


L16

Practice 4: Find v_c , i_L under DC condition

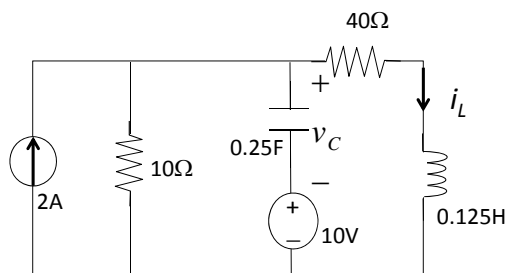

Practice 5: Find i_L , v_C , v_R under DC condition.

L16

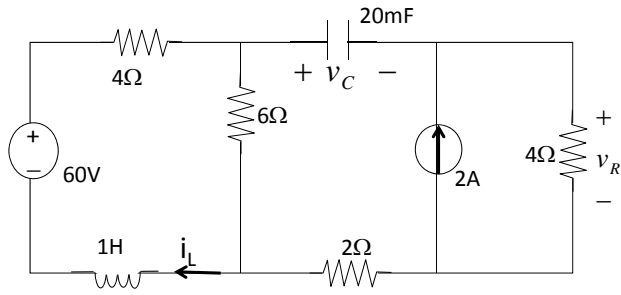

Practice 6: Find v_C and v_R under DC condition.

L16

