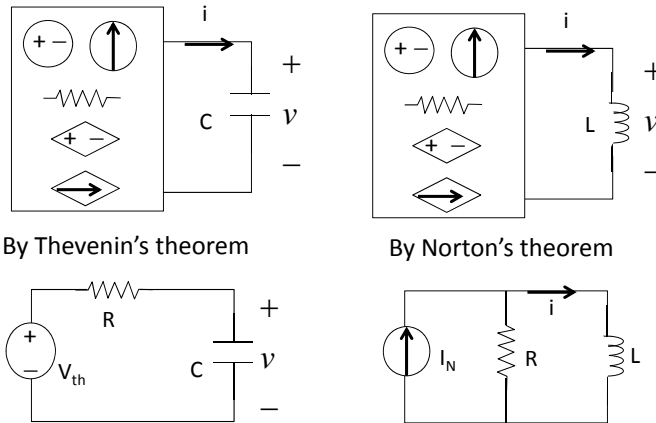


L17

Chapter 7 First-order Circuits


A circuit with one capacitor or inductor



Need to know how to solve the above two simple circuits
 Left : When $V_{th}=0$, source free RC circuit ; Otherwise, step response of RC circuit
 Right: When $I_N=0$, source free RL circuit Otherwise, step response of RL circuit

§ 7.2 The source free RC circuits

L17

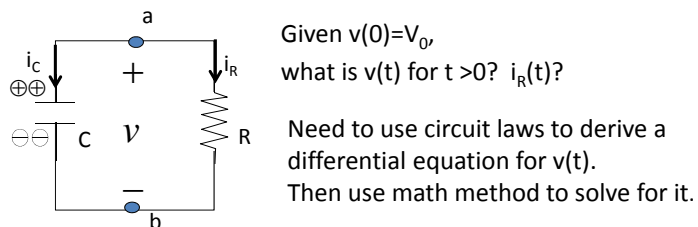

$$\text{By KCL: } i_R + i_C = 0 \quad (1)$$

By property of resistor and capacitor:


$$i_R = \frac{v}{R}; \quad i_C = C \frac{dv}{dt}$$

$$\text{Plug into (1) to obtain: } \frac{v}{R} + C \frac{dv}{dt} = 0$$

$$\Rightarrow \frac{dv}{dt} = -\frac{1}{RC} v \quad (2)$$

A first order differential equation

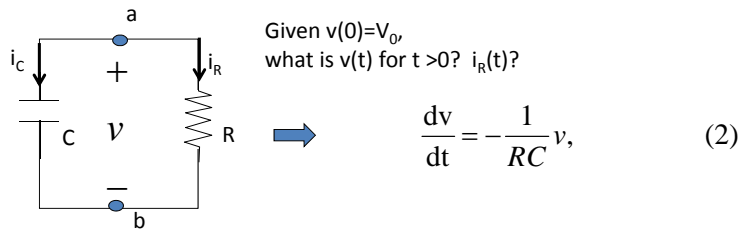The source free RC circuits can be described with a 1st order differential equation L17



Combined with initial condition $v(0)=V_0$, unique solution $v(t)$ can be found.

(2) Can be rearranged as
$$\frac{dv}{v} = -\frac{1}{RC}dt \quad (3)$$


Integrating both sides
$$\int_0^t \frac{dv}{v} = -\frac{1}{RC} \int_0^t dt = -\frac{t}{RC} \quad (4)$$

Since
$$\int_0^t \frac{dv}{v} = \ln v(t) \Big|_0^t = \ln v(t) - \ln v(0) = \ln \frac{v(t)}{v(0)}$$

$$\ln \frac{v(t)}{v(0)} = -\frac{t}{RC} \quad \frac{v(t)}{v(0)} = e^{-\frac{t}{RC}} \quad \boxed{v(t) = v(0) e^{-\frac{t}{RC}}} \quad \boxed{v(t) = V_0 e^{-\frac{t}{RC}}}$$

L17

In summary: For source free RC circuit,

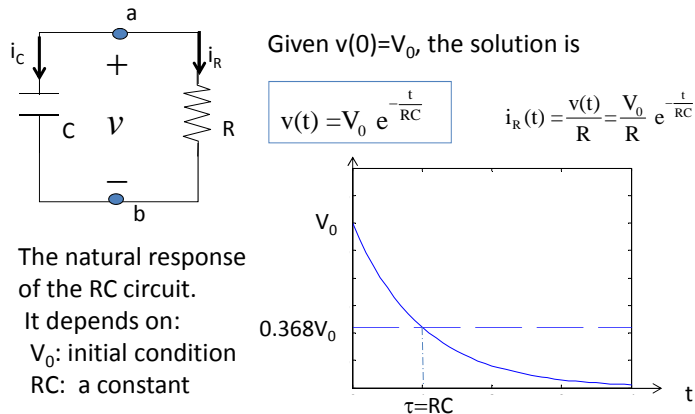

RC is called the time constant, denoted as τ : $\tau \triangleq RC$

$$\boxed{v(t) = V_0 e^{-\frac{t}{\tau}}}$$

RC is called the time constant, denoted as τ : $\tau \triangleq RC$


$$v(t) = V_0 e^{-\frac{t}{\tau}}$$

L17

At $t = \tau$, $v(t) = V_0 e^{-1} = 0.368V_0$

At $t = 2\tau$, $v(t) = V_0 e^{-2} = 0.13534V_0$;

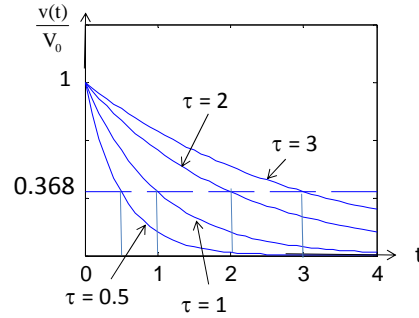At $t = 5\tau$, $v(t) = 0.00674V_0$ Capacitor almost fully discharged



Smaller $\tau = RC$, faster decay

$$\frac{v(t)}{V_0} = e^{-\frac{t}{RC}}$$

The power dissipated in R: $p = v i_R = \frac{V_0^2}{R} e^{-\frac{2t}{RC}}$

L17


Energy absorbed by resistor from 0 to t

$$\int_0^t p dt = \int_0^t \frac{V_0^2}{R} e^{-\frac{2t}{RC}} dt = \frac{1}{2} C V_0^2 (1 - e^{-\frac{2t}{RC}})$$

As $t \Rightarrow \infty$, all energy stored in C will be dissipated via R.

Example: Given $v_c(0)=15V$, find $v_c(t)$, $v_x(t)$ for $t > 0$.

L17

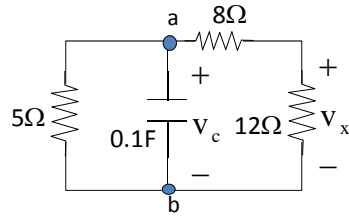


For RC circuit, always choose capacitor voltage v_c as key variable
Find $v_c(t)$ first, then express other variables in terms of it.

For this circuit,

$$v_x(t) = \frac{12}{12+8} v_c(t) = 0.6v_c(t)$$

To find $v_c(t)$, consider the rest as a single resistor R_{eq} ,
We call it R_{eq} with respect to (w.r.t) the capacitor

$$R_{eq} = 5 // (8+12) = 4\Omega$$

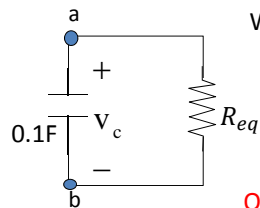

With $v_c(0) = 15V$, $1/R_{eq}C = 1/(4 \times 0.1) = 2.5$

$$v(t) = v_c(0) e^{-\frac{t}{RC}}$$

$$v_c(t) = 15e^{-2.5t}V$$

$$v_x(t) = 0.6 \times 15e^{-2.5t} = 9e^{-2.5t}V$$

Question:

How initial condition is established?

L17

Generally, there is a source to store energy in the capacitor for $t < 0$.


At $t = 0$, the source is turned off by a switch and the circuit becomes a source free RC circuit, for $t > 0$.

Recall two important facts about a capacitor:

1. At DC condition, a capacitor behaves like an open circuit
2. $v_c(t)$ is a continuous function of time.


These facts will be used to determine the initial condition $v_c(0)$.

Operations of switch:

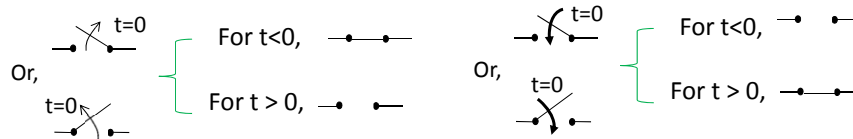

Example: The switch has been closed for a long time before it is open at $t = 0$. Find $v_c(t)$ for $t > 0$.

L17

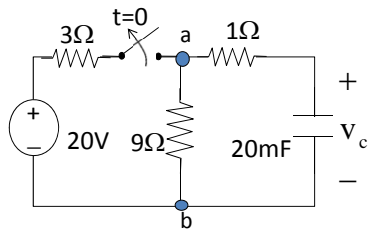

Interpret the condition:
Switch closed for a long time means that a DC condition has been reached at $t = 0^-$.

The value of v_c right before switch, $v_c(0^-)$, can be found by considering the circuit before switch under DC condition.

Since $v_c(t)$ is continuous,

$$v_c(0^+) = v_c(0^-) = v_c(0)$$

Step 1: Find $v_c(0)$ from the DC circuit before switch ($t < 0$).


Step 2: Find R_{eq} with respect to C for circuit after switch ($t > 0$)

Step 3: plug in the general formula

$$v_c(t) = v_c(0)e^{-\frac{t}{R_{eq}C}}$$

Step 1: For $t < 0$, or before switch.

L17

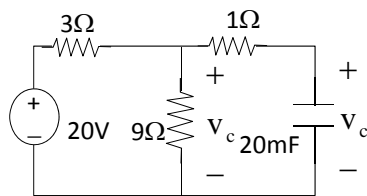

Consider the circuit under DC condition


- Capacitor behaves like an open circuit
- No current through 1Ω , thus no voltage drop
- voltage across $9\Omega = v_c$

By voltage division:

$$v_c = \frac{9}{9+3} \times 20 = 15V \quad \Rightarrow \quad v_c(0) = 15V$$

Step 2: For $t > 0$, (or, after switch)

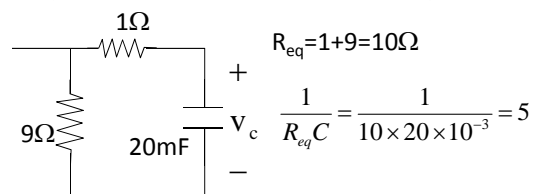Voltage source disconnected from the right side. It has no effect to the capacitor




Step 3 : form $v_c(t)$

$$v_c(t) = v_c(0)e^{-\frac{t}{R_{eq}C}}$$

$$v_c(t) = 15e^{-5t}V$$

Source free RC circuit guideline

L17

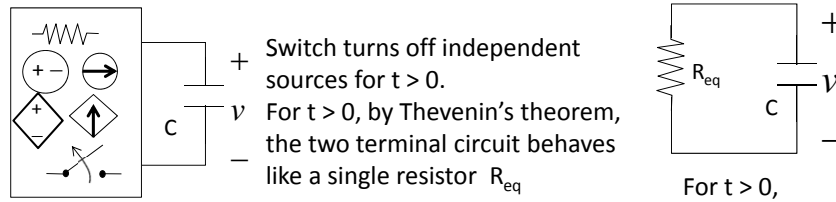

$$\text{For } t > 0, \quad v_c(t) = v_c(0)e^{-\frac{t}{R_{eq}C}}$$

Two key parameters:


1. $v_c(0)$, initial condition for capacitor voltage.
 Established by independent sources before switch ($t < 0$).
 Determined from the circuit before switch.
 Assume a DC condition has been reached. Capacitor behaves like open circuit
2. R_{eq} , equivalent resistance with respect to the capacitor for circuit after switch ($t > 0$).

After $v(t)$ of capacitor is found, other variables can be obtained using basic laws

Example:


Practice 1: Find $v_c(t)$ and $i_1(t)$ for $t > 0$.

R17

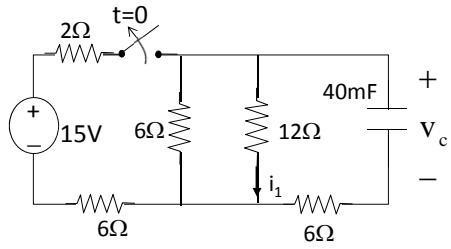


Practice 2: Find $v_c(t)$ and $v_1(t)$ for $t > 0$.

R17

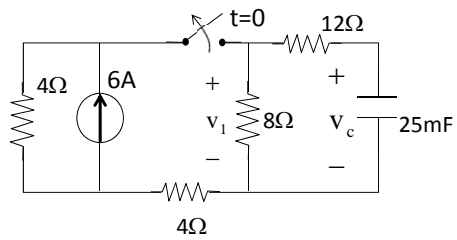


Practice 3: The switch has been closed for a long time before open at $t=0$. Find $i_x(t)$ for $t > 0$.

R17

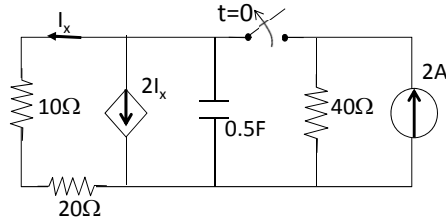

7.3 The source free RL circuit

L18

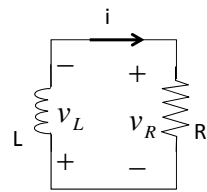

Given $i(0)=i_0$.
Need to find $i(t)$, for all $t > 0$.

Assign v_L and v_R according to passive sign convention. Then

$$v_L = L \frac{di}{dt}, \quad v_R = Ri$$

By KVL, $v_L + v_R = 0$

$$\Rightarrow L \frac{di}{dt} + Ri = 0$$

Compared with equation for source free RC circuit


$$\Rightarrow \frac{di}{dt} = -\frac{R}{L} i \quad \begin{matrix} i \Leftrightarrow v \\ \frac{R}{L} \Leftrightarrow \frac{1}{RC} \end{matrix} \quad \frac{dv}{dt} = -\frac{1}{RC} v \quad v(t) = v(0)e^{-\frac{t}{RC}}$$

Same math problem.

Solution: $i(t) = i(0)e^{-\frac{Rt}{L}}$

The source free RL circuit

L18

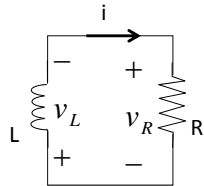

Given $i(0)=I_0$.

Time constant:

$$\tau \triangleq \frac{L}{R}$$

Solution:

$$i(t) = i(0)e^{-\frac{Rt}{L}} \quad i(t) = i(0)e^{-\frac{t}{\tau}}$$

Other variables: $v_R(t) = Ri(t) = Ri(0)e^{-\frac{Rt}{L}}$

Energy stored in inductor: $w_L(t) = \frac{1}{2}Li^2(t) = \frac{1}{2}i^2(0)e^{-\frac{2t}{\tau}}$

Energy consumed by resistor: $w_R(t) = \frac{1}{2}Li^2(0) - \frac{1}{2}i^2(0)e^{-\frac{2t}{\tau}}$


$$w_R(t) + w_L(t) = \frac{1}{2}Li^2(0) = \text{constant}$$

Two key parameters:

1. $i(0)$, initial inductor current. Obtained from circuit before switch, ($t < 0$), by treating inductor as a short circuit (under DC condition). Inductor current is continuous function of time: $i(0^-) = i(0^+) = i(0)$.
2. R , equivalent resistance with respect to inductor for circuit after switch ($t > 0$).


Example: Given $i(0)=10A$, find $i(t)$, $i_x(t)$ for $t > 0$.

L18

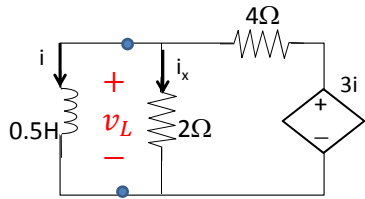

Need to find R_{eq} with respect to inductor. Recall Thevenin's equivalent resistance from Chapter 4. Due to the dependent source, need to supply external source

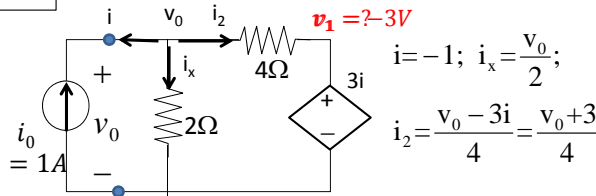Supply $i_0 = 1A$ current, Then $R_{eq} = v_0 / 1 = v_0$
 $v_0 = ?$
 Use nodal analysis



$$i = -1; \quad i_x = \frac{v_0}{2};$$

$$i_2 = \frac{v_0 - 3i}{4} = \frac{v_0 + 3}{4}$$

KCL at v_0 , $i + i_x + i_2 = 0$

$$-1 + \frac{v_0}{2} + \frac{v_0 + 3}{4} = 0$$

$$v_0 = 1/3V \quad R_{eq} = 1/3 \Omega$$

$$i(t) = i(0)e^{-\frac{R_{eq}t}{L}} = 10e^{-\frac{1/3t}{0.5}} = 10e^{-\frac{2}{3}t} A$$

$i_x(t) = ?$


Since 2Ω in parallel with inductor:

$$i_x = v_L / 2 = L \frac{di}{dt} / 2$$

$$i_x(t) = 0.5 \times 10 \times (-\frac{2}{3})e^{-\frac{2}{3}t} / 2 = -\frac{5}{3}e^{-\frac{2}{3}t} A$$

Example: The switch has been closed for a long time before open at $t=0$. Find $i(t), v(t)$ for $t > 0$.


L18

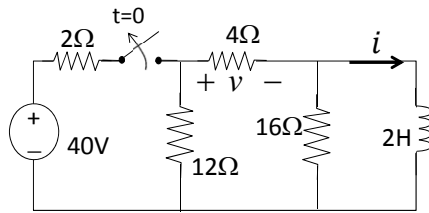

Important facts for finding initial condition $i(0)$:

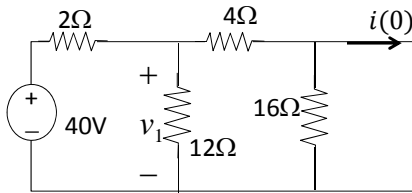1. DC condition for $t < 0$
2. Under DC condition, inductor \Leftrightarrow short circuit
3. Inductor $i(t)$ continuous
 $i(0^-) = i(0^+) = i(0)$

Step 1: Find $i(0)$ from circuit before switch ($t < 0$).



$16//0=0$
No current, no voltage drop across 16Ω
4 and 12 in parallel


Voltage division:

$$v_1 = \frac{4//12}{2 + 4//12} \times 40 \quad i(0) = \frac{v_1}{4} = \frac{24}{4} = 6A$$

$$= \frac{3}{2+3} \times 40 = 24V$$

Step 2: For $t > 0$, 40V disconnected

L18

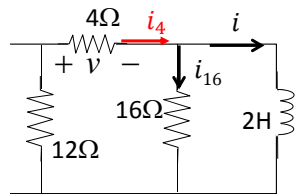

R_{eq} with respect to inductor

$$R_{eq} = 16 // (4 + 12) = 8\Omega \quad R_{eq}/L = 4$$

Step 3: $i(t) = i(0)e^{-\frac{R_{eq}}{L}t} = 6e^{-4t}A$

Step 4: $v(t) = 4(i + i_{16})$
 $= 4(6 - 3)e^{-4t}$
 $= 12e^{-4t}V$

$$i_{16}(t) = \frac{v_L}{16} = \frac{1}{16}L \frac{di}{dt}$$

$$= \frac{2}{16} \times 6 \times (-4)e^{-4t} = -3e^{-4t}A$$


A simpler method:

$$i_4(t) = \frac{1}{2}i(t) \quad \text{By current division.}$$

$$= 3e^{-4t}A$$

$$v(t) = 4i_4(t) = 12e^{-4t}V$$

Example: Find $i(t)$ for $t > 0$.

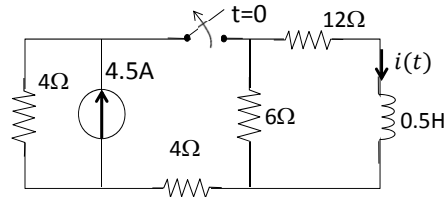


For $t > 0$, R_{eq} with respect to L

$$R_{eq} = 6 + 12 = 18\Omega$$

Put together:

$$\begin{aligned} i(t) &= i(0)e^{-\frac{R_{eq}}{L}t} \\ &= 0.5 e^{-\frac{18}{0.5}t} = 0.5e^{-36t} A \end{aligned}$$

Find $i(0)$ From circuit before switch:

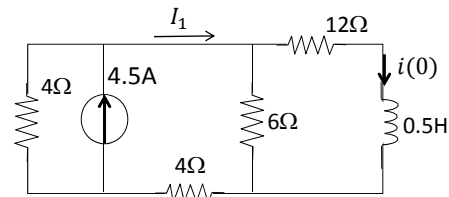

Current division:

$$I_1 = \frac{4}{4 + (4 + 6 // 12)} \times 4.5 = 1.5A$$

$$i(0) = \frac{6}{6 + 12} \times 1.5 = 0.5A$$

§ 7.4 Singularity functions

L18

We saw switches in previous circuits.


They change the structure of the circuit, e.g., at $t = 0$.

At switching time $t=0$, some variables, such as $v_c(t)$, $i_L(t)$ are continuous, but $i_c(t)$, $v_L(t)$ may be discontinuous.

Singular functions are those having discontinuous derivative, or, being discontinuous

Step function: a basic singular function

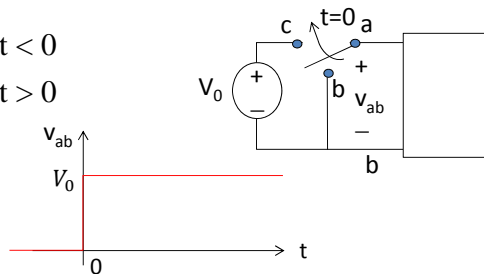
$$v_{ab}(t) = \begin{cases} 0, & t < 0 \\ V_0, & t > 0 \end{cases}$$



- A step function can be realized by switch, in other words,
- The operation of switch can be described by a step function

The unit step function:
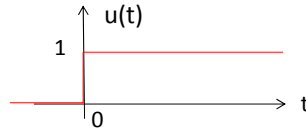
$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$




L18

General step function can be expressed in terms of unit step:

$$v_{ab}(t) = V_0 u(t) = \begin{cases} 0, & t < 0 \\ V_0, & t > 0 \end{cases}$$


- Unit step with a time shift:
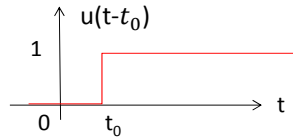
$$u(t-t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$




- Time-reversed unit step
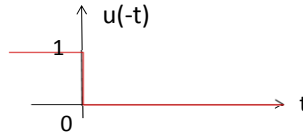
$$u(-t) = \begin{cases} 1, & t < 0 \\ 0, & t > 0 \end{cases}$$



- The impulse function: the derivative of unit step

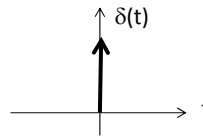
$$\delta(t) = \begin{cases} 0, & t < 0 \\ \text{undefined}, & t = 0 \\ 0, & t > 0 \end{cases}$$



L18


- The unit ramp function: the integration of unit step

$$r(t) = \begin{cases} 0, & t < 0 \\ t, & t > 0 \end{cases}$$

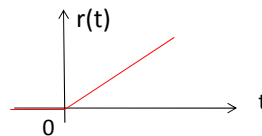


Practice 4: Find $i(t)$, $i_1(t)$, $i_2(t)$ for $t > 0$.

R18

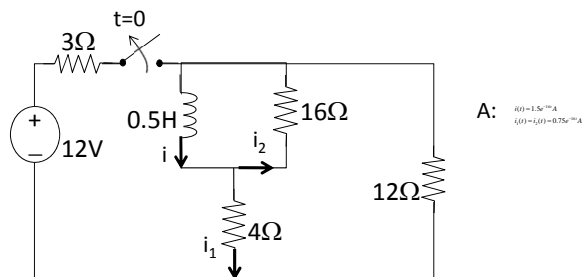


Practice 5: Find $I_1(t)$ and $v_2(t)$ for $t > 0$.

R18

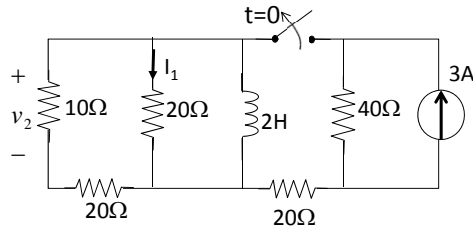

§ 7.5 Step response of an RC circuit

L19

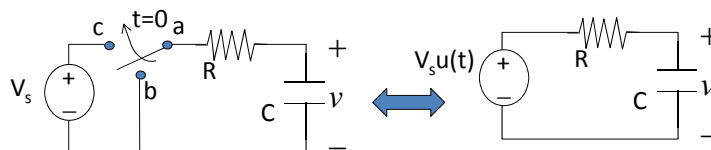


Step function:

$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$

Assume $v(0) = V_0$. Find $v(t)$ for $t > 0$.

- $v(t)$ is the response to a step function $V_s u(t) \Rightarrow$ called step response.

For $t > 0$, $V_s u(t) = V_s$:

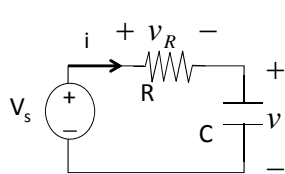

To derive a differential equation for v , assign i and v_R


$$i = C \frac{dv}{dt}; \quad v_R = Ri = RC \frac{dv}{dt}$$

By KVL, $v_R + v = V_s$

$$RC \frac{dv}{dt} + v = V_s \quad \text{With initial condition: } v(0) = V_0$$

For $t > 0$, $V_s u(t) = V_s$:

L19

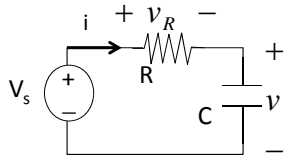

$$RC \frac{dv}{dt} + v = V_s \quad \text{With initial condition: } v(0)=V_0$$

$$\frac{dv}{dt} = -\frac{1}{RC}(v - V_s)$$

$$\int_0^t \frac{dv}{v - V_s} = -\frac{1}{RC} \int_0^t dt$$

$$\ln(v - V_s) \Big|_0^t = -\frac{t}{RC}$$

$$\ln \frac{v(t) - V_s}{V_0 - V_s} = -\frac{t}{RC}$$

$$\frac{v(t) - V_s}{V_0 - V_s} = e^{-\frac{t}{RC}}$$

$$v(t) = V_s + (V_0 - V_s) e^{-\frac{t}{RC}} \quad \text{for } t > 0$$


Step response

Step response:

L19

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s) e^{-\frac{t}{RC}}, & t > 0 \end{cases}$$

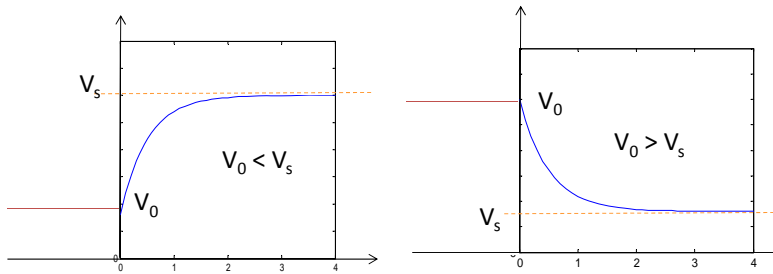A step response brings a circuit from one DC condition to another DC condition




Special cases:

1. When $V_s = 0$, $v(t) = V_0 e^{-\frac{t}{RC}}$ for $t > 0$ Reduce to source free circuit

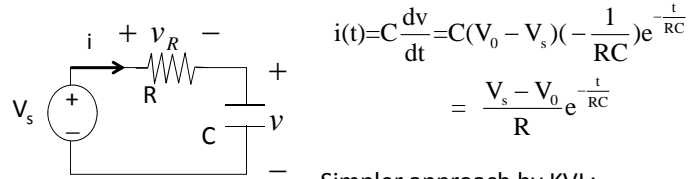2. When $V_0 = 0$, $v(t) = V_s - V_s e^{-\frac{t}{RC}}$ for $t > 0$

Step response: $v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s) e^{-\frac{t}{RC}}, & t > 0 \end{cases}$ L19

You can use $v(t)$ to find other variables:




$$i(t) = C \frac{dv}{dt} = C(V_0 - V_s) \left(-\frac{1}{RC}\right) e^{-\frac{t}{RC}} = \frac{V_s - V_0}{R} e^{-\frac{t}{RC}}$$

Simpler approach by KVL:


$$i(t) = \frac{V_s - v(t)}{R} = \frac{V_s - V_0}{R} e^{-\frac{t}{RC}}$$

Step response of general RC circuit L19

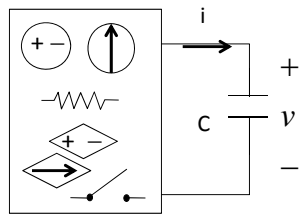

One or more switches changes structure of circuit at $t = 0$ (or $t = t_0$).
 Problem: need to find $v(t)$ or, other variables for $t > 0$.
 For $t < 0$, circuit behaves like a DC circuit. Find the initial condition $v(0)$ from this DC circuit.

For $t > 0$, use Thevenin's theorem:

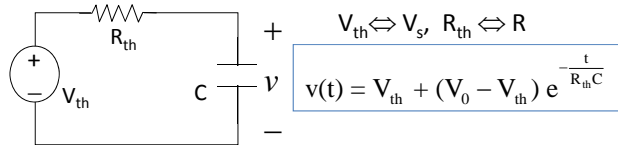

$$V_{th} \leftrightarrow V_s, R_{th} \leftrightarrow R$$

$$v(t) = V_{th} + (V_0 - V_{th}) e^{-\frac{t}{R_{th}C}}$$

Note that: $v(0) = V_{th} + (V_0 - V_{th}) e^{-0} = V_0$

$$v(\infty) = V_{th} + (V_0 - V_{th}) e^{-\infty} = V_{th}$$

Solution can also be written as

$$v(t) = v(\infty) + (v(0) - v(\infty)) e^{-\frac{t}{R_{th}C}}$$

Solution can also be written as

$$v(t) = v(\infty) + (v(0) - v(\infty)) e^{-\frac{t}{R_{th}C}}$$

L19

$v(\infty)$: The final value. Capacitor voltage under DC condition for circuit after $t > 0$

A short cut to form step response, – without deriving differential equation

Three key parameters:


1. Initial condition $v(0)=V_0$,
Established from circuit before switch. Obtained by solving a DC circuit, $t < 0$ (capacitor = open circuit)
2. Final condition $v(\infty)$
Established from circuit after switch. Obtained by solving another DC circuit, $t > 0$ (capacitor = open circuit)
3. Equivalent resistance R_{th} , or R_{eq}
with respect to capacitor for circuit after switch

Since $v(\infty) = V_{th}$, (V_{th} , R_{th}) can be together considered as the Thevenin's equivalent, with respect to the capacitor, from circuit after switch.


The problem of finding step response breaks down to several DC circuit problems in Chapters 2 and 4.

Example: Find the capacitor voltage $v(t)$ for $t > 0$.

L19

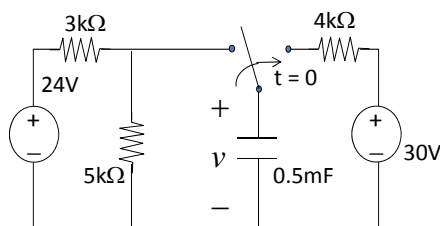


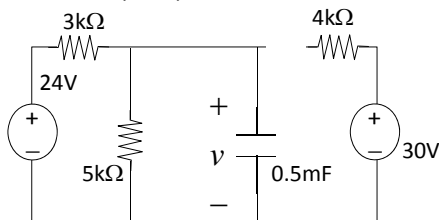Step 1: For $v(0)$, use circuit before switch ($t < 0$)



By voltage division, $v(0) = \frac{5}{5+3} \times 24 = 15V$

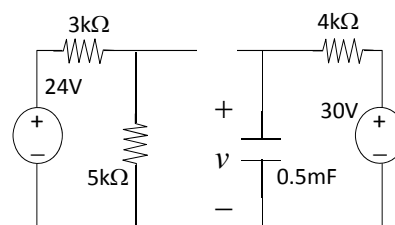Step 2: For R_{th} , V_{th} , w.r.t capacitor, use circuit after switch



$R_{th}=4k\Omega$; $V_{th}=30V = v(\infty)$

$$\frac{1}{R_{th}C} = \frac{1}{4 \times 10^3 \times 0.5 \times 10^{-3}} = 0.5$$


Step response:

$$v(t) = v(\infty) + (v(0) - v(\infty)) e^{-\frac{t}{R_{th}C}}$$

$$v(t) = 30 + (15 - 30) e^{-0.5t} \\ = 30 - 15 e^{-0.5t} \text{ V}$$

L19

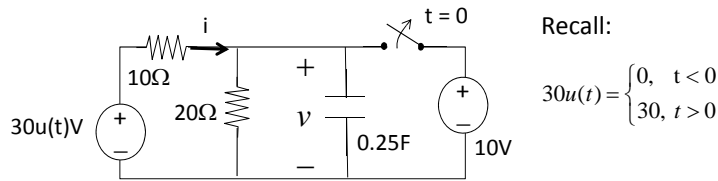
Example: Find the capacitor voltage $v(t)$ for $t > 0$.



Recall:



$$30u(t) = \begin{cases} 0, & t < 0 \\ 30, & t > 0 \end{cases}$$

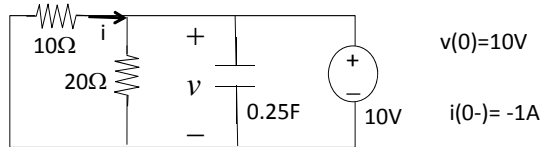Step 1: For $v(0)$, use circuit for $t < 0$



Step 2: For V_{th}, R_{th} , use circuit for $t > 0$

L19

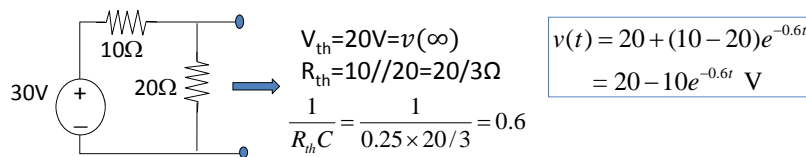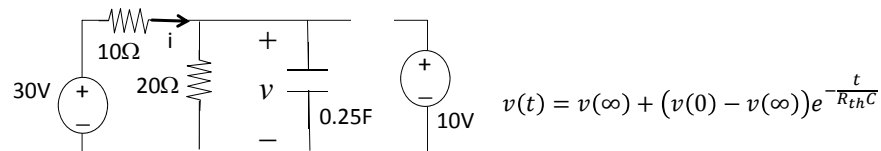

Step 3: How to express $i(t)$ in terms of $v(t)$?

$$i(t) = \frac{30 - v(t)}{10} = 1 + e^{-0.6t} A$$

Is $i(t)$ continuous at $t = 0$? $i(0^+) = 2A$ $i(0^-) = -1A$

In RC circuit, the only variable that is guaranteed to be continuous is capacitor voltage. Other variables, such as capacitor current, resistor voltage/current can be discontinuous.


Don't make generalization like:

~~$$v_R(t) = v_R(\infty) + (v_R(0) - v_R(\infty))e^{-\frac{1}{R_{th}C}t}$$~~

$v_R(0^-) \neq v_R(0^+)$

§ 7.6 Step response of RL circuits

L19

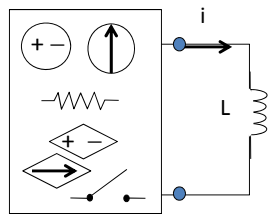


One or more switches changes structure of circuit at $t = 0$ (or $t = t_0$).

Problem: need to find $i(t)$ or, other variables for $t > 0$.

For $t < 0$, circuit behaves like a DC circuit.

Find the initial condition $i(0)$ from this DC circuit.

For $t > 0$, by Norton's theorem

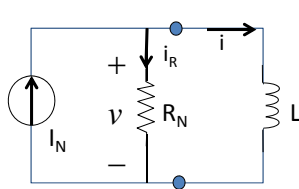

By KCL, $i_R + i = I_N$ $i_R = \frac{v}{R_N} = \frac{L}{R_N} \frac{di}{dt}$

$$\frac{L}{R_N} \frac{di}{dt} + i = I_N \quad \frac{di}{dt} = -\frac{R_N}{L} (i - I_N)$$

Same math problem as RC circuit


Step response: $i(t) = I_N + (i(0) - I_N)e^{-\frac{R_N}{L}t}$

Note that: $i(\infty) = I_N$. As $t \rightarrow \infty$, a DC condition will be reached.

$i(\infty)$ is inductor current for the DC circuit for $t > 0$

Step response of RL circuits

L19

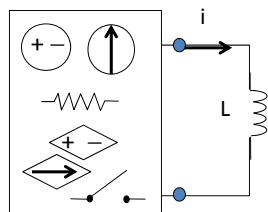

Step response:

$$i(t) = I_N + (i(0) - I_N)e^{-\frac{R_N}{L}t}$$

Since $i(\infty) = I_N$, can also be written as:


$$i(t) = i(\infty) + (i(0) - i(\infty))e^{-\frac{R_N}{L}t}$$

Three key parameters:


1. $i(0)$, initial condition, from the DC circuit for $t < 0$.
2. $i(\infty) = I_N$, final value, from DC circuit for $t > 0$.
3. $R = R_N = R_{th}$, equivalent resistance w.r.t inductor from circuit for $t > 0$

(I_N, R_N) together as Norton's equivalent, w.r.t inductor, for $t > 0$.

Example: Find $i(t)$ for $t > 0$.

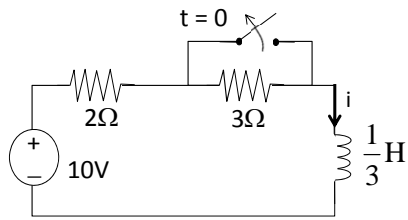


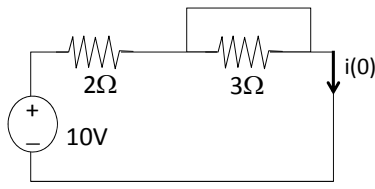Step 1: find $i(0)$. Consider DC circuit for $t < 0$.



$$i(0) = 10/2 = 5A$$

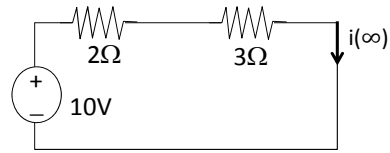Step 2: Find $i(\infty) = I_N$ from DC circuit for $t > 0$.



$$i(\infty) = 10/5 = 2A$$

R_N w.r.t. L for $t > 0$:


$$R_N = 2 + 3 = 5\Omega \quad \frac{R_N}{L} = \frac{5}{1/3} = 15$$

Step response:


$$i(t) = i(\infty) + (i(0) - i(\infty))e^{-\frac{R_N t}{L}}$$

$$i(t) = 2 + (5 - 2)e^{-15t} A = 2 + 3e^{-15t} A$$

Example: Find $i(t)$ for $t > 0$.

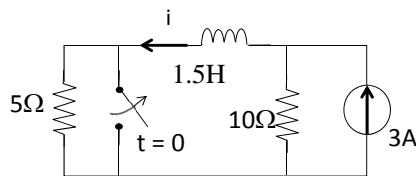


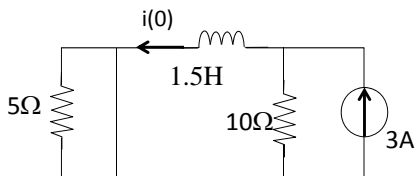Step 1: Find $i(0)$. Consider DC circuit ($t < 0$)



$$i(0) = 3A$$

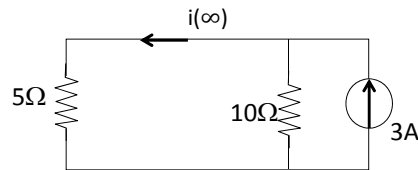
Step 2: Find $i(\infty) = I_N$ from DC circuit ($t > 0$)



By current division:

$$i(\infty) = \frac{10}{10+5} \times 3 = 2A$$

R_N w.r.t. L for $t > 0$:

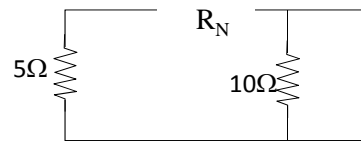


$$R_N = 15\Omega, \quad R_N/L = 10$$

$$i(t) = i(\infty) + (i(0) - i(\infty))e^{-\frac{R_N t}{L}}$$

$$i(t) = 2 + (3 - 2)e^{-10t} A = 2 + e^{-10t} A$$

Practice 6: Find $v(t)$, $i_x(t)$ for $t > 0$.


R19

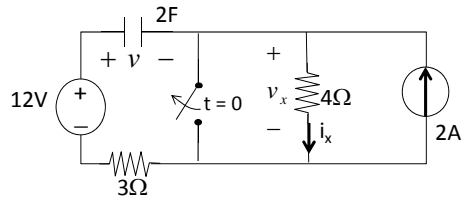

A:

Practice 7: Find $i_x(t)$ for $t > 0$.


R19

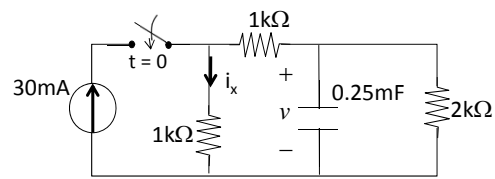

A:

Practice 8: Find $i(t)$ for all t .


R19

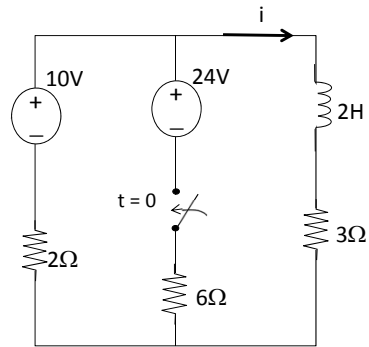

A:

Practice 9: Switch connected to "a" for a long time before connected to "b" at $t=0$. Find $v(t)$ for $t > 0$.

R19

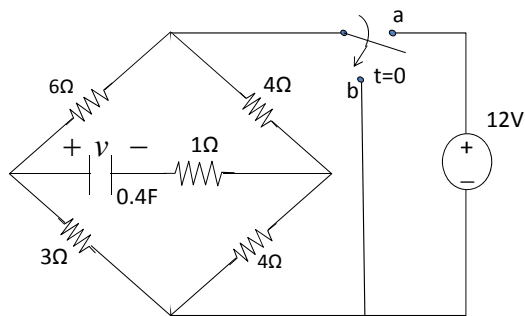

A: