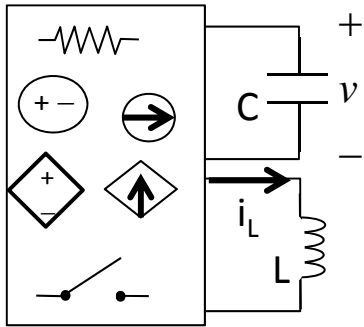


Step response of RC circuit:  $v(t) = v(\infty) + (v(0) - v(\infty)) e^{-\frac{1}{R_{th}C}t}$


Step response of RL circuit:  $i(t) = i(\infty) + (i(0) - i(\infty)) e^{-\frac{R_{th}}{L}t}$

Key points for step resp. of series RLC circuits:



Obtain  $v(0)$ ,  $i_L(0)$  from circuit before switch

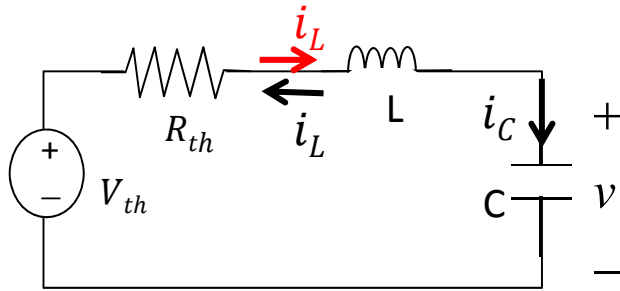For circuit after switch ( $t > 0$ ), obtain Thevenin's equivalent ( $V_{th}, R_{th}$ ) w.r.t LC



Assign  $i_C$  by passive sign convention

$$i_C(0^+) = \pm i_L(0)$$

For  $t > 0$ ,  $\frac{d^2v}{dt^2} + \frac{R_{th}}{L} \frac{dv}{dt} + \frac{1}{LC}v = \frac{V_{th}}{LC}$ ; Depending on how  $i_L$  is assigned. Then  $\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C}$

$$\alpha = \frac{R_{th}}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}, \quad v(\infty) = V_{th}$$

- Key parameters to obtain:
- $v(0), i_L(0)$  from circuit before switch
  - $V_{th}, R_{th}$  from circuit after switch.

Then follow straightforward math:

Case 1:  $\alpha > \omega_0$ ;  $s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$ ,  $v(t) = v(\infty) + A_1 e^{s_1 t} + A_2 e^{s_2 t}$

Find  $A_1, A_2$  from

$$\begin{cases} v(0) = v(\infty) + A_1 + A_2 \\ \frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2 \end{cases}$$

Case 2:  $\alpha = \omega_0$ ;  $s_1 = s_2 = -\alpha$ ,  $v(t) = v(\infty) + (A_1 + A_2 t) e^{-\alpha t}$

Find  $A_1, A_2$  from

$$\begin{cases} v(0) = v(\infty) + A_1 \\ \frac{dv(0^+)}{dt} = -\alpha A_1 + A_2 \end{cases}$$

Case 3:  $\alpha < \omega_0$ ;  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ ,  $s_1, s_2 = -\alpha \pm j\omega_d$ ,  $v(t) = v(\infty) + e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$

Find  $B_1, B_2$  from

$$\begin{cases} v(0) = v(\infty) + B_1 \\ \frac{dv(0^+)}{dt} = -\alpha B_1 + \omega_d B_2 \end{cases}$$