
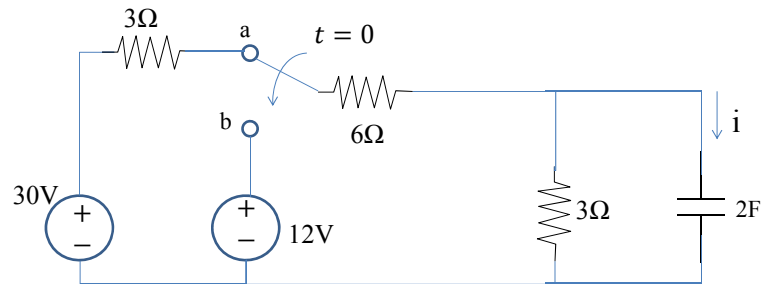


Problem 1

The switch in the circuit has been in position a for a long time. At $t=0$, it moves to position b. Calculate $i(t)$ for all $t > 0$.



**Problem 2**

In the following circuit, $i_s(t) = 5u(t)$. Find $v(t)$.

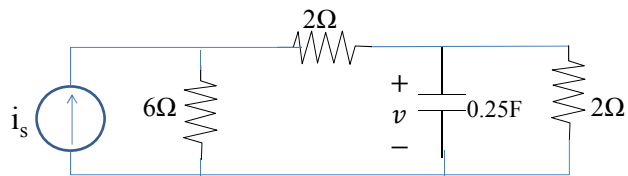


Problem 3

Obtain the inductor current for both $t < 0$ and $t > 0$ in each of the circuits.

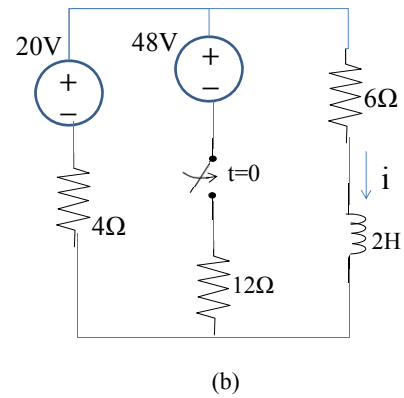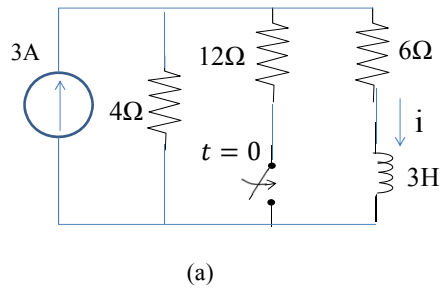
**Problem 4**

For $t < 0$, the switch is closed. Assume that a steady state has been reached by $t = 0$. At $t = 0$, the switch is open. Find $v(t)$, $v_R(t)$ for $t > 0$.

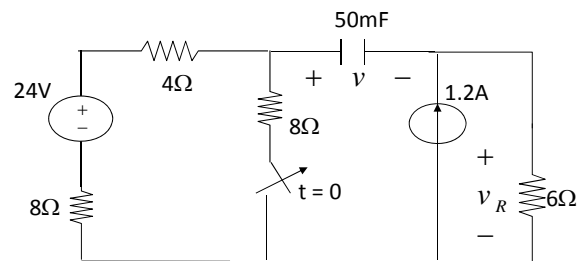


Problem 5

For the network shown in the following circuit. Find $v(t)$ for $t > 0$.

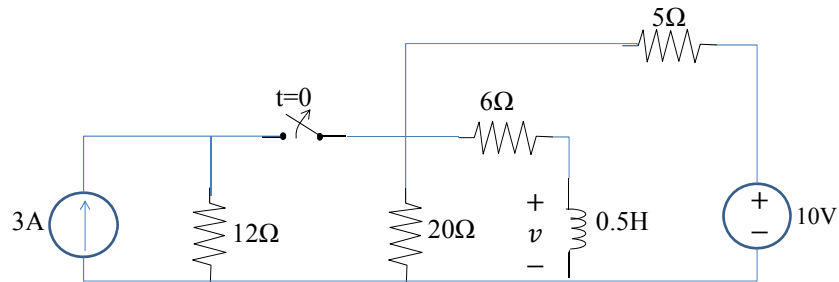
**Problem 6**

Determine the step response $v_0(t)$ to $v_s=9u(t)$ V in the following circuit.

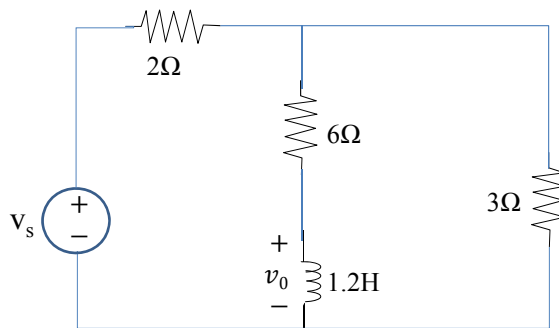

Problem 7

Obtain $v(t)$ and $i(t)$ in the following circuit.

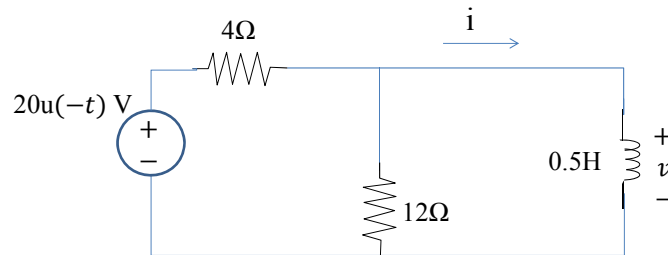**Problem 8**

Find $v_0(t)$ for $t > 0$ in the following circuit.

