

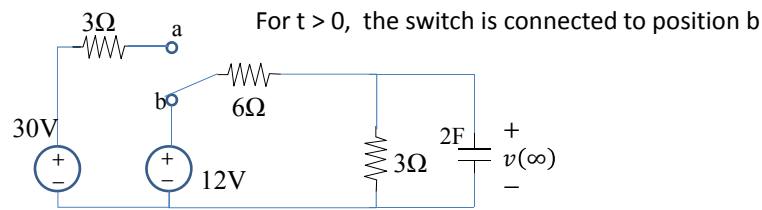


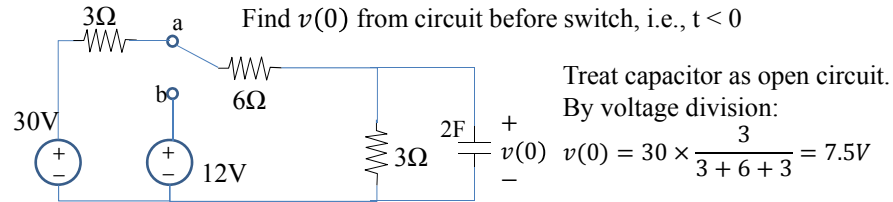Problem 1: No matter what is asked, for RC circuit, always find capacitor voltage first. Need $v(0)$, $v(\infty)$ and R_{eq} with respect to capacitor.



Find $v(\infty)$ as the capacitor voltage under DC condition. Also by voltage division:
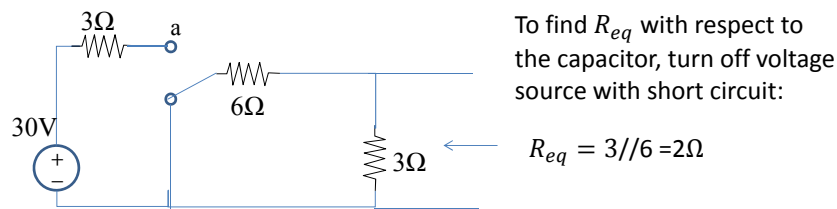
$$v(\infty) = \frac{3}{3 + 6} \times 12 = 4V$$



Now form the solution: $\frac{1}{R_{eq}C} = \frac{1}{2 \times 2} = \frac{1}{4}$

$$\begin{aligned} v(t) &= v(\infty) + (v(0) - v(\infty))e^{-\frac{t}{R_{eq}C}} \\ &= 4 + (7.5 - 4)e^{-\frac{1}{4}t} = 4 + 3.5e^{-0.25t}V \end{aligned}$$


Find $i(t)$ from $v(t)$ by the property of capacitor:

$$i(t) = C \frac{dv}{dt} = 2 \times (-0.25) \times 3.5e^{-0.25t}A = -1.75e^{-0.25t}A$$

Problem 2

For $t < 0$, $i_s(t) = 5u(t) = 0$. No power supply, $v(0) = 0V$

For $t > 0$, $i_s(t) = 5u(t) = 5A$

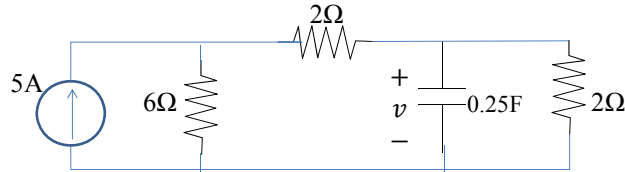

To find $v(\infty)$, consider the above circuit under DC condition.



The voltage across 5A = $5 \times 6 // (2+2) = 5 \times 2.4 = 12V$

By voltage division: $v(\infty) = \frac{2}{2+2} \times 12 = 6V$

To find R_{eq} with respect to capacitor, turn off 5A with open circuit.

$$R_{eq} = 2 // (2+6) = 1.6\Omega, \quad \frac{1}{R_{eq} \times C} = \frac{1}{1.6 \times 0.25} = 2.5$$


$$v(t) = 6 + (0 - 6)e^{-\frac{t}{0.4}} = 6 - 6e^{-2.5t}V$$

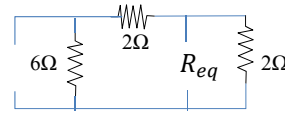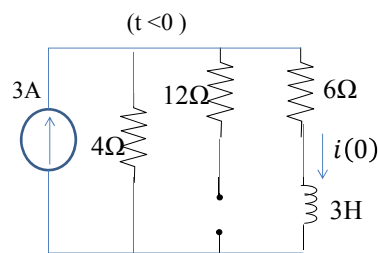**Problem 3 (a)**

For $t < 0$, under DC condition, inductor is short circuit.

By current division:

$$i(0) = \frac{4}{4+6} \times 3 = 1.2A$$

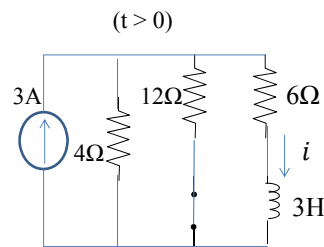



At $t = \infty$, under DC condition, inductor is also short circuit.

Also by current division:

$$i(\infty) = \frac{4 // 12}{4 // 12 + 6} \times 3 = 1A$$

For $t > 0$, R_{eq} with respect to inductor is: $R_{eq} = 6 + 4 // 12 = 9\Omega$

Form the solution: $i(t) = 1 + (1.2 - 1)e^{-3t} = 1 + 0.2e^{-3t}A$

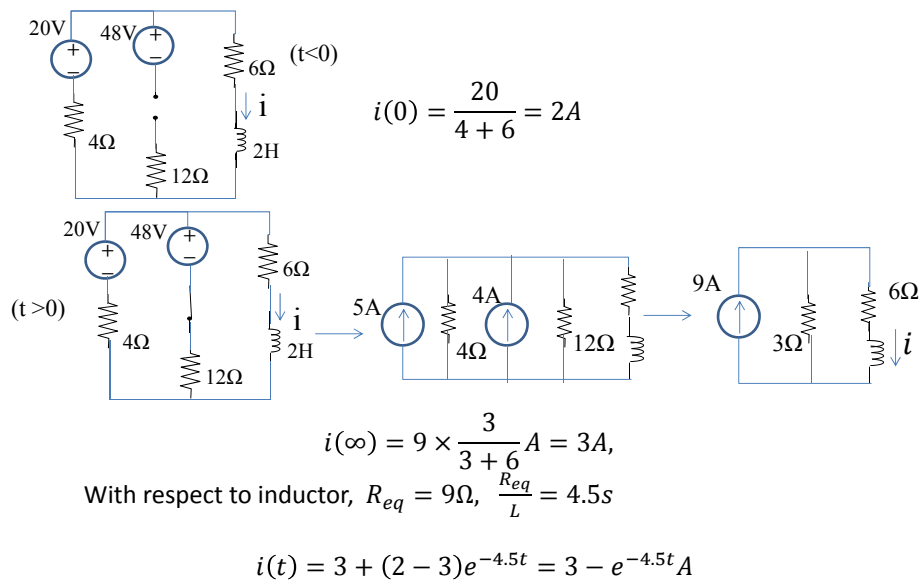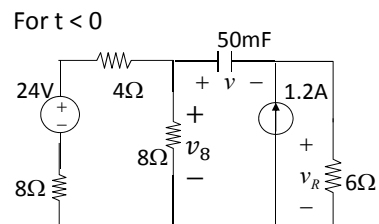Problem 3 (b)**Problem 4:** For RC circuit, Always find capacitor voltage first. Need $v(0)$, $v(\infty)$, R_{eq} 

For $t < 0$, capacitor open, the right side loop and the left side loop are not related:


$$v_8 = \frac{8}{8 + 4 + 8} \times 24 = 9.6V$$

$$v_R = 1.2 \times 6 = 7.2V;$$

$$v(0) = v_8 - v_R = 9.6 - 7.2 = 2.4V$$

$$v_R(t) = 6 \left(1.2 + C \frac{dv}{dt} \right) = 6(1.2 + 0.05 \times (-14.4) \times (-1.11)e^{-1.11t})$$

$$= 7.2 + 4.8e^{-1.11t}V$$

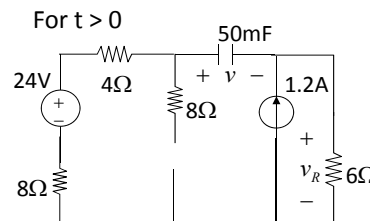


At $t = \infty$, capacitor open,
No current through 8Ω, 4Ω,
 $v(\infty) = 24 - 1.2 \times 6 = 16.8V$

With respect to capacitor,
 $R_{eq} = 8 + 4 + 6 = 18\Omega$

$$\frac{1}{R_{eq}C} = \frac{1}{18 \times 0.05} = 1.11$$

$$v(t) = 16.8 + (2.4 - 16.8)e^{-1.11t}V$$

$$= 16.8 - 14.4e^{-1.11t}V$$

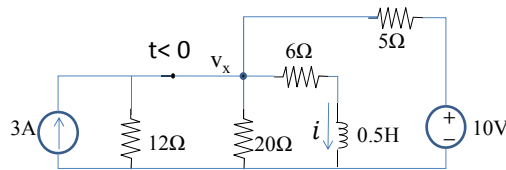Problem 5

For RL circuit, always find inductor current first

To find $i(0)$, consider circuit for $t < 0$,


Treat inductor as short, use nodal analysis:

$$\text{KCL at } V_x, \quad 3 + \frac{10 - v_x}{5} = \frac{v_x}{12} + \frac{v_x}{20} + \frac{v_x}{6}$$

$$v_x = 10\text{V}$$

$$i(0) = \frac{v_x}{6} = 1.667\text{A}$$

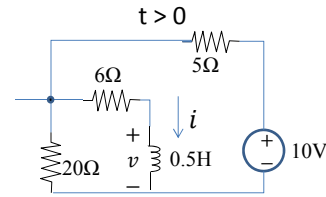You may also find $i(0)$ by using source transformation.



At $t = \infty$, also treat inductor as short,

$$i(\infty) = \frac{10}{5 + 20 \parallel 6} \times \frac{20}{20 + 6} = 0.8\text{A},$$

With respect to inductor,

$$R_{eq} = 6 + 20 \parallel 5\Omega = 10\Omega$$

$$\frac{R_{eq}}{L} = \frac{10}{0.5} = 20\text{s}$$

$$i(t) = 0.8 + (1.667 - 0.8)e^{-20t}\text{A} = 0.8 + 0.867e^{-20t}\text{A}$$

$$v(t) = L \frac{di}{dt} = 0.5 \times 0.867 \times (-20)e^{-20t}\text{V} = -8.67e^{-20t}\text{V}$$


Problem 6

Find inductor current first.

For $t < 0$, $V_s = 9\text{u}(t) = 0$,

No power supply,

$$i(0) = 0\text{A}$$

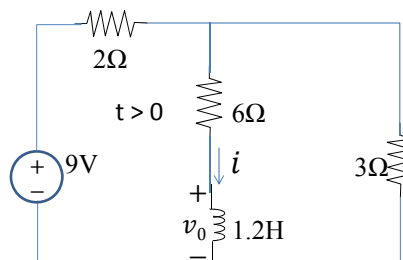

$$\text{At } t = \infty, \quad i(\infty) = \frac{9}{2 + 6 \parallel 3} \times \frac{3}{3 + 6} \text{A} = 0.75\text{A},$$


With respect to inductor, $R_{eq} = 6 + 2 \parallel 3\Omega = 7.2\Omega$

$$\frac{R_{eq}}{L} = \frac{7.2}{1.2} = 6\text{s}$$



$$i(t) = 0.75 - 0.75e^{-6t}\text{A}$$

$$v_0(t) = L \frac{di}{dt} = 1.2 \times (-0.75) \times (-6)e^{-6t}\text{V}$$
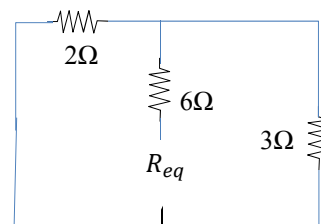
$$v_0(t) = 5.4e^{-6t}\text{u}(t)\text{V}$$



Problem 7 For $t < 0$, $20 u(-t) = 20V$,

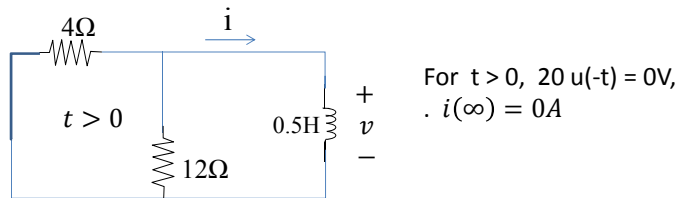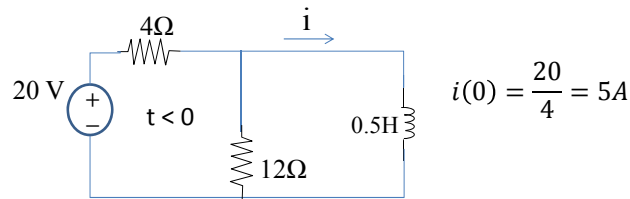



With respect to inductor: $R_{eq} = 4 || 12\Omega = 3\Omega$, $\frac{R_{eq}}{L} = \frac{3}{0.5} = 6s$

$$i(t) = 0 + (5 - 0)e^{-6t} A = 5e^{-6t} A$$

$$v(t) = L \frac{di}{dt} = 0.5 \times 5 \times (-6)e^{-6t} V$$

$$v(t) = -15e^{-6t} u(t) V$$

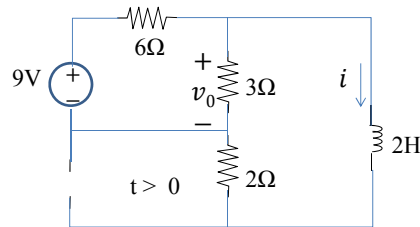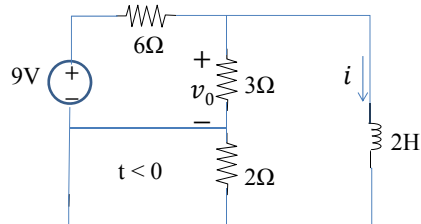Problem 8: Find inductor current first. Need $i(0)$, $i(\infty)$, R_{eq}



For $t < 0$, both 2Ω and 3Ω are short circuited: $i(0) = \frac{9}{6} A = 1.5A$,

At $t = \infty$, inductor is short circuit, 2Ω and 3Ω are in parallel,

$$i(\infty) = \frac{9}{6+3||2} \times \frac{3}{2+3} A = 0.75A,$$

For $t > 0$, with respect to inductor, $R_{eq} = 2 + 3 || 6\Omega = 4\Omega$,

$$\therefore \frac{R_{eq}}{L} = \frac{4}{2} = 2s$$

$$i(t) = 0.75 + (1.5 - 0.75)e^{-2t} = 0.75 + 0.75e^{-2t} A$$

$$v_0(t) = L \frac{di}{dt} + 2i = 2 \times (-2) \times 0.75e^{-2t} + 2(0.75 + 0.75e^{-2t}) V = 1.5 - 1.5e^{-2t} V$$

