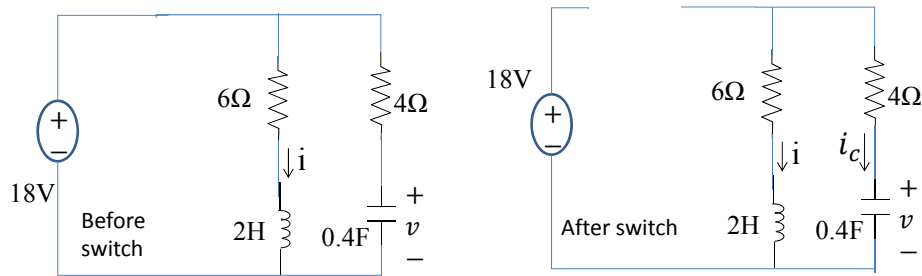


Problem 1

- (a) Since inductor current and capacitor voltage are continuous, to find $i(0^+)$ and $v(0^+)$, consider the circuit before switch. Under DC condition, inductor short, capacitor open:
 $i(0^+) = i(0^-) = 18/6 \text{ A} = 3\text{A}$, $v(0^+) = v(0^-) = 18\text{V}$
- (b) To find $\frac{dv(0^+)}{dt}$, consider circuit at $t = 0^+$ (After switch)
 $i_c(0^+) = -i(0^+) = -3\text{A}$, $\frac{dv(0^+)}{dt} = \frac{i_c}{C} = -\frac{3}{0.4} = -7.5\text{V/s}$
- (c) To find $i(\infty)$ and $v(\infty)$, consider circuit after switch under DC condition. Since no power supply, $i(\infty) = 0$, $v(\infty) = 0$.

Problem 2

$$\alpha = \omega_0 = 5, \quad b = 0, \quad \Rightarrow A_\infty = 0$$

$$\text{Thus } i(t) = (A_1 + A_2 t)e^{-5t}$$

From initial condition:

$$i(0) = A_1 = 3$$

$$i'(0) = -5A_1 + A_2 = 1 \Rightarrow A_2 = 1 + 5A_1 = 16$$

$$\Rightarrow i(t) = (3 + 16t)e^{-5t} \text{ A}$$

Problem 3

$$\alpha = 2, \omega_0 = 2\sqrt{2}, \quad b = 48, \quad \text{Since } \omega_0 > \alpha, \text{ use solution for case 3}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 2, \quad A_\infty = \frac{48}{8} = 6$$

$$\text{The general solution: } v(t) = 6 + e^{-2t}(A\cos 2t + B\sin 2t)$$


From initial condition:

$$v(0) = 6 + A = 4 \Rightarrow A = -2$$

$$v'(0) = -2e^{-2t}(A\cos 2t + B\sin 2t) + e^{-2t}(-2A\sin 2t + 2B\cos 2t)|_{t=0}$$

$$= -2A + 2B = -20 \Rightarrow B = -10 + A = -12$$


$$v(t) = 6 + e^{-2t}(-2\cos 2t - 12\sin 2t)$$

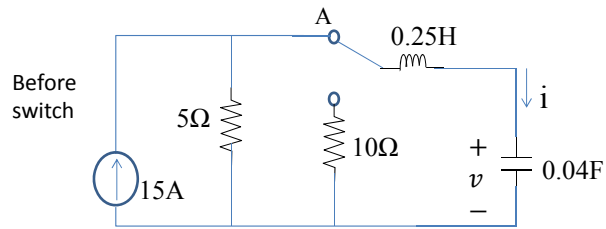Problem 4

Step 1: Find initial condition from circuit before switch.

Under DC condition: $v(0) = 5 \times 15 = 75V$, $i(0) = 0A$

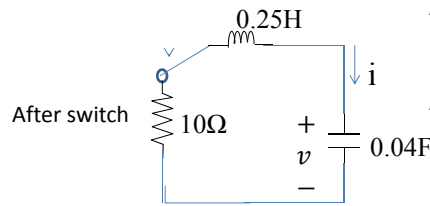Step 2: Find $\frac{dv(0^+)}{dt}$ and $v(\infty)$ From circuit after switch



At $t = 0^+$, $i_c(0^+) = i(0) = 0A$,

$$\frac{dv(0^+)}{de} = 0 V/s$$

At $t = \infty$, No power supply, $v(\infty) = 0V$

With respect to LC, $R = 10\Omega$

Step 3: Math computation

$$\alpha = \frac{R}{2L} = \frac{10}{0.5} = 20, \omega_0 = \frac{1}{\sqrt{CL}} = \frac{1}{0.1} = 10, v(\infty) = 0$$

Since $\alpha > \omega_0$, case 1.

$$s_1, s_2 = -20 \pm \sqrt{400 - 100} = -20 \pm 10\sqrt{3} = -2.679, -37.32$$

The general solution:

$$v(t) = Ae^{-2.679t} + Be^{-37.32t}$$

From initial condition:


$$v(0) = A + B = 75$$

$$v'(0) = -2.679A - 37.32B = 0$$

$$\longrightarrow \begin{cases} A = 80.801 \\ B = -5.801 \end{cases}$$

$$v(t) = 80.801e^{-2.679t} - 5.801e^{-37.32t} V$$

Problem 5

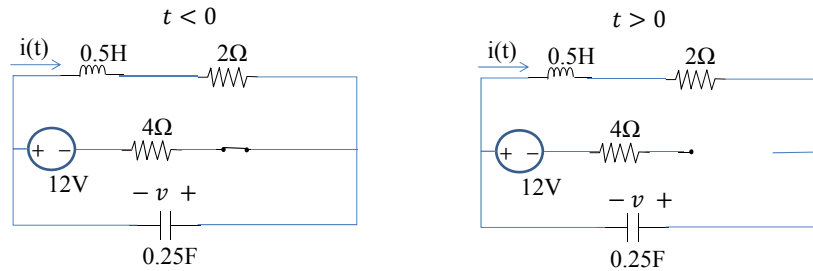

It is more convenient to find capacitor voltage first. Then take derivative to find loop current. Assign capacitor voltage as in figures.

Step 1: find $v(0)$, $i(0)$ from circuit for $t < 0$. Under DC condition:

$$i(0) = \frac{12}{6} = 2A, \quad v(0) = -2A \times 2\Omega = -4V \text{ (capacitor and } 2\Omega \text{ in parallel)}$$

Step 2: At $t = 0^+$, capacitor and inductor in series, $i_c(0^+) = i(0) = 2A$,

$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{2}{0.25} = 8V/s$$

At $t = \infty$, 12V not connected to LC, $v(\infty) = 0$

With respect to LC, $R = 2\Omega$

Step 3: Math computation

$$\alpha = \frac{R}{2L} = \frac{2}{1} = 2, \quad \omega_0 = \frac{1}{\sqrt{CL}} = \frac{1}{\frac{1}{2\sqrt{2}}} = 2\sqrt{2},$$

Since $\alpha < \omega_0$, use Case 3

$$\omega_d = \sqrt{8 - 4} = 2,$$

General solution: $v(t) = e^{-2t}(A\cos 2t + B\sin 2t)$

From initial condition:


$$v(0) = A = -4$$


$$v'(0) = -2A + 2B = 8 \quad \Rightarrow \quad B = 4 + A = 0$$

Thus $v(t) = -4e^{-2t}\cos 2t V$

Since $i(t)$ and $i_c(t)$ are the same,

$$\begin{aligned} i(t) &= C \frac{dv}{dt} = 0.25(-4(-2)e^{-2t}\cos 2t \\ &\quad + 8e^{-2t}\sin 2t) \\ &= 2e^{-2t}(\cos 2t + \sin 2t)A \end{aligned}$$

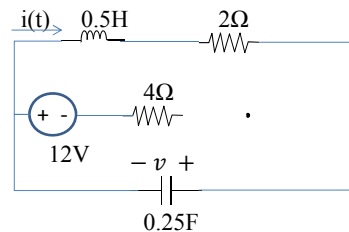

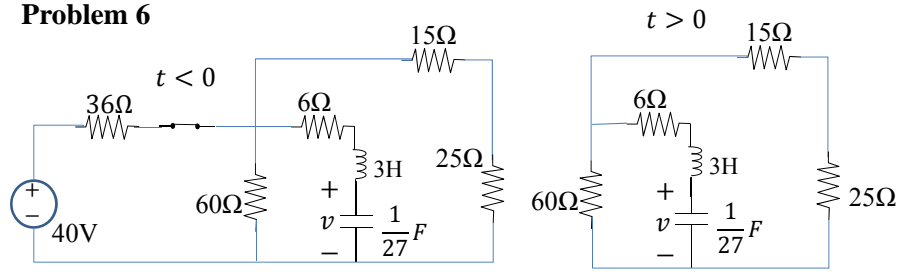Problem 6

Step 1: Find $v(0)$ and inductor current $i(0)$ from circuit for $t < 0$.
 Since no voltage across 6Ω , $v(0)$ is the same as voltage across 60Ω ,
 which is in parallel with $15\Omega + 25\Omega$, $60 // (15+25)\Omega = 24\Omega$

By voltage division,

$$v(0) = 40 \times \frac{24}{36+24} = 16V, \text{ And } i(0) = 0.$$

Step 2: At $t = 0^+$, $v'(0^+) = \frac{i(0)}{C} = 0$

At $t = \infty$, since no power supply, $v(\infty) = 0$

With respect to LC, $R = 6 + 60 || (15 + 25) = 30\Omega$

Step 3: Math

$$\alpha = \frac{R}{2L} = \frac{30}{6} = 5, \quad \omega_0 = \frac{1}{\sqrt{CL}} = \frac{1}{\frac{1}{3}} = 3,$$

Since $\alpha > \omega_0$, case 1,


$$s_1, s_2 = -5 \pm \sqrt{25 - 9} = -9, -1$$

The general solution: $v(t) = Ae^{-9t} + Be^{-t}$

From initial condition:

$$\left. \begin{array}{l} v(0) = A + B = 16 \\ v'(0) = -9A - B = 0 \end{array} \right\} \longrightarrow \begin{cases} A = -2 \\ B = 18 \end{cases}$$

$$v(t) = -2e^{-9t} + 18e^{-t} V$$

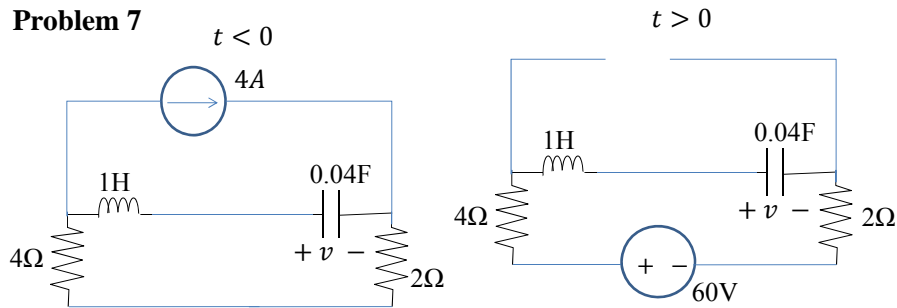

Step 1: For $t < 0$, $4u(-t) = 4A$, current source on;
 $60u(t) = 0V$, voltage source off (short).
 $v(0) = -4 \times 6V = -24V$, $i(0) = 0$, $v'(0) = 0$.

Step 2: For $t > 0$, $4u(-t) = 0$, current source off (open), $60u(t) = 60V$,
voltage source on,
At $t = \infty$, $v(\infty) = 60V$,
 R with respect to LC, $R = 4 + 2 = 6\Omega$

Step 3:

$$\alpha = \frac{R}{2L} = \frac{6}{2} = 3, \omega_0 = \frac{1}{\sqrt{CL}} = \frac{1}{0.2} = 5,$$

$\omega_0 > \alpha$, Case 3

$$\omega_d = \sqrt{25 - 9} = 4,$$

The general solution: $v(t) = 60 + e^{-3t}(A\cos 4t + B\sin 4t)$


From initial condition :

$$v(0) = 60 + A = -24 \Rightarrow A = -84$$

$$v'(0) = -3A + 4B = 0 \Rightarrow B = 0.75A = -63$$

$$v(t) = 60 + e^{-3t}(-84\cos 4t - 63\sin 4t)V$$

Problem 8

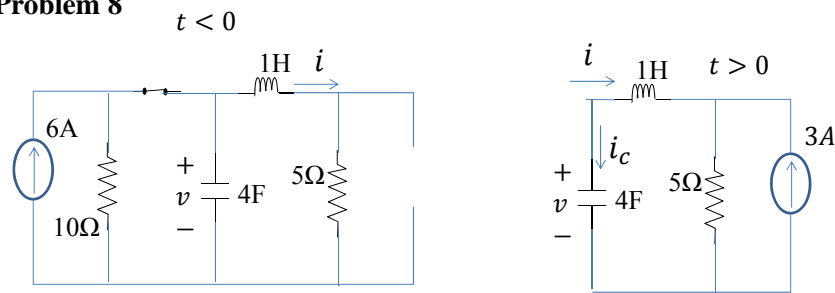

Step 1: For $t < 0$, $3u(t) = 0A$, right side source off (open)

$$v(0) = 6 \times (10 \parallel 5) = 6 \times \frac{5 \times 10}{5+10} = 20V,$$

$$i(0) = \frac{v(0)}{5} = \frac{20}{5} = 4A,$$

Step 2: For $t > 0$, i and i_c are opposite, $i_c(0^+) = -i(0) = -4A$

$$v'(0) = -\frac{i(0)}{C} = -1V/s$$

$$\text{At } t = \infty, v(\infty) = 3 \times 5V = 15V,$$

$$R = 5\Omega$$

Step 3:

$$\alpha = \frac{R}{2L} = \frac{5}{2} = 2.5, \omega_0 = \frac{1}{\sqrt{CL}} = \frac{1}{2} = 0.5$$

$$\text{Case 1: } s_1, s_2 = -2.5 \pm \sqrt{6.25 - 0.25} = -4.949, -0.0505$$

General solution:

$$v(t) = 15 + Ae^{-4.949t} + Be^{-0.0505t}$$

Using initial condition:


$$v(0) = 15 + A + B = 20$$

$$v'(0) = -4.949A - 0.0505B = -1$$

$$\rightarrow \begin{cases} A = 0.1526 \\ B = 4.8474 \end{cases}$$

$$v(t) = 15 + 0.1526e^{-4.949t} + 4.8474e^{-0.0505t}V$$

Problem 9

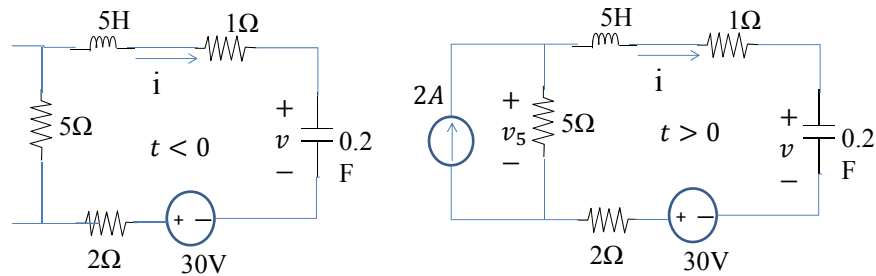

For $t < 0$, $2u(t)=0A$, current source off (open circuit)

$$v(0) = 30V, \quad i(0) = 0A$$

For $t > 0$, $v'(0^+) = \frac{i(0)}{C} = 0V/s$.

At $t = \infty$, $i = 0$, $v_5 = 2 \times 5 = 10V$,

By KVL, $v(\infty) = 30 + v_5 = 40V$,

$$R=2+1+5=8\Omega$$

$$\alpha = \frac{R}{2L} = \frac{8}{10} = 0.8, \quad \omega_0 = \frac{1}{\sqrt{CL}} = 1,$$

$$\alpha < \omega_0, \text{ Case 3, } \omega_d = \sqrt{1 - 0.64} = 0.6$$

General solution:

$$v(t) = 40 + e^{-0.8t}(A\cos 0.6t + B\sin 0.6t)$$


Compute A and B from initial condition:

$$v(0) = 40 + A = 30 \Rightarrow A = -10$$

$$v'(0) = -0.8A + 0.6B = 0 \Rightarrow B = -13.33$$

$$v(t) = 40 - e^{-0.8t}(10\cos 0.6t + 13.33\sin 0.6t) \text{ V}$$

$$\begin{aligned} i(t) &= C \frac{dv}{dt} = 0.2(0.8e^{-0.8t}(10\cos 0.6t + 13.33\sin 0.6t) \\ &\quad - e^{-0.8t}(-6\sin 0.6t + 8\cos 0.6t)) \\ &= 3.33e^{-0.8t}\sin 0.6t \text{ A} \end{aligned}$$

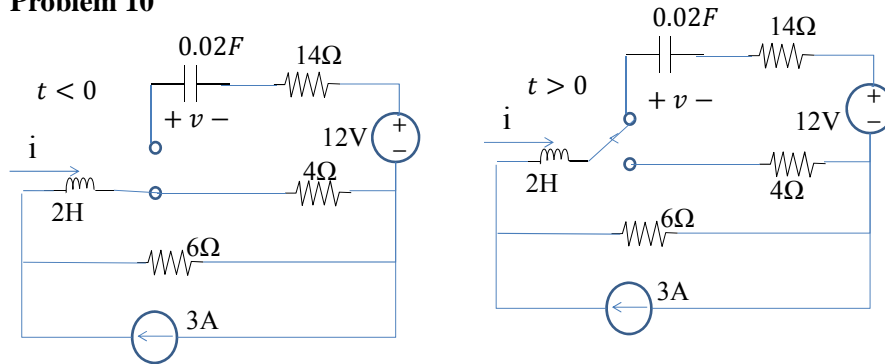Problem 10

Assign capacitor voltage v .

For $t < 0$, $v(0) = 0$, since no current to charge the capacitor

By current division, $i(0) = \frac{6}{4+6} \times 3 = 1.8A$

For $t > 0$, $v'(0^+) = \frac{i(0)}{C} = 1.8/0.02 = 90V/s$,

At $t = \infty$, $v(\infty) = 3 \times 6 - 12 = 6V$

With respect to LC, $R = 6 + 14 = 20\Omega$

$$\alpha = \frac{R}{2L} = \frac{14+6}{4} = 5,$$

$$\omega_0 = \frac{1}{\sqrt{CL}} = \frac{1}{0.2} = 5, \quad \alpha = \omega_0, \text{ case 2}$$

General solution:


$$v(t) = 6 + (A + Bt)e^{-5t}$$

$$v(0) = 6 + A = 0 \quad \Rightarrow \quad A = -6$$

$$v'(0) = -5A + B = 90 \quad \Rightarrow \quad B = 90 + 5A = 60$$

$$\begin{aligned} v(t) &= 6 + (-6 + 60t)e^{-5t} \\ i(t) &= C \frac{dv}{dt} = 0.02(-5(-6 + 60t)e^{-5t} + 60e^{-5t}) \\ &= (1.8 - 6t)e^{-5t} A \end{aligned}$$


Problem 11

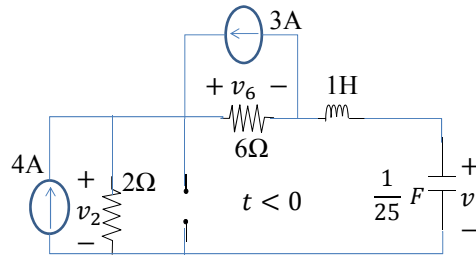

For $t < 0$, $v_2 = 4 \times 2 = 8V$,
 $v_6 = 6 \times 3 = 18V$
 By KVL,

$$v(0) = v_2 - v_6 = 8 - 18 = -10V$$

$$i(0) = 0A$$

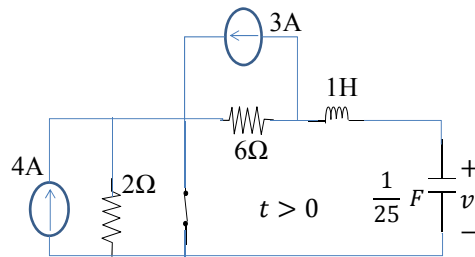

For $t > 0$,
 At $t = 0^+$, $v'(0^+) = \frac{i(0)}{C} = 0$
 At $t = \infty$,
 $v(\infty) = -3 \times 6 = -18V$
 (No voltage across 2Ω due to short circuit)
 $R = 6\Omega$

$$\alpha = \frac{R}{2L} = \frac{6}{2} = 3, \quad \omega_0 = \frac{1}{\sqrt{CL}} = \frac{1}{0.2} = 5,$$

$\omega_0 > \alpha$, Case 3

$$\omega_d = \sqrt{25 - 9} = 4$$

General solution:

$$v(t) = -18 + e^{-3t}(A\cos 4t + B\sin 4t)$$

To satisfy initial condition:

$$v(0) = -18 + A = -10 \quad A = 8$$

$$v'(0) = -3A + 4B = 0 \quad B = 6$$

$$v(t) = -18 + e^{-3t}(8\cos 4t + 6\sin 4t)V$$