

problem 1 solution

$$R = v^2 / P = \frac{14400}{80} \Omega = 180 \Omega$$

problem 2 solution

$$(a) \quad i = 15/80 = 0.1875 A = 187.5 \text{mA}$$

$$(b) \quad i = 15/75 = 0.2 A = 200 \text{mA}$$

problem 3 solution

$$i_1 = -6 + 11 A = 5 A$$

$$i_2 = 11 - 5 A = 6 A$$

$$i_3 = 13 - i_2 = 13 - 6 A = 7 A$$

problem 4 solution

$$-10 - 25 + 25 + v_1 = 0 \Rightarrow v_1 = 10 V$$

$$20 - 25 - v_2 = 0 \Rightarrow v_2 = -5 V$$

$$-v_1 + v_2 + v_3 = 0 \Rightarrow v_3 = 15 V$$

problem 5 solution

$$-18 + v + 3 = 0 \Rightarrow v = 15 V$$

$$-3 + 12 + 3i_x = 0 \Rightarrow 3i_x = -9 \Rightarrow i_x = -3 A$$

problem 6 solution

$$-22 + 3I - 8 + 5I + 6 = 0$$


$$I = 3 A$$

$$-V_{ab} + 5I + 6 = 0 \Rightarrow V_{ab} = v_2 + 6 = 5 \times 3 + 6 V = 21 V$$

problem 7 solution

$$-36 + 4i_0 + 5i_0 + 3i_0 = 0$$

$$i_0 = 3 A$$

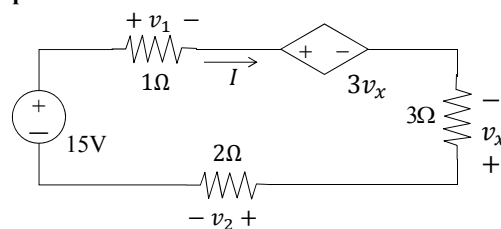problem 8 solution

Assign loop current I .
Assign v_1, v_2 by passive sign convention.
By Ohm's Law,
 $v_1 = I, v_2 = 2I$
Since I enters "-" of v_x ,
 $v_x = -3I$.

$$\text{KVL along clockwise direction: } v_1 + 3v_x - v_x + v_2 - 15 = 0,$$


$$I + 3v_x - v_x + 2I - 15 = 0$$

$$I + 3(-3I) - (-3I) + 2I - 15 = 0$$

$$-3I = 15$$

$$I = -5A, \quad v_x = -3(-5) = 15V$$

problem 9 solution

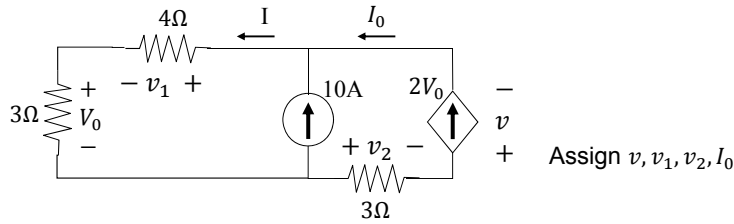

By KCL, same current I flows through 4Ω and 3Ω resistor on left side.

By Ohm's Law, $I = \frac{V_0}{3}$. By the dependent current source, $I_0 = 2V_0$

By KCL at top node, $I = 10 + I_0 \Rightarrow \frac{V_0}{3} = 10 + 2V_0 \Rightarrow V_0 = -6V$

Thus, $I = \frac{V_0}{3} = -2A$, $v_1 = 4I = -8V$.

To find the power dissipated by the controlled source, assign v (passive sign).

Need v_2 to compute v . By Ohm's Law, $v_2 = 3(2V_0) = 3(-12) = -36V$.


By KVL along outer loop: $-v_1 - v - v_2 - V_0 = 0$

$$v = -v_1 - v_2 - V_0 = -(-8) - (-36) - (-6) = 50V$$

Power dissipated by controlled source $p = v \times 2V_0 = 50(-12) = -600W$.

$V_0 = -6V, \quad p = -600W$

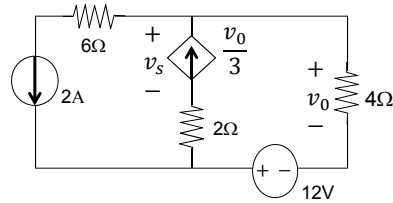
Problem 10 solution: Determine v_0 and v_s for the circuit below:



Main idea:

Express branch current in terms of v_0 ,
and use KCL to make an equation for v_0 ,
Then use KVL to find v_s

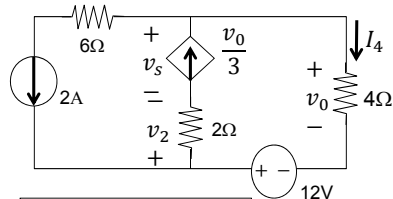Assign current through 4Ω , I_4 , voltage across 2Ω v_2 , by passive sign convention



$v_0 = 24V; v_s = 28V$

By ohm's law: $I_4 = \frac{v_0}{4}$;

By KCL: $\frac{v_0}{3} = 2 + I_4 = 2 + \frac{v_0}{4}$

Solving above equation: $v_0 = 24V$;

To find v_s , form KVL for the right loop:

$$v_0 - 12 + v_2 - v_s = 0;$$

$$v_s = v_0 - 12 + v_2$$

By Ohm's Law, $v_2 = 2 \times \frac{v_0}{3} = 2 \times \frac{24}{3} = 16V$

Thus, $v_s = 24 - 12 + 16 = 28V$

Note: the current through 2Ω , is the same as that through the dependent source, which is $v_0/3$