

**Problem 1 solution**

$$V_0 = 8 \times 10^{-3} \times 10 \times 10^3 V = 80V$$

$$I_{20} = \frac{5}{5+20} \times (0.01 \times 80) A = 0.16 A$$

$$V_{20} = 0.16 \times 20 \times 10^3 V = 3200V$$

$$P_{20} = V_{20} \cdot I_{20} = 3200 \times 0.16 W = 512W$$

**Problem 2 solution**

All resistors in parallel, same voltage  $v$  across each resistor

By ohm's law,

$$v = 16i_0 = 16 \times 3 V = 48V$$

$$i_1 = v/24 = 48/24 A = 2A$$


$$i_2 = v/6 = 48/6 A = 8A$$

$$i_3 = v/2 = 48/2 A = 24A$$

By KCL,

$$i_x = i_0 + i_1 + i_2 + i_3 = 3 + 2 + 8 + 24 A = 37A$$


$$p = vi_x = 48 \times 37 W = 1776W$$

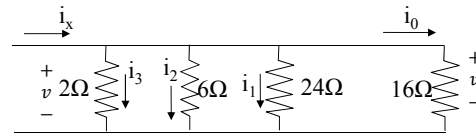


Answer:


$$i_x = 37A,$$

$$p = 1776W$$

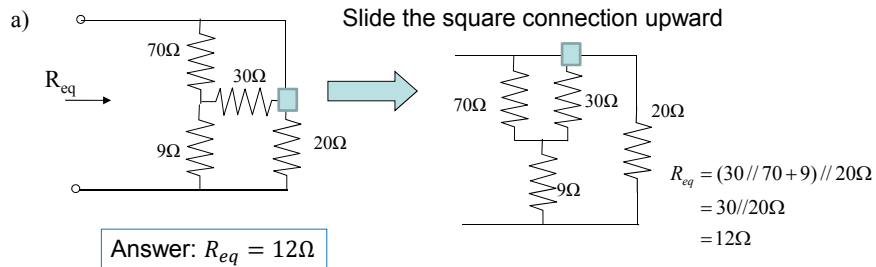**Problem 3 solution**

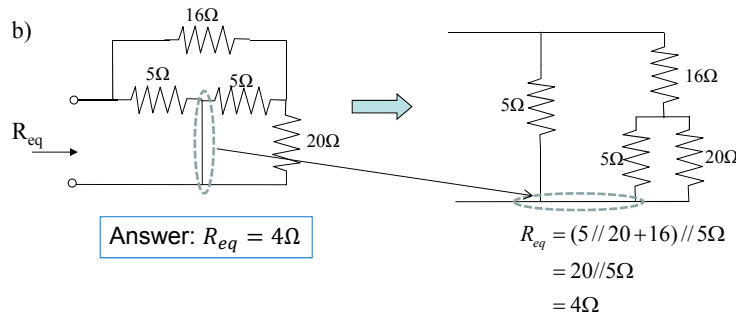

**Problem 4 solution**

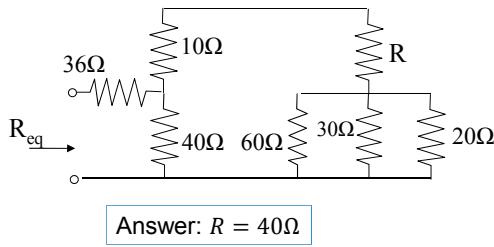

$$R_{eq} = (60 // 30 // 20 + R + 10) // 40 + 36$$

$$= (20 + R) // 40 + 36$$

$$R_{eq} = 60$$

$$(20 + R) // 40 + 36 = 60$$

$$\frac{40(20 + R)}{20 + R + 40} = 24$$

$$800 + 40R = 1440 + 24R$$


$$R = 40\Omega$$

**Problem 5 solution**


- a)  $R_{eq} = 10 // 15 + 20 // 5 \quad \Omega = 6 + 4 \quad \Omega = 10\Omega$
- b)  $R_{eq} = (24 // 4 // 24 + 7) // 30 \quad \Omega = (3 + 7) // 30 \quad \Omega = 7.5\Omega$

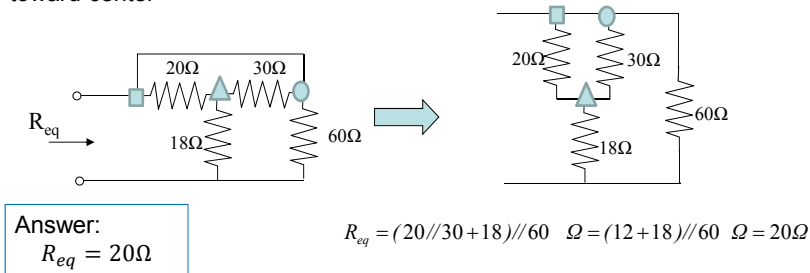**Problem 6 solution**


Straighten the top wire and slide the square and round connections toward center



**Problem 7 solution**

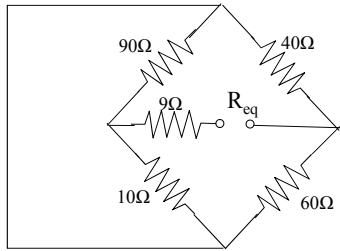


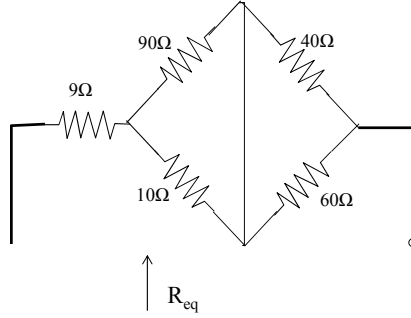
Flip 7Ω and straighten the wire from top to bottom



*Answer:*  
 $R_{eq} = 42\Omega$

$$R_{eq} = 9 + 90 // 10 + 40 // 60 = 9 + 9 + 24 = 42\Omega$$

**Problem 8 solution**

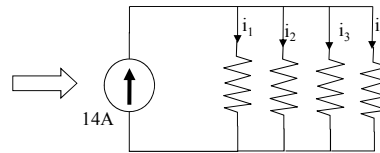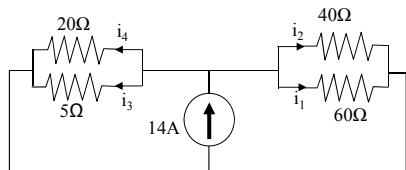

$$R_{eq} = 20 // 5 // 40 // 60 \Omega = \frac{24}{7} \Omega$$

$$V = IR_{eq} = 14 \times \frac{24}{7} V = 48V$$

$$i_1 = \frac{V}{60} = \frac{48}{60} A = 0.8A;$$

$$i_2 = \frac{V}{40} = \frac{48}{40} A = 1.2A$$

$$i_3 = \frac{V}{5} = \frac{48}{5} A = 9.6A;$$

$$i_4 = \frac{V}{20} = \frac{48}{20} A = 2.4A$$


*Answer:*

$$i_1 = 0.8A;$$

$$i_2 = 1.2A;$$

$$i_3 = 9.6A;$$

$$i_4 = 2.4A$$

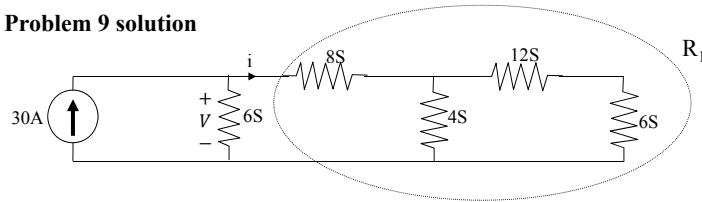**Problem 9 solution**

Conductances are given. Note that  $G=1/R$ , or  $R=1/G$ .  
 $6S \rightarrow 1/6 \Omega$ ;  $8S \rightarrow 1/8\Omega$ ;  $4S \rightarrow 1/4\Omega$ ;  $12S \rightarrow 1/12\Omega$

$$R_1 = \left[ \left( \frac{1}{12} + \frac{1}{6} \right) // \frac{1}{4} \right] + \frac{1}{8} \Omega = \frac{1}{4} \Omega$$


$$\text{By current division, } i_1 = 30 \times \frac{\frac{1}{6}}{\frac{1}{4} + \frac{1}{6}} A = 12A$$

$$V = i_1 R_1 = 12 \times \frac{1}{4} V = 3V$$

**Answer:**

$$i = 12A;$$


$$v = 3V$$

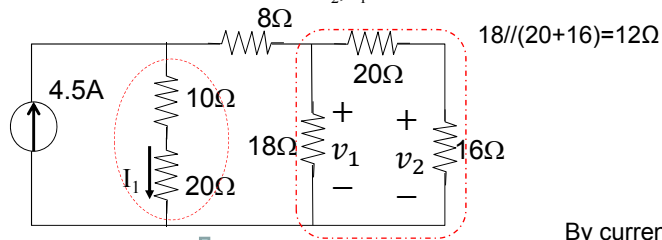**Problem 10 Solution:** Find  $v_2$ ,  $I_1$ .**Answer:**

$$I_1 = 1.8A;$$

$$v_2 = 14.4V$$

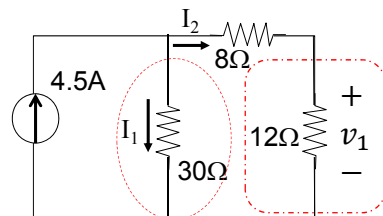Combine resistors, be careful which variables are still there in simplified circuit



By current division:

$$I_1 = \frac{(12 + 8)}{30 + 12 + 8} \times 4.5 = 1.8A$$

$$I_2 = \frac{16}{30 + 12 + 8} \times 4.5 = 2.7A$$

Ohm's Law:  $v_1 = 12I_2 = 32.4V$ ,To find  $v_2$ , need to go back to original circuit. By voltage division:

$$v_2 = \frac{16}{20+16} \times 32.4 = 14.4V$$

**Problem 11 solution:***Answer:*

$$i_0 = -0.333A$$

$$v_0 = 40V$$

Assign currents  $I$ ,  $i_1$ ,  $i_2$ . To find  $I$ ,  
need the total  $R_{eq}$  with respect to 50V

$$R_{eq} = 10 // 10 + 30 // 60 = 5 + 20 = 25\Omega$$

By Ohms Law,  $I = 50/25 = 2A$

By current division,


$$i_1 = \frac{10}{10 + 10} \times 2 = 1A$$

$$i_2 = \frac{60}{30 + 60} \times 2 = 1.333A$$

By KCL,  $i_0 = i_1 - i_2 = 1 - 1.333 = -0.333A$

Since 60Ω and 30Ω are in parallel, same voltage,

$$v_0 = 30 i_2 = 30 \times 1.333 = 40V$$

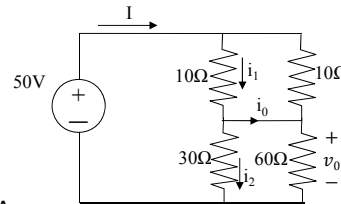**Problem 12 solution:***Answer:*

$$i = 1A; v_0 = 3.6V$$

$$R_1 = 20 // (12 + 18)\Omega = 12\Omega$$

$$R_2 = 9 + 70 // 30\Omega = 30\Omega$$

$$R_{eq} = (R_1 + 18) // R_2 + 5\Omega$$


$$= (12 + 18) // 30 + 5\Omega$$

$$= 20\Omega$$


$$i = V/R_{eq} = \frac{20}{20} A = 1A$$

$$i_1 = \frac{R_2}{R_1 + R_2 + 18} i = \frac{30}{12 + 30 + 18} \times 1A = 0.5A; \quad i_2 = \frac{20}{20 + 30} i_1 = 0.4 \times 0.5A = 0.2A$$

$$v_0 = 18i_2 = 18 \times 0.2V = 3.6V$$

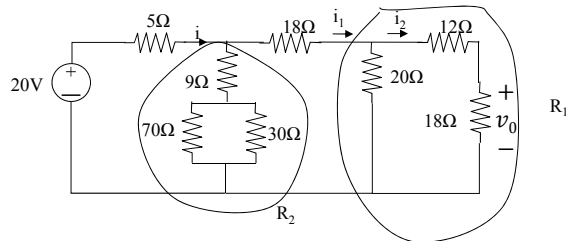

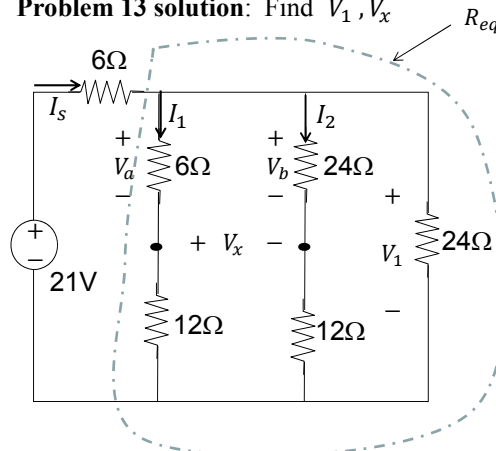**Problem 13 solution:** Find  $V_1, V_x$



**Answer:**

$$V_1 = 12V;$$

$$V_x = 4V$$

$$R_{eq} = (6 + 12) // (24 + 12) // 24$$

$$= 18 // 36 // 24 = 12 // 24 = 8\Omega$$

This  $R_{eq}$  is in series with  $6\Omega$

They share a total voltage of  $21V$

By voltage division:

$$V_1 = \frac{R_{eq}}{R_{eq} + 6} \times 21 = \frac{8}{8 + 6} \times 21$$

$$= 12V$$

By voltage division again:

$$V_a = \frac{6}{6 + 12} \times 12 = 4V;$$

$$V_b = \frac{24}{24 + 12} \times 12 = 8V$$

Alternatively:

$$I_1 = \frac{12}{18} = \frac{2}{3}A; I_2 = \frac{12}{36} = \frac{1}{3}A$$

$$V_a = 6I_1 = 4V; V_b = 24I_2 = 8V$$

By KVL:

$$V_b - V_x - V_a = 0,$$

$$V_x = V_b - V_a = 8 - 4 = 4V$$