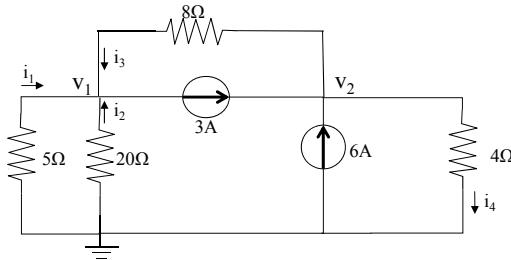


## Homework #4 solution

## Problem 1 solution



KCL at  $v_1$ :  $i_1 + i_2 + i_3 = 3$ ;  
at  $v_2$ :  $-i_3 - i_4 + 3 + 6 = 0 \Rightarrow i_3 + i_4 = 9$

Express resistor currents:


$$i_1 = -\frac{v_1}{5}; i_2 = -\frac{v_1}{20}; i_3 = \frac{v_2 - v_1}{8}; i_4 = \frac{v_2}{4}$$

Plug into KCL equations:

$$\begin{aligned} -\frac{v_1}{5} - \frac{v_1}{20} + \frac{v_2 - v_1}{8} &= 3; \\ \frac{v_2 - v_1}{8} + \frac{v_2}{4} &= 9; \end{aligned} \Rightarrow \begin{aligned} -3v_1 + v_2 &= 24; \\ -v_1 + 3v_2 &= 72 \end{aligned}$$

$v_1 = 0V$   
 $v_2 = 24V$

## Problem 2 solution

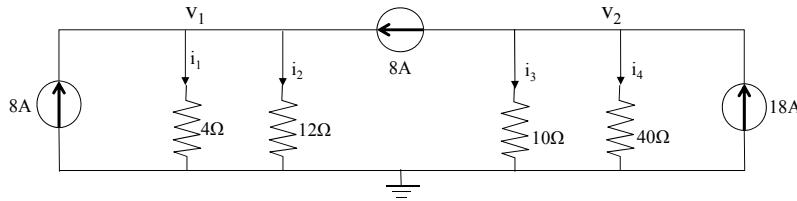


KCL at  $v_1, v_2$ :  $i_1 + i_2 = 8 + 8 = 16$ ;  
 $i_3 + i_4 = 18 - 8 = 10$ ;

Resistor currents:  $i_1 = \frac{v_1}{4}; i_2 = \frac{v_1}{12}; i_3 = \frac{v_2}{10}; i_4 = \frac{v_2}{40}$

$$\begin{aligned} \frac{v_1}{4} + \frac{v_1}{12} &= 16; \\ \frac{v_2}{10} + \frac{v_2}{40} &= 10 \end{aligned}$$

$v_1 = 48V; v_2 = 80V;$   
 $i_1 = 12A; i_2 = 4A;$   
 $i_3 = 8A; i_4 = 2A$

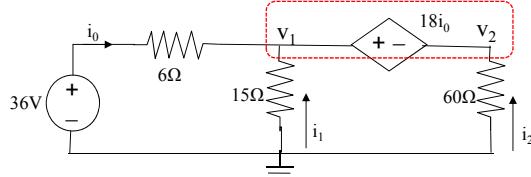**Problem 3 solution**

Due to the floating dependent voltage source, a super-node need to be formed


$$\text{KCL at super-node: } i_0 + i_1 + i_2 = 0$$

$$\text{By the dependent voltage source: } v_1 - v_2 = 18i_0$$

$$\text{Resistor currents: } i_0 = \frac{36 - v_1}{6}, \quad i_1 = -\frac{v_1}{15}, \quad i_2 = -\frac{v_2}{60}$$

$$\text{Plug in: } \begin{cases} \frac{36 - v_1}{6} - \frac{v_1}{15} - \frac{v_2}{60} = 0 \\ v_1 - v_2 = 18 \cdot \frac{36 - v_1}{6} \end{cases} \Rightarrow \begin{cases} 14v_1 + v_2 = 360 \\ 4v_1 - v_2 = 108 \end{cases} \Rightarrow \begin{cases} v_1 = 26V \\ v_2 = -4V \end{cases}$$

$$i_0 = \frac{36 - 26}{6} A = 1.667A \quad i_0 = 1.667A$$

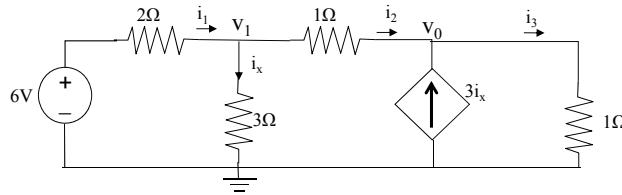
**Problem 4 solution**

$$i_1 = i_x + i_2$$

$$i_2 + 3i_x = i_3$$

$$i_1 = \frac{6 - v_1}{2}, \quad i_2 = \frac{v_1 - v_0}{1}, \quad i_3 = \frac{v_0}{1}, \quad i_x = \frac{v_1}{3}$$

$$\begin{cases} \frac{6 - v_1}{2} = \frac{v_1}{3} + \frac{v_1 - v_0}{1} \\ \frac{v_1 - v_0}{1} + v_1 = v_0 \end{cases} \Rightarrow \begin{cases} v_1 = 3.6V \\ v_0 = 3.6V \end{cases}$$

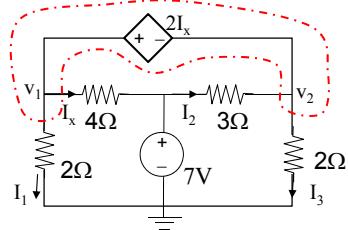**Problem 5 solution**

$$I_1 = \frac{v_1}{2}; \quad I_2 = \frac{7 - v_2}{3};$$

$$I_3 = \frac{v_2}{2}; \quad I_x = \frac{v_1 - 7}{4}$$

Combine  $v_1$  and  $v_2$  into a super node:

At super node:  $I_1 + I_x - I_2 + I_3 = 0$

$$\frac{v_1}{2} + \frac{v_1 - 7}{4} - \frac{7 - v_2}{3} + \frac{v_2}{2} = 0, \quad \times 12$$

$$\Rightarrow 6v_1 + 3v_1 - 21 - 28 + 4v_2 + 6v_2 = 0 \\ 9v_1 + 10v_2 = 49 \quad (1)$$

By the dependent voltage source  $2I_x$ :  $v_1 - v_2 = 2I_x$

$$\Rightarrow v_1 - v_2 = 2 \times \frac{v_1 - 7}{4}$$

$$2v_1 - 2v_2 = v_1 - 7$$


$$v_1 - 2v_2 = -7 \quad (2)$$

Solving (1) and (2):

$$v_1 = 1V;$$

$$v_2 = 4V;$$

$$I_x = (v_1 - 7)/4 = -1.5A$$

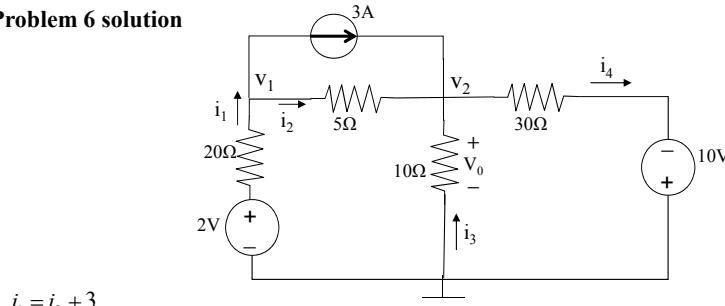**Problem 6 solution**


$$i_1 = i_2 + 3$$

$$i_2 + 3 + i_3 = i_4$$

$$i_1 = \frac{2 - v_1}{20}, \quad i_2 = \frac{v_1 - v_2}{5}, \quad i_3 = -\frac{v_0}{10}, \quad i_4 = \frac{v_2 + 10}{30}$$

$$\begin{cases} \frac{2 - v_1}{20} = \frac{v_1 - v_2}{5} + 3 \\ \frac{v_1 - v_2}{5} + 3 - \frac{v_0}{10} = \frac{v_2 + 10}{30} \end{cases} \Rightarrow \begin{cases} 5v_1 - 4v_2 = -58 \\ 3v_1 - 5v_2 = -40 \end{cases} \Rightarrow \begin{cases} v_1 = -10V \\ v_2 = 2V \\ v_0 = 2V \end{cases}$$

$$v_1 = -10V; \\ v_2 = 2V; \\ v_0 = 2V$$

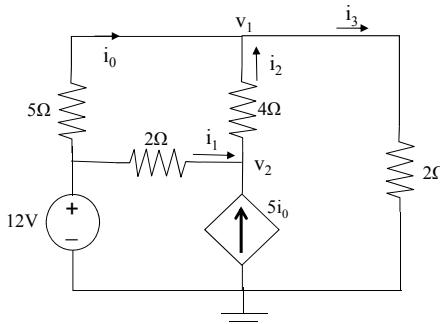**Problem 7 solution**

$$i_0 + i_2 = i_3$$


$$i_1 + 5i_0 = i_2$$

$$i_0 = \frac{12 - v_1}{5}, \quad i_1 = \frac{12 - v_2}{2}, \quad i_2 = \frac{v_2 - v_1}{4}, \quad i_3 = \frac{v_1}{2}$$

$$\begin{cases} \frac{12 - v_1}{5} + \frac{v_2 - v_1}{4} = \frac{v_1}{2} \\ \frac{12 - v_2}{2} + 12 - v_1 = \frac{v_2 - v_1}{4} \end{cases} \Rightarrow \begin{cases} 19v_1 - 5v_2 = 48 \\ v_1 + v_2 = 24 \end{cases} \Rightarrow \begin{cases} v_1 = 7V \\ v_2 = 17V \end{cases}$$

$$i_0 = \frac{12 - v_1}{5} = 1A$$

$v_1 = 7V;$   
 $v_2 = 17V;$   
 $i_0 = 1A$

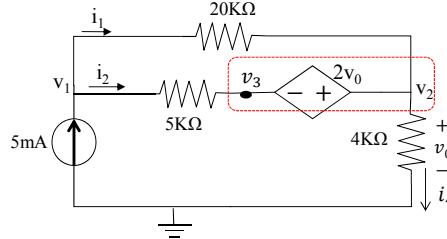**Problem 8 solution**

There is an additional voltage  $v_3$  which is different from  $v_1, v_2$ . Due to the floating voltage source, form a super-node.

$$\text{Resistor voltages: } i_1 = \frac{v_1 - v_2}{20K}; \quad i_2 = \frac{v_1 - v_3}{5K}; \quad i_4 = \frac{v_2}{4K}$$


$$\text{KCL at } v_1: \quad i_1 + i_2 = 5m;$$

$$\text{KCL at Supernode: } i_1 + i_2 - i_4 = 0$$

$$\text{By the voltage source: } v_2 - v_3 = 2v_0 = 2v_2$$

Put current expressions into KCL equations:

$$\begin{aligned} \frac{v_1 - v_2}{20K} + \frac{v_1 - v_3}{5K} &= 5m; & 5v_1 - v_2 - 4v_3 &= 100; \\ \frac{v_1 - v_2}{20K} + \frac{v_1 - v_3}{5K} - \frac{v_2}{4K} &= 0; & 5v_1 - 6v_2 - 4v_3 &= 0; \\ v_2 - v_3 &= 2v_2 & v_2 + v_3 &= 0 \end{aligned} \quad \boxed{v_1 = 8V; v_2 = 20V, v_3 = -20V}$$

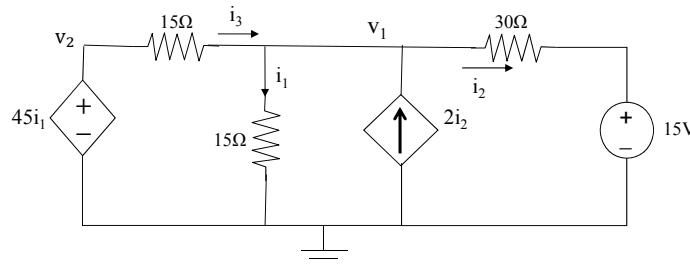**Problem 9 solution**

$$\text{Assign } v_2, \text{ Then } v_2 = 45i_1 \quad (1)$$

$$\text{Resistor currents: } i_1 = \frac{v_1}{15}; \quad i_2 = \frac{v_1 - 15}{30}; \quad i_3 = \frac{v_2 - v_1}{15}$$

$$\text{KCL at } v_1: \quad i_1 + i_2 - 2i_2 - i_3 = 0 \Rightarrow i_1 - i_2 - i_3 = 0$$

$$\text{Put in current expressions: } \frac{v_1}{15} - \frac{v_1 - 15}{30} - \frac{v_2 - v_1}{15} = 0$$

$$\text{Simplify to obtain: } 3v_1 - 2v_2 = -15; \quad (2)$$

$$\text{From (1): } v_2 = 45 \frac{v_1}{15} = 3v_1 \quad (3)$$

$$\text{Solving (2) and (3): } v_1 = 5V; \quad v_2 = 15V;$$

$$\boxed{i_1 = \frac{v_1}{15} = \frac{5}{15} = 0.333A}$$

$$i_2 = \frac{v_1 - 15}{30} = \frac{5 - 15}{30} = -0.333A$$