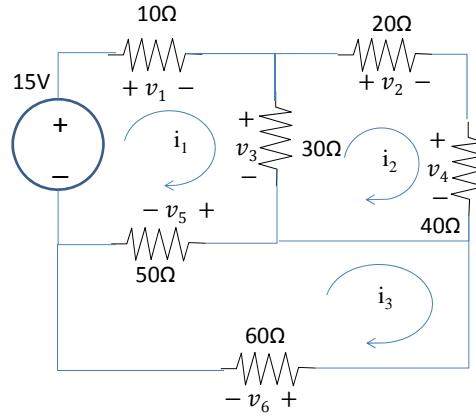
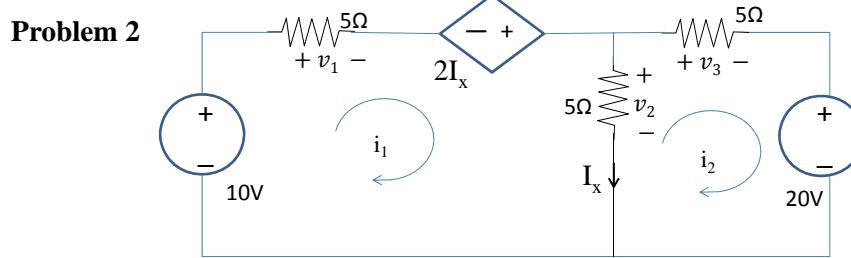


Problem 1

$$\begin{aligned} v_1 &= 10i_1, v_2 = 20i_2, v_3 = 30(i_1 - i_2) \\ v_4 &= 40i_2, v_5 = 50(i_1 - i_3), v_6 = 60i_3 \end{aligned}$$

KVL around 3 meshes:

$$\begin{aligned} \left\{ \begin{array}{l} v_1 + v_3 + v_5 - 15 = 0 \\ v_2 + v_4 - v_3 = 0 \\ v_6 - v_5 = 0 \end{array} \right. &\quad \downarrow \\ \left\{ \begin{array}{l} 10i_1 + 30(i_1 - i_2) + 50(i_1 - i_3) - 15 = 0 \\ 20i_2 + 40i_2 - 30(i_1 - i_2) = 0 \\ 60i_3 - 50(i_1 - i_3) = 0 \end{array} \right. &\quad \downarrow \\ \left\{ \begin{array}{l} 18i_1 - 6i_2 - 10i_3 = 3 \\ -i_1 + 3i_2 = 0 \\ -5i_1 + 11i_3 = 0 \end{array} \right. &\quad \Rightarrow \quad \boxed{\begin{array}{l} i_1 = 261.9 \text{mA} \\ i_2 = 87.30 \text{mA} \\ i_3 = 119.0 \text{mA} \end{array}} \end{aligned}$$

**Problem 2**

$$I_x = i_1 - i_2, v_1 = 5i_1, v_2 = 5I_x = 5(i_1 - i_2), v_3 = 5i_2$$

$$\left\{ \begin{array}{l} v_1 - 2I_x + v_2 - 10 = 0 \\ v_3 + 20 - v_2 = 0 \end{array} \right. \quad \Rightarrow \quad \left\{ \begin{array}{l} 5i_1 - 2(i_1 - i_2) + 5(i_1 - i_2) - 10 = 0 \\ 5i_2 + 20 - 5(i_1 - i_2) = 0 \end{array} \right.$$

$$\Rightarrow \left\{ \begin{array}{l} 8i_1 - 3i_2 = 10 \\ -i_1 + 2i_2 = -4 \end{array} \right. \quad \Rightarrow \quad \boxed{\begin{array}{l} i_1 = 0.615 \text{A} \\ i_2 = -1.692 \text{A} \end{array}}$$

$$\boxed{I_x = i_1 - i_2 = 2.307 \text{A}}$$


Problem 3

$$\begin{aligned} v_1 &= 9i_1, v_2 = 10(i_2 - i_1), v_3 = -6i_2 \\ v_4 &= 7(i_2 - i_3), v_5 = 8i_3 \end{aligned}$$

$$\begin{cases} v_1 - 8 - v_2 = 0 \\ v_2 + v_4 + 5 - v_3 = 0 \\ 8 + v_5 - 5 - v_4 = 0 \end{cases}$$

$$\begin{cases} 9i_1 - 8 - 10(i_2 - i_1) = 0 \\ 10(i_2 - i_1) + 7(i_2 - i_3) + 5 + 6i_2 = 0 \\ 8 + 8i_3 - 5 - 7(i_2 - i_3) = 0 \end{cases}$$
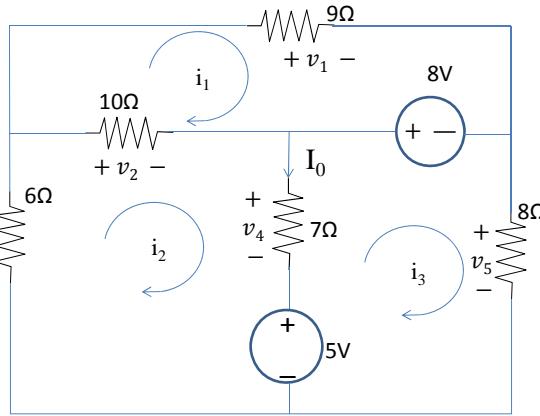
$$\begin{cases} 19i_1 - 10i_2 = 8 \\ -10i_1 + 23i_2 - 7i_3 = -5 \\ -7i_2 + 15i_3 = -3 \end{cases}$$



$$\begin{cases} i_1 = 0.3414A \\ i_2 = -0.1513A \\ i_3 = -0.2706A \end{cases}$$


$$I_0 = i_2 - i_3 = 0.1193A$$

Problem 4

$$\begin{aligned} v_1 &= 20i_1, v_2 = 20(i_2 - i_1), v_3 = -20i_2 \\ v_4 &= 30(i_3 - i_1), v_5 = 30(i_2 - i_3), v_{ab} = 30i_3 \end{aligned}$$

$$\begin{cases} -50 + v_1 - v_4 - v_2 = 0 \\ -20 + v_2 + v_5 - v_3 = 0 \\ v_4 + V_{ab} - v_5 = 0 \end{cases}$$
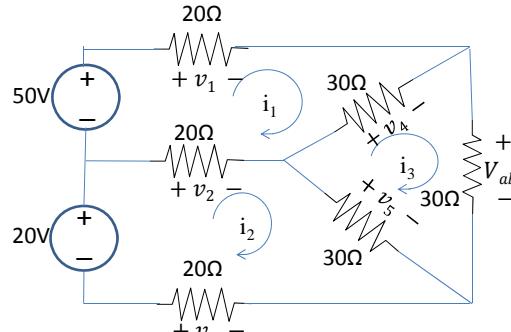
$$\begin{cases} -50 + 20i_1 - 30(i_3 - i_1) - 20(i_2 - i_1) = 0 \\ -20 + 20(i_2 - i_1) + 30(i_2 - i_3) + 20i_2 = 0 \\ 30(i_3 - i_1) + 30i_3 - 30(i_2 - i_3) = 0 \end{cases}$$



$$\begin{cases} i_1 = 1.333A \\ i_2 = 1A \\ i_3 = 0.778A \end{cases}$$

$$V_{ab} = 30i_3 = 23.33V$$

Problem 5

$$\begin{aligned} v_1 &= -2i_1, v_2 = -5i_2, v_3 = 4(i_2 - i_1) \\ v_4 &= 3(i_1 - i_3) \end{aligned}$$


Due to the current source,
a super-mesh needs to be formed

$$\begin{aligned} \text{mesh 1: } & 8 + v_4 - v_3 - v_2 = 0; \\ \text{supermesh: } & 20 - v_2 + v_3 - v_4 = 0; \\ \text{by current source: } & i_3 - i_2 = 1 \end{aligned}$$



$$\begin{aligned} 8 + 4(i_1 - i_3) - 4(i_2 - i_1) + 2i_1 &= 0; \\ 20 + 5i_2 + 4(i_2 - i_1) - 4(i_1 - i_3) &= 0; \\ i_3 - i_2 &= 1 \end{aligned}$$

$$\Rightarrow \begin{array}{l} 9i_1 - 4i_2 - 3i_3 = -8; \\ -7i_1 + 9i_2 + 3i_3 = -20; \\ -i_2 + i_3 = 1 \end{array} \Rightarrow \boxed{\begin{array}{l} i_1 = -3.746A \\ i_2 = -4.102A \\ i_3 = -3.102A \end{array}} \quad \boxed{i_0 = i_2 - i_1 = -0.356A}$$

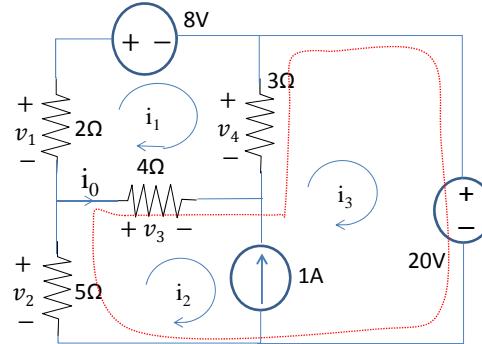**Problem 6**

$$\begin{aligned} v_1 &= 4i_1, v_2 = 5i_2, v_3 = 3(i_3 - i_1), v_4 = 8(i_4 - i_2) \\ v_5 &= 7(i_3 - i_4), v_6 = 6i_4 \end{aligned}$$


$$\text{Supermesh: } v_1 + v_2 - v_4 - v_3 = 0;$$

$$\text{Mesh 3: } v_3 + v_5 - 10 = 0;$$

$$\text{Mesh 4: } v_4 + v_6 - v_5 = 0;$$

$$\text{Current source: } i_2 - i_1 = 3$$
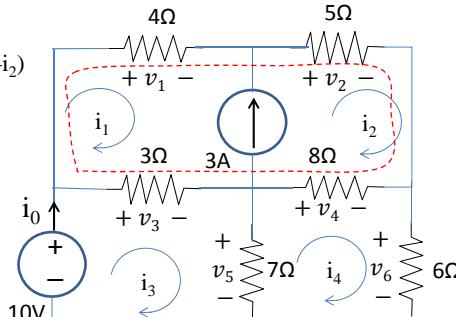
$$\begin{aligned} 4i_1 + 5i_2 - 8(i_4 - i_2) - 3(i_3 - i_1) &= 0 \\ 3(i_3 - i_1) + 7(i_3 - i_4) &= 10 \\ 8(i_4 - i_2) + 6i_4 - 7(i_3 - i_4) &= 0 \\ i_2 - i_1 &= 3 \end{aligned}$$



$$\begin{array}{l} 7i_1 + 13i_2 - 3i_3 - 8i_4 = 0 \\ -3i_1 + 10i_3 - 7i_4 = 10 \\ -8i_2 - 7i_3 + 21i_4 = 0 \\ -i_1 + i_2 = 3 \end{array} \Rightarrow \boxed{\begin{array}{l} i_1 = -1.297A \\ i_2 = 1.703A \\ i_3 = 1.389A \\ i_4 = 1.112A \end{array}} \quad \boxed{i_0 = i_3 = 1.389A}$$


Problem 7

$$\begin{aligned} v_1 &= 8i_1, v_2 = 6(i_2 - i_1), v_3 = -9i_2 \\ v_4 &= 7(i_3 - i_1), \quad i_0 = -i_2 \end{aligned}$$

$$\begin{aligned} \text{Mesh 1: } & v_1 - v_4 - v_2 = 0 \\ \text{Supermesh: } & v_2 + v_4 + 15 - v_3 = 0 \\ \text{Current source: } & i_3 - i_2 = 2i_0 \end{aligned}$$

$$\begin{aligned} & 8i_1 - 7(i_3 - i_1) - 6(i_2 - i_1) = 0 \\ & 6(i_2 - i_1) + 7(i_3 - i_1) + 15 + 9i_2 = 0 \\ & i_3 - i_2 = -2i_2 \end{aligned}$$
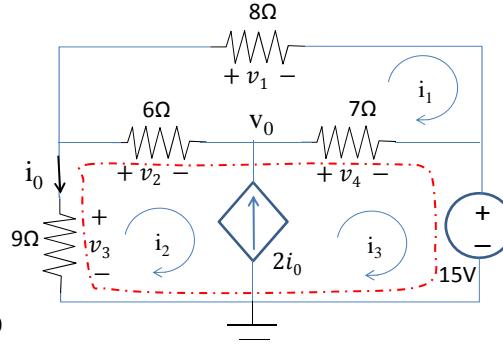
$$\begin{aligned} & 21i_1 - 6i_2 - 7i_3 = 0 \\ & -13i_1 + 15i_2 + 7i_3 = -15 \\ & i_2 + i_3 = 0 \end{aligned}$$



$$\begin{aligned} i_1 &= 0.0829A \\ i_2 &= -1.740A \\ i_3 &= 1.740A \end{aligned}$$

$$\begin{aligned} i_0 &= -i_2 = 1.740A \\ v_0 &= 15 + v_4 = 15 + 7(1.740 - 0.0829)V = 26.600V \end{aligned}$$


Problem 8

$$i_1 = \frac{V_x}{2}$$

KCL at center node:

$$i_1 + 6 + \frac{V_x}{4} = 0$$

$$V_x = -8V, \quad i_1 = -4A$$

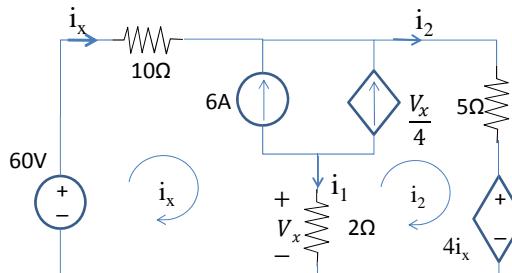

$$10i_x + 5i_2 + 4i_x = 60; \text{ KVL along outer mesh}$$

$$i_x - i_2 = i_1 = -4, \text{ KCL at bottom node}$$

$$\begin{aligned} 14i_x + 5i_2 &= 60; \\ i_x - i_2 &= -4 \end{aligned}$$

$$\begin{aligned} i_2 &= 6.105A; \\ i_x &= 2.105A; \\ V_x &= -8V \end{aligned}$$