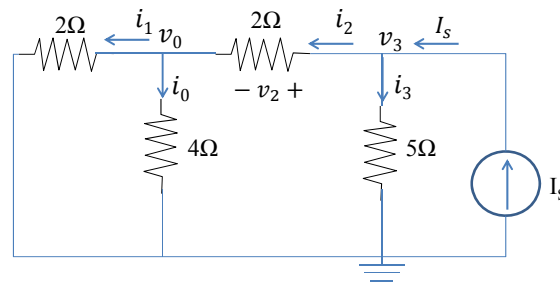


Problem 1 Find I_s so that $i_0 = 1A$. Also find i_0 for $I_s = 15A$. Use Linearity.



Pick the ground and assign node voltages, resistor voltages and currents

Start from $i_0 = 1A$, then by basic laws:

$$v_0 = 4i_0 = 4 \times 1 = 4V$$

$$i_1 = \frac{v_0}{2} = \frac{4}{2} = 2A$$

$$i_2 = i_0 + i_1 = 1 + 2 = 3A$$

$$v_2 = 2i_2 = 2 \times 3 = 6V$$

$$v_3 = v_0 + v_2 = 4 + 6 = 10V$$

$$i_3 = \frac{v_3}{5} = \frac{10}{5} = 2A$$

$$I_s = i_2 + i_3 = 3 + 2 = 5A$$

$$\text{Thus, } \frac{i_0}{I_s} = \frac{1}{5} \Rightarrow i_0 = \frac{1}{5}I_s$$

So when $I_s = 15A$,

$$i_0 = \frac{1}{5}I_s = \frac{1}{5} \times 15 = 3A$$

Problem 2: Find V_s so that $v_0 = 5V, 8V, 3V$ respectively. What is v_0 when $V_s = 26V$?
Use Linearity.

Start from $v_0 = 8V$,
then other variables
will be whole numbers.
Then,

$$i_1 = v_0/8 = 1A$$

$$v_1 = 2i_1 = 2V$$

$$v_2 = v_0 + v_1 = 2 + 8 = 10V$$

$$i_0 = \frac{v_2}{5} = 10/5 = 2A$$

$$i_2 = i_0 + i_1 = 2 + 1 = 3A$$

$$v_3 = 2i_2 = 2 \times 3 = 6V$$


$$v_4 = v_2 + v_3 = 6 + 10 = 16V$$

$$i_3 = \frac{v_4}{8} = \frac{16}{8} = 2A$$

$$i_4 = i_2 + i_3 = 3 + 2 = 5A$$

$$v_5 = 2i_4 = 2 \times 5 = 10V$$

$$V_s = v_4 + v_5 = 16 + 10 = 26V$$

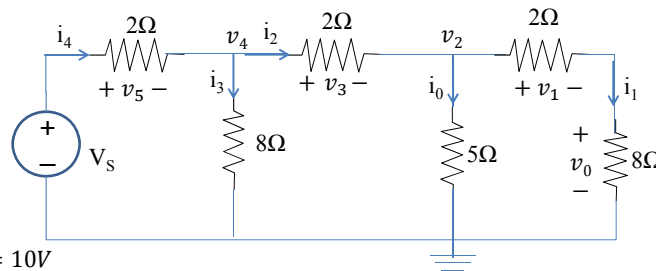

$$v_0 = 8V \longleftrightarrow V_s = 26V$$

$$k = \frac{v_0}{V_s} = \frac{8}{26} = 0.3077 \Rightarrow v_0 = 0.3077V_s$$

$$\text{So when } v_0 = 5V, V_s = 5/0.3077 = 16.25V$$

$$\text{when } v_0 = 8V, V_s = 8/0.3077 = 26V$$

$$\text{when } v_0 = 3V, V_s = 3/0.3077 = 9.75V$$

$$\text{When } V_s = 26V, v_0 = 26 \times 0.3077V = 8V$$


You may start v_0 with a different number, but other variables may not be whole numbers.

Problem 3: Apply Linearity to calculate v_0 .

Assign ground and other variables.
Assume v_0 to be a certain number;
Use basic laws to find the
corresponding V_s
(ignore the given value 51V)

Start with $v_0 = 2V$:
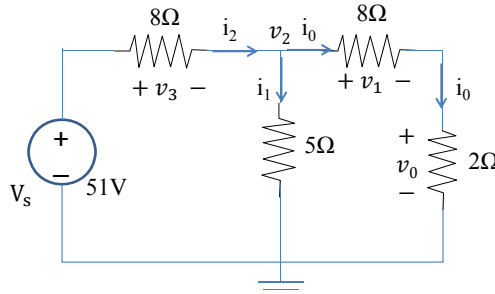
$$\begin{aligned} v_0 &= 2V \\ i_0 &= \frac{v_0}{2} = 1A \\ v_1 &= 8i_0 = 8V \\ v_2 &= v_1 + v_0 = 8 + 2 = 10V \\ i_1 &= \frac{v_2}{5} = \frac{10}{5} = 2A \\ i_2 &= i_0 + i_1 = 1 + 2 = 3A \\ v_3 &= 8i_2 = 8 \times 3 = 24V \\ V_s &= v_2 + v_3 = 10 + 24 = 34V \end{aligned}$$



In summary: $v_0 = 2V \Rightarrow V_s = 34$

$$\text{Thus } k = \frac{v_0}{V_s} = \frac{2}{34} = \frac{1}{17}$$


$$\Rightarrow v_0 = \frac{1}{17}V_s$$

So when $V_s = 51V$,

$$v_0 = \frac{1}{17} \times 51 = 3V$$

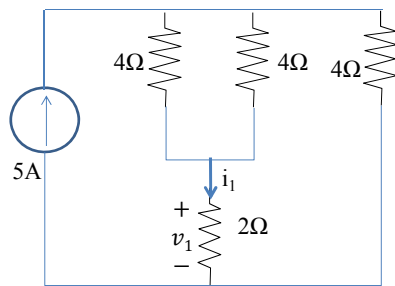Problem 4: Determine v_0 by superposition.

Due to 5A: turn off 8V with short circuit.




Since $4//4+2\Omega$ is in parallel with 4Ω ,

By current division:

$$\begin{aligned} i_1 &= \frac{4}{4+4} \times 5 = 2.5V; \\ v_1 &= 2i_1 = 5V \end{aligned}$$

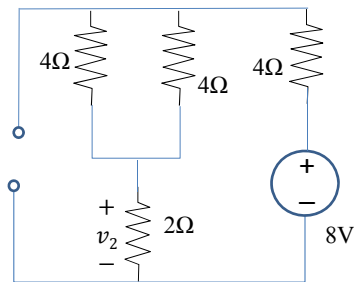Due to 8V, turn off 5A with open circuit:






By voltage division,


$$v_2 = \frac{2}{2+2+4} \times 8 = 2V$$

Thus by superposition:

$$v_0 = v_1 + v_2 = 5 + 2 = 7V$$

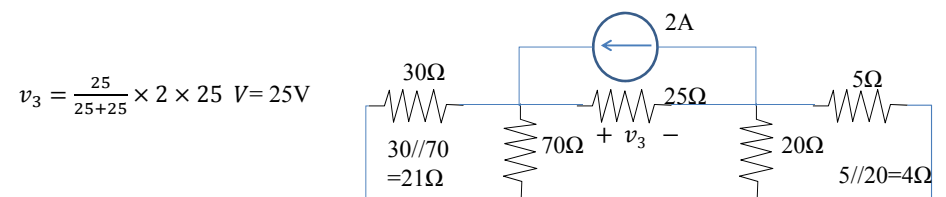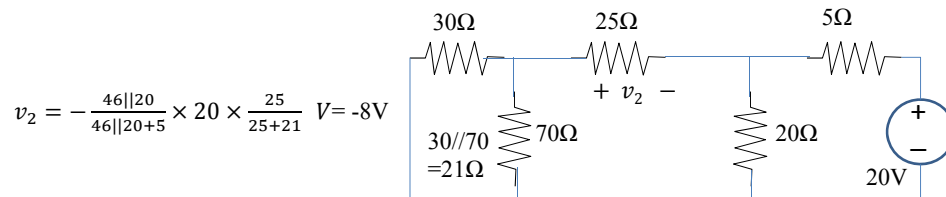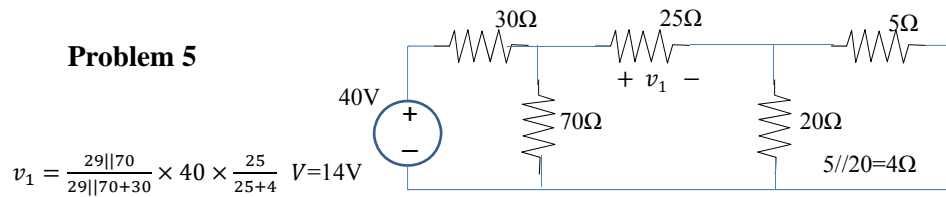
Problem 5

$$v_0 = v_1 + v_2 + v_3 = 14 - 8 + 25 \text{ V} = 31V$$

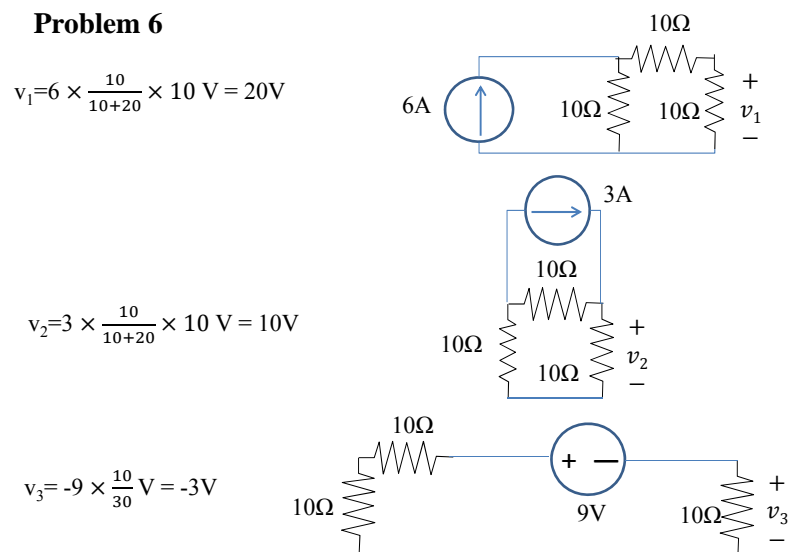
Problem 6

$$v_0 = v_1 + v_2 + v_3 = 20 + 10 - 3 \text{ V} = 27V$$


Problem 7

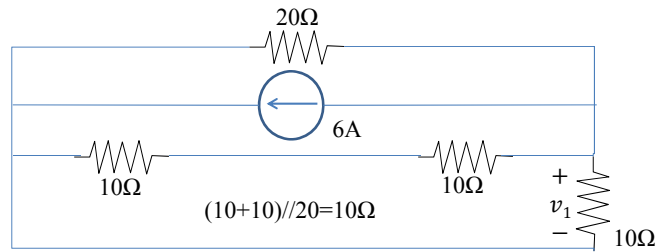
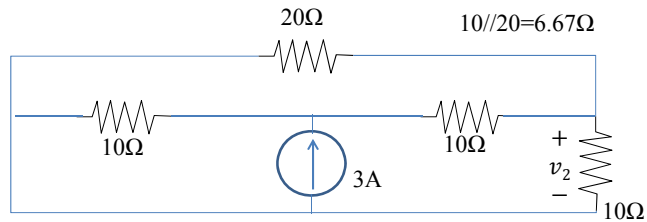
$$v_1 = -6 \times \frac{10}{10+10} \times 10 = -30V$$


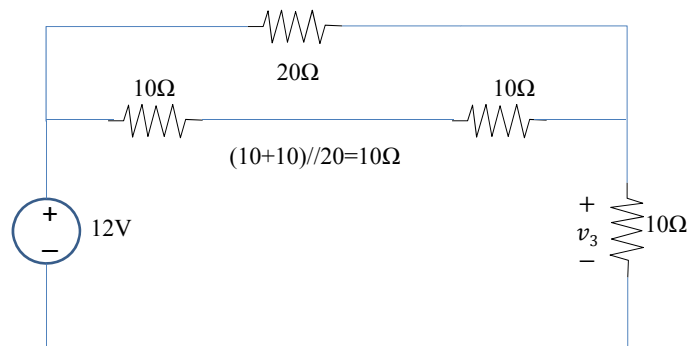
$$v_2 = 3 \times \frac{10}{6.67+10+10} \times \frac{20}{10+20} \times 10 = 7.5V$$




$$v_3 = 12 \times \frac{10}{10+10} V = 6V$$


$$v_0 = v_1 + v_2 + v_3 = -30 + 7.5 + 6 V = -16.5V$$

Problem 8

Better to keep the 5Ω resistor in every step

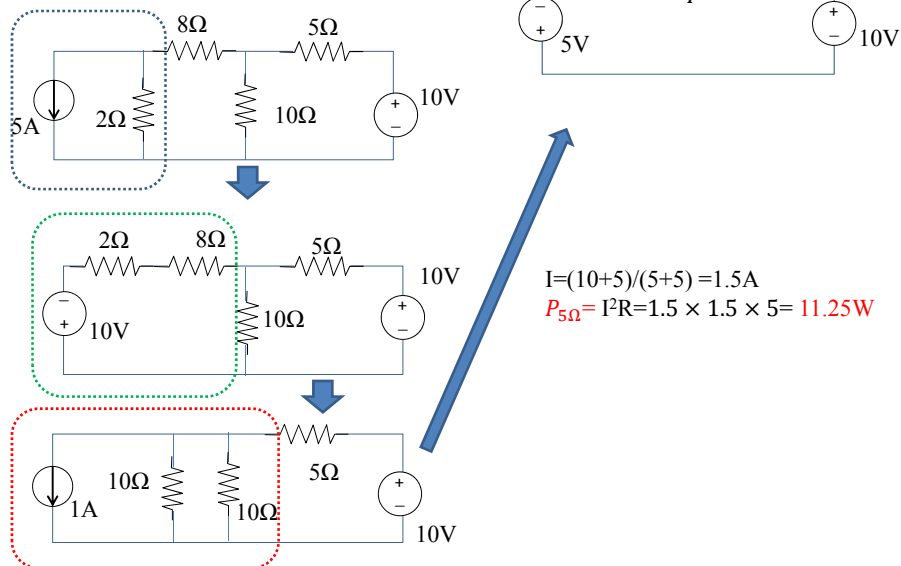


Problem 9

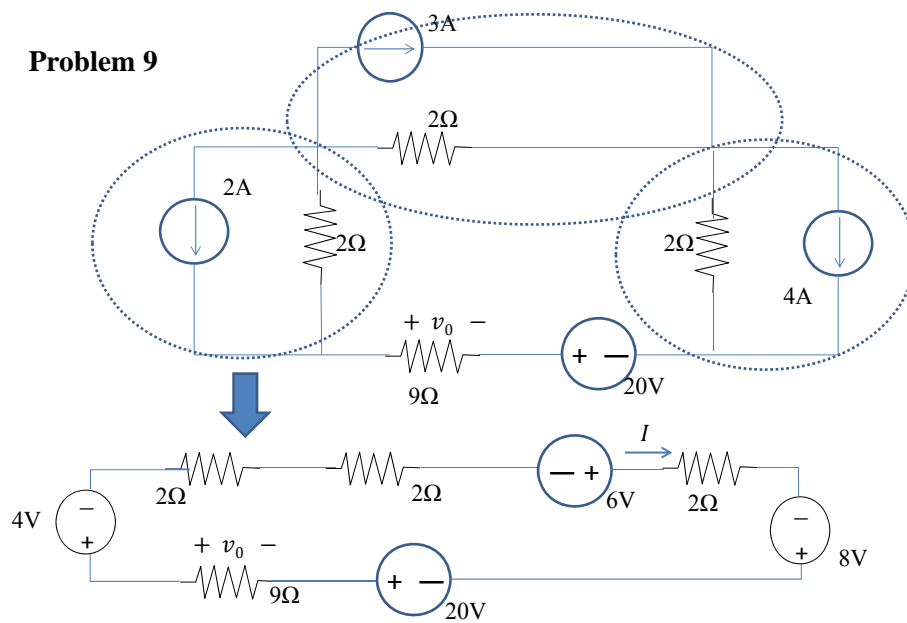

$$\text{Loop current: } I = \frac{20+8+6-4}{2+2+2+9} = \frac{30}{15} = 2A; \quad v_0 = -9I = -9 \times 2 = -18V$$

Problem 10

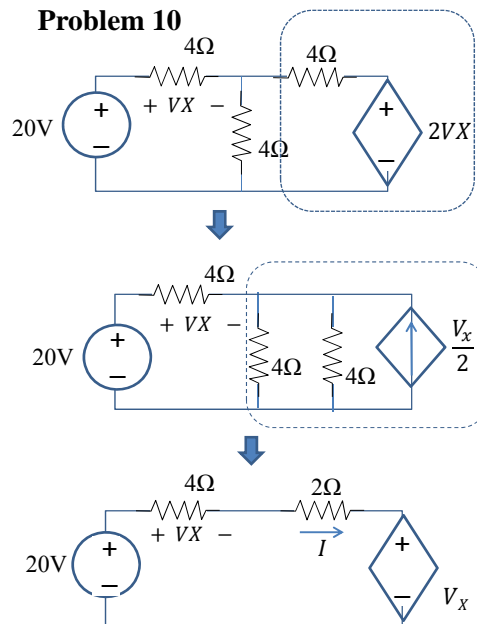

$$\begin{aligned}
 V_x &= 4I; \\
 \text{KVL: } V_x + 2I + V_x &= 20; \\
 4I + 2I + 4I &= 20; \\
 I &= 2A; \\
 V_x &= 4I = 8V
 \end{aligned}$$