
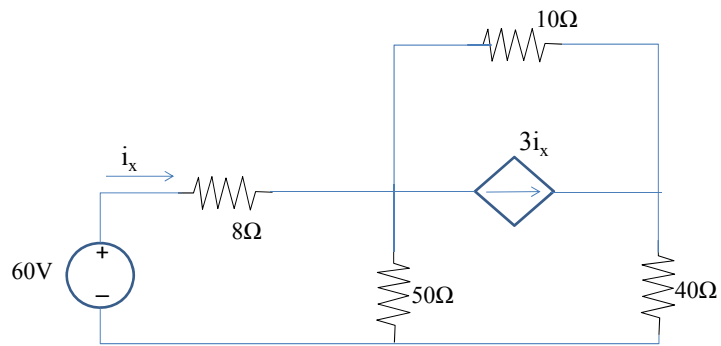
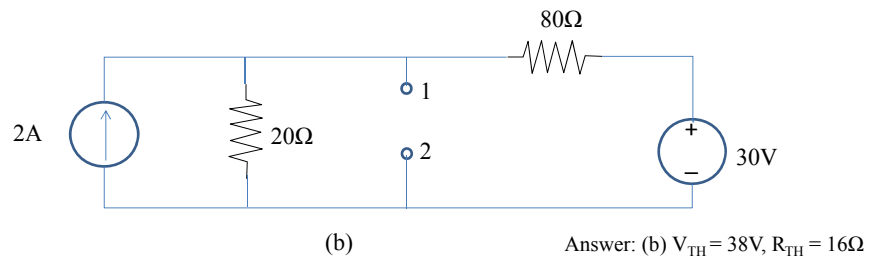


Problem 1

Use source transformation to find i_x in the circuit. ($I_x=3.33A$)

**Problem 2**


Determine R_{TH} and V_{TH} at terminals 1-2 of each circuit.

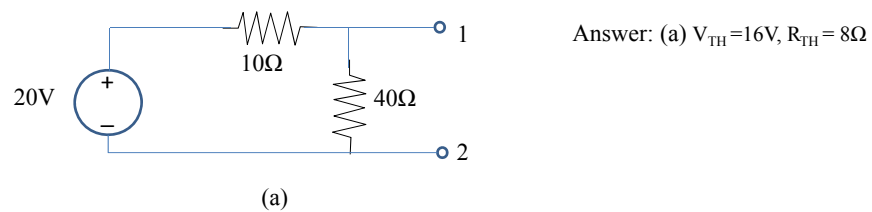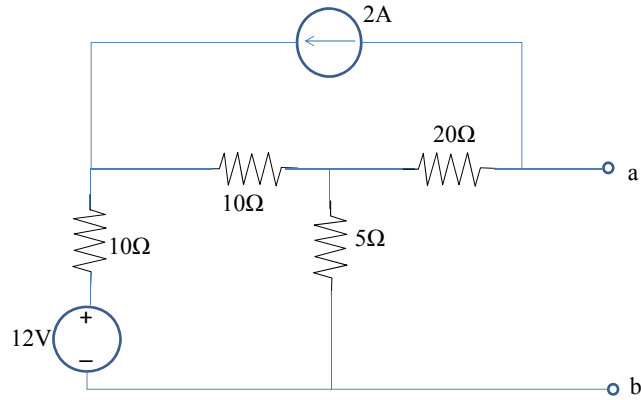


Problem 3

Obtain the Thevenin equivalent at terminals a-b of the circuit.

Answer: $V_{TH} = -41.6V$, $R_{TH} = 24\Omega$

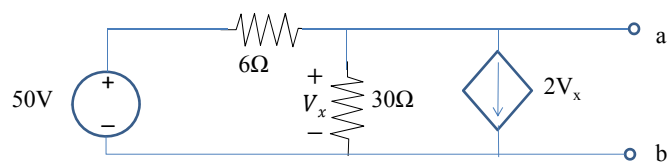**Problem 4**

Obtain the Thevenin and Norton equivalent circuits of the following circuit with respect to terminals a and b.




Answer: $V_{TH} = 3.788V$, $R_{TH} = R_N = 0.455\Omega$, $I_N = 8.325A$

Problem 5

Determine the Norton's equivalent at terminals a-b for the following circuit.

Answer: $I_N = 1.714\text{A}$, $R_N = 7\Omega$

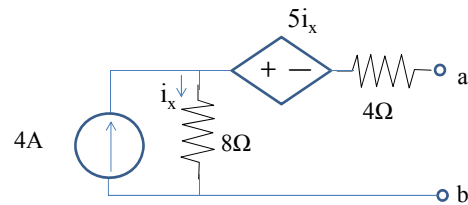**Problem 6**


Obtain the Norton's equivalent as viewed from terminals:

(a) a-b

(b) c-d

Answer: (a) a-b $R_N = 2\Omega$, $I_N = 6\text{A}$


(b) c-d $R_N = 1.5\Omega$, $I_N = 8\text{A}$

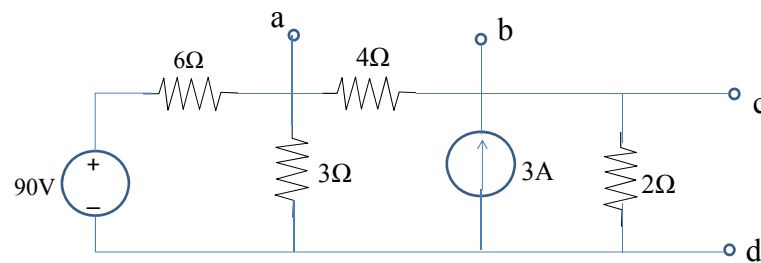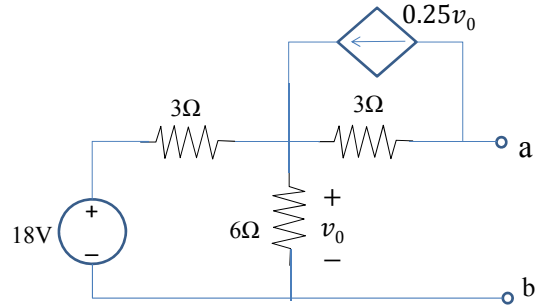

Problem 7


Find the Thevenin equivalent at terminals a-b of the circuit.

Answer: $V_{TH} = 3V$, $R_{TH} = 3.5\Omega$

**Problem 8**


Determine the Thevenin's and Norton's equivalents at terminals a-b

Answer: $I_N = -1.371A$, $R_N = R_{TH} = 29.167\Omega$, $V_{TH} = -40V$

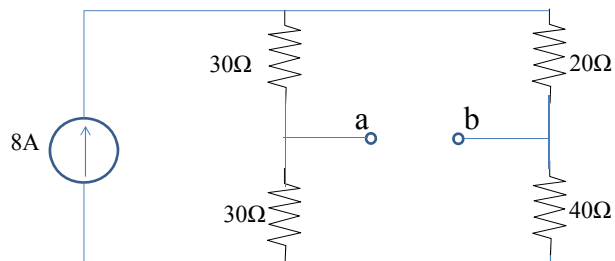


Problem 9

Find the maximum power that can be delivered to the resistor R in the following circuit. Answer: $V_{TH} = 4V$, $R_{TH} = 3.2\Omega$, $P_{max} = 1.25W$

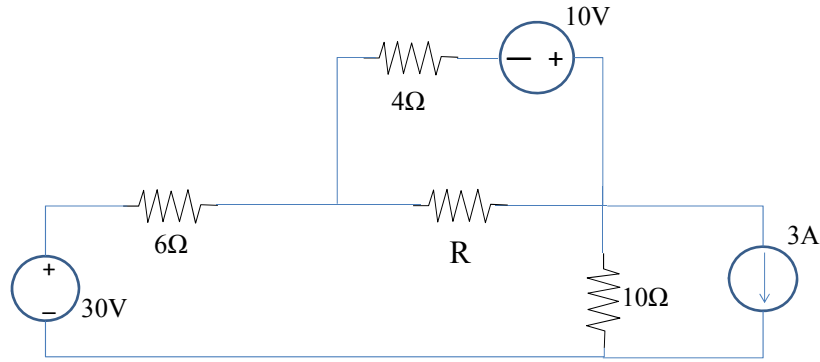**Problem 10**

Determine the maximum power delivered to the variable resistor R shown in the circuit. Answer: $V_{th} = 8V$, $R_{th} = 26\Omega$, $p_{max} = 0.615W$

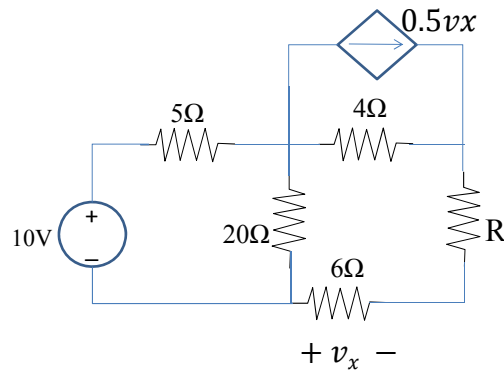

Problem 11

Determine the maximum power that can be delivered to the variable resistor R in the circuit. Answer: $P_{\max}=14.424\text{W}$

