
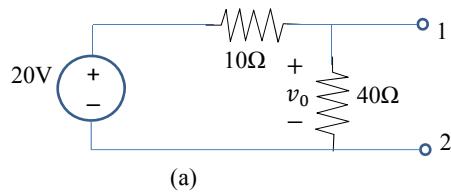
**Problem 2**

By voltage division:


$$V_{TH} = v_0 = 20 \times \frac{40}{10+40} V = 16V$$

$$R_{TH} = 10//40\Omega = 8\Omega$$

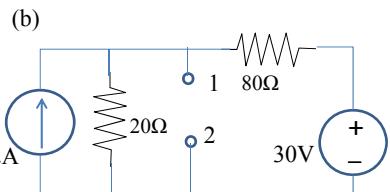


$$R_{TH} = 80//20 = 16\Omega$$
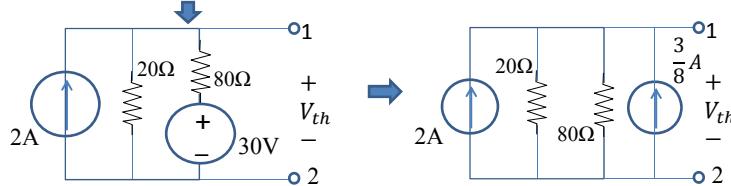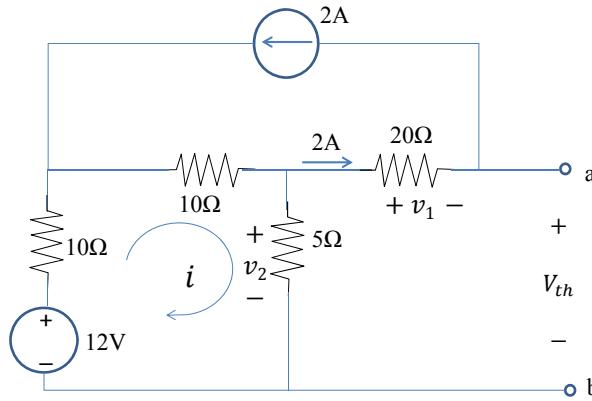
$$V_{TH} = (80//20)(2 + \frac{3}{8}) \\ = 16 \times \frac{19}{8} = 38V$$

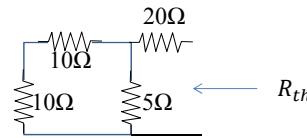


Problem 3

$$V_{th} = v_2 - v_1 \\ v_1 = 20 \times 2 = 40V \\ \text{To find } v_2, \text{ apply KVL to the bottom loop,}$$



$$-12 + 10i + 10(2+i) + 5i = 0 \\ \Rightarrow i = -0.32A \\ v_2 = 5i = -0.32 \times 5 = -1.6V \\ V_{TH} = v_2 - v_1 = -1.6 - 40 = -41.6V \\ R_{TH} = 20 + 5/(10+10) \Omega = 24\Omega$$

**Problem 4**

By KCL,
 $I = \frac{V_x}{30} + 2V_x$

KVL around left loop:

$$6\left(\frac{V_x}{30} + 2V_x\right) + V_x - 50 = 0 \\ \Rightarrow V_x = 3.788V$$



$V_{TH} = Vx = 3.788V$

To find R_{th} , turn off 50V with short circuit, supply 1A source,
 Need to find v_0 . Note $v_0 = V_x$
 KCL at top node:

$$\frac{V_x}{30} + \frac{V_x}{6} + 2V_x = 1, V_x = 0.455V, \\ \Rightarrow v_0 = 0.455V \\ \Rightarrow R_{th} = \frac{v_0}{1} = 0.455\Omega$$

$I_N = V_{TH}/R_{TH} = 8.325A$

$V_{TH} = 3.788V, R_{TH} = R_N = 0.455\Omega, I_N = 8.325A$

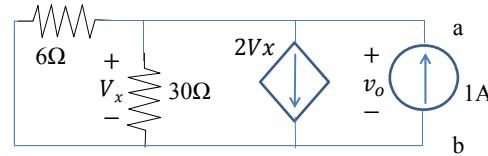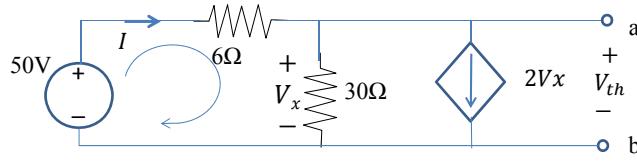

Problem 5


$$I_N = 4 - ix$$

KVL along right mesh:

$$5i_x + 4(4 - ix) - 8ix = 0$$

$$i_x = 2.286A$$

$$I_N = 4 - ix = 1.714A$$

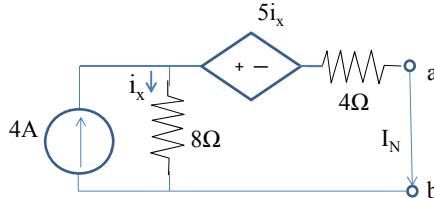


To find R_N , turn off 4A, supply 1A source, need to find v_0

Since $i_x = 1A$, by KVL


$$v_0 = 4i_x - 5i_x + 8i_x = 7i_x = 7V$$

Then,

$$R_N = v_0/1 = 7\Omega$$

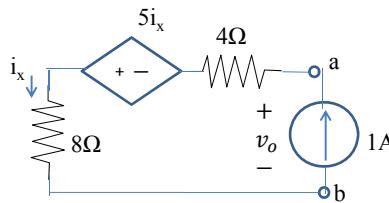

$$I_N = 1.714A, R_N = 7\Omega$$

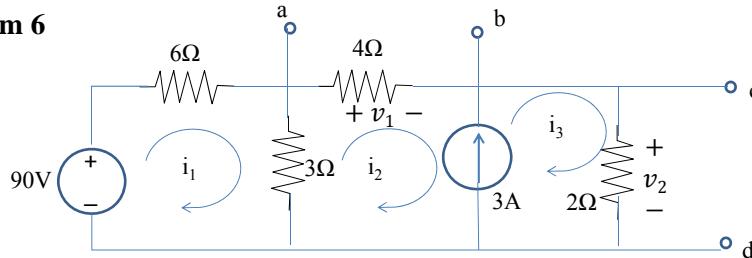Problem 6

$$\begin{cases} 6i_1 + 3(i_1 - i_2) - 90 = 0 \\ 4i_2 + 2i_3 - 3(i_1 - i_2) = 0 \\ i_3 - i_2 = 3 \end{cases} \rightarrow \begin{cases} i_1 = 11A \\ i_2 = 3A \\ i_3 = 6A \end{cases} \quad \begin{aligned} V_{ab} &= v_1 = 4i_2 = 12V \\ V_{cd} &= v_2 = 2i_3 = 12V \end{aligned}$$

(a) a-b

$$\begin{aligned} R_N &= 4/(6/3 + 2)\Omega = 2\Omega \\ I_N &= V_{ab}/2 = 6A \end{aligned}$$

(b) c-d

$$\begin{aligned} R_N &= 2//(6/3 + 4)\Omega = 1.5\Omega \\ I_N &= V_{cd}/1.5 = 8A \end{aligned}$$

You may also use source transformation to obtain the same results


Problem 7

Since same current goes through the left 3Ω , and 6Ω , voltage division can be applied to find v_o

$$v_0 = 18 \times \frac{6}{3+6} V = 12V$$

$$v_1 = 3 \times 0.25v_0 = 9V$$

$$V_{TH} = v_0 - v_1 = 3V$$

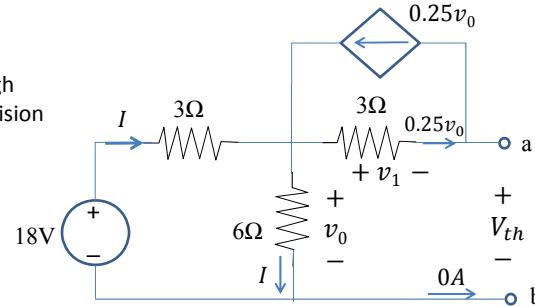


To find R_{th} , turn off 18V, supply 1A source, need to find v_s . In this case 3Ω and 6Ω are in parallel

$$v_0 = (3//6) \times 1 = 2V$$


$$v_1 = 3I_3 = 3 \times (0.25v_0 - 1) = -1.5V$$

$$v_s = v_0 - v_1 = 3.5V$$

$$R_{TH} = v_s / 1 = 3.5\Omega$$

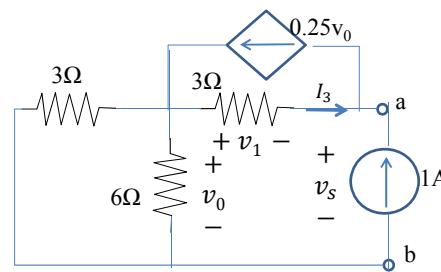

$$V_{TH} = 3V, R_{TH} = 3.5\Omega$$

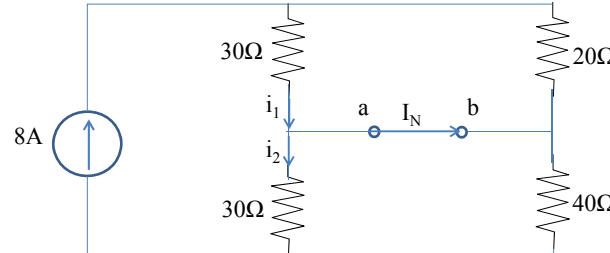
Problem 8

By KCL, $I_N = i_1 - i_2$
 i_1, i_2 can be found by current division:

$$I_N = i_1 - i_2 = 8 \times \frac{20}{30+20} - 8 \times \frac{40}{30+40} A = -1.371A$$

$$R_N = R_{TH} = (30+20)/(30+40)\Omega = 29.167\Omega$$

$$V_{TH} = I_N R_{TH} = -40V$$

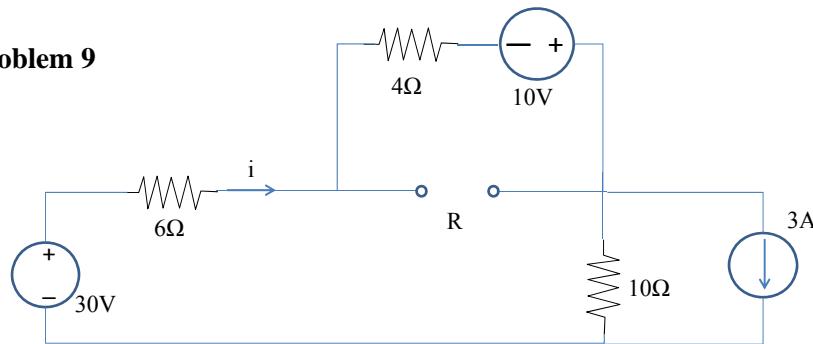Problem 9

Need to compute Thevenin's equivalent with respect to the two terminals:

$$-30 + 6i + 4i - 10 + 10(i - 3) = 0$$

$$i = 3.5 \text{ A}$$


$$V_{TH} = 4i - 10 = 4 \text{ V}$$

$$R_{TH} = 4/(6+10) = 3.2 \Omega$$

$$P_{max} = (V_{TH})^2 / (4R_{TH}) = 1.25 \text{ W}$$

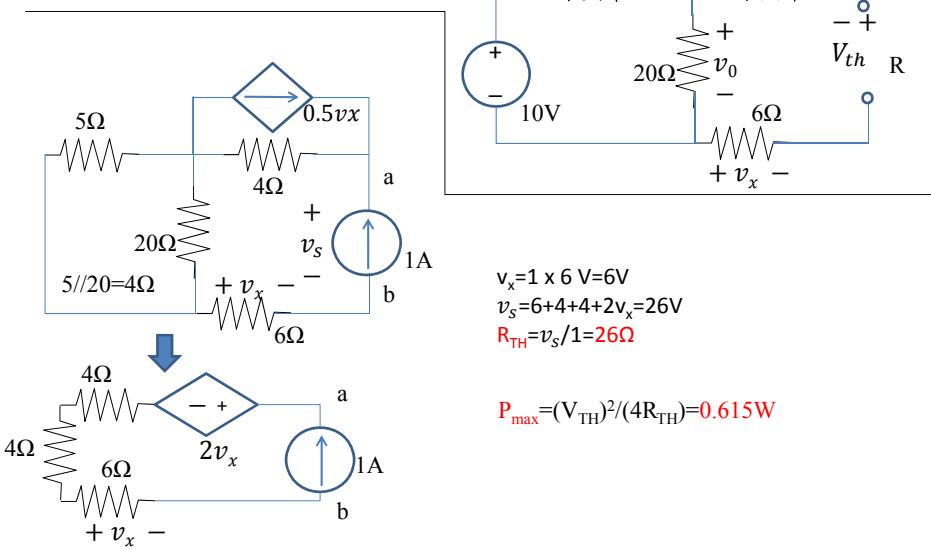Problem 10

$$V_{TH} = v_0 = 10 \times \frac{20}{20+5} V = 8 \text{ V}$$



$$v_x = 1 \times 6 \text{ V} = 6 \text{ V}$$

$$v_s = 6 + 4 + 4 + 2v_x = 26 \text{ V}$$

$$R_{TH} = v_s / 1 = 26 \Omega$$

$$P_{max} = (V_{TH})^2 / (4R_{TH}) = 0.615 \text{ W}$$

Problem 11

$$\begin{aligned} V_{TH} &= V_{20\Omega} - V_{5\Omega} \\ &= 50 \times \frac{20}{30} - 50 \times \frac{5}{30} \\ &= 25V \end{aligned}$$

$$R_{TH} = 10//20 + 25//5 \Omega = 10.833\Omega$$

$$P_{max} = (V_{TH})^2 / (4R_{TH}) = 14.424W$$

