

Problem 1

A 20- μF capacitor has energy $w(t) = 10\sin^2 360t$ J.
Determine the current through the capacitor

Problem 2

A 4-mF capacitor has the terminal voltage

$$v = \begin{cases} 15V, & t \leq 0 \\ Ae^{-100t} + Be^{-500t} V, & t \geq 0 \end{cases}$$

If the capacitor has initial current of 2A, find:

- the constants A and B,
- the energy stored in the capacitor at $t=0$,
- the capacitor current for $t>0$.


Hint: Make two equations for A and B using $v(0)=15$ and $i(0)=2$.

Problem 3

The current through a 0.5-F capacitor is $6(1 - e^{-2t})$ A.
Determine the voltage and power at $t=2$ s. Assume $v(0)=0$.

Problem 4

Find the voltage v_1 and v_2 across the capacitors in the following circuit.

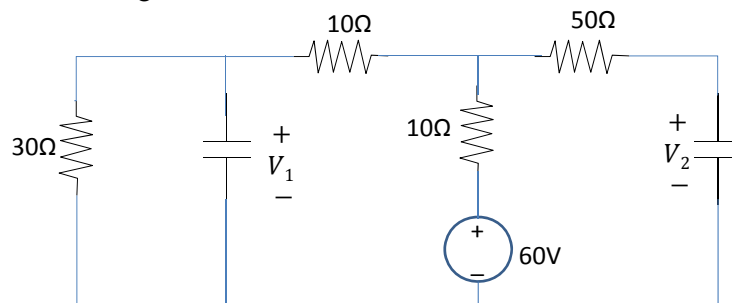

Problem 5

The current through a 12-mH inductor is $4\sin 200t$ A. Find the voltage, and also the energy stored in the inductor for $0 < t < \pi/200$ s.

Problem 6


The voltage across a 200-mH inductor is given by

$$v(t) = 6t^2 + 2t + 3 \text{ V for } t > 0$$

Determine the current $i(t)$ through the inductor. Assume that $i(0) = 1$ A.

Problem 7

For the circuit in following circuit, calculate the value of R that will make the energy stored in the capacitor the same as that stored in the inductor under dc conditions.

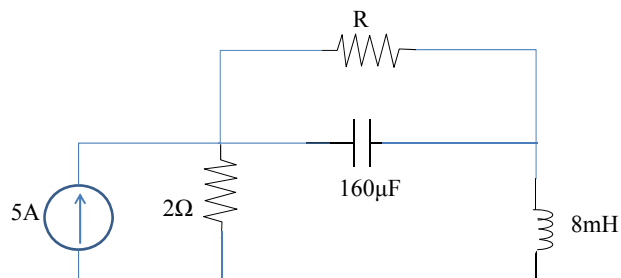

Problem 8

Under steady-state dc conditions, find I and v in the following circuit.

