

**Problem 1**

$$(a) R = \frac{v}{i} = \frac{10e^{-2t}}{0.4e^{-2t}} = 25 \Omega$$

$$\tau = RC = \frac{1}{\frac{1}{2}} = C = \frac{1}{2R} = 0.02F$$

$$(b) \tau = RC = \frac{1}{2} s = 0.5 s$$

$$(c) v(0)=10V, w_0 = \frac{1}{2}Cv(0)^2 = 0.5 \times 0.02 \times 100J = 1J$$

$$(d) 0.5w_0=0.5J, \frac{1}{2}Cv^2 = 0.5, \Rightarrow v = 7.071V$$

$$10e^{-2t} = 7.071 \Rightarrow t=0.173s$$

**Problem 2**

$$\text{When } t<0, v_0 = 6 \times \frac{4||12}{4||12+2} V = 3.6V.$$

$$\text{When } t>0, R=4//12K\Omega=3K\Omega$$

$$\tau = RC = 3 \times 10^3 \times 50 \times 10^{-6}s = 0.15s$$

$$v_0 = v_t = 3.6e^{-\frac{t}{0.15}} = 3.6e^{-\frac{20}{3}t} V$$


**Problem 3**

$$\text{When } t<0, R_{eq}=8+6//20//30\Omega=12\Omega, I=24/12A=2A$$

$$i_L = I \cdot \frac{6}{6+20||30} = 2 \times \frac{1}{3}A = 0.667A$$

$$\text{When } t > 0, R_{th}=20//30+6\Omega=18\Omega, \tau = \frac{R}{L} = \frac{18}{4}s = 4.5s$$

$$i_L = 0.667e^{-4.5t}A, i_0 = \frac{30}{20+30}i_L = 0.4e^{-4.5t}A$$

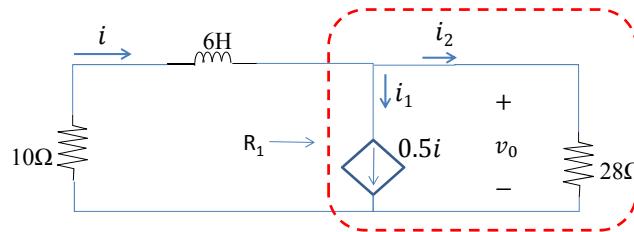**Problem 4**

When  $t = 0$ ,  $i(0) = 2A$ ,  $i_1 = 0.5i = 1A$ ,  $i_2 = i - i_1 = 1A$ ,

$$R_1 = \frac{v_0}{i} = \frac{28i_2}{i} = \frac{28}{2} = 14\Omega$$

When  $t > 0$ ,  $R = R_1 + 10\Omega = 24\Omega$

$$\tau = \frac{R}{L} = \frac{24}{6} s = 4s$$

$$i(t) = 2e^{-4t} A$$

**Problem 5**

$$R = 3 + 5 // 20\Omega = 7\Omega \quad \tau = \frac{R}{L} = \frac{7}{2} s = 3.5s$$

$$i(t) = 20e^{-3.5t} A$$

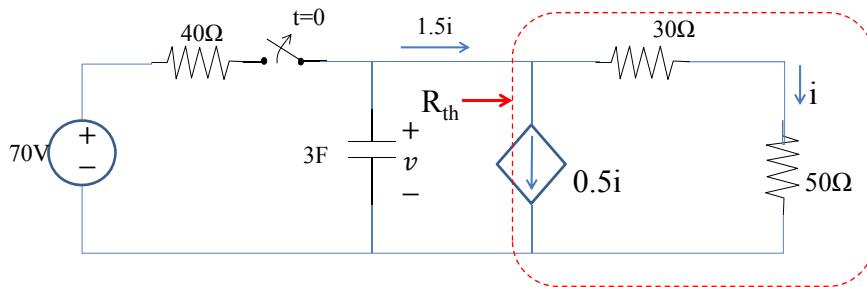
$$v(t) = -i(t) \cdot \frac{5}{20+5} \times 20 = -80e^{-3.5t} V$$

**Problem 6**

$$\text{When } t < 0 \quad v_0 = 14 - 2 \times 4V = 6V$$

$$\text{When } t > 0 \quad R = 3\Omega, \quad \tau = RC = 3 \times 2s = 6s$$

$$v(t) = 6e^{-\frac{t}{6}} V$$

**Problem 7**

When  $t < 0$ ,  $40 \times 1.5i + (30 + 50)i = 70 \Rightarrow i = 0.5A$   
 $v(0) = 80i = 40V$

For  $t > 0$ ,  $R_{th} = 80i / 1.5i = 53.33\Omega$ ,  $\tau = RC = 53.33 \times 3s = 160s$

$$v(t) = 40e^{-\frac{t}{160}}V$$

$$i(t) = \frac{v(t)}{80} = 0.5e^{-\frac{t}{160}}A$$