
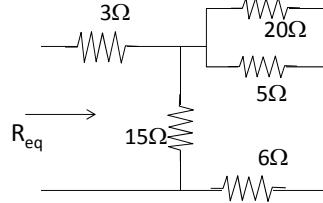


Practice 6: Find R_{eq}


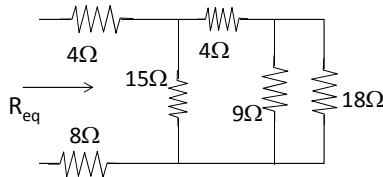


Solution:

$$\begin{aligned} R_{eq} &= (9//18+4)//15+4+8 \Omega \\ &= 10//15+12 \Omega \\ &= 18\Omega \end{aligned}$$

$$\begin{aligned} R_{eq} &= (20//5+6)//15+3 \Omega \\ &= 10//15+3 \Omega \\ &= 9 \Omega \end{aligned}$$


Practice 7: Find I_s

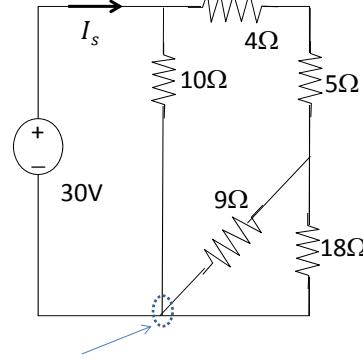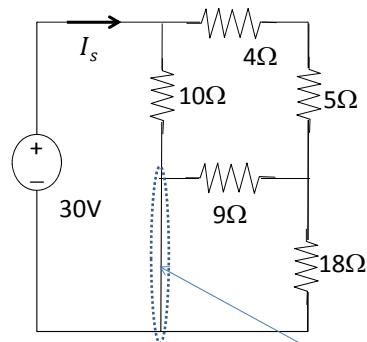

Solution: Shrink the wire to one point

$$\begin{aligned} R_{eq} &= (9//18+4+5)//10 \Omega \\ &= 15//10 \Omega = 6 \Omega \\ I_s &= 30/6 \text{ A} = 5 \text{ A} \end{aligned}$$

Practice 8: Find v_s

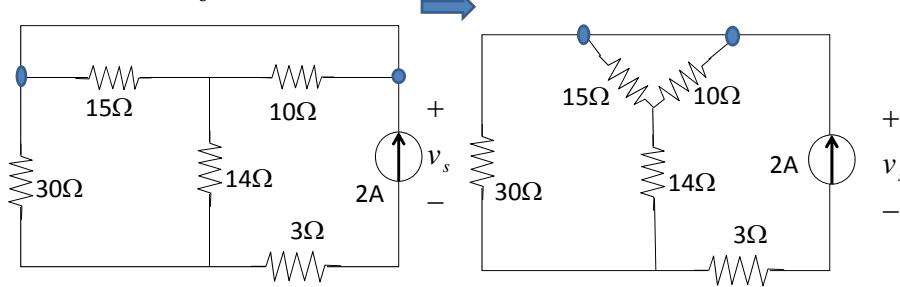


Solution:

$$R_{eq} = (10//15+14)/30+3 \Omega = 15 \Omega$$

$$V_s = 2 \times 15 = 30 \text{ V}$$

Practice 9: Find v_1, v_2

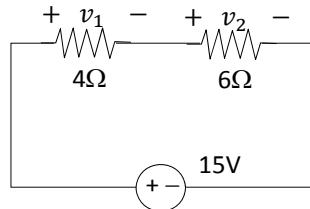


Solution:

$$v_1 = \frac{4}{4+6} \times 15V = 6V$$

$$v_2 = \frac{6}{4+6} \times 15V = 9V$$

Practice 10: Find i_1, i_2


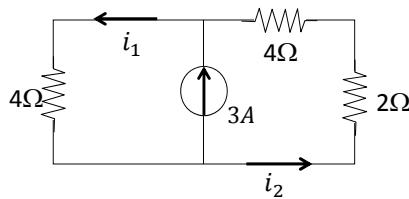


Solution:

$$i_1 = \frac{6}{4+6} \times 3A = 1.8A$$

$$i_2 = -\frac{4}{4+6} \times 3A = -1.2A$$

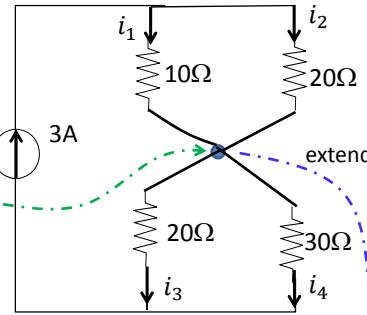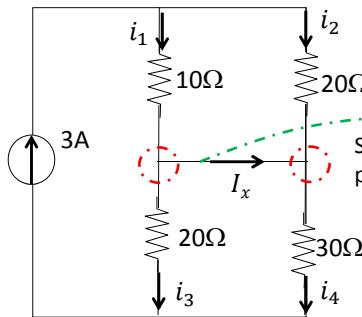Practice 11: Find i_1, i_2, i_3, i_4, I_x



In all three circuits, i_1, i_2, i_3, i_4 are the same
How about I_x, I_0 ?


$$I_0 = i_1 + i_2 = i_3 + i_4 = 3A$$

$$I_x = i_1 - i_3 = i_4 - i_2$$

By current division:

$$i_1 = \frac{20}{30} \times 3 = 2A; i_2 = 1A; \quad I_x = i_1 - i_3 = 0.2A$$

$$i_3 = 1.8A; i_4 = 1.2A; \quad I_x = i_4 - i_2 = 0.2A$$

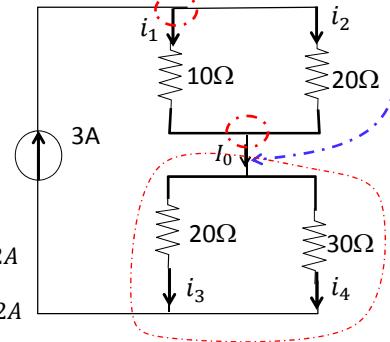

Practice 12: Find I_1, I_2, v_4

Solution: equivalent R_{eq} w.r.t. 30V,

$$R_{eq} = 15//10+3+6 \Omega = 15 \Omega$$

The current should leave the positive terminal of a voltage source


Thus I_2 must be negative:

$$I_2 = -30/15 A = -2 A$$


By current division:

$$I_1 = \frac{10}{10+15} \times (-I_2) = 0.8A, \quad I_3 = -I_2 - I_1 = 1.2A$$

$$v_4 = 4I_3 = 4.8V$$

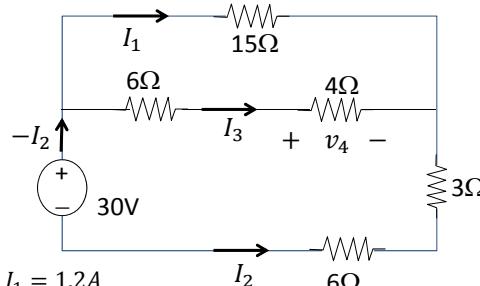

Practice 13: Find I_0, v_4

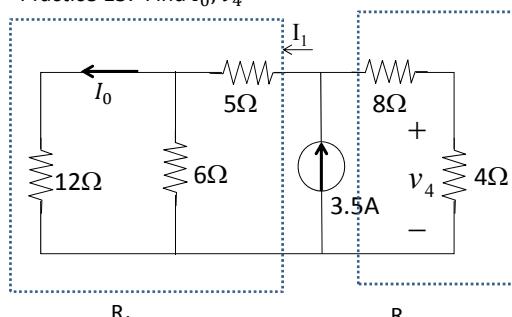

Solution:

$$R_1 = 12//6 + 5 \Omega = 9\Omega$$


$$R_2 = 4 + 8 \Omega = 12\Omega$$

$$I_1 = 3.5 \times \frac{R_2}{R_1 + R_2} = 2A$$

$$I_0 = \frac{6}{12 + 6} \times I_1 = 0.667A$$

$$v_4 = (3.5 - I_1) \times 4V = 6V$$

Practice 14: Find I_0, v_2

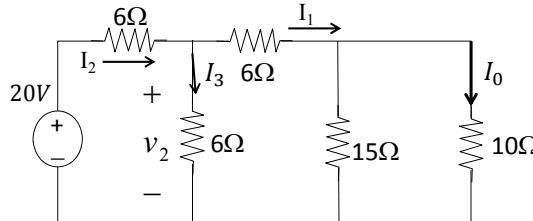

Solution: Equivalent resistance w.r.t. 20V:

$$R_{eq} = (15//10+6)//6+6\Omega = 10\Omega$$

$$I_2 = \frac{20}{10} A = 2A, \text{ by ohms Law}$$


$$I_1 = 2 \times \frac{6}{6+6+6} A = \frac{2}{3} A, \text{ by current division}$$

$$I_0 = \frac{2}{3} \times \frac{15}{15+10} A = 0.4A, \text{ also by current division}$$

$$\text{By KCL, } I_3 = I_2 - I_1 = 2 - \frac{2}{3} = \frac{4}{3} A$$

$$v_2 = 6I_3 = 8V$$

Practice 15: Find the voltage v_x

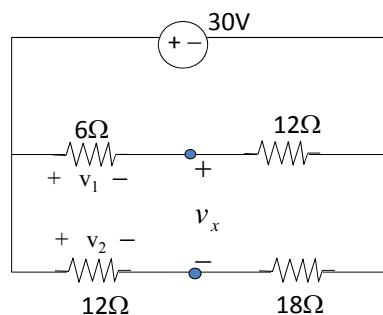

Solution:

By voltage division:


$$v_1 = 30 \times \frac{6}{12+6} V = 10V,$$

$$v_2 = 30 \times \frac{12}{12+18} V = 12V,$$

By KVL, $v_1 + v_x - v_2 = 0$

$$v_x = v_2 - v_1 = 12 - 10V = 2V$$

Practice 16: Find v_0, I_x ,

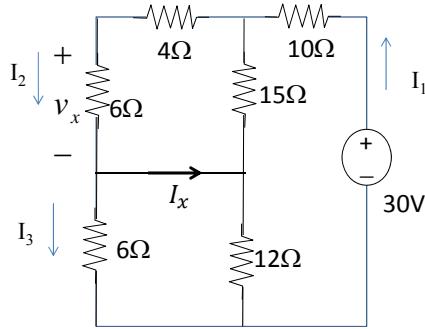

Solution:

$$R_{eq} = 10 + 10 // 15 + 6 // 12 \Omega = 20 \Omega$$

$$I_1 = \frac{30}{20} A = 1.5 A$$


$$I_2 = 1.5 \times \frac{15}{15 + 10} A = 0.9 A$$

$$I_3 = 1.5 \times \frac{12}{6 + 12} A = 1 A$$

$$I_x = I_2 - I_3 = -0.1 A$$

$$v_x = 0.9 \times 6 V = 5.4 V$$

Practice 16a: Find v_1, I_0 ,

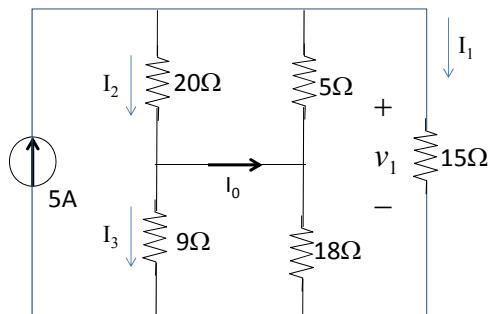

Solution:

$$I_1 = 5 \times \frac{20 || 5 + 9 || 18}{20 || 5 + 9 || 18 + 15} A = 2 A$$


$$I_2 = (5 - 2) \times \frac{5}{20 + 5} A = 0.6 A$$

$$I_3 = (5 - 2) \times \frac{18}{9 + 18} A = 2 A$$

$$I_0 = I_2 - I_3 = 0.6 - 2 A = -1.4 A$$

$$v_1 = 2 \times 15 V = 30 V$$

Practice 17: Find v_x, I ,

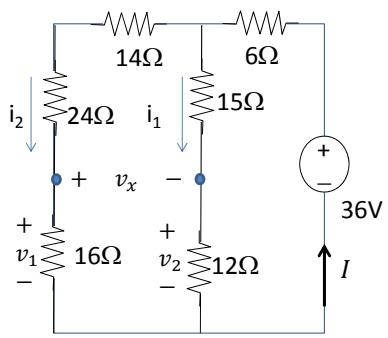

Solution:

Equivalent resistance w.r.t. 36V:

$$R_{eq} = 6 + (15+12)/(14+24+16)\Omega = 24\Omega$$

$$I = 36/24 \text{ A} = 1.5 \text{ A}$$


By current division and KCL:

$$i_1 = 1.5 \times \frac{54}{54 + 27} \text{ A} = 1 \text{ A}$$

$$i_2 = 1.5 - 1 \text{ A} = 0.5 \text{ A}$$

$$v_x = v_1 - v_2 = 16i_2 - 12i_1 = -4V$$


Practice 18: Find i_0

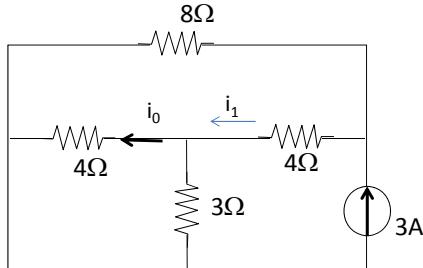

Solution:

$$i_1 = 3 \times \frac{8}{8 + 4 + 4||3} \text{ A} = 1.75 \text{ A}$$
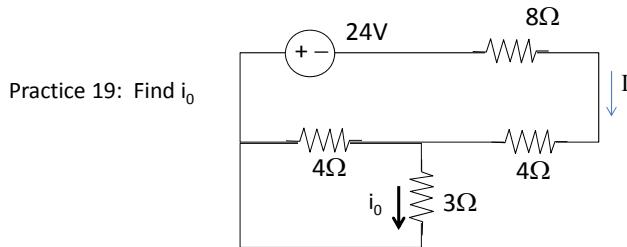
$$i_0 = 1.75 \times \frac{3}{3 + 4} \text{ A} = 0.75 \text{ A}$$




Solution:

$$I = -\frac{24}{8 + 4 + 3||4} A = -1.75A$$

$$i_0 = -1.75 \times \frac{4}{3 + 4} A = -1A$$

Practice 20: Find R for the circuit

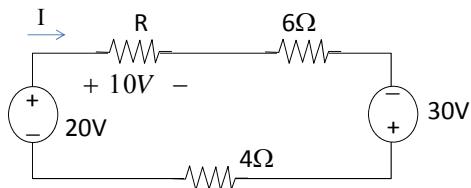


Solution:

$$I = \frac{10}{R}$$

$$\longrightarrow R=2.5\Omega$$

$$(R + 6 + 4)I - 30 - 20 = 0$$

Practice 21: Find V_s for the circuit

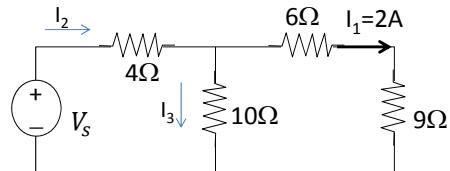

Solution:


$$R_{eq} = (6+9) // 10 + 4\Omega = 10\Omega$$

$$I_3 = \frac{2 \times (6 + 9)}{10} A = 3A$$

$$I_2 = I_1 + I_3 = 2 + 3A = 5A$$

$$V_s = 5 \times 10V = 50V$$

Practice 22: Find R so that I_s is 10A

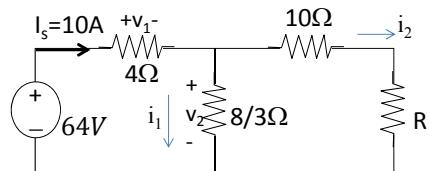

Solution:

$$v_1 = 4 \times 10V = 40V$$

$$v_2 = 64 - 40V = 24V$$

$$i_1 = \frac{24}{8/3} A = 9A$$

$$i_2 = 10 - 9A = 1A$$

$$(10 + R) \times 1 = 24 \quad \longrightarrow \quad R = 14\Omega$$