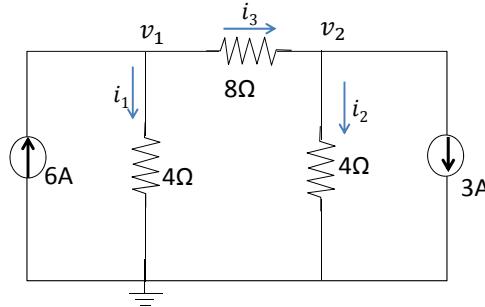


Practice problem 1:Find v_1 and v_2 by using nodal analysis method**Solution:**

Express resistor currents:

$$i_1 = \frac{v_1}{4}$$

$$i_2 = \frac{v_2}{4}$$

$$i_3 = \frac{v_1 - v_2}{8}$$

$$\begin{aligned} KCL \text{ at } v_1: \quad & i_1 + i_3 = 6 \\ \text{at } v_2: \quad & -i_2 + i_3 = 3 \end{aligned} \rightarrow \begin{cases} \frac{v_1}{4} + \frac{v_1 - v_2}{8} = 6 \\ -\frac{v_2}{4} + \frac{v_1 - v_2}{8} = 3 \end{cases}$$

$$\rightarrow \begin{cases} 3v_1 - v_2 = 48 \\ v_1 - 3v_2 = 24 \end{cases} \rightarrow \boxed{\begin{cases} v_1 = 15V \\ v_2 = -3V \end{cases}}$$

Practice problem 2:Find i_1 by using nodal analysis method.

How many node voltages?

Solution:


$$i_1 = \frac{v_2 - v_1}{1}; \quad i_2 = \frac{v_1}{2}$$

$$i_3 = \frac{v_2}{3}$$

$$\text{KCL at } v_1: \quad i_1 - i_2 - 3i_1 = -4$$

$$\text{at } v_2: \quad 3i_1 - i_1 - i_3 = -5$$

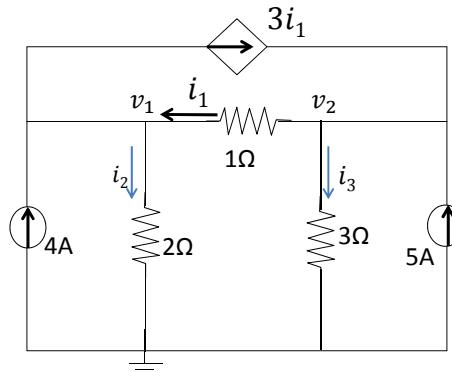
$$\rightarrow \begin{cases} 2i_1 + i_2 = 4 \\ 2i_1 - i_3 = -5 \end{cases} \rightarrow \begin{cases} 2\frac{v_2 - v_1}{1} + \frac{v_1}{2} = 4 \\ 2(v_2 - v_1) - \frac{v_2}{3} = -5 \end{cases} \rightarrow \begin{cases} -3v_1 + 4v_2 = 8 \\ -6v_1 + 5v_2 = -15 \end{cases}$$



$$i_1 = v_2 - v_1 = -\frac{7}{9}A = -0.778A$$

$$\begin{cases} v_1 = \frac{100}{9}V \\ v_2 = \frac{31}{3}V \end{cases}$$

R8

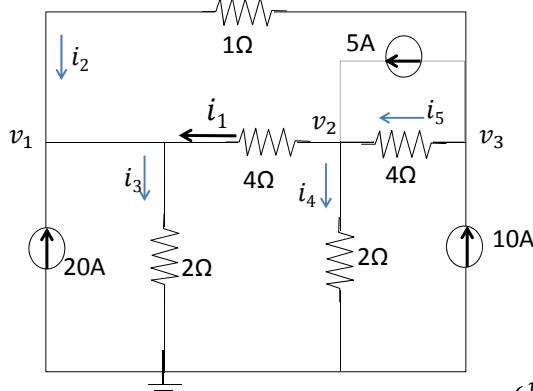Practice problem 3: Form 3 equations for v_1, v_2, v_3 

Solution:

$$i_1 = \frac{v_2 - v_1}{4}; \quad i_2 = \frac{v_3 - v_1}{1}$$

$$i_3 = \frac{v_1}{2}; \quad i_4 = \frac{v_2}{2};$$

$$i_5 = \frac{v_3 - v_2}{4}$$


KCL at v_1 : $i_1 + i_2 - i_3 = -20$;at v_2 : $-i_1 - i_4 + i_5 = -5$;at v_3 : $i_2 + i_5 = 5$

$$\begin{cases} -7v_1 + v_2 + 4v_3 = -80 \\ v_1 - 4v_2 + v_3 = -20 \\ -4v_1 - v_2 + 5v_3 = 20 \end{cases}$$

$$\begin{cases} \frac{v_2 - v_1}{4} + \frac{v_3 - v_1}{1} - \frac{v_1}{2} = -20 \\ \frac{v_2 - v_1}{4} - \frac{v_2}{2} + \frac{v_3 - v_2}{4} = -5 \\ \frac{v_3 - v_1}{1} + \frac{v_3 - v_2}{4} = 5 \end{cases}$$

Practice 4: Form 3 equations for the three node voltages

R9

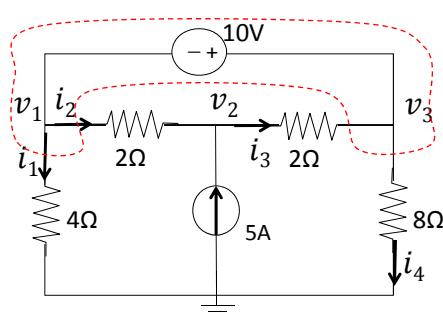

Solution:

$$i_1 = \frac{v_1}{4} \quad i_2 = \frac{v_1 - v_2}{2}$$

$$i_3 = \frac{v_2 - v_3}{2} \quad i_4 = \frac{v_3}{8}$$

Due to the floating voltage source,
a supernode needs to be formed:KCL at supernode: $-i_1 - i_2 + i_3 - i_4 = 0$ KCL at v_2 : $i_2 - i_3 = -5$;By the 10V source: $v_3 - v_1 = 10$

$$\begin{cases} -\frac{v_1}{4} - \frac{v_1 - v_2}{2} + \frac{v_2 - v_3}{2} - \frac{v_3}{8} = 0 \\ \frac{v_1 - v_2}{2} - \frac{v_2 - v_3}{2} = -5 \\ v_3 - v_1 = 10 \end{cases}$$



$$\begin{cases} -6v_1 + 8v_2 - 5v_3 = 0 \\ v_1 - 2v_2 + v_3 = -10 \\ -v_1 + v_3 = 10 \end{cases}$$

R9


Practice 5: Form 4 equations for the four node voltages

Solution:

$$i_x = \frac{v_1 - v_4}{3}$$

$$i_2 = \frac{v_1}{2} \quad i_4 = \frac{v_4}{1}$$
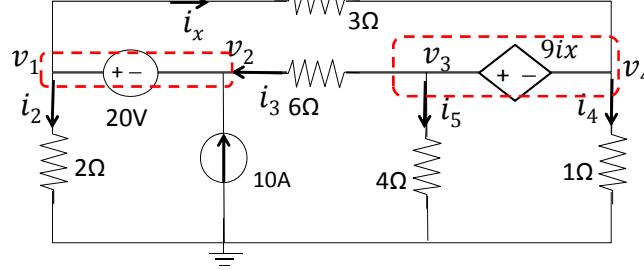
$$i_3 = \frac{v_3 - v_2}{6} \quad i_5 = \frac{v_3}{4}$$



Due to the two floating voltage sources, two supernodes need to be formed:

KCL at supernode $v_1 v_2$: $-i_2 - i_x + i_3 = -10$;at supernode $v_3 v_4$: $i_x - i_3 - i_4 - i_5 = 0$;By 20V source: $v_1 - v_2 = 20$ By $9i_x$ source: $v_3 - v_4 = 9i_x$

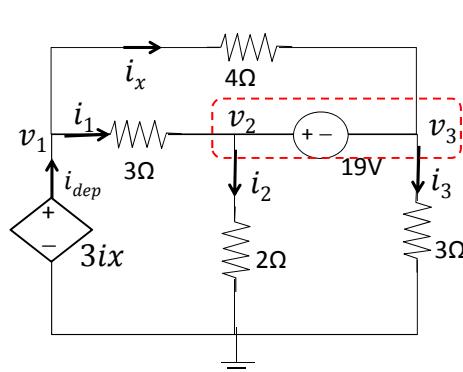
$$\rightarrow \begin{cases} -\frac{v_1}{2} - \frac{v_1 - v_4}{3} + \frac{v_3 - v_2}{6} = -10 \\ \frac{v_1 - v_4}{3} - \frac{v_3 - v_2}{6} - \frac{v_4}{1} - \frac{v_3}{4} = 0 \\ v_1 - v_2 = 20 \\ v_3 - v_4 = 9 \frac{v_1 - v_4}{3} \end{cases} \rightarrow \boxed{\begin{cases} -5v_1 - v_2 + v_3 + 2v_4 = -60 \\ 4v_1 + 2v_2 - 5v_3 - 16v_4 = 0 \\ v_1 - v_2 = 20 \\ 3v_1 - v_3 - 2v_4 = 0 \end{cases}}$$

Practice 6: Find v_1, v_2, v_3 and i_{dep}

$$\text{Solution: } i_1 = \frac{v_1 - v_2}{3};$$

$$i_2 = \frac{v_2}{2}; \quad i_3 = \frac{v_3}{3}; \quad i_x = \frac{v_1 - v_3}{4}$$

Due to the floating voltage source, a supernode needs to be formed

KCL at supernode: $i_1 - i_2 - i_3 + i_x = 0$ By 19V source: $v_2 - v_3 = 19$ By $3i_x$ dep source: $v_1 = 3i_x$ 

$$\begin{cases} \frac{v_1 - v_2}{3} - \frac{v_2}{2} - \frac{v_3}{3} + \frac{v_1 - v_3}{4} = 0 \\ v_2 - v_3 = 19 \\ v_1 = 3 \frac{v_1 - v_3}{4} \end{cases} \rightarrow \begin{cases} 7v_1 - 10v_2 - 7v_3 = 0 \\ v_2 - v_3 = 19 \\ v_1 + 3v_3 = 0 \end{cases} \rightarrow \boxed{\begin{cases} v_1 = 15V \\ v_2 = 14V \\ v_3 = -5V \end{cases}}$$

$$i_{dep} = i_1 + i_x = \frac{15 - 14}{3} + \frac{15 + 5}{4} A = \frac{16}{3} A = 5.333A$$