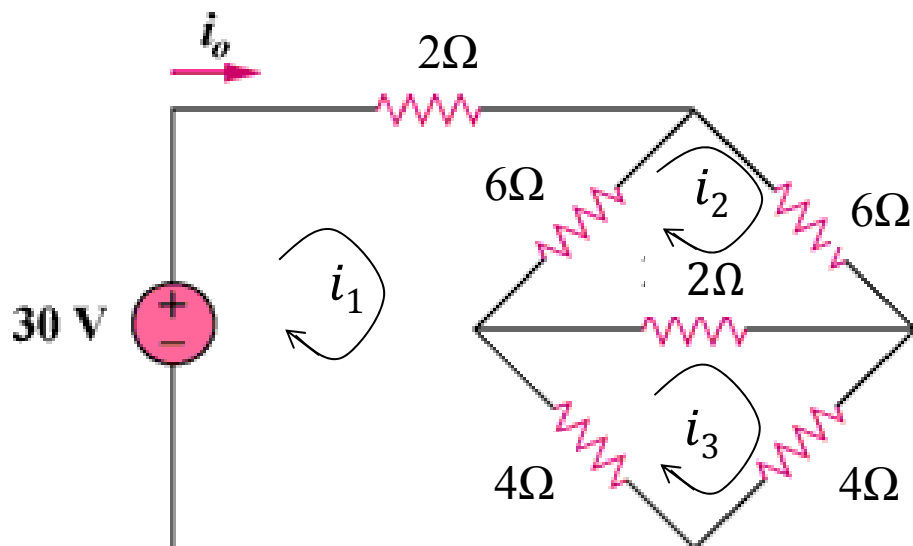


Practice 1: Form 3 mesh equations for i_1, i_2, i_3



Use the short cut without assigning resistor voltages:

KVL along mesh 1:

$$2i_1 + 6(i_1 - i_2) + 4(i_1 - i_3) - 30 = 0 \text{ (note: } i_1 \text{ terms with “+”)}$$

Simplify to get

$$\rightarrow 12i_1 - 6i_2 - 4i_3 = 30 \quad (1)$$

KVL along mesh 2:

$$6i_2 + 2(i_2 - i_3) + 6(i_2 - i_1) = 0 \text{ (note: } i_2 \text{ terms with “+”)}$$

$$\rightarrow -6i_1 + 14i_2 - 2i_3 = 0 \quad (2)$$


KVL along mesh 3:

$$2(i_3 - i_2) + 4i_3 + 4(i_3 - i_1) = 0 \text{ (note: } i_3 \text{ terms with “+”)}$$

$$\rightarrow -4i_1 - 2i_2 + 10i_3 = 0 \quad (3)$$

$$\begin{aligned} 12i_1 - 6i_2 - 4i_3 &= 30 \\ -6i_1 + 14i_2 - 2i_3 &= 0 \\ -4i_1 - 2i_2 + 10i_3 &= 0 \end{aligned}$$

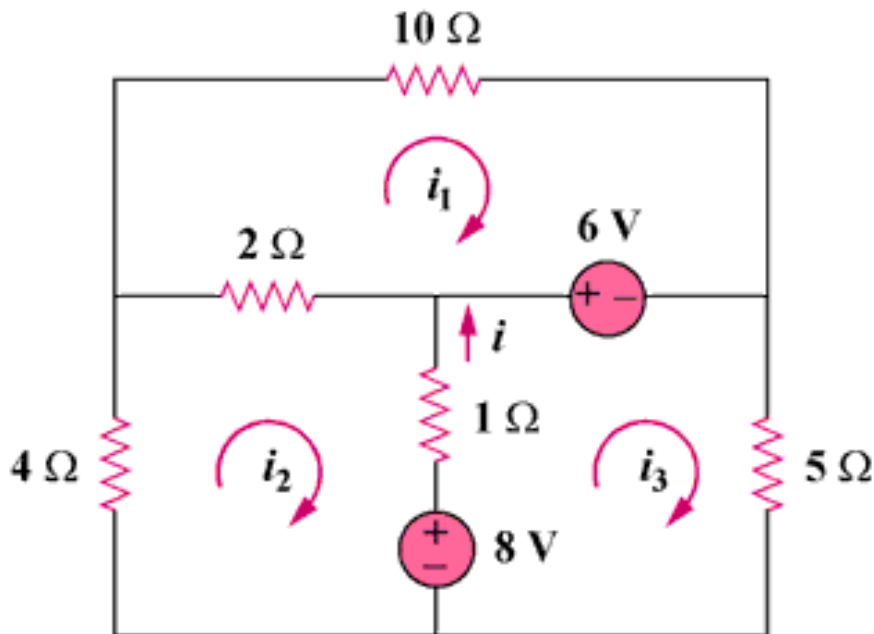Practice 2: Form 3 mesh equations for i_1, i_2, i_3



KVL along mesh 1:

$$10i_1 - 6 + 2(i_1 - i_2) = 0 \quad (\text{note: } i_1 \text{ terms with “+”})$$
$$\rightarrow 12i_1 - 2i_2 = 6 \quad (1)$$

Mesh 2:


$$2(i_2 - i_1) + 1(i_2 - i_3) + 8 + 4i_2 = 0 \quad (i_2 \text{ terms with “+”})$$
$$\rightarrow -2i_1 + 7i_2 - i_3 = -8 \quad (2)$$

Mesh 3:

$$6 + 5i_3 - 8 + 1(i_3 - i_2) = 0 \quad (i_3 \text{ terms with “+”})$$
$$\rightarrow -i_2 + 6i_3 = 2 \quad (3)$$


$$\begin{aligned} 12i_1 - 2i_2 &= 6 \\ -2i_1 + 7i_2 - i_3 &= -8 \\ -i_2 + 6i_3 &= 2 \end{aligned}$$

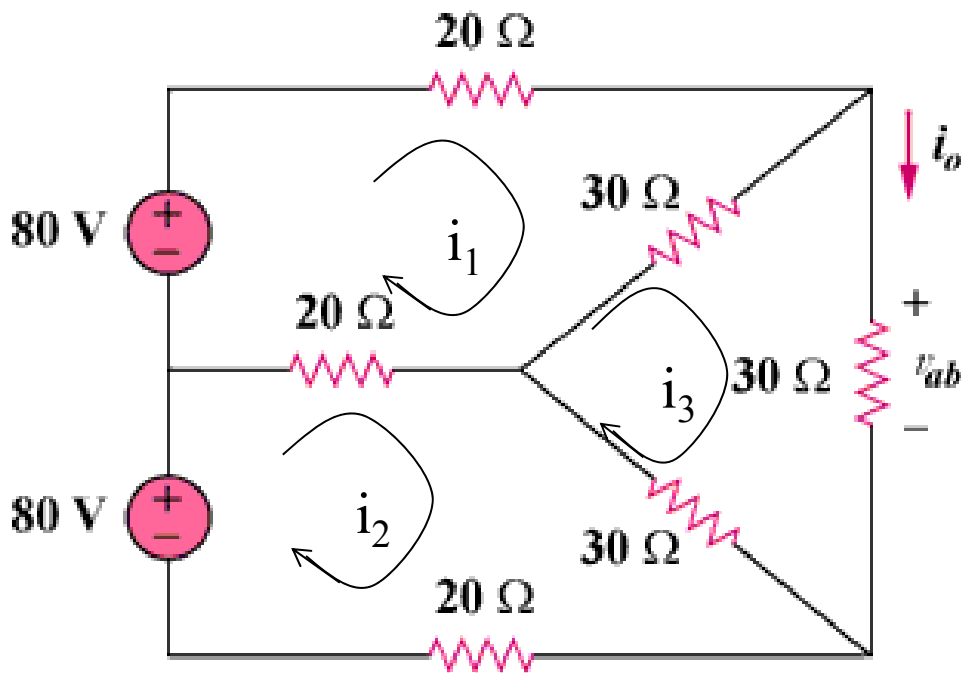Practice 3: Form 3 mesh equations for i_1, i_2, i_3



$$\begin{aligned} 70i_1 - 20i_2 - 30i_3 &= 80 \\ -20i_1 + 70i_2 - 30i_3 &= 80 \\ -30i_1 - 30i_2 + 90i_3 &= 0 \end{aligned}$$

Practice 4: Find i_1, i_2 and v_0

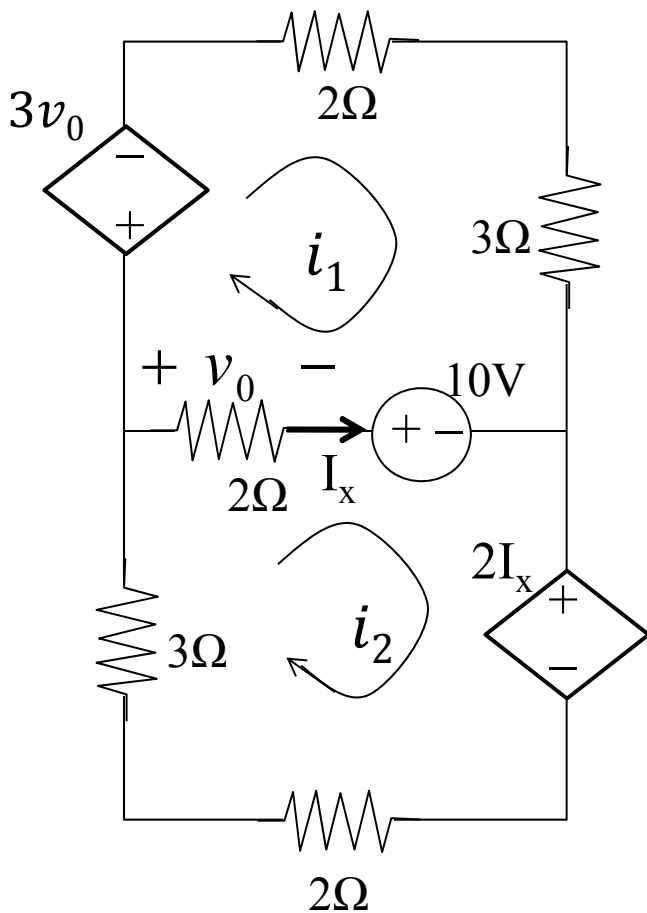

Express controlling variables:

$$v_0 = 2(i_2 - i_1), I_x = i_2 - i_1$$

KVL along mesh 1:

$$\begin{aligned} 5i_1 - 10 + 2(i_1 - i_2) + 3v_0 &= 0 \\ 5i_1 - 10 + 2i_1 - 2i_2 + 3 \times 2(i_2 - i_1) &= 0 \\ i_1 + 4i_2 &= 10 \end{aligned} \quad (1)$$

Along mesh 2:


$$\begin{aligned} 2(i_2 - i_1) + 10 + 2I_x + 5i_2 &= 0 \\ 2i_2 - 2i_1 + 10 + 2(i_2 - i_1) + 5i_2 &= 0 \\ -4i_1 + 9i_2 &= -10 \end{aligned} \quad (2)$$

Solving (1) and (2) to get

$$i_1 = 5.2A; \quad i_2 = 1.2A$$

$$v_0 = 2(i_2 - i_1) = -8V$$

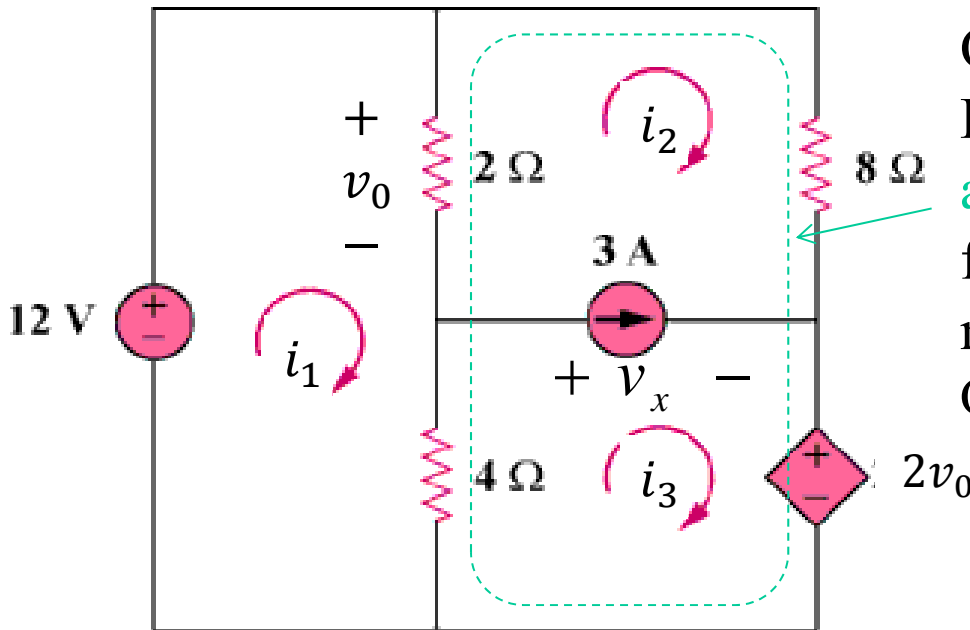Practice 5: Find the mesh currents and v_x



Overview:

Due to 3A current source, a **super mesh** needs to be formed by combining mesh 2 and mesh 3

One equation from mesh 1

One from super mesh

One from 3A source

First, express controlling voltage v_0 : $v_0 = 2(i_1 - i_2)$

$$\begin{aligned} \text{KVL along mesh 1: } & 2(i_1 - i_2) + 4(i_1 - i_3) = 12 \\ \Rightarrow & \mathbf{6i_1 - 2i_2 - 4i_3 = 12} \quad (1) \end{aligned}$$

$$\begin{aligned} \text{Along super mesh: } & 2(i_2 - i_1) + 8i_2 + 2v_0 + 4(i_3 - i_1) = 0 \\ \Rightarrow & 2(i_2 - i_1) + 8i_2 + 2 * 2(i_1 - i_2) + 4(i_3 - i_1) = 0 \\ \Rightarrow & \mathbf{-2i_1 + 6i_2 + 4i_3 = 0} \quad (2) \end{aligned}$$

$$\text{By the 3A current source: } \mathbf{i_3 - i_2 = 3} \quad (3)$$


$$\text{Solving (1)-(3): } \mathbf{i_1 = 3.5A; i_2 = -0.5A; i_3 = 2.5A}$$

To find v_x , apply KVL along mesh 2:

$$v_x = -v_0 + 8i_2 = -2(3.5 + 0.5) + 8(-0.5) = -12V$$

$$\mathbf{v_x = -12V}$$

Practice 6: Find i_0 and v_0 :

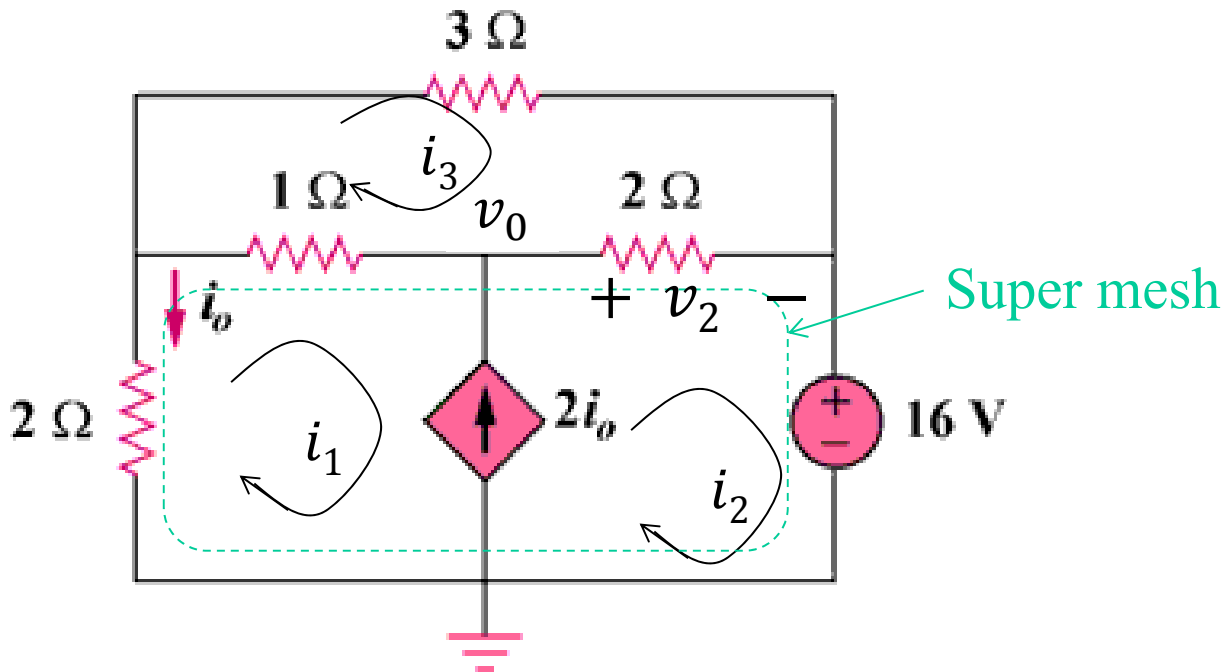

First, express controlling current i_0 : $i_0 = -i_1$ (0)

$$\begin{aligned} \text{KVL along mesh 3: } 3i_3 + 2(i_3 - i_2) + (i_3 - i_1) &= 0 \\ \Rightarrow -i_1 - 2i_2 + 6i_3 &= 0 \end{aligned} \quad (1)$$

$$\begin{aligned} \text{KVL along super mesh: } 2i_1 + (i_1 - i_3) + 2(i_2 - i_3) + 16 &= 0 \\ 3i_1 + 2i_2 - 3i_3 &= -16 \end{aligned} \quad (2)$$

$$\begin{aligned} \text{By dependent current source: } 2i_0 = i_2 - i_1, \text{ plug in (0)} \\ -2i_1 = i_2 - i_1, \quad \rightarrow \quad i_1 + i_2 = 0 \end{aligned} \quad (3)$$


Solving (1)-(3), $i_1 = -10.667A$, $i_2 = 10.667A$, $i_3 = 1.778A$

To find v_0 , assign v_2 , then

$$v_0 = v_2 + 16 = 2(i_2 - i_3) + 16 = 33.778V$$

$$\begin{aligned} i_0 &= -i_1 = 10.667A \\ v_0 &= 33.778V \end{aligned}$$

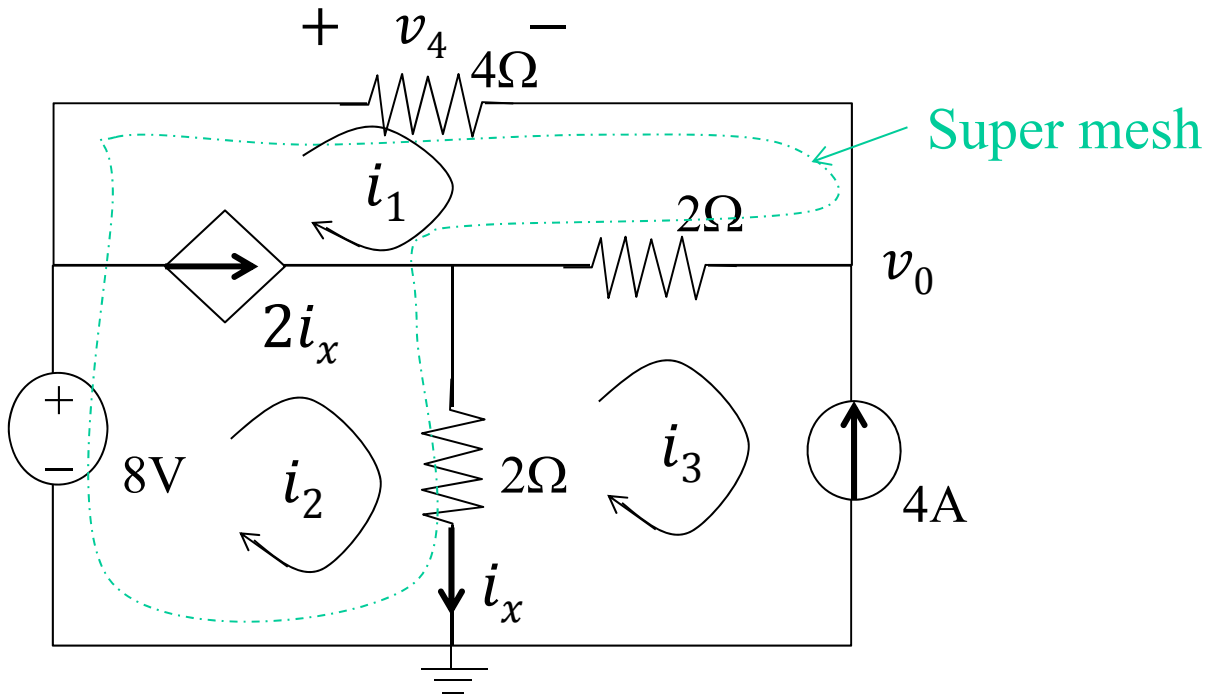Practice 7: Use mesh analysis method to find i_x and v_0 :



First, notice, $i_3 = -4A$ (a)

Express controlling current i_x :

$$i_x = i_2 - i_3 \rightarrow i_x = i_2 + 4 \quad (b)$$

KVL along super mesh: $4i_1 + 2(i_1 + 4) + 2(i_2 + 4) = 8$
 $\Rightarrow 6i_1 + 2i_2 = -8 \quad (1)$

By dependent current source: $i_2 - i_1 = 2i_x = 2(i_2 + 4)$
 $\rightarrow -i_1 - i_2 = 8 \quad (2)$

Solving (1) and (2): $i_1 = 2A; i_2 = -10A$

$$i_x = i_2 + 4 = -10 + 4 = 6A$$

To find v_0 , assign v_4 : $v_0 = 8 - v_4 = 8 - 4i_1 = 0V$

$$v_0 = 0V$$