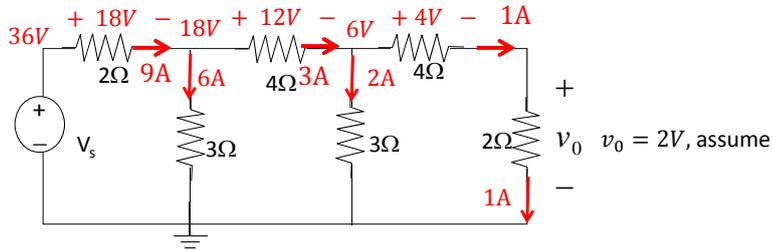


R12

Practice 1: Find v_0 for $V_s=27V$ by linearity



Step 1: Find k such that $v_0=kV_s$ by assuming $v_0=$ some value

Assume $v_0 = 2V, \rightarrow V_s = 36V$


$$2 = k \cdot 36, \quad k = \frac{1}{18} \quad v_0 = \frac{1}{18}V_s$$

Step 2: For $V_s=27V, v_0= k V_s$

$$v_0 = \frac{1}{18} \cdot 27 = 1.5V$$

R12

Practice 2: Find I using linearity

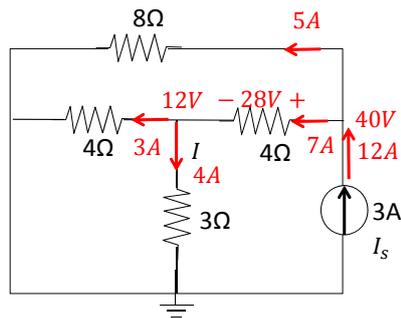

Input: I_s
Output: I

Need to find k such that $I = kI_s$

Assign the ground

Assume $I = 4A$



$$I_s = 12A$$

$$k = \frac{I}{I_s} = \frac{4}{12} = \frac{1}{3}$$

$$I = \frac{1}{3}I_s$$



$$\text{For } I_s = 3A, I = \frac{1}{3} \times 3 = 1A$$

Practice 3: Find I using superposition.

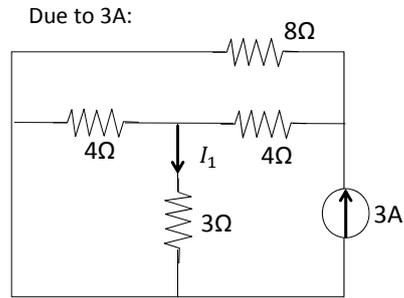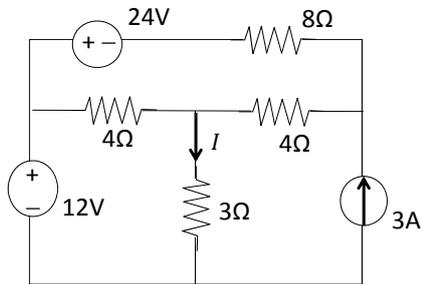

From previous slide, $I_1 = 1A$

Due to 12V:

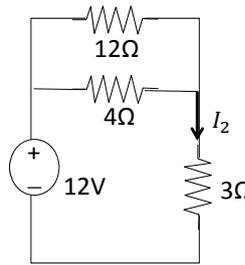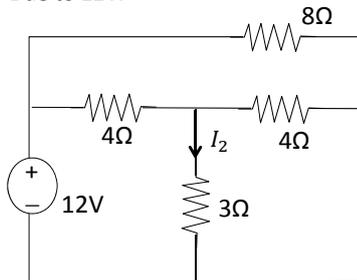


$$R_{eq} \text{ w.r.t } 12V$$

$$R_{eq} = 3 + 4 // 12$$

$$= 6\Omega$$

$$I_2 = 2A$$

Due to 24V:

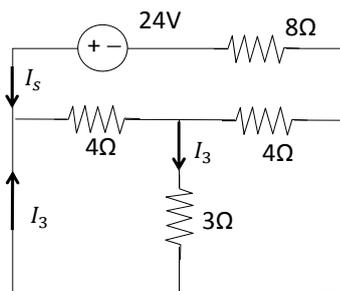

$$R_{eq} \text{ w.r.t } 24V$$

$$R_{eq} = 8 + 4 + 4 // 3$$

$$= 96/7$$

$$I_s = 24 \times \frac{7}{96} = \frac{7}{4}A$$


By current division:

$$I_3 = -\frac{4}{7} \times I_s = -1A$$


$$\text{Finally: } I = I_1 + I_2 + I_3 = 1 + 2 - 1 = 2A$$

Practice 4: Find I using superposition.



R12

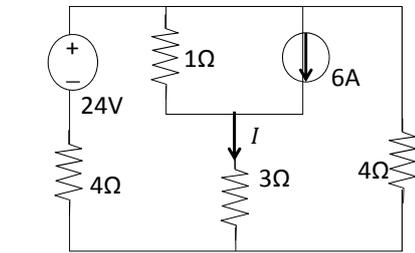

Due to 6A:

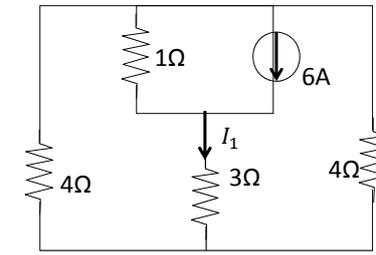


Due to 24V

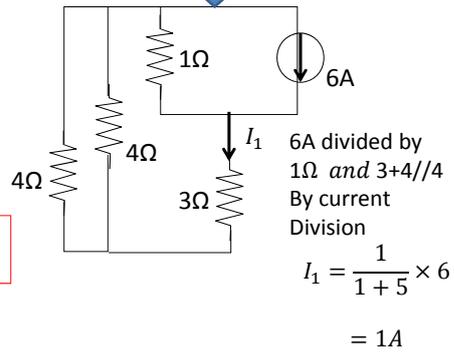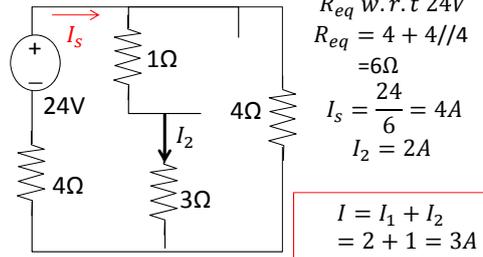

Practice 5: Find v_0 using source transformation

R13

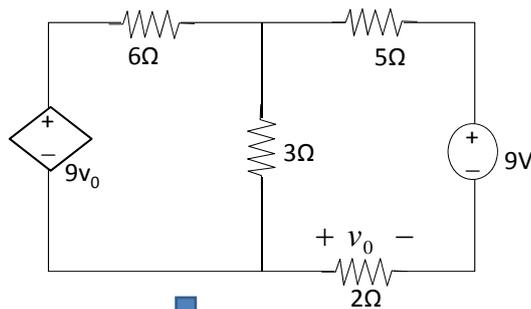

Assign loop current I

$$v_0 = 2I$$

By KVL along counter clockwise direction


$$5I + 2I + 3v_0 + 2I = 9$$

$$9I + 3v_0 = 9$$

$$9I + 3(2I) = 9;$$


$$I = \frac{9}{15} = 0.6A$$

$$v_0 = 1.2V$$

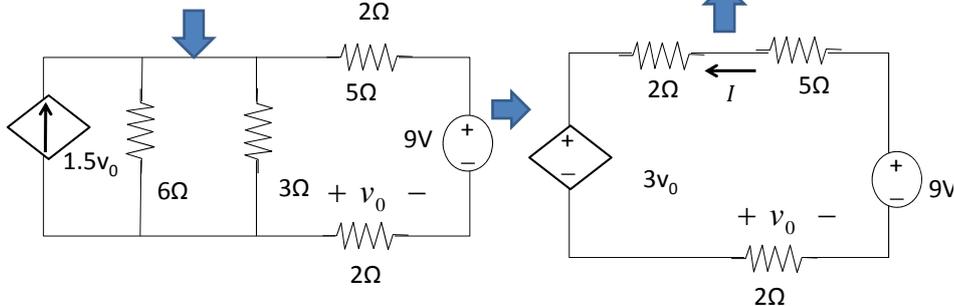


R13

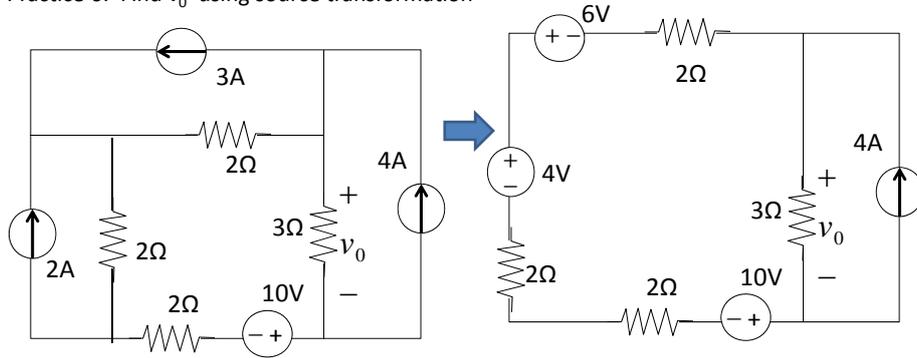Practice 6: Find v_0 using source transformation



R13


Approach 1:

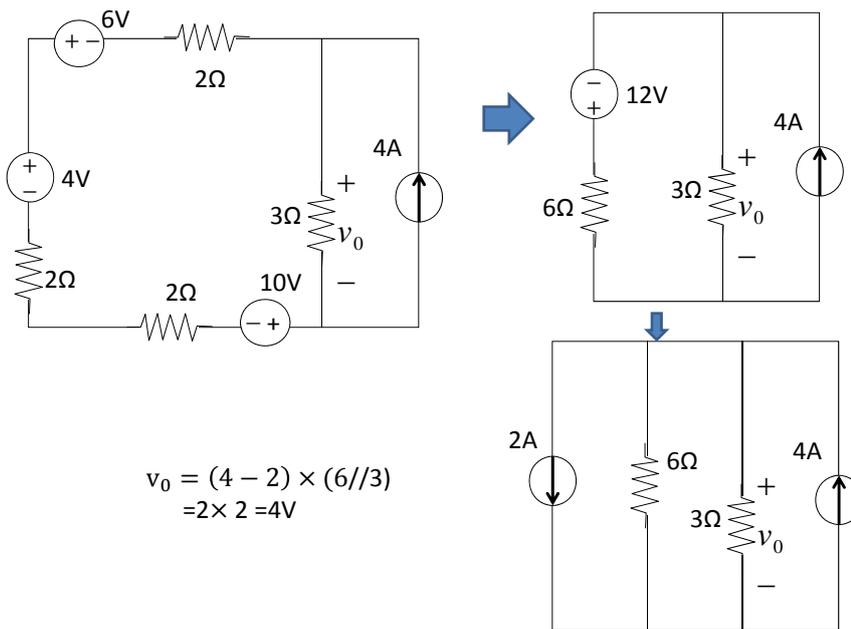

$$v_0 = (4 - 2) \times (6/3) = 2 \times 2 = 4V$$

Approach 2:

R13

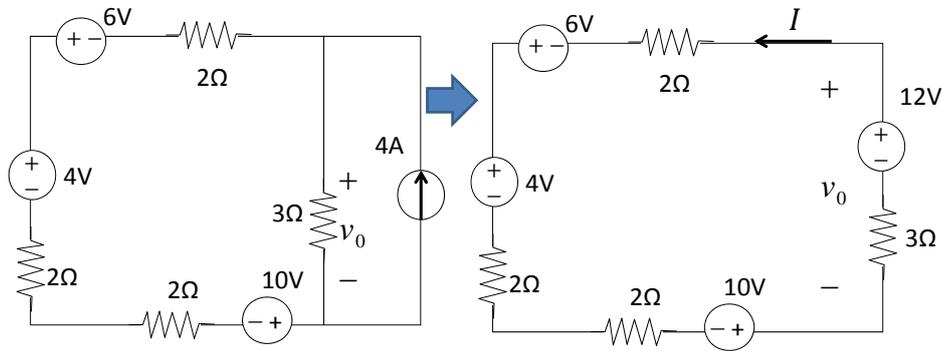



Assign loop current I

$$I = \frac{12 + 6 - 4 + 10}{9} = \frac{24}{9} = \frac{8}{3} A$$

$$v_0 = 12 - 3I = 4V$$

Practice 7: Find I_0 using source transformation

R13

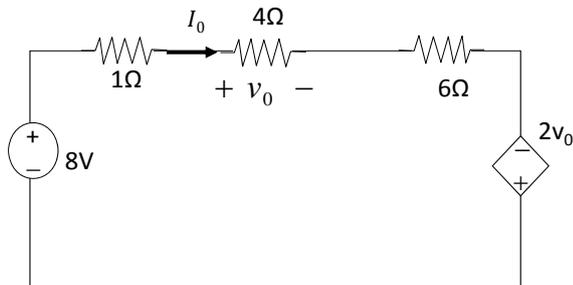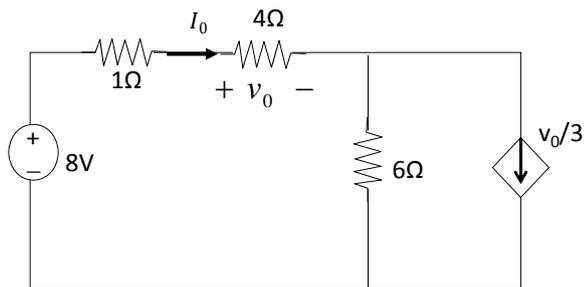

$$v_0 = 4I_0$$

KVL clockwise

$$I_0 + v_0 + 6I_0 - 2v_0 = 8$$

$$7I_0 - v_0 = 8$$

$$7I_0 - 4I_0 = 8$$

$$I_0 = \frac{8}{3} A$$