

L16

Practice 1: For a capacitor with $C=2F$, given $i(t) = 6\sin 4t$ A,
 $v(0)=1V$. Find $v(t)$ for $t \geq 0$.

$$\begin{aligned} v(t) &= v(0) + \frac{1}{C} \int_0^t i(t) dt = 1 + \frac{1}{2} \int_0^t 6\sin 4t dt = 1 + \frac{1}{2} \left(-\frac{6}{4} \right) \cos 4t \Big|_0^t \\ &= 1 + \left(-\frac{3}{4} \cos 4t - \left(-\frac{3}{4} \right) \cos 0 \right) = \frac{7}{4} - \frac{3}{4} \cos 4t \text{ V} \end{aligned}$$

Practice 2: For an inductor with $L=0.1H$, given $i(t) = 10t e^{-5t}$ A.
 Find $v(t)$, $w(t)$.

$$\begin{aligned} v(t) &= L \frac{di}{dt} = 0.1(10t(-5)e^{-5t} + 10e^{-5t}) = (-5t + 1)e^{-5t} \text{ V} \\ w(t) &= \frac{1}{2} Li^2(t) = \frac{1}{2} (0.1) 100t^2 e^{-10t} = 5e^{-10t} \text{ J} \end{aligned}$$

L16

Practice 3: Given $C= 4mF$, $i(0)=2A$, and

$$v(t) = \begin{cases} 50V, & t < 0 \\ Ae^{-100t} + Be^{-600t}, & t \geq 0 \end{cases}$$

Find A and B.

Use initial condition and continuity to form two equations for A and B:
 By continuity,

$$v(0) = Ae^0 + Be^0 = A + B = 50 \quad (1)$$


Use the initial condition $i(0)=2A$ and $i=Cdv/dt$, we obtain

$$\begin{aligned} C \frac{dv}{dt} \Big|_{t=0} &= 4 \times 10^{-3} (-100A - 600B) = 2 \\ -0.4A - 2.4B &= 2 \quad (2) \end{aligned}$$

Solve (1) and (2), we have $A=61$, $B=-11$

L16

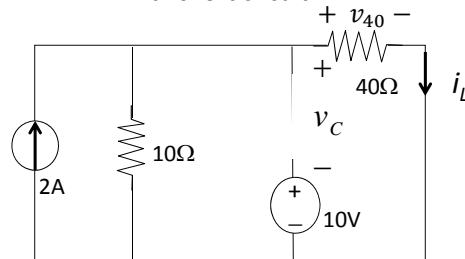
Practice 4: Find v_C , i_L under DC condition. Replace C with open circuit, L with short circuit:



Since 10V is not connected, 10ohm and 4ohm share 2A, in parallel
 By current division, $i_L = \frac{10}{40+10} * 2 = 0.4A$, $v_{40} = 0.4 \times 40 = 16V$
 By KVL $v_{40} - 10 - v_C = 0$,
 $v_C = 16 - 10 = 6V$

L16

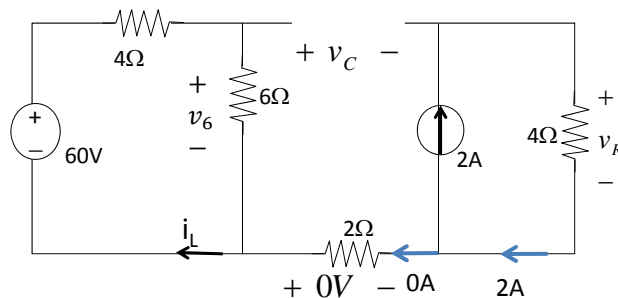Practice 5: Find i_L , v_C , v_R under DC condition. Replace C with open, L with short.



Since capacitor is open, all 2A runs through 4ohm (on the right hand side). Thus no current and voltage across 2ohm. Thus by KVL,

$$v_C = v_6 - v_R$$

$$v_R = 2 \times 4 = 8V$$


Again, since capacitor is open, 4ohm (on top) and 6ohm are in series,

By voltage division, $v_6 = \frac{6}{4+6} 60 = 36V$, Thus $v_C = 36 - 8 = 28V$

i_L can be obtained by ohm's law: $i_L = \frac{60}{4+6} = 6A$

L16

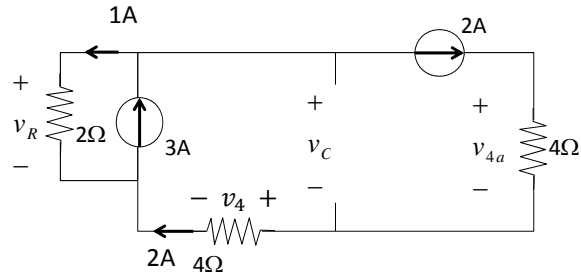Practice 6: Find v_C and v_R under DC condition. Replace C with open, L with short.



Because C is open, same 2A current through the two 4ohm resistors.

$$v_4 = 2 \times 4 = 8V$$

By KCL, 1A through 2ohm resistor. Thus $v_R = 1 \times 2 = 2V$

$$\text{By KVL, } v_c = v_R - v_4 = 2 - 8 = -6V$$

A common mistake is make $v_c = v_{4a} = 8V$. This is incorrect since the voltage across 2A is not 0.