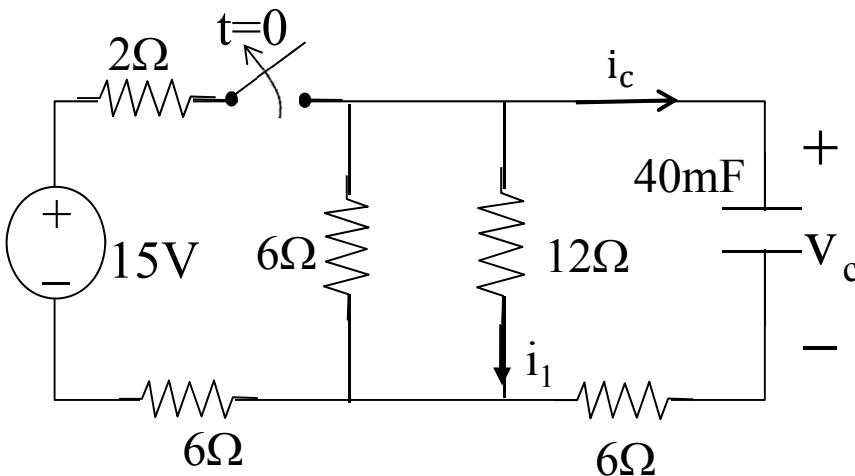


Practice 1: Find $v_c(t)$ and $i_1(t)$ for $t > 0$.



$$v_c(0) = \frac{6/12}{2 + 6 + 6/12} \times 15 \\ = \frac{4}{12} \times 15 = 5V$$

For $t > 0$,


$$R_{th} = 6/12 + 6 = 10\Omega \\ \frac{1}{R_{th}C} = \frac{1}{10 \times 0.04} = 2.5$$

$$v_c(t) = 5e^{-2.5t}V \text{ for } t \geq 0$$

$$i_c(t) = C \frac{dv}{dt} \\ = 0.04 \times 5 \times (-2.5)e^{-2.5t} \\ = -0.5e^{-2.5t}A$$

$$i_1(t) = -\frac{6}{6+12} i_c(t), \text{ by current div.} \\ = 0.1667e^{-2.5t} A$$

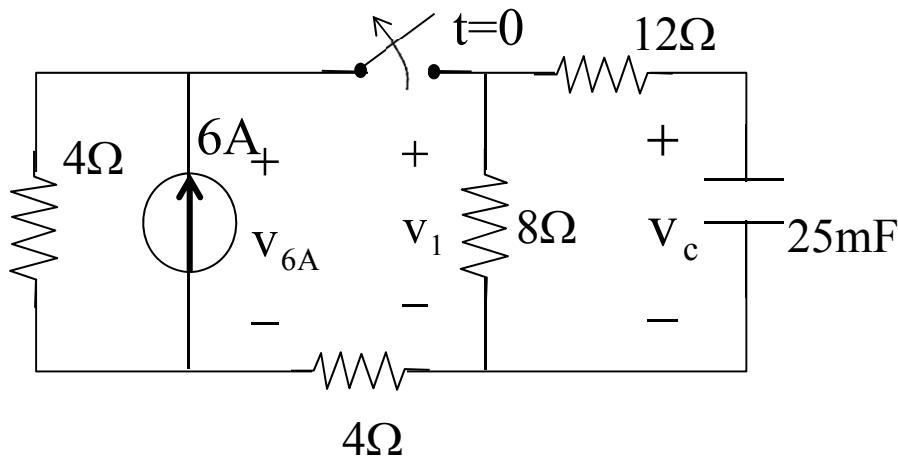Practice 2: Find $v_c(t)$ and $v_1(t)$ for $t > 0$.



For $t < 0$,

$$v_{6A} = 6 \times 4/12 = 18V$$

By voltage division

$$v_c(0^-) = v_1(0^-) \\ = \frac{8}{8+4} 18 = 12V$$


For $t > 0$, $R_{th} = 12 + 8 = 20\Omega$

$$\frac{1}{R_{th}C} = \frac{1}{20 \times 0.025} = 2 \quad v_c(t) = 12e^{-2t}V$$

By voltage division,


$$v_1(t) = \frac{8}{20} \times 12e^{-2t} = 4.8e^{-2t}V$$

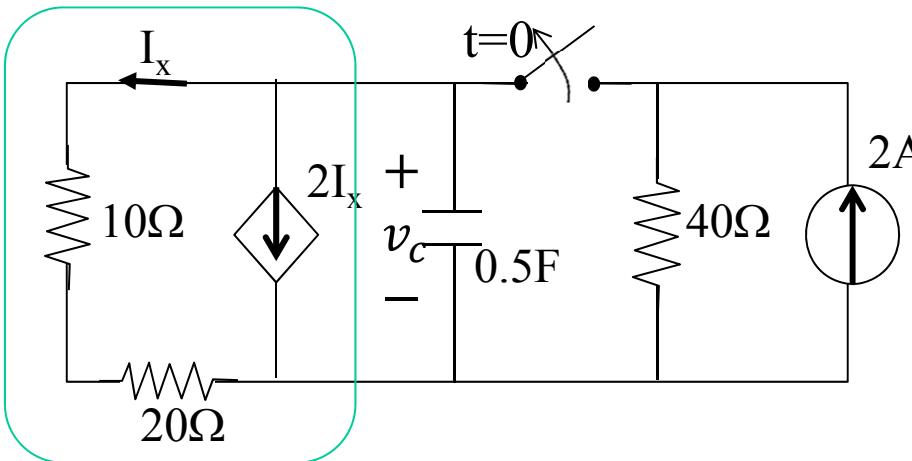Practice 3: The switch has been closed for a long time before open at $t=0$. Find $I_x(t)$ for $t > 0$.



Assign v_c .
Then by ohms law,
for all t ,
 $I_x(t) = \frac{v_c(t)}{30}$ (Eq1)

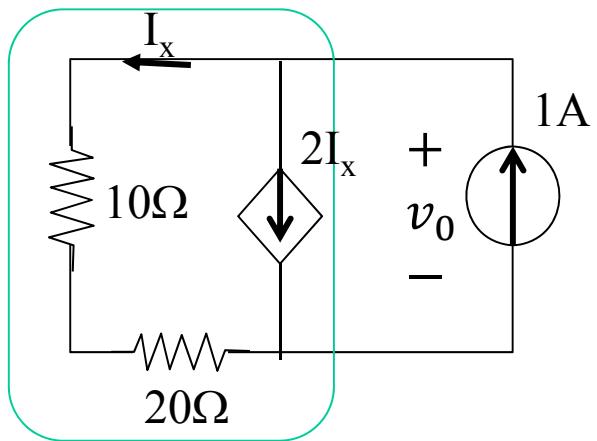Just need to find $v_c(t)$.
For simplicity, replace
the circuit inside the green box
with an equivalent resistance



$$I_x + 2I_x = 1, \rightarrow I_x = \frac{1}{3} A, v_0 = 10V$$

$$R_{eq} = \frac{v_0}{1} = 10\Omega$$

The equivalent circuit :
(Same $v_c(t)$ as original circuit)

For $t < 0$,


$$v_c(0^-) = 2(40//10) = 16V$$

For $t > 0$,



$$\frac{1}{R_{th}C} = \frac{1}{10 \times 0.5} = 0.2$$

$$\text{Thus, } v_c(t) = 16e^{-0.2t}V$$

Finally, plug into (eq1), $I_x(t) = \frac{16}{30} e^{-0.2t} A, \text{ for } t > 0$.

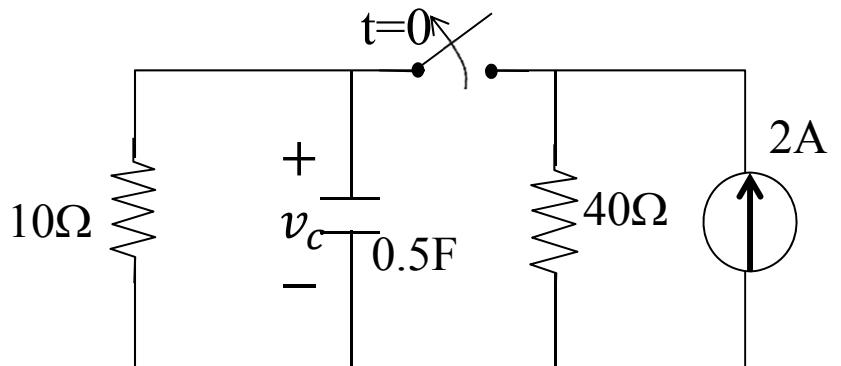

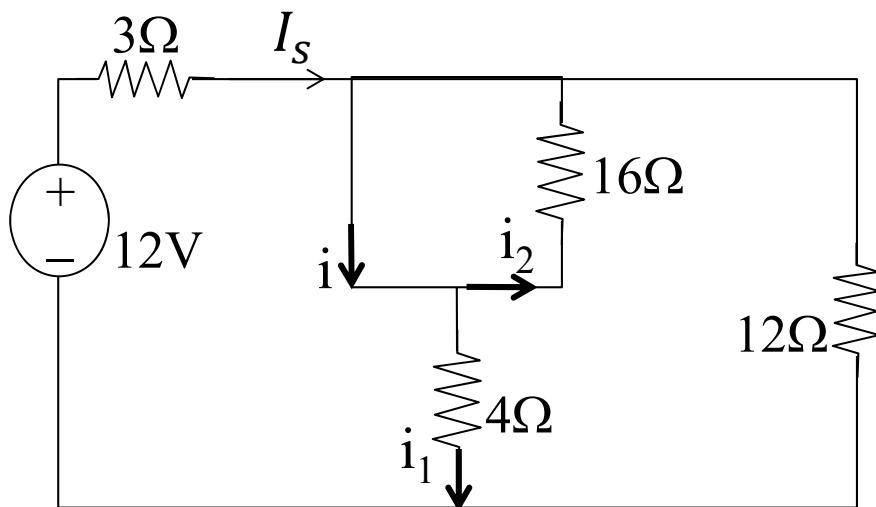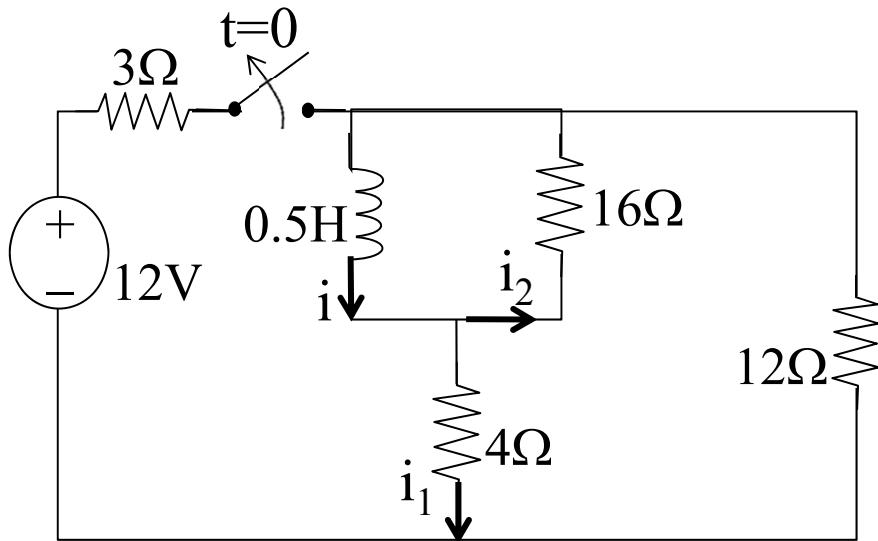Practice 4: Find $i(t)$, $i_1(t)$, $i_2(t)$ for $t > 0$.



For $t < 0$,

R_{eq} with respect to 12V:

$$R_{eq} = 3 + 4//12 = 6\Omega$$

$$I_s = \frac{12}{6} = 2A;$$

By current division:

$$i(0^-) = \frac{12}{4+12} 2 = 1.5A$$

For $t > 0$,

R_{th} with respect to L:


$$R_{th} = 16//16 = 8\Omega$$

$$\frac{R_{th}}{L} = \frac{8}{0.5} = 16$$



$$i(t) = 1.5e^{-16t}A$$

By current division:


$$i_1(t) = i_2(t) = \frac{16}{32} i(t) \\ = 0.75e^{-16t}A$$

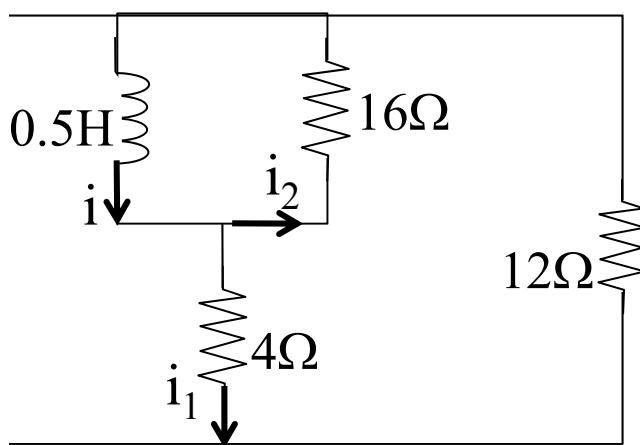

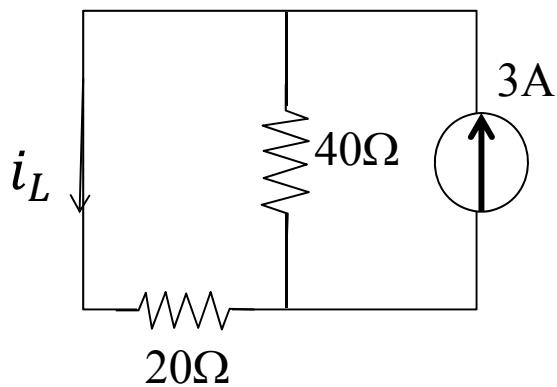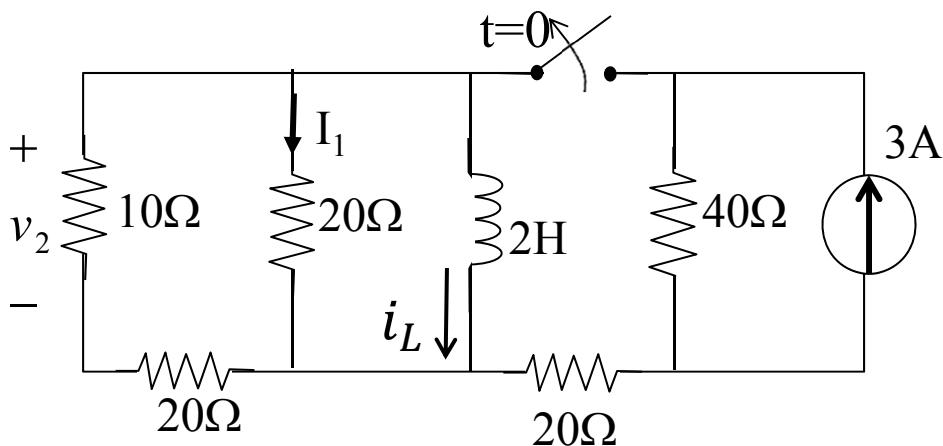Practice 5: Find $I_1(t)$ and $v_2(t)$ for $t > 0$.


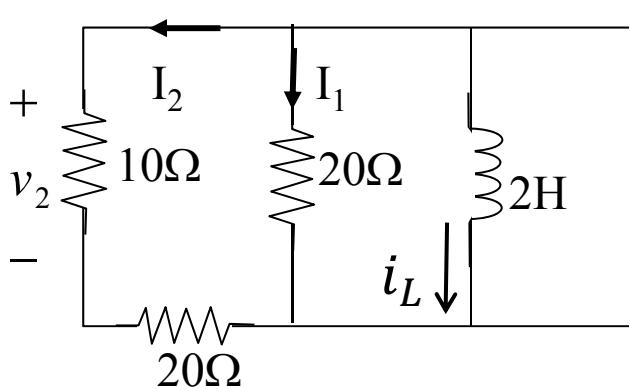
$$\text{For } t < 0, \\ i_L(0^-) = \frac{40}{40+20} \times 3 = 2A$$




For $t > 0$:

$$R_{th} = 30/20 = 12\Omega \\ \frac{R_{th}}{L} = \frac{12}{2} = 6 \\ i_L(t) = 2e^{-6t}A$$

By current division:

$$I_1(t) = -\frac{30}{50}i_L(t) \\ = -1.2e^{-6t}A \\ I_2(t) = -0.8e^{-6t}A \\ v_2(t) = 10I_2 = -8e^{-6t}V$$

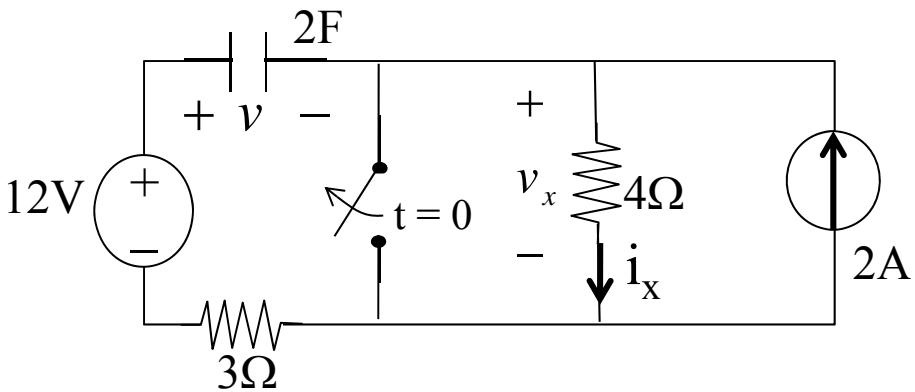
Practice 6: Find $v(t)$, $i_x(t)$ for $t > 0$.



$$A: \begin{aligned} v(t) &= 4 + 8e^{-t/14}V \\ i_x(t) &= 2 - (8/7)e^{-t/14}A \end{aligned}$$

$$\begin{aligned} v(0) &= 12V \\ v(\infty) &= 12 - 2 \times 4 = 4V \\ R_{th} \text{ w.r.t } C: \\ R_{th} &= 7\Omega \\ \frac{1}{R_{th}C} &= \frac{1}{14} \\ v(t) &= 4 + 8e^{-t/14}V \\ i_x(t) &= 2 + i_c(t) \\ &= 2 + 2(8) \left(-\frac{1}{14} \right) e^{-t/14} \\ &= 2 - \frac{8}{7}e^{-t/14}A \end{aligned}$$

Practice 7: Find $i_x(t)$ for $t > 0$.

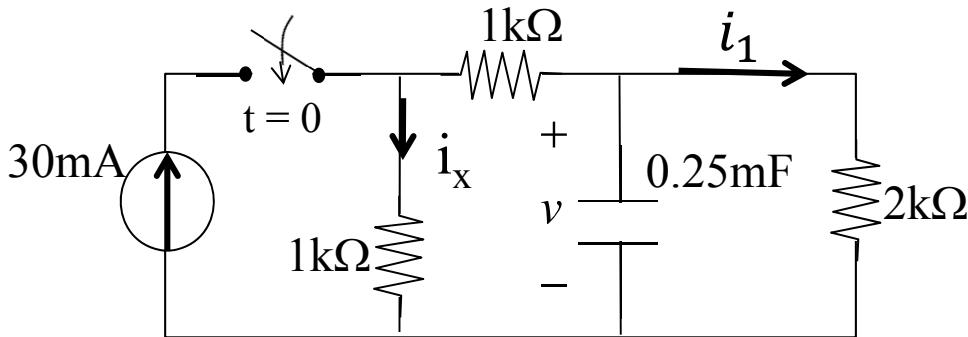

$$A: \begin{aligned} v(t) &= 15(1 - e^{-4t})V \\ i_x(t) &= 22.5 \times 10^{-3} - 7.5 \times 10^{-3}e^{-4t}A \end{aligned}$$

$$\begin{aligned} v(0) &= 0; \\ \text{For } t > 0, \\ R_{th} &= 2k/(1k + 1k) \\ &= 1k\Omega \\ \frac{1}{R_{th}C} &= 4 \end{aligned}$$

$$v_{30mA}(\infty) = 0.03(1k//3k) = 22.5V$$

$$v(\infty) = \frac{2}{3}v_{30mA} = 15V$$


$$v(t) = 15(1 - e^{-4t})V;$$

$$i_c(t) = C \frac{dv}{dt} = 0.25m(15)(4)e^{-4t} = 15e^{-4t}mA$$

$$i_1(t) = \frac{v}{2k} = 7.5(1 - e^{-4t})mA$$

$$i_x(t) = 30 - i_c - i_1 = 22.5 - 7.5e^{-4t}mA$$

Practice 8: Find $i(t)$ for all t .

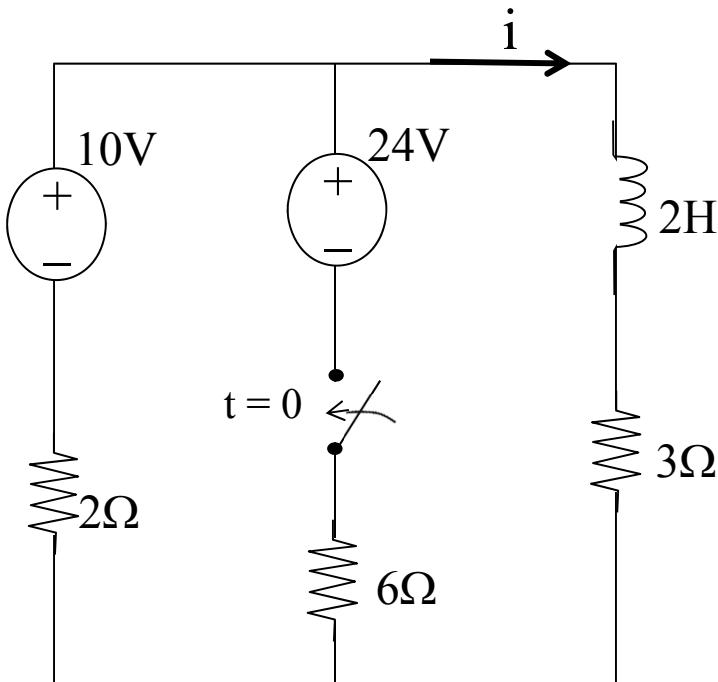


$$A: \begin{aligned} i(0) &= 2A, i(\infty) = 3A, R_N = 4.5\Omega \\ i(t) &= 3 - e^{-2.25t} A \end{aligned}$$

$$i(0) = \frac{10}{2+3} = 2A$$

For $t > 0$, $R_{th} = 3 + 6//2 = 4.5\Omega$, $\frac{R_{th}}{L} = 2.25$

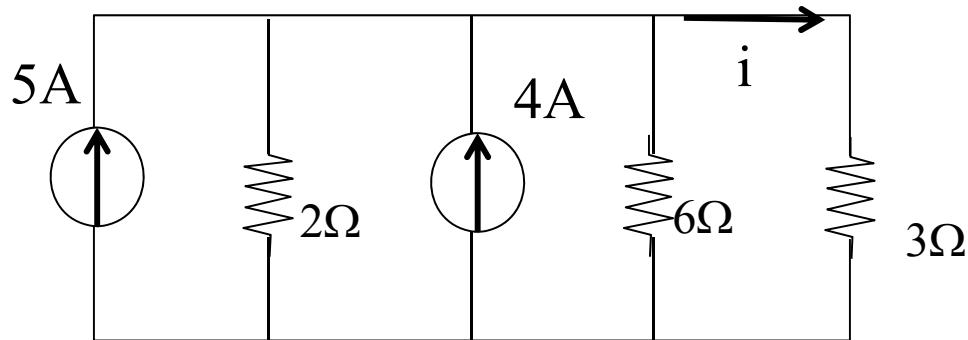
$i(\infty)$ can be found using source transformation:




$$i(\infty) = \frac{2//6}{2//6+3} (4 + 5) = 3A$$

$$i(t) = 3 + (2 - 3)e^{-2.25t} A$$

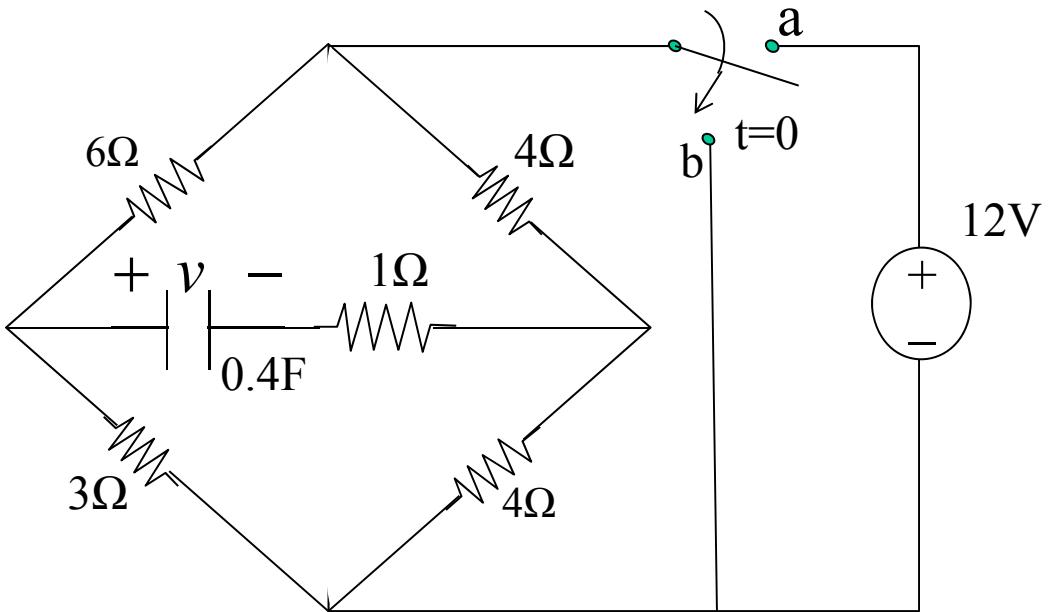Practice 9: Switch connected to “a” for a long time before connected to “b” at $t=0$. Find $v(t)$ for $t > 0$.



$$A: \quad v(t) = -2e^{-t/2}V$$

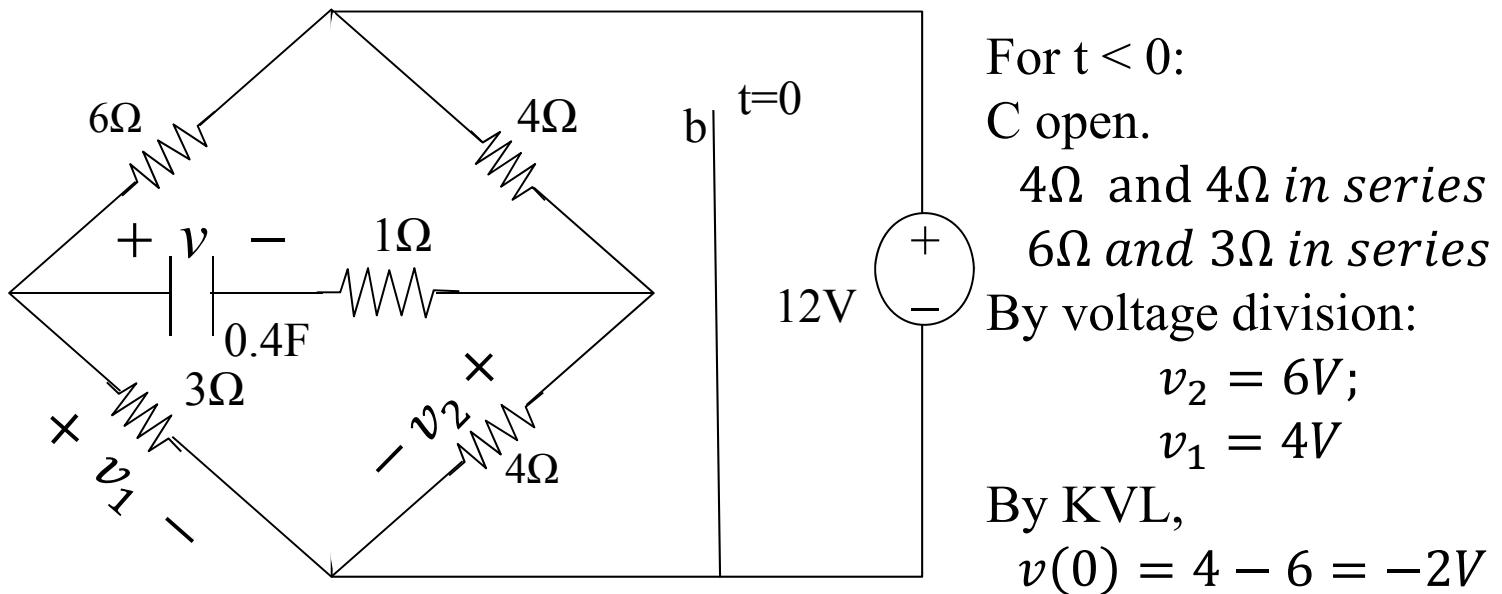

For $t > 0$, $v(\infty) = 0$.

Since $12V$ replaced by a short circuit, 4Ω and 4Ω in parallel, 3Ω and 6Ω in parallel. Thus,

$$R_{th} = 1 + 4//4 + 3//6 = 5\Omega, \quad \frac{1}{R_{th} C} = 0.5$$

$$v(t) = -2e^{-0.5t}V$$