

Practice 1: Solve  $\ddot{v} + 5\dot{v} + 6v = 18$ ,  $v(0) = 0$ ;  $\dot{v}(0) = 4$

Solution:  $\alpha = \frac{5}{2} = 2.5$ ;  $\omega_0 = \sqrt{6}$ ,  $\alpha > \omega_0$ , *Case 1.*

$$s_1, s_2 = -2.5 \pm \sqrt{2.5^2 - 6} = -2.5 \pm 0.5 = -2, -3$$

$$v(\infty) = \frac{18}{6} = 3.$$

The general solution:  $v(t) = 3 + A_1 e^{-2t} + A_2 e^{-3t}$

To satisfy initial condition:

$$v(0) = 3 + A_1 + A_2 = 0;$$

$$\dot{v}(0) = -2A_1 - 3A_2 = 4;$$

$$\rightarrow A_1 = -5, A_2 = 2;$$

$$\text{Final solution: } v(t) = 3 - 5e^{-2t} + 2e^{-3t}$$

Practice 2: Solve  $\ddot{v} + 4\dot{v} + 4v = 8$ ,  $v(0) = 1$ ;  $\dot{v}(0) = -1$

Solution:  $\alpha = \frac{4}{2} = 2$ ;  $\omega_0 = 2$   $\alpha = \omega_0$ , *Case 2*

$$v(\infty) = \frac{8}{4} = 2.$$

The general solution:  $v(t) = 2 + (A_1 + A_2 t)e^{-2t}$

To satisfy initial condition:

$$v(0) = 2 + A_1 = 1;$$

$$\dot{v}(0) = -2A_1 + A_2 = -1;$$

$$\rightarrow A_1 = -1, A_2 = -3;$$

$$\text{Final solution: } v(t) = 2 - (1 + 3t)e^{-2t}$$

Practice 3: Solve  $\ddot{v} + 4\dot{v} + 13v = 39$ ,  $v(0) = 1$ ;  $\dot{v}(0) = -1$

Solution:  $\alpha = \frac{4}{2} = 2$ ;  $\omega_0 = \sqrt{13}$ ,  $\alpha < \omega_0$ , *Case 3*.

$$\omega_d = \sqrt{13 - 4} = 3$$

$$v(\infty) = \frac{39}{13} = 3.$$

The general solution:

$$v(t) = 3 + e^{-2t}(B_1 \cos 3t + B_2 \sin 3t)$$

To satisfy initial condition:

$$v(0) = 3 + B_1 = 1;$$


$$\dot{v}(0) = -2B_1 + 3B_2 = -1;$$

$$\rightarrow B_1 = -2, B_2 = -\frac{5}{3};$$


$$\text{or } B_2 = \frac{V_1 + \alpha B_1}{\omega_d} = \frac{-1 - 4}{3} = -\frac{5}{3}$$

$$\text{Final solution: } v(t) = 3 - e^{-2t}(2\cos 3t e^{-3t} + \frac{5}{3}\sin 3t)$$

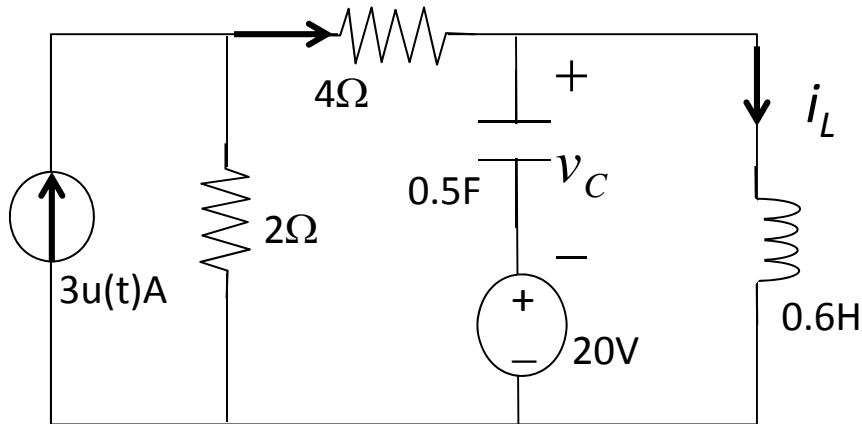Practice 4: Find  $v_C(0^+)$ ,  $i_L(0^+)$ ,  $\frac{dv_C(0^+)}{dt}$ ,  $\frac{di_L(0^+)}{dt}$




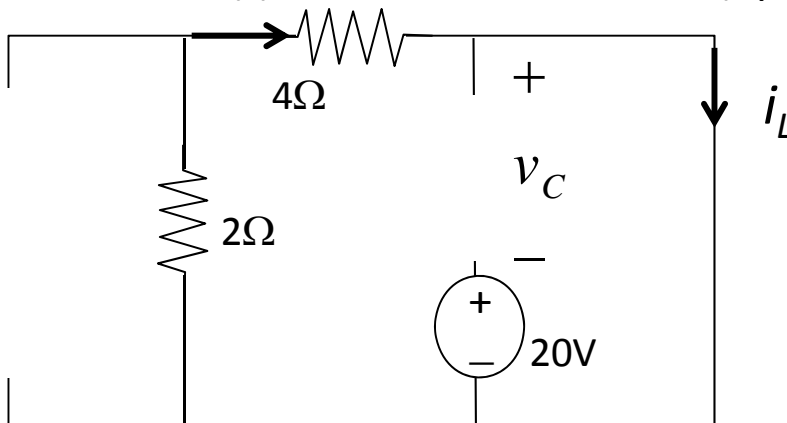For  $t < 0$ ,  $3u(t) = 0$ , current source off (open), C open, L short



$i_L(0) = 0$ ;  
 $v_C(0) = -20V$  by KVL  
 No voltage in resistors  
 Since 20V does not  
 supply power

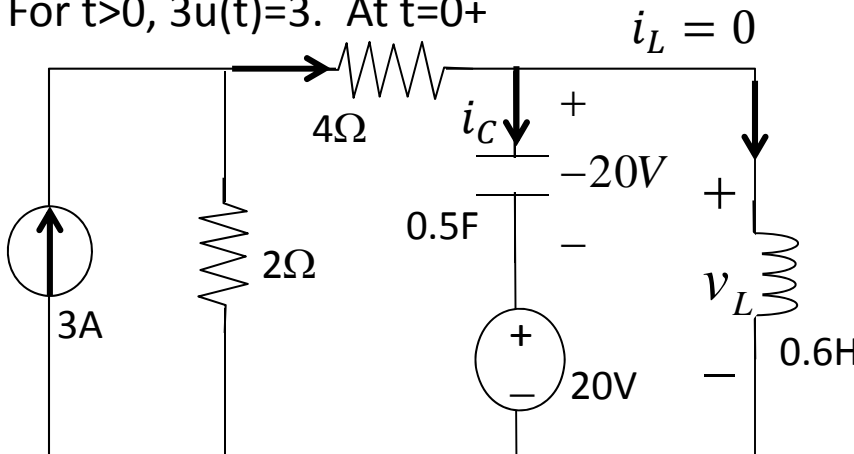
For  $t > 0$ ,  $3u(t) = 3$ . At  $t = 0^+$




By KVL,  
 $v_L(0^+) = -20 + 20 = 0V$   
 $4\Omega$  and  $2\Omega$  in parallel  
 By current division  
 $i_{4\Omega} = \frac{2}{4+2} 3 = 1A$ ;  
 By KCL,  
 $i_C(0^+) = i_{4\Omega} - i_L = 1A$

Thus,  $\frac{dv_C(0^+)}{dt} = \frac{1}{C} i_C(0^+) = \frac{1}{0.5} = 2V/s$ ,  $\frac{di_L(0^+)}{dt} = \frac{1}{L} v_L(0^+) = 0$

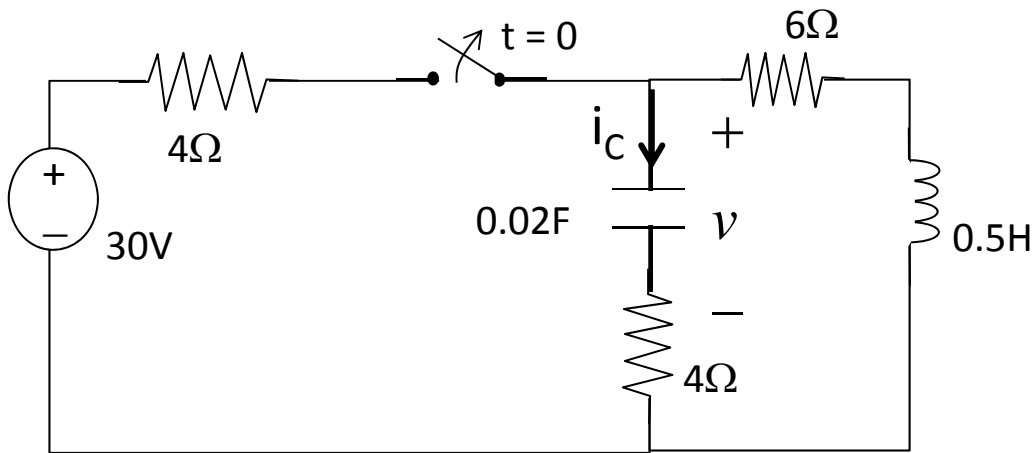**Practice 5:** Find  $v(t)$  for  $t > 0$ .



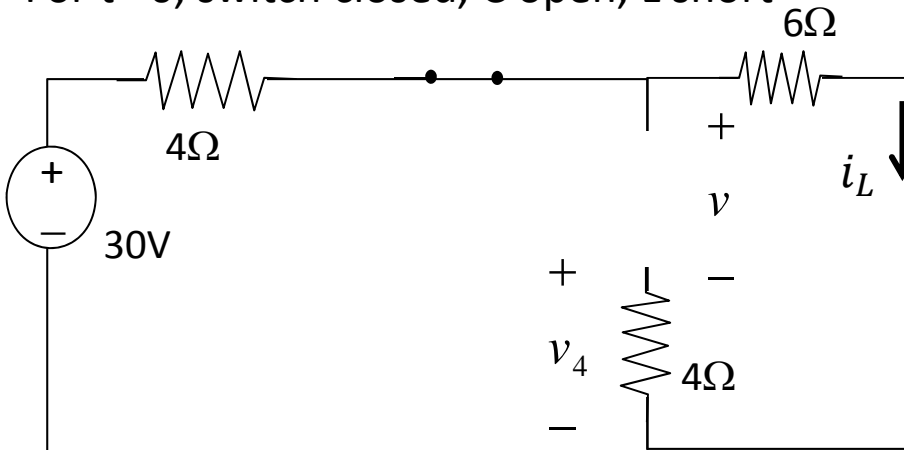For  $t < 0$ , switch closed, C open, L short




since  $v_4 = 0$ ,  
 $v$  is the voltage  
 across  $6\Omega$ .

By voltage division,

$$v(0) = \frac{6}{6+4} 30 = 18V$$

$$i_L(0) = \frac{30}{10} = 3A$$

For  $t > 0$ .

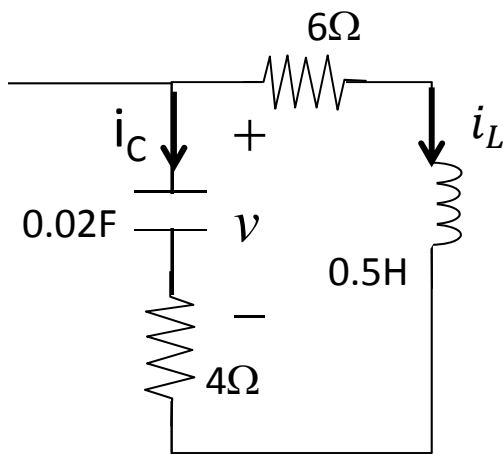

Since  $i_L = -i_c$ ,  $i_c(0+) = -3A$

$$\frac{dv(0^+)}{dt} = -\frac{3}{0.02} = -150V/s$$

$$\alpha = \frac{4+6}{2 \times 0.5} = 10, \omega_0 = \sqrt{\frac{1}{0.01}} = 10$$

Case 2. Since  $v(\infty) = 0$ ,

$$v(t) = (A_1 + A_2 t)e^{-10t}$$

To satisfy initial condition


$$v(0) = A_1 = 18;$$

$$\dot{v}(0) = -10A_1 + A_2 = -150$$

$$\rightarrow A_2 = 30$$

$$\text{Finally, } v(t) = (18 + 30t)e^{-10t}V$$

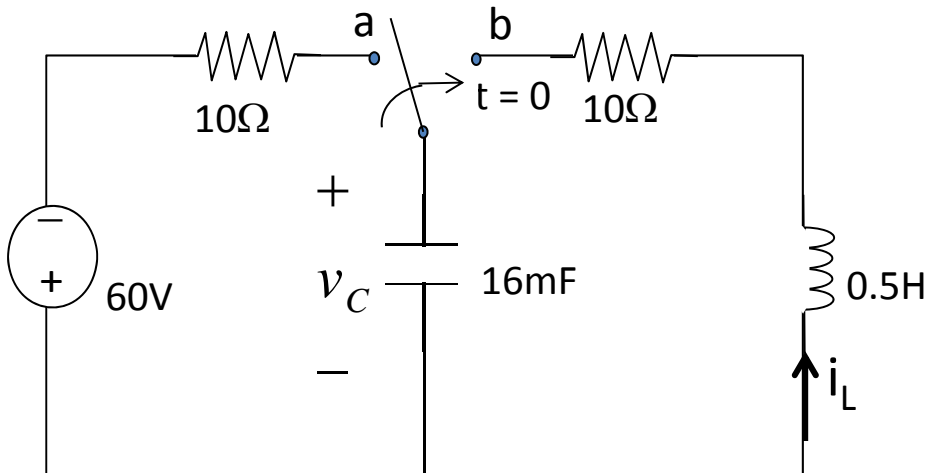**Practice 6:** The switch is at position a for a long time before swinging to position b at  $t = 0$ . Find  $i_L(t)$ ,  $v_C(t)$  for  $t > 0$ .



$$v_C(0) = -60V, \quad i_L(0) = 0A, \quad \frac{dv_C(0^+)}{dt} = \frac{0V}{s}$$

$$\alpha = 10, \omega_0 = \sqrt{125}, \quad \alpha < \omega_0$$

$$\text{Case 3: } \omega_d = \sqrt{125 - 100} = 5$$

$$\text{Since } v_C(\infty) = 0, v(t) = e^{-10t}(B_1 \cos 5t + B_2 \sin 5t)$$

To satisfy initial conditions:

$$B_1 = -60$$

$$-10B_1 + 5B_2 = 0, B_2 = -120$$


$$\text{Or, use } B_2 = \frac{v(0) + \alpha B_1}{\omega_d} = \frac{10 \times (-60)}{5} = -120$$

$$\text{Thus } v(t) = e^{-10t}(-60 \cos 5t - 120 \sin 5t) \text{ V}$$

$$\begin{aligned} i_L(t) &= i_C(t) = C \frac{dv_C}{dt} \\ &= 0.016((-10)e^{-10t}(-60 \cos 5t - 120 \sin 5t) \\ &\quad + e^{-10t}(300 \sin 5t - 600 \cos 5t)) \\ &= 24e^{-10t} \sin 5t \text{ A} \end{aligned}$$


**Practice 7:** Find  $v_C(t)$  for  $t > 0$ .

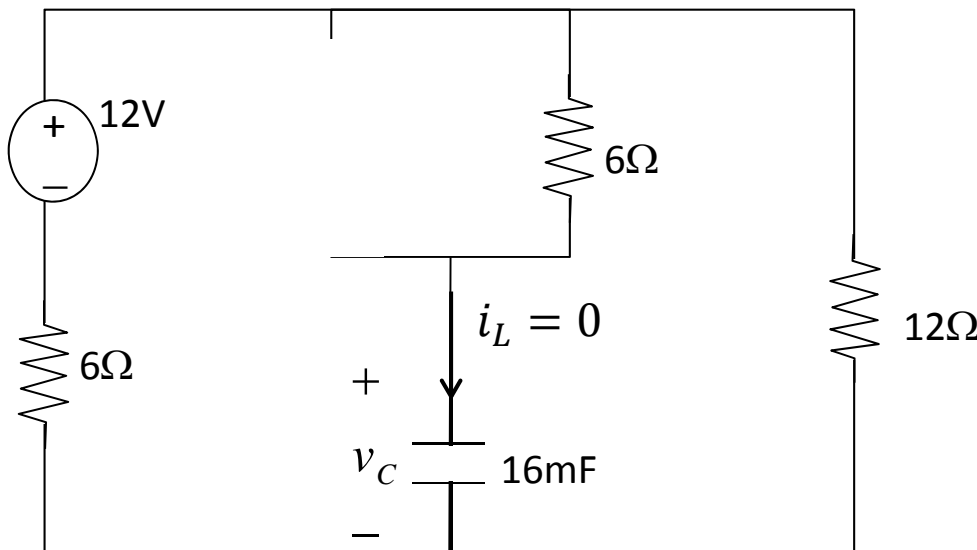For  $t < 0$ ,  $3u(t)A=0$ , current source open, C open, L short



$$v_C(0) = v_R = \frac{12}{6 + 12} \times 12 = 8V, \quad i_L(0) = 0, \quad \frac{dv_C(0)}{dt} = 0$$

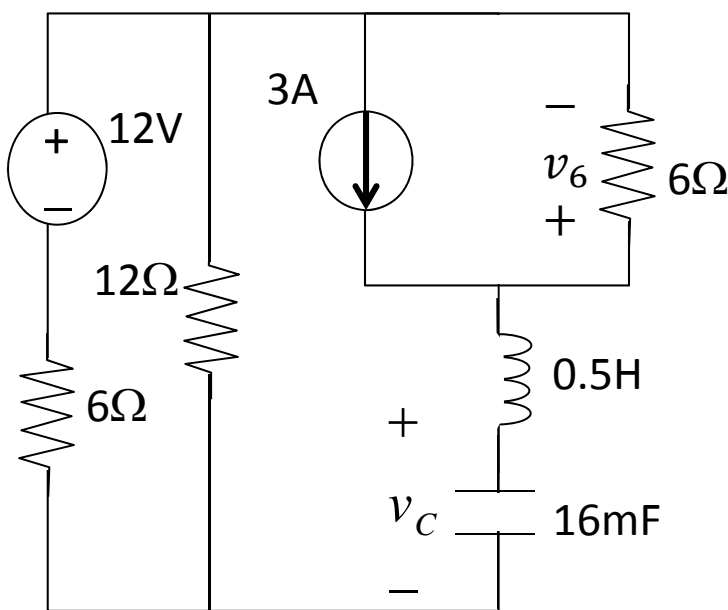For  $t > 0$ ,  $3u(t)=3$ . To see connection better, move  $12\Omega$  to the left



$$R_{th} = 6 + 12 // 6 = 10\Omega$$

Under DC condition,

$$v_R = 8V, v_6 = 18V,$$

$$v_C(\infty) = V_{th} = 8 + 18 = 26V$$

$$\alpha = \frac{10}{2 \times 0.5} = 10;$$

$$\omega_0 = 1/(0.5 \times 0.016)^{0.5}$$

$$= \sqrt{125},$$

$$\alpha < \omega_0, \quad \text{case 3}$$

$$\omega_d = \sqrt{125 - 100} = 5$$

$$v_c(t) = 26 + e^{-10t}(B_1 \cos 5t + B_2 \sin 5t)$$

To satisfy initial condition:

$$v_c(0) = 26 + B_1 = 8$$


$$\dot{v}_c(0) = -10B_1 + 5B_2 = 0$$

Solving equations to get  $B_1 = -18; B_2 = -36$


Step response:

$$v_c(t) = 26 + e^{-10t}(-18 \cos 5t - 36 \sin 5t)V$$

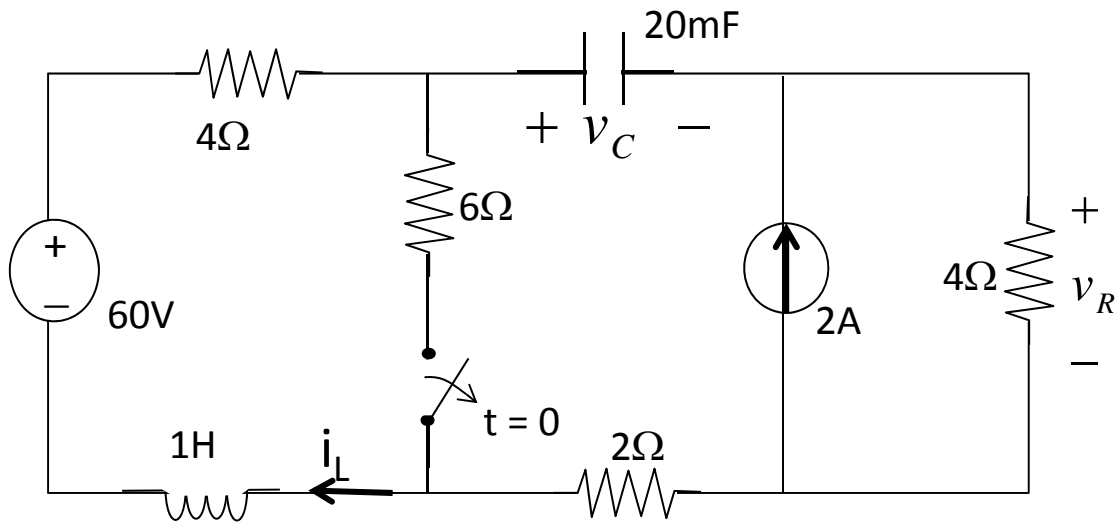**Practice 8:** Find  $i_L(t)$ ,  $v_C(t)$ ,  $v_R(t)$  for  $t > 0$ .




Step 1: For  $t < 0$

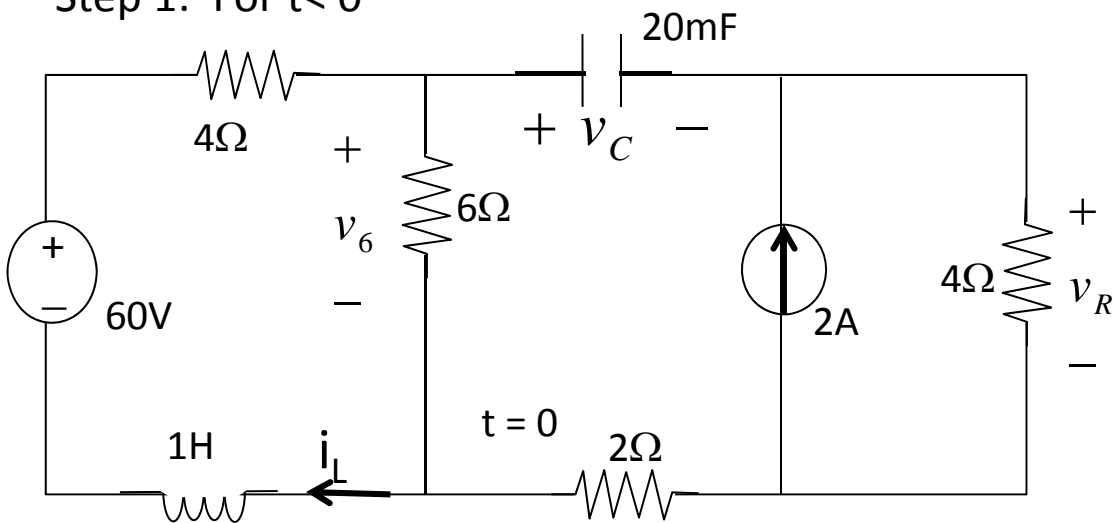

Since C open, L short,  $i_L(0) = \frac{60}{6+4} = 6A$ ,  $v_6 = 36V$ ,  $v_R = 8V$   
 No current and voltage drop in  $2\Omega$ ,  $v_C(0) = v_6 - v_R = 28V$



For  $t > 0$ ,

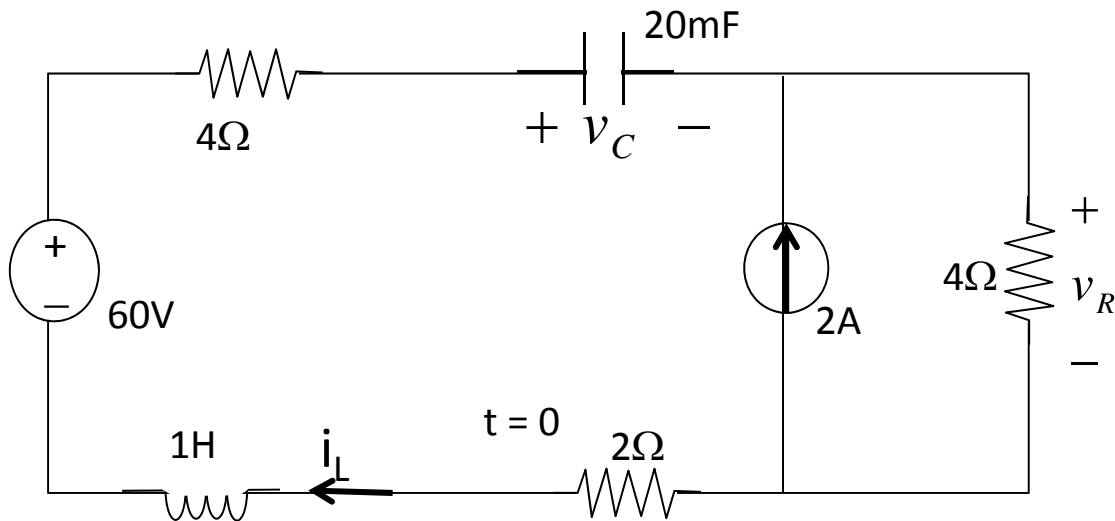

$$\text{Step 2: } i_c(0^+) = i_L(0) = 6A, \quad \frac{dv_c(0^+)}{dt} = \frac{6}{0.02} = 300V/s$$

$$R_{th} = 4 + 2 + 4 = 10\Omega, \quad V_{th} = v_c(\infty) = 60 - 8 = 52V$$

*Step 3: Math computation*

$$\alpha = \frac{10}{2} = 5, \quad \omega_0 = \frac{1}{(0.02)^{0.5}} = \sqrt{50}$$

$$\alpha < \omega_0, \quad \text{Case 3,} \quad \omega_d = 5:$$

$$\text{General solution: } v_c(t) = 52 + e^{-5t}(B_1 \cos 5t + B_2 \sin 5t)$$

By initial condition:

$$v_c(0) = 52 + B_1 = 28;$$

$$\dot{v}_c(0) = -5B_1 + 5B_2 = 300;$$


$$B_1 = -24, \quad B_2 = 36;$$

$$v_c(t) = 52 + e^{-5t}(-24 \cos 5t + 36 \sin 5t) V$$


$$\text{Other variables: } i_L(t) = i_c(t) = C \frac{dv_c}{dt}$$

$$v_R(t) = 4 \left( 2 + C \frac{dv_c}{dt} \right) = 8 + e^{-5t}(24 \cos 5t - 4.8 \sin 5t) V$$

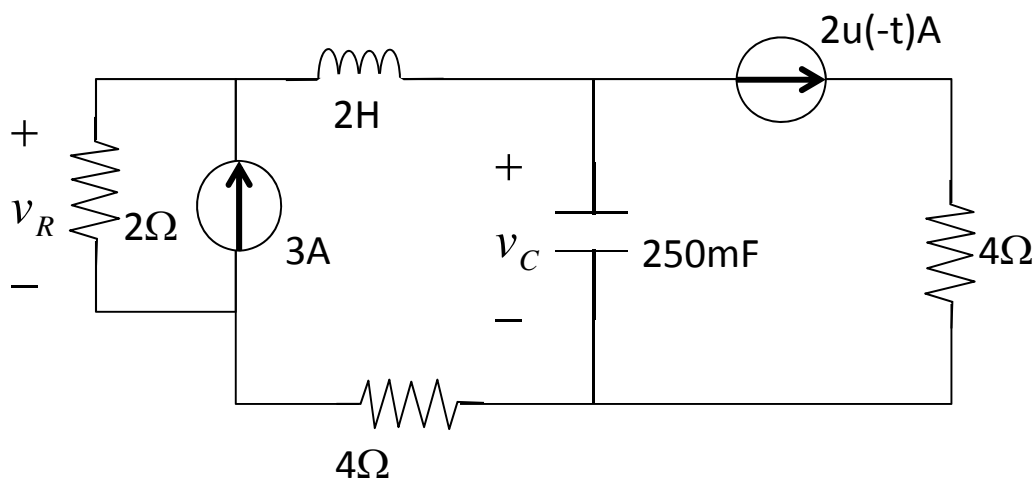**Practice 9:** Find  $v_C(t)$  and  $v_R(t)$  for  $t > 0$ .




Step 1:  $t < 0$ .  $2u(-t) = 2$

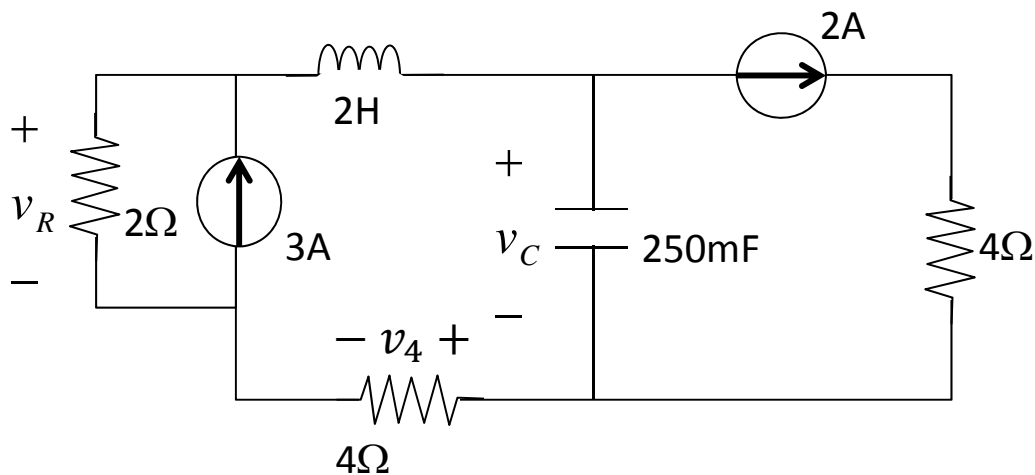

$$v_R = 2(3 - 2) = 2V; \quad v_4 = 2(4) = 8V;$$
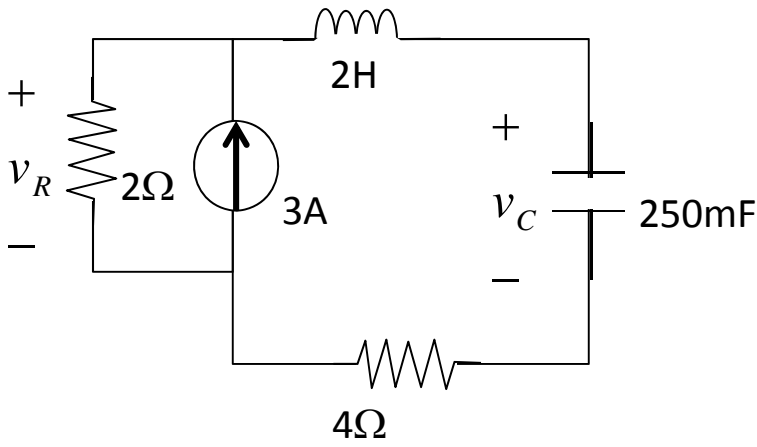
$$v_C(0) = v_R - v_4 = -6V, \quad i_L(0) = 2A$$



Step 2:  $t > 0$ .  $2u(-t) = 0$ ,

$$i_c(0+) = i_L(0) = 2A; \quad \dot{v}_c(0+) = \frac{2}{0.25} = 8V/s$$

$$v_{th} = v_c(\infty) = 6V; \quad R_{th} = 6\Omega$$

Step 3: Math computation

$$\alpha = \frac{6}{(2 \times 2)} = 1.5; \quad \omega_0 = \sqrt{2}$$

$$\alpha > \omega_0, \quad \text{Case 1}$$

$$s_1, s_2 = -1.5 \pm \sqrt{1.5^2 - 2} = -1, -2$$

General solution:

$$v_c(t) = 6 + A_1 e^{-t} + A_2 e^{-2t}$$

$$v_c(0) = 6 + A_1 + A_2 = -6$$

$$\dot{v}_c(0+) = -A_1 - 2A_2 = 8;$$

$$A_1 = -16, \quad A_2 = 4$$

$$v_c(t) = 6 - 16e^{-t} + 4e^{-2t} V$$

$$\begin{aligned} \text{For } v_R(t), \quad v_R(t) &= 2(3 - i_c) = 2 \left( 3 - C \frac{dv}{dt} \right) \\ &= 6 - 8e^{-t} + 4e^{-2t} V \end{aligned}$$