

EECE.3600 Exam I

10/16/2017

Name: _____

Signature: _____

1. (30%) For a wave with frequency $f = 1$ MHz, the amplitude phasor at different position z can be written as: $\tilde{A}(z) = 5e^{-j100z}$. (1) What is the instantaneous value of the amplitude $A(z, t)$ at different position z ? (2) What is the direction the wave travels? (3) What is the wavelength of the wave?

Solution:

(1) $\tilde{A}(z) = 5e^{-j100z} = \text{Re}[5e^{-j100z} e^{j\omega t}] = 5 \cos(\omega t - 100z) = 5 \cos(2\pi 10^6 t - 100z)$.

(2) The wave travels in the +z direction.

(3) $\beta = \frac{2\pi}{\lambda} = 100$, $\lambda = \frac{2\pi}{100} = 0.0628(m)$.

2. (30%) An air spaced lossless 50-Ω line ($\epsilon_r = 1$) is terminated in a load with impedance of $Z_L = 60 + j60\text{-}\Omega$ at frequency 5GHz, Find (1) the reflection coefficient; (2) the voltage standing wave ratio (S) and (3) the location of the first voltage maximum from the load in centimeters.

$$(1) \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{60 + j60 - 50}{60 + j60 + 50} = 0.49 \angle 0.91.$$


$$(2) S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.49}{1 - 0.49} = 2.9.$$

$$(3) l_{\max} = \frac{\theta_r}{4\pi} \lambda = 0.072\lambda.$$

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/s}}{5 \times 10^9 \text{ Hz}} = 6 \text{ cm}$$

$$l_{\max} = 0.43 \text{ cm}.$$

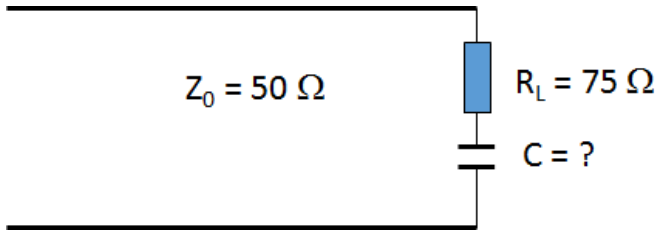3. (40%) A lossless 50-Ω line is terminated with a load. The capacitance is unknown. The voltage standing wave ratio (S) was measured to be S=3 at the frequency of 5GHz. (1) Find the capacitance; (2) what is the shortest length of the transmission line to make the Z_{in} real?



Solution:

$$(1) S = \frac{1+|\Gamma|}{1-|\Gamma|} = 3, |\Gamma| = 0.5.$$

$$|\Gamma| = \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| = \left| \frac{75 + \frac{1}{j\omega C} - 50}{75 + \frac{1}{j\omega C} + 50} \right| = \left| \frac{25 + \frac{1}{j\omega C}}{125 + \frac{1}{j\omega C}} \right| = \left[\frac{25^2 + \left(\frac{1}{\omega C}\right)^2}{125^2 + \left(\frac{1}{\omega C}\right)^2} \right]^{1/2}$$

$$\frac{25^2 + \left(\frac{1}{\omega C}\right)^2}{125^2 + \left(\frac{1}{\omega C}\right)^2} = \frac{1}{4}, \left(\frac{1}{\omega C}\right)^2 = 4375 \Omega^2, \left(\frac{1}{\omega C}\right) = 66.1 \Omega$$

$$\omega C = 0.015 \Omega^{-1}, C = \frac{0.015 \Omega^{-1}}{\omega} = 0.48 \text{ pF}.$$

$$(2) Z_L = 75 + \frac{1}{j\omega C} \Omega = 75 + j66.1 \Omega$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \left| \frac{75 + j66.1 - 50}{75 + j66.1 + 50} \right| = 0.5 \angle 0.72.$$

Z_{in} is real at $|V|_{\max}$ or $|V|_{\min}$.

$$l_{\max} = \frac{\theta_r}{4\pi} \lambda = 0.057 \lambda, l_{\min} = \frac{\theta_r}{4\pi} \lambda + \frac{1}{4} \lambda = 0.307 \lambda$$

Voltage maximum	$ \tilde{V} _{\max} = V_0^+ [1 + \Gamma]$
Voltage minimum	$ \tilde{V} _{\min} = V_0^+ [1 - \Gamma]$
Positions of voltage maxima (also positions of current minima)	$l_{\max} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2}, \quad n = 0, 1, 2, \dots$
Position of first maximum (also position of first current minimum)	$l_{\max} = \begin{cases} \frac{\theta_r \lambda}{4\pi}, & \text{if } 0 \leq \theta_r \leq \pi \\ \frac{\theta_r \lambda}{4\pi} + \frac{\lambda}{2}, & \text{if } -\pi \leq \theta_r \leq 0 \end{cases}$
Positions of voltage minima (also positions of first current maxima)	$l_{\min} = \frac{\theta_r \lambda}{4\pi} + \frac{(2n+1)\lambda}{4}, \quad n = 0, 1, 2, \dots$
Position of first minimum (also position of first current maximum)	$l_{\min} = \frac{\lambda}{4} \left(1 + \frac{\theta_r}{\pi}\right)$
Input impedance	$Z_{\text{in}} = Z_0 \left(\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right)$
Positions at which Z_{in} is real	at voltage maxima and minima
Z_{in} at voltage maxima	$Z_{\text{in}} = Z_0 \left(\frac{1 + \Gamma }{1 - \Gamma } \right)$
Z_{in} at voltage minima	$Z_{\text{in}} = Z_0 \left(\frac{1 - \Gamma }{1 + \Gamma } \right)$
Z_{in} of short-circuited line	$Z_{\text{in}}^{\text{sc}} = jZ_0 \tan \beta l$
Z_{in} of open-circuited line	$Z_{\text{in}}^{\text{oc}} = -jZ_0 \cot \beta l$
Z_{in} of line of length $l = n\lambda/2$	$Z_{\text{in}} = Z_L, \quad n = 0, 1, 2, \dots$
Z_{in} of line of length $l = \lambda/4 + n\lambda/2$	$Z_{\text{in}} = Z_0^2/Z_L, \quad n = 0, 1, 2, \dots$
Z_{in} of matched line	$Z_{\text{in}} = Z_0$
$ V_0^+ $ = amplitude of incident wave, $\Gamma = \Gamma e^{j\theta_r}$ with $-\pi < \theta_r < \pi$; θ_r in radians.	

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$