

**EECE.3600 Exam I**

**03/05/2018**

Name: \_\_\_\_\_

Signature: \_\_\_\_\_

1. (30%) A wave with the frequency of 1-MHz travels in the  $-z$  direction in air. Assume the wave travels at the speed of light ( $c = 3.0 \times 10^8 \text{ m/s}$  in air). If the wave reaches a peak value of 1.5 at  $z = 100 \text{ m}$  when  $t = 0.2 \text{ } \mu\text{s}$ . Find:

1) (10 points) Wavelength in air

2) (10 points) Expression for the instantaneous of the wave (time domain)

3) (10 points) Expression for the wave in the phasor domain

Solution:

$$1). \lambda f = c, \lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/s}}{10^6 \text{ Hz}} = 300 \text{ m}$$

$$2). y(z, t) = 1.5 \cos\left(\omega t + \frac{2\pi}{\lambda} z + \varphi_0\right)$$

$$1.5 = 1.5 \cos\left(2\pi 10^6 \times 0.2 \times 10^{-6} + \frac{2\pi}{300} 100 + \varphi_0\right) \varphi_0 = 0.933\pi$$

$$y(z, t) = 1.5 \cos\left(\omega t + \frac{2\pi}{\lambda} z + 0.933\pi\right)$$

$$3) \tilde{y}(z) = 1.2\pi e^{j\left(\frac{2\pi}{\lambda} z + 0.933\pi\right)}$$

2 (35%) An air spaced lossless  $50\text{-}\Omega$  line ( $\epsilon_r = 1$ ) is terminated in a load with impedance of  $Z_L = 100 + j60\text{-}\Omega$  at frequency  $5\text{GHz}$ . Find (1) the reflection coefficient; (2) the voltage standing wave ratio ( $S$ ) and (3) the location of the first voltage maximum from the load in centimeters.

Solutions:

$$(1) \Gamma = \frac{100 + j60 - 50}{100 + j60 + 50} = 0.48 \angle 28.4^\circ$$

$$(2) S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = 2.85$$

$$(3) l_{max} = \frac{\theta_r}{4\pi} \lambda = 0.04\lambda = 0.24\text{cm}$$

3. (35%) A lossless  $50\text{-}\Omega$  line  $\lambda/8$  is terminated in an unknown impedance. If the input impedance is  $Z_{in} = -j60\text{-}\Omega$ . Find the load  $Z_L$ .

Solutions:

$$\beta L = \frac{2\pi}{\lambda} \frac{\lambda}{8} = \frac{\pi}{4},$$

$$\frac{Z_{in}}{Z_0} = \frac{Z_L + jZ_0 \tan \beta L}{Z_0 + jZ_L \tan \beta L} = \frac{Z_L + jZ_0}{Z_0 + jZ_L} = -j1.2$$

$$Z_L = j550\Omega$$

Voltage maximum	$ \tilde{V} _{\max} =  V_0^+ [1 +  \Gamma ]$
Voltage minimum	$ \tilde{V} _{\min} =  V_0^+ [1 -  \Gamma ]$
Positions of voltage maxima (also positions of current minima)	$l_{\max} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2}, \quad n = 0, 1, 2, \dots$
Position of first maximum (also position of first current minimum)	$l_{\max} = \begin{cases} \frac{\theta_r \lambda}{4\pi}, & \text{if } 0 \leq \theta_r \leq \pi \\ \frac{\theta_r \lambda}{4\pi} + \frac{\lambda}{2}, & \text{if } -\pi \leq \theta_r \leq 0 \end{cases}$
Positions of voltage minima (also positions of first current maxima)	$l_{\min} = \frac{\theta_r \lambda}{4\pi} + \frac{(2n+1)\lambda}{4}, \quad n = 0, 1, 2, \dots$
Position of first minimum (also position of first current maximum)	$l_{\min} = \frac{\lambda}{4} \left( 1 + \frac{\theta_r}{\pi} \right)$
Input impedance	$Z_{\text{in}} = Z_0 \left( \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right)$
Positions at which $Z_{\text{in}}$ is real	at voltage maxima and minima
$Z_{\text{in}}$ at voltage maxima	$Z_{\text{in}} = Z_0 \left( \frac{1 +  \Gamma }{1 -  \Gamma } \right)$
$Z_{\text{in}}$ at voltage minima	$Z_{\text{in}} = Z_0 \left( \frac{1 -  \Gamma }{1 +  \Gamma } \right)$
$Z_{\text{in}}$ of short-circuited line	$Z_{\text{in}}^{\text{sc}} = jZ_0 \tan \beta l$
$Z_{\text{in}}$ of open-circuited line	$Z_{\text{in}}^{\text{oc}} = -jZ_0 \cot \beta l$
$Z_{\text{in}}$ of line of length $l = n\lambda/2$	$Z_{\text{in}} = Z_L, \quad n = 0, 1, 2, \dots$
$Z_{\text{in}}$ of line of length $l = \lambda/4 + n\lambda/2$	$Z_{\text{in}} = Z_0^2/Z_L, \quad n = 0, 1, 2, \dots$
$Z_{\text{in}}$ of matched line	$Z_{\text{in}} = Z_0$
$ V_0^+ $ = amplitude of incident wave, $\Gamma =  \Gamma e^{j\theta_r}$ with $-\pi < \theta_r < \pi$ ; $\theta_r$ in radians.	

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$