

EECE.3600 Exam I

10/03/2016

Name: _____

Signature: _____

1. (35%) An air spaced lossless $50\text{-}\Omega$ line ($\epsilon_r = 1$) is terminated in a load with impedance of $Z_L = 60 + j60\text{-}\Omega$ at frequency 5GHz , Find (1) the reflection coefficient; (2) the voltage standing wave ratio (S) and (3) the location of the first voltage maximum from the load in centimeters.

Solutions:

$$(1) \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{60 + j60 - 50}{60 + j60 + 50} = 0.49 \angle 0.91.$$


$$(2) S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.49}{1 - 0.49} = 2.9.$$

$$(3) l_{\max} = \frac{\theta_r}{4\pi} \lambda = 0.072 \lambda.$$

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/s}}{5 \times 10^9 \text{ Hz}} = 6 \text{ cm}$$

$$l_{\max} = 0.43 \text{ cm}.$$

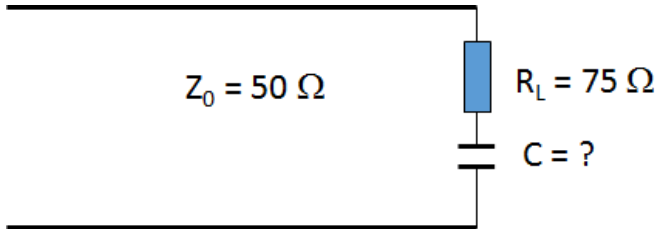2. (30%) A lossless $50\text{-}\Omega$ line is terminated with a load. The capacitance is unknown. The voltage standing wave ratio (S) was measured to be 3 at the frequency of 5GHz , Find the capacitance.



Solution:

$$S = \frac{1+|\Gamma|}{1-|\Gamma|} = 3, \quad |\Gamma| = 0.5$$

$$|\Gamma| = \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| = \left| \frac{75 + \frac{1}{j\omega C} - 50}{75 + \frac{1}{j\omega C} + 50} \right| = \left| \frac{25 + \frac{1}{j\omega C}}{125 + \frac{1}{j\omega C}} \right| = \left[\frac{25^2 + \left(\frac{1}{\omega C}\right)^2}{125^2 + \left(\frac{1}{\omega C}\right)^2} \right]^{1/2}$$

$$\frac{25^2 + \left(\frac{1}{\omega C}\right)^2}{125^2 + \left(\frac{1}{\omega C}\right)^2} = \frac{1}{4}, \quad \left(\frac{1}{\omega C}\right)^2 = 4375\ \Omega^2,$$

$$\omega C = 0.015\ \Omega^{-1}, \quad C = \frac{0.015\ \Omega^{-1}}{\omega} = 0.48\ \text{pF}.$$

3. (35%) A 5GHz voltage source is connected to a lossless transmission line is terminated with $Z_L = -j75\text{-}\Omega$. The characteristic impedance of the transmission line is $50\text{-}\Omega$. Assuming the phase velocity of the transmission line is $0.8c$, where c is the speed of light. (1) What's the voltage reflection coefficient? (2) Find out the location of the first $|V|_{\min}$ from the load, (3) What's the standing wave ratio S ? (4) how long the transmission line will make it equivalent to an open circuit?

Solutions:

$$(1) \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{-j75 - 50}{j75 + 50} = 1 \angle -1.18.$$

$$(2) l_{\min} = \frac{\theta_r}{4\pi} \lambda + \frac{\lambda}{4} = 0.16\lambda, \quad \lambda = \frac{0.8c}{5\text{GHz}} = 4.8\text{cm}.$$

$$l_{\min} = 0.16\lambda = 0.77\text{cm}.$$

$$(3) S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \infty.$$

$$(4) Z_{in} = \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} = \infty,$$

$$Z_0 + jZ_L \tan \beta l = 0, \quad Z_0 + jZ_L \tan \beta l = 0$$

$$50 + 75 \tan \beta l = 0, \quad \tan \beta l = -\frac{2}{3}, \quad \tan(\pi - \beta l) = \frac{2}{3}, \quad \pi - \beta l = 0.588,$$

$$\beta l = \pi - 0.588, \quad l = \frac{\pi - 0.588}{4\pi} \lambda = 1.97\text{cm}.$$

Another method:

$$Z_{in} = Z_0 \frac{e^{j\beta l} + \Gamma e^{-j\beta l}}{e^{j\beta l} - \Gamma e^{-j\beta l}} = \infty, \quad e^{j\beta l} - \Gamma e^{-j\beta l} = 0, \quad e^{j2\beta l} = \Gamma,$$

$$e^{j2\beta l} = e^{-j1.18}, \quad e^{j2\beta l} = e^{j(2\pi - 1.18)}, \quad 2\beta l = (2\pi - 1.18),$$

$$l = \frac{(2\pi - 1.18)}{4\pi} \lambda = 1.97\text{cm}.$$

Voltage maximum	$ \tilde{V} _{\max} = V_0^+ [1 + \Gamma]$
Voltage minimum	$ \tilde{V} _{\min} = V_0^+ [1 - \Gamma]$
Positions of voltage maxima (also positions of current minima)	$l_{\max} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2}, \quad n = 0, 1, 2, \dots$
Position of first maximum (also position of first current minimum)	$l_{\max} = \begin{cases} \frac{\theta_r \lambda}{4\pi}, & \text{if } 0 \leq \theta_r \leq \pi \\ \frac{\theta_r \lambda}{4\pi} + \frac{\lambda}{2}, & \text{if } -\pi \leq \theta_r \leq 0 \end{cases}$
Positions of voltage minima (also positions of first current maxima)	$l_{\min} = \frac{\theta_r \lambda}{4\pi} + \frac{(2n+1)\lambda}{4}, \quad n = 0, 1, 2, \dots$
Position of first minimum (also position of first current maximum)	$l_{\min} = \frac{\lambda}{4} \left(1 + \frac{\theta_r}{\pi} \right)$
Input impedance	$Z_{\text{in}} = Z_0 \left(\frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right)$
Positions at which Z_{in} is real	at voltage maxima and minima
Z_{in} at voltage maxima	$Z_{\text{in}} = Z_0 \left(\frac{1 + \Gamma }{1 - \Gamma } \right)$
Z_{in} at voltage minima	$Z_{\text{in}} = Z_0 \left(\frac{1 - \Gamma }{1 + \Gamma } \right)$
Z_{in} of short-circuited line	$Z_{\text{in}}^{\text{sc}} = jZ_0 \tan \beta l$
Z_{in} of open-circuited line	$Z_{\text{in}}^{\text{oc}} = -jZ_0 \cot \beta l$
Z_{in} of line of length $l = n\lambda/2$	$Z_{\text{in}} = Z_L, \quad n = 0, 1, 2, \dots$
Z_{in} of line of length $l = \lambda/4 + n\lambda/2$	$Z_{\text{in}} = Z_0^2/Z_L, \quad n = 0, 1, 2, \dots$
Z_{in} of matched line	$Z_{\text{in}} = Z_0$
$ V_0^+ $ = amplitude of incident wave, $\Gamma = \Gamma e^{j\theta_r}$ with $-\pi < \theta_r < \pi$; θ_r in radians.	

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$