

1.(a) (10%) If a voltage  $V(t) = 10\sin(100\pi t + \pi/4)$ , what is the phasor of the voltage?

$$\tilde{V} = 10 e^{j(\frac{\pi}{4} - \frac{\pi}{2})} \quad \text{or}$$

$$\tilde{V} = 10 e^{-j(\frac{\pi}{4} - \frac{\pi}{2})}$$

1.(b) (30%) A voltage source  $V(t) = 10\sin(6 \times 10^9 \pi)$  (V) with a resistance of  $10\text{-}\Omega$  is connected to  $12\text{-cm}$  long lossless transmission line. The characteristic impedance of the transmission line is  $50\text{-}\Omega$ . If the transmission line is terminated with  $Z_L = j25\text{-}\Omega$ . Find out the location of the first  $|V|_{\max}$  from the load, and the value of  $|V|_{\max}$ , assuming the phase velocity of the transmission line equals the speed of light.

$$(a) \quad f = 3 \times 10^9 \text{ (Hz)} \quad , \quad \lambda = \frac{c}{f} = \frac{3 \times 10^8}{3 \times 10^9} = 0.1 \text{ m} = 10 \text{ cm}$$

$$\text{For } |V|_{\max}, \quad 2\beta L + \theta_r = 2n\pi. \quad \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{j25 - 50}{j25 + 50}$$

$$= 1 \angle 126^\circ$$

$$\Rightarrow 2\beta L = -126^\circ$$

$$\Rightarrow L = 0.0175 \text{ m} = 1.75 \text{ cm}.$$

$$(b) \quad |V|_{\max} = (1 + |\Gamma|) |V_0^+|, \quad |V_0^+| = |V_g| \cdot \frac{Z_0}{Z_g + Z_0}$$

$$= 10 \cdot \frac{5}{6} = 8.3 \text{ (V)}$$

$$\therefore |V|_{\max} = 2 \cdot 8.3 \text{ (V)}$$


$$= 16.6 \text{ (V)}$$

For Graphic solution, see Smith Chart.

$$L = 0.074\lambda - 0.25\lambda$$

$$= 0.176\lambda$$

$$L = 1.76 \text{ cm}$$

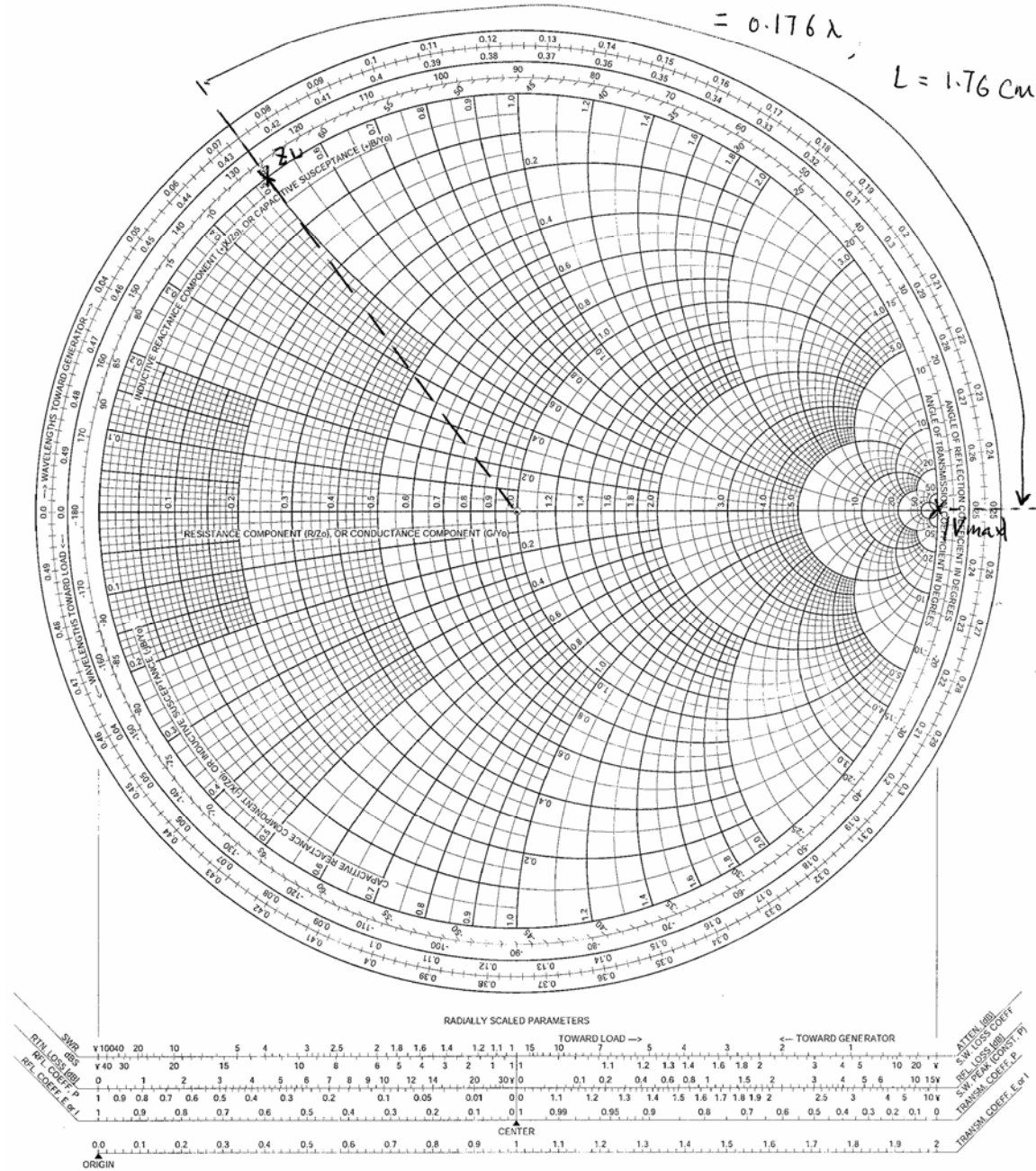

2. (30%) On a lossless  $50\text{-}\Omega$  transmission line terminated with a  $Z_L = 50 + j80\ \Omega$ . If this transmission line is to be matched to the load using a shorted load stub. Determine the stub length and distance between the load and stub. Two possible answers. You only need to show one of them.


$$Z_L = \frac{Z_L}{Z_0} = 1 + j1.6, \quad \text{point A}$$

$$Y_L = 0.28 - j0.44, \quad \text{point B}$$


$$d = 0.25\lambda, \quad L = 0.338 - 0.25 = 0.084\lambda$$

or  $d = 0.25 + 0.338 - 0.18\lambda = 0.31\lambda$
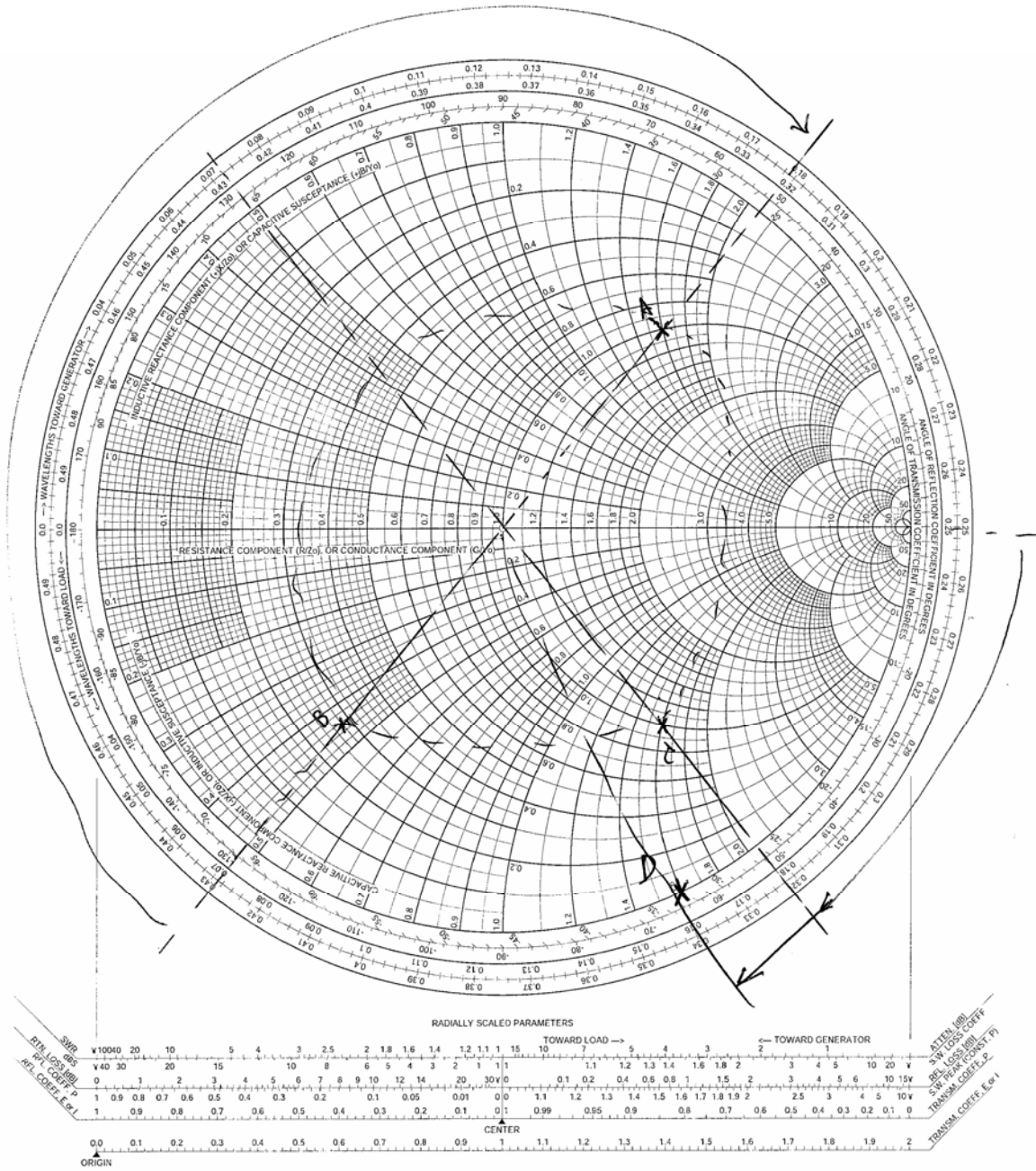
$$L = 0.18 + 0.5 - 0.25\lambda = 0.43\lambda$$



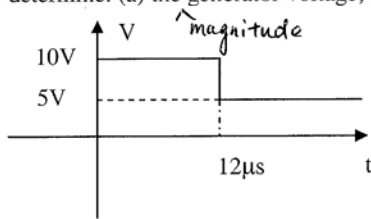3. (30%) A time domain reflector is an instrument to locate faults on a transmission line. A voltage meter is connected to beginning of a  $50\text{-}\Omega$  lossless matched transmission line, and the measured voltage waveform is shown in following figure. The line insulating material is Teflon with  $\epsilon_r = 2.0$ . If we know that the resistance of the generator is  $25\text{-}\Omega$ , determine: (a) the generator voltage, and (b) the location of the fault.



$$(a) \quad |V_0^+| = |V_g| \cdot \frac{z_0}{z_0 + z_g} = |V_g| \cdot \frac{50}{25 + 50}$$

$$\Rightarrow |V_g| = \frac{75}{50} \cdot |V_0^+| = 1.5 \cdot 10 \text{ (V)} = 15 \text{ (V)}$$

$$(b). \quad V_p = \frac{c}{\sqrt{\epsilon_r}} = \frac{c}{\sqrt{2}} = 2.1 \times 10^8 \text{ m/s}$$

$$\frac{2 \cdot l}{V_p} = t_d = 12 \mu\text{s}$$

$$\Rightarrow l = V_p \cdot \frac{t_d}{2} = 2 \times 10^8 \text{ m/s} \cdot \frac{12}{2} \times 10^{-6}$$

$$= 1.26 \times 10^3 \text{ m}$$

$$\sim 1.3 \times 10^3 \text{ m}$$