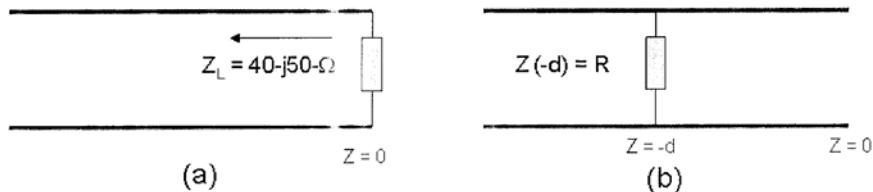


A 50Ω lossless transmission line is terminated with a load Z_L . The phase velocity is $2.0 \times 10^{10} \text{ cm/s}$ at the frequency of 10GHz. The impedance of the load is $Z_L = 40-j50\Omega$ (see figure (a)). When the load is removed and reconnected into the transmission line at a distance d from the original point ($z = -d$). The total impedance measured at this point was pure resistive (see figure (b)). Find out: (1) the distance d ; (2) the total impedance at the point.



$$\text{Solution: (1) normalized load } Z_L = \frac{Z_L}{Z_0} = 0.8 - j1,$$

$$\text{the normalized admittance } y_L = 0.5 + j0.6$$

the total admittance y_{total} @ $z = -d$

$$y_{\text{total}} = y_L + y_{\text{open}} \Big|_{z = -d} \\ = 0.5 + j0.6 + y_{\text{open}} \leftarrow \text{pure resistor}$$

$$\Rightarrow y_{\text{open}} \Big|_{z = -d} = -j0.6, \text{ point A}$$

open circuit point @ B

$$\Rightarrow d = 0.414 \lambda$$

$$\lambda = \frac{V_p}{f} = \frac{2 \times 10^{10} \text{ cm/s}}{10 \times 10^9 \text{ /s}} = 2 \text{ cm}$$

$$\Rightarrow d = 0.414 \lambda = 0.828 \text{ cm}$$

$$(2) \quad y_{\text{total}} = 0.5 \Rightarrow z_{\text{total}} = 2 \Rightarrow$$

$$Z_{\text{total}} = Z_0 \cdot Z_{\text{total}} = 100 \Omega$$

$$d = 0.414 \lambda$$

