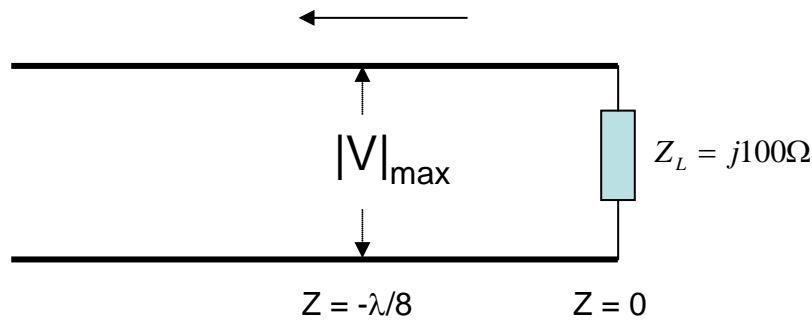


EE Problem 8

A lossless transmission line is terminated with a load  $Z_L$ ,  $Z_L = j100\Omega$  (see figure below). The characteristic impedance  $Z_0$  of the transmission line is unknown. The first voltage maximum  $|V|_{\max}$  is located at  $z = -\lambda/8$  from load.

- (1) Calculate the voltage standing wave ratio (VSWR);
- (2) Find out the characteristic impedance  $Z_0$  of the transmission line



Solution:

- (1) The voltage reflection coefficient  $\Gamma$  is:  $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$ ,

Therefore:

$$|\Gamma| = \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| = \frac{\sqrt{(100)^2 + Z_0^2}}{\sqrt{(100)^2 + Z_0^2}} = 1, \quad Z_0 \text{ is real for a lossless transmission line.}$$

The formula for voltage standing wave ratio (VSWR) is:

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \infty$$

- (2) The first voltage maximum occurs at

$$2\beta(-\lambda/8) + \theta_r = 0, \quad \theta_r \text{ is the angle of the reflection coefficient.}$$

$$\text{so, } 2 \frac{2\pi}{\lambda} \left(-\frac{\lambda}{8}\right) + \theta_r = 0, \quad \Rightarrow \theta_r = 0.5\pi,$$

$$\Gamma = 1 \angle 0.5\pi = 0 + j1,$$

$$Z_0 = Z_L \frac{1 - \Gamma}{1 + \Gamma} = j100 \frac{1 - j1}{1 + j1} = 100\Omega$$

Graphic solution:

