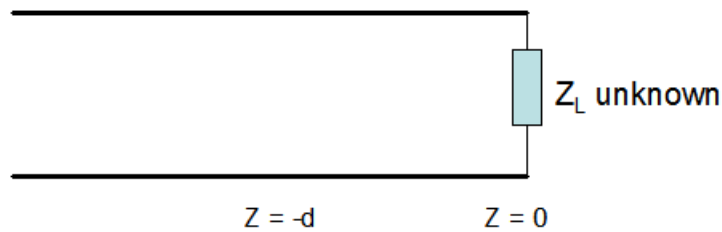


EE Problem 7

A 50Ω lossless transmission line is terminated with an unknown load Z_L (see figure below). The minimum voltages on the transmission line are zeros. The first voltage minimum $|V|_{\min}$ is located at $z = -d$ from load, $d = \lambda/8$.

- (1) Calculate the voltage standing wave ratio (VSWR);
- (2) Find out the load impedance Z_L ;
- (3) Find out the voltage reflection coefficient Γ



Solution:

- (1) The formula for voltage standing wave ratio (VSWR) is:

$$VSWR = \frac{|V|_{\max}}{|V|_{\min}} = \frac{|V|_{\max}}{0} = \infty,$$

$$\text{Since } VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \infty, |\Gamma| = 1.$$

- (2) The first voltage minimum occurs at

$$2\beta(-\lambda/8) + \theta_r = -\pi, \theta_r \text{ is the angle of the reflection coefficient.}$$

$$\text{so, } 2\frac{2\pi}{\lambda}\left(-\frac{\lambda}{8}\right) + \theta_r = 0, \Rightarrow \theta_r = -0.5\pi,$$

$$\Gamma = 1\angle -0.5\pi = 0 - j1.$$

- (3) The normalized load is

$$\frac{Z_L}{Z_0} = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 - j1}{1 + j1} = -j,$$

Therefore, the load impedance $Z_L = -j50\Omega$.

Graphic solution:

