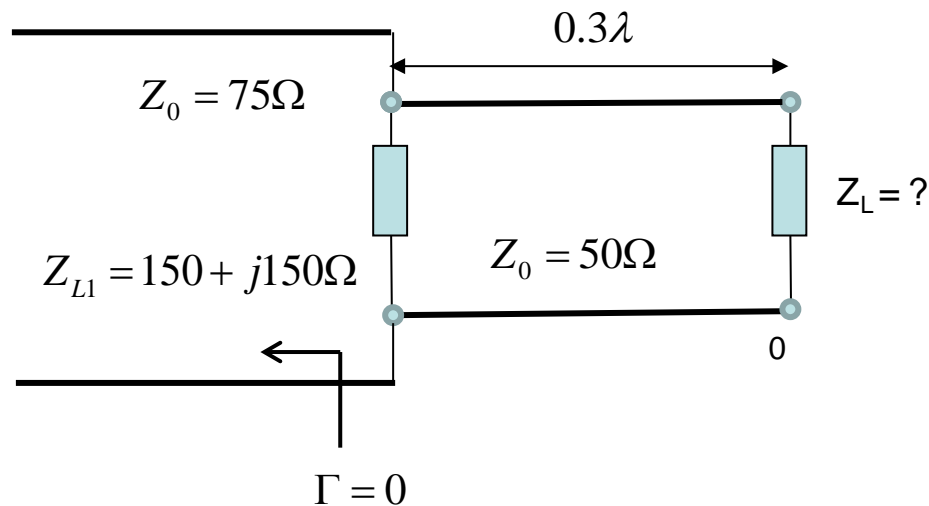


EE Problem 8

Solve the following problem using Smith chart

A $50\text{-}\Omega$ lossless transmission line of length 0.3λ is terminated with an unknown load impedance. The input end of the $50\text{-}\Omega$ line is attached to the load end of a $75\text{-}\Omega$ lossless transmission line with another load $Z_{L1} = 150 + j150\Omega$. Find out the unknown load impedance on the $50\text{-}\Omega$ lossless transmission line that can make the reflection coefficient Γ of the $75\text{-}\Omega$ lossless transmission line is zero, i.e. $\Gamma = 0$.



Solution:

- (1) The load impedance $Z_{L1} = 150 + j150\Omega$ on the $75\text{-}\Omega$ line is located at point Z_{L1} on Smith chart. The normalized admittance of the load is $y_{L1} = 0.23 - j0.24$.
- (2) Since the total normalized admittance $y_{total} = y_{L1} + y_L$ needs to be 1 to make the reflection $\Gamma = 0$, the normalized admittance corresponding to Z_L is therefore $y_L = 0.77 + j0.24$.
- (3) The normalized impedance is $z_L = 1.35 - j0.35$
- (4) The impedance is $Z_L = 101 - j26\Omega$. This corresponds to the input impedance of the $50\text{-}\Omega$ line.
- (5) The normalized input impedance is $z_{in} = 2 - j0.5$, which is point B on Smith chart.
- (6) The normalized load impedance of the $50\text{-}\Omega$ line $z_L = 0.5 - j0.1$, point C on Smith chart
- (7) The load impedance on the $50\text{-}\Omega$ line is therefore $Z_L = 25 - j5\Omega$.

