
Service Learning Project

SLICE

Prototype Fabrication Experience


Interactive Toy Modification

Interactive Toy for Special Need Students




Electronic Circuit

FIGURE 1-7 Cutaway drawing of a flashlight.

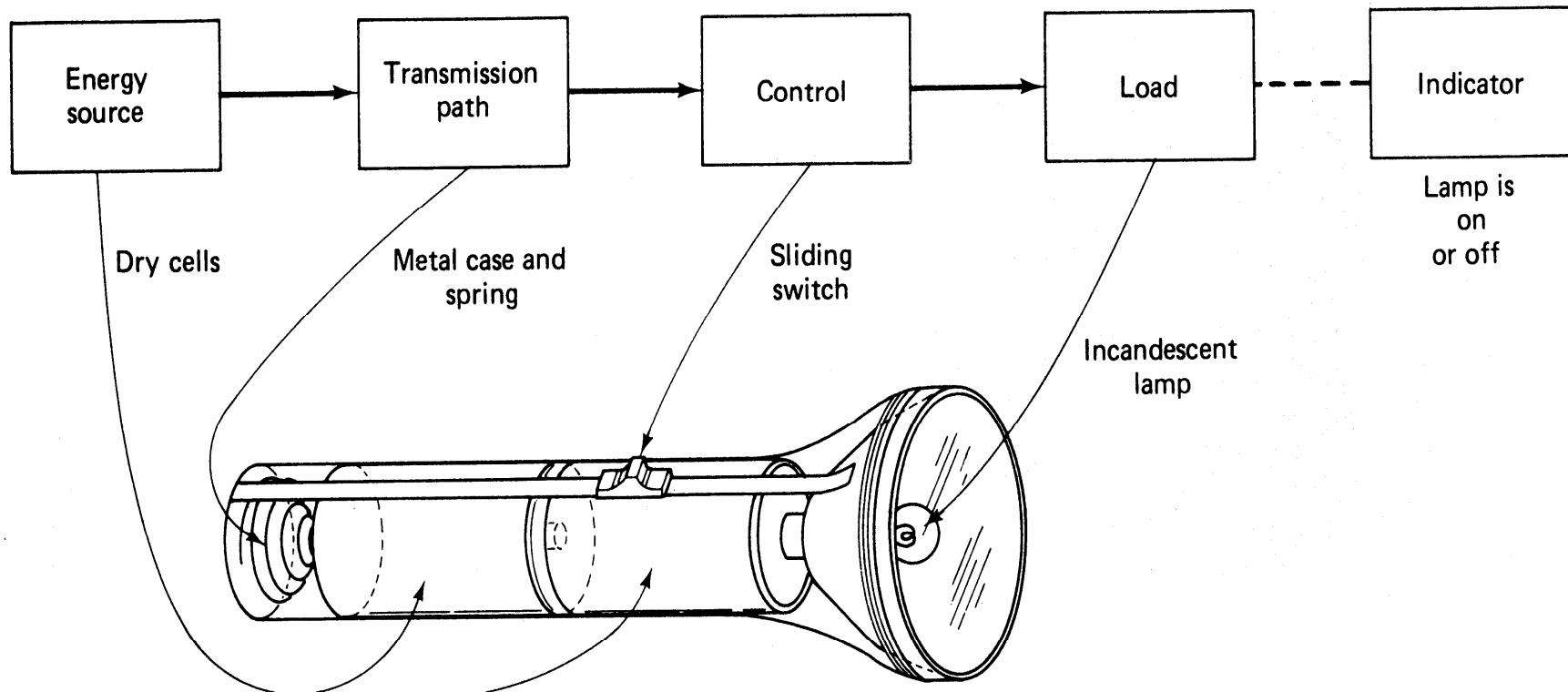

Electronic Circuit

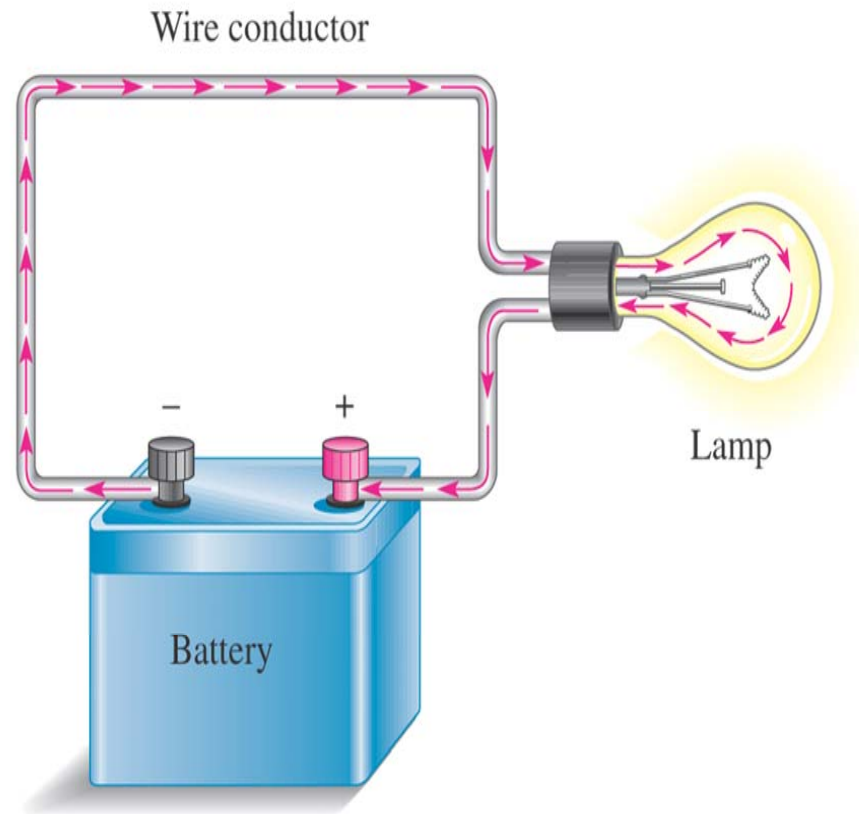- Power source
- Current Path
- Load
- Control
- Indicator



Schematic Diagram



Switches Push Button




**NOPB
switch**

Switches Push Button




**NCPB
switch**

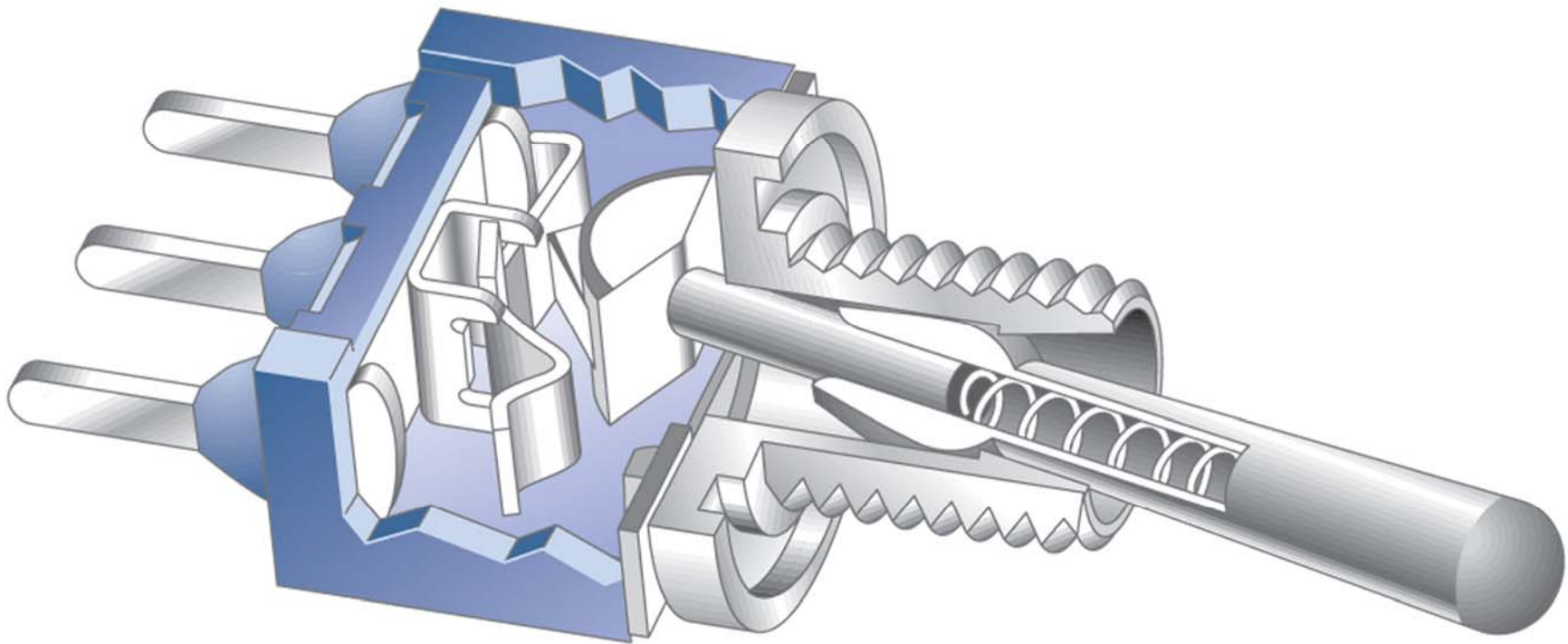Construction view of a typical toggle switch




Switches Toggle

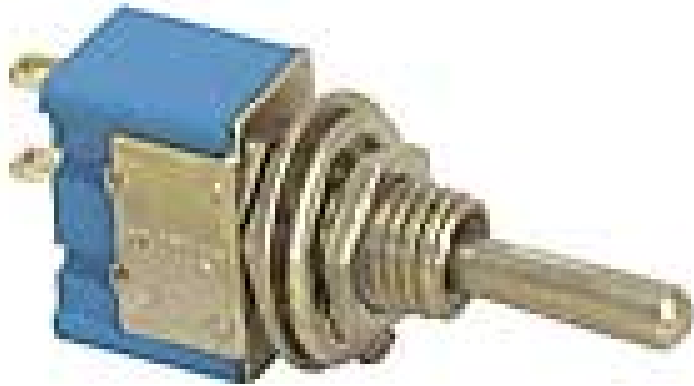


SPST
switch

Open Circuit

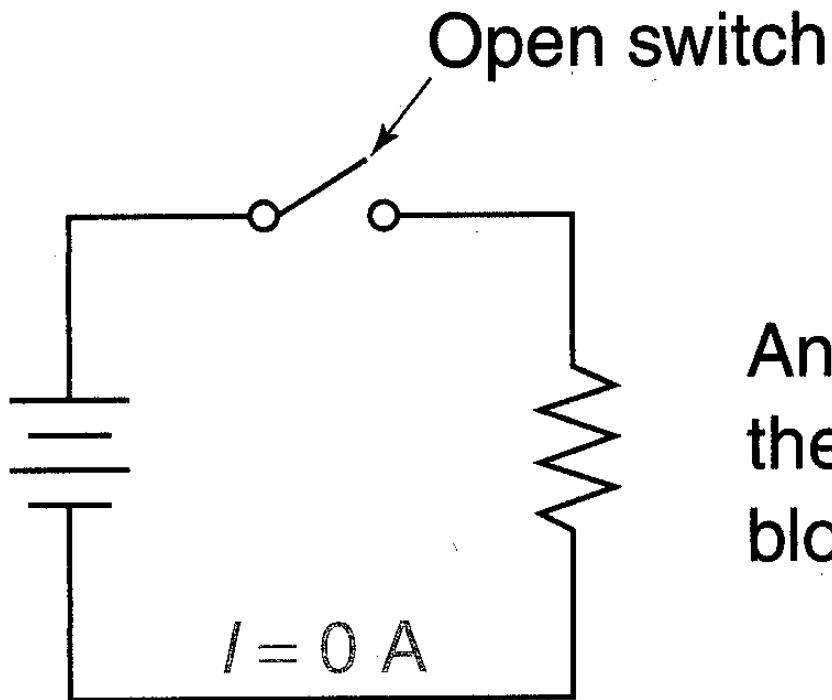


An open switch breaks the conduction path and blocks current.

Open Circuit

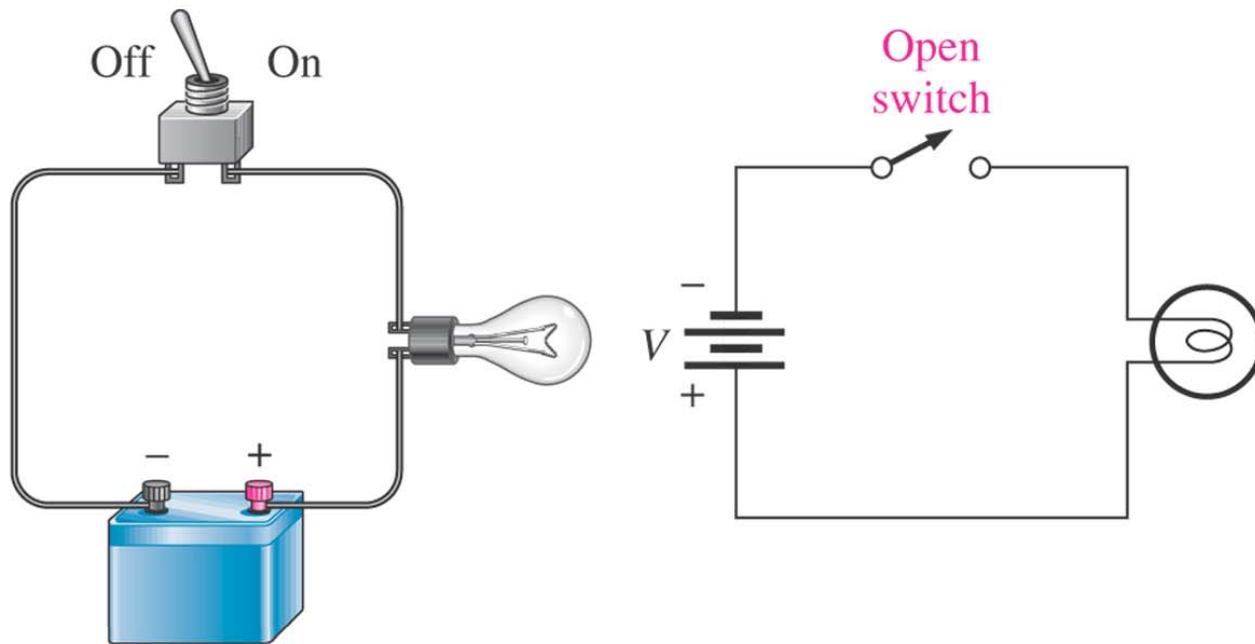


- (b) There is no current in an *open* circuit because the path is broken (switch is OFF or in the *open* position).

Closed Circuit

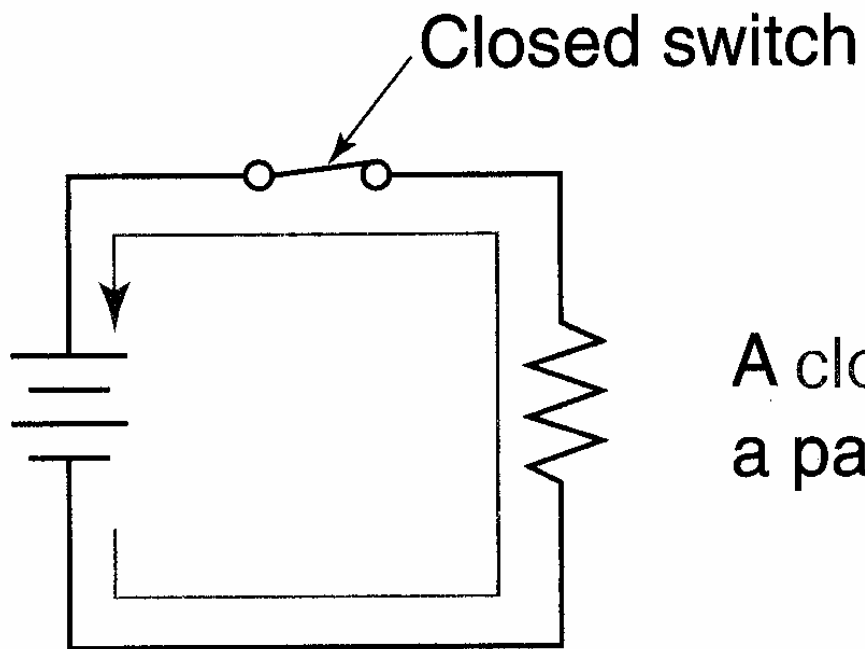


A closed switch provides a path for current.

Closed Circuit

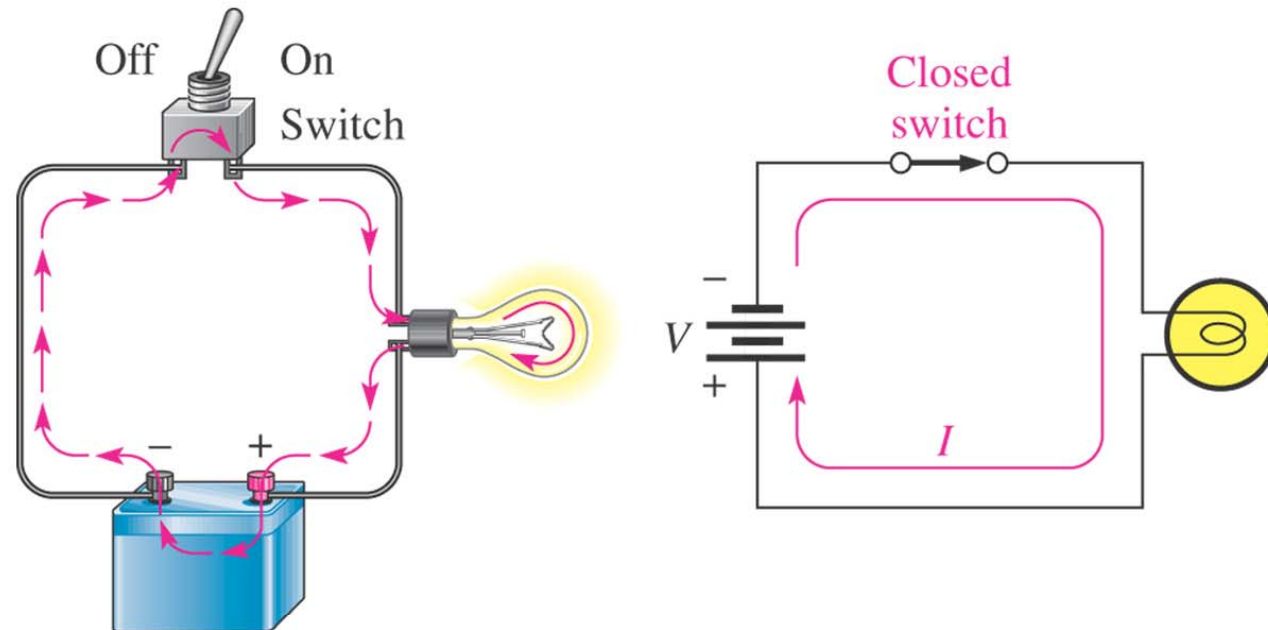

- (a) There is current in a *closed* circuit because there is a complete current path (switch is ON or in the *closed* position). Current is almost always indicated by a red arrow in this text.


A few Schematic Symbols

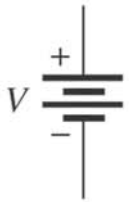


Battery



Resistor

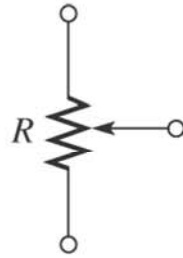

Potentiometer

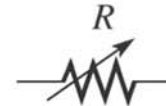


Rheostat



Lamp



Ground

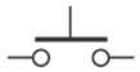


NOPB
switch




NCPB
switch



SPST
switch

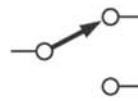


SPDT
switch

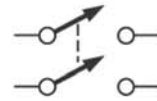

DPST
switch



DPDT
switch

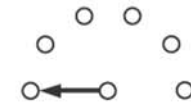


Rotary
switch




Fuse




Circuit breaker

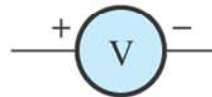

Voltmeter

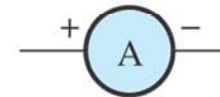

Ammeter

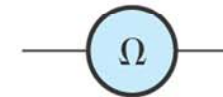

Ohmmeter

Ability Switch for Special Need Students



Switches Push Button



**NOPB
switch**

Phono Plug



Phono Jack



Phono Jack



Typical portable multimeters





(a)




(b)

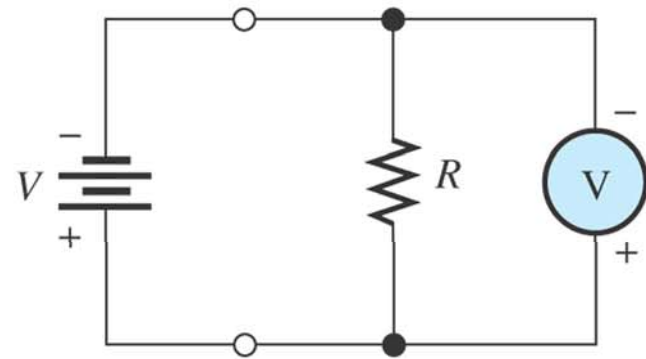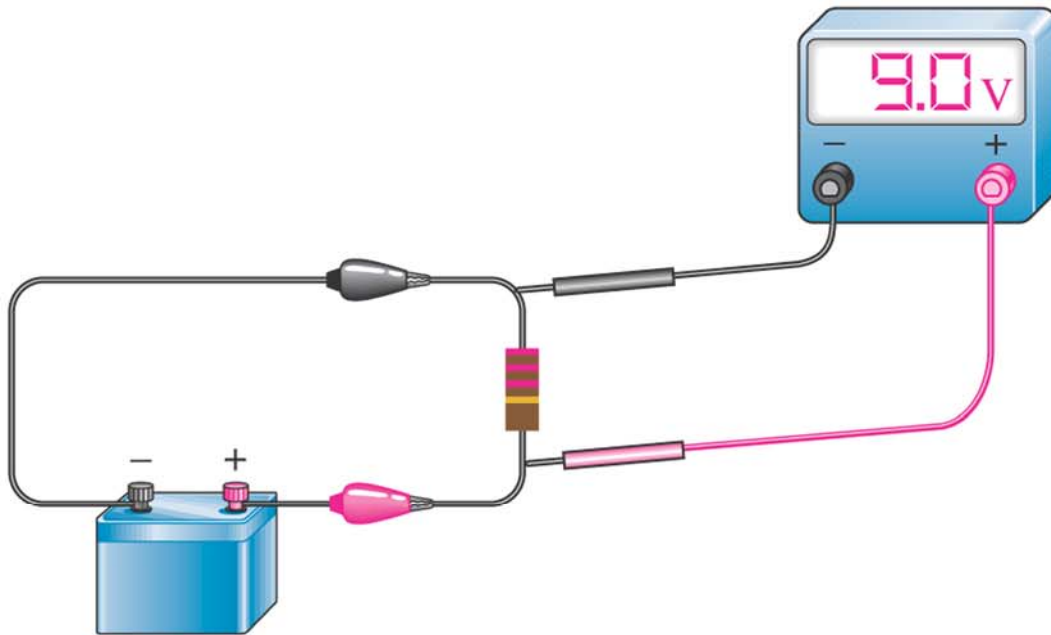
Example of a voltmeter connection to measure voltage in a simple circuit.



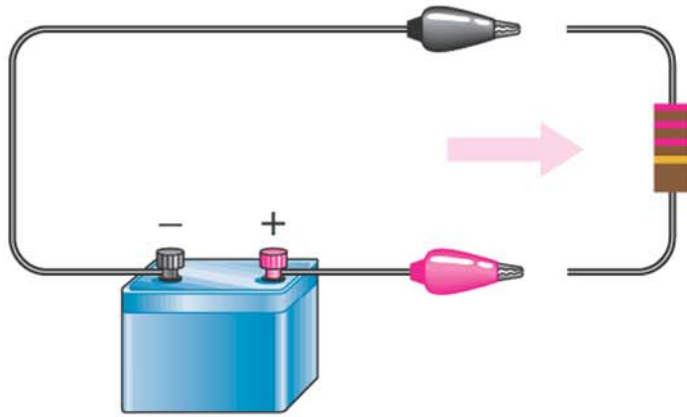Example of using an ohmmeter to measure resistance.



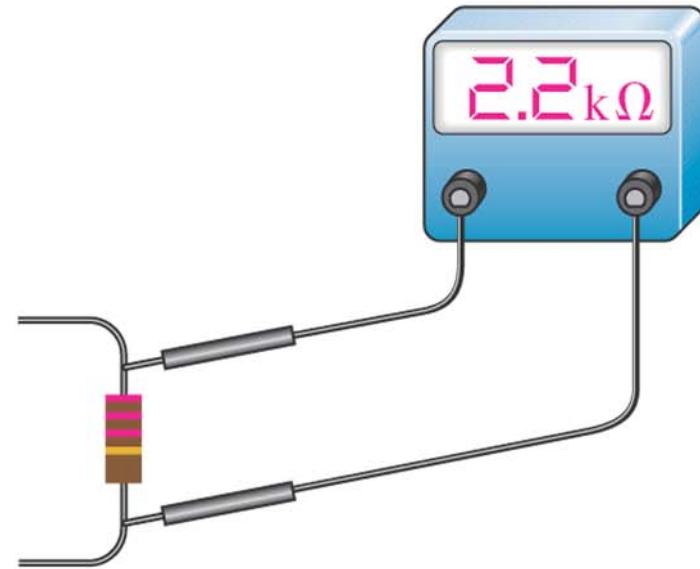(a) Disconnect the resistor from the circuit to avoid damage to the meter and/or incorrect measurement.




 (b) Measure the resistance.
(Polarity is not important.)

Build a **Interactive Toy** for **Special Need Students**



Sesame Street: Double Fun Giggle Ball
- Bert & Ernie





Soldering Iron with Iron Holder




\$ 35.00



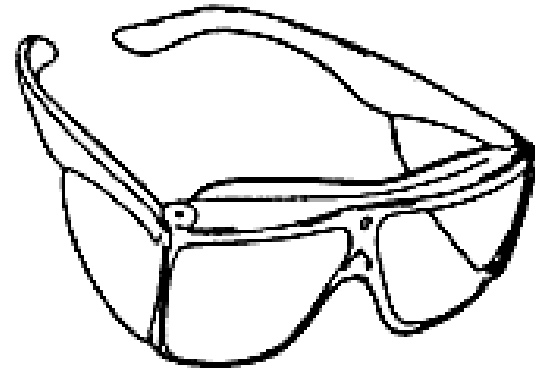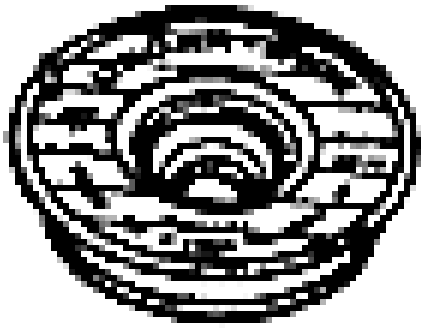Solder, Safety Glasses, Tip Cleaner, and Solder Wick



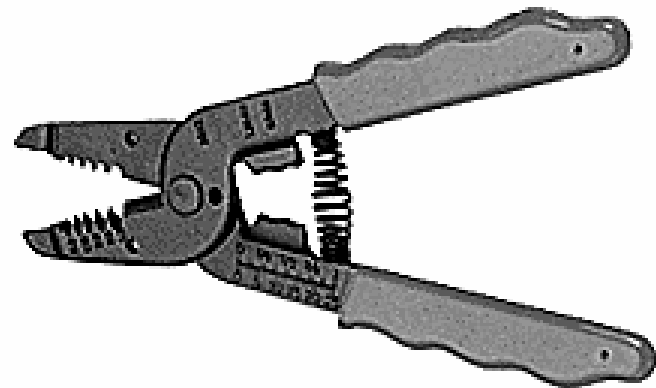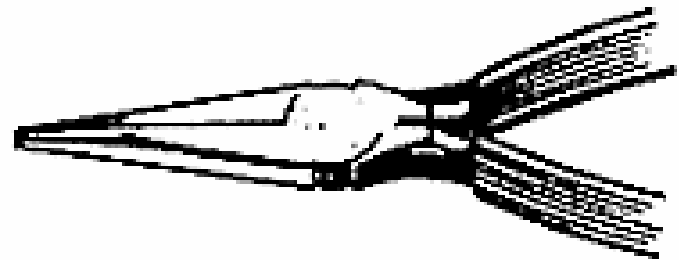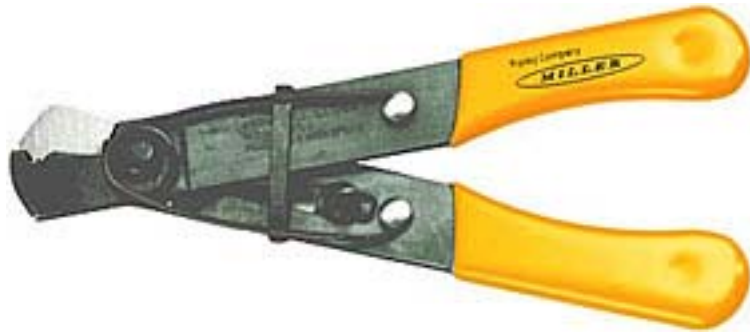
Wire Stripper, Long Noise Pliers, Cutters, and 7 in One Tool



How to Solder



How to Solder



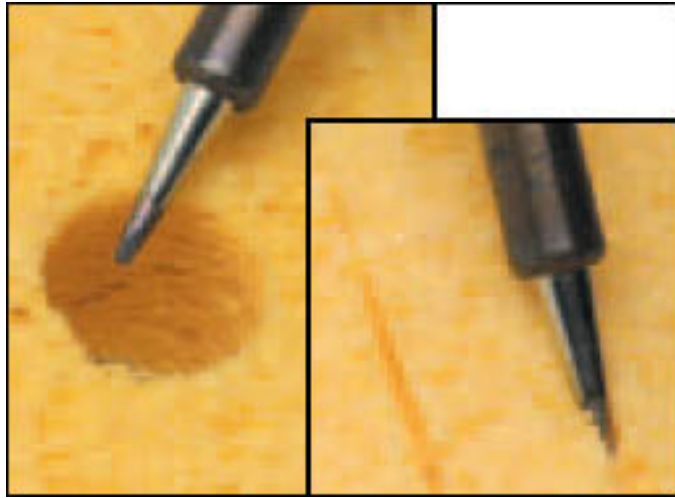


© 2007 CuriousInventor.com




© 2007 CuriousInventor.com

How to Solder

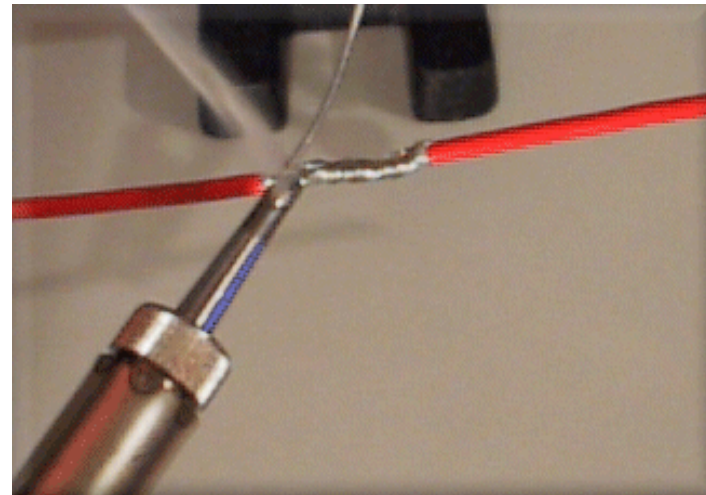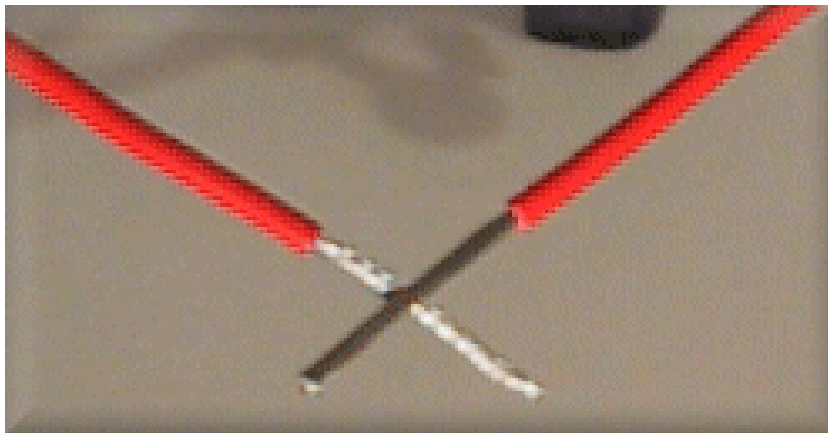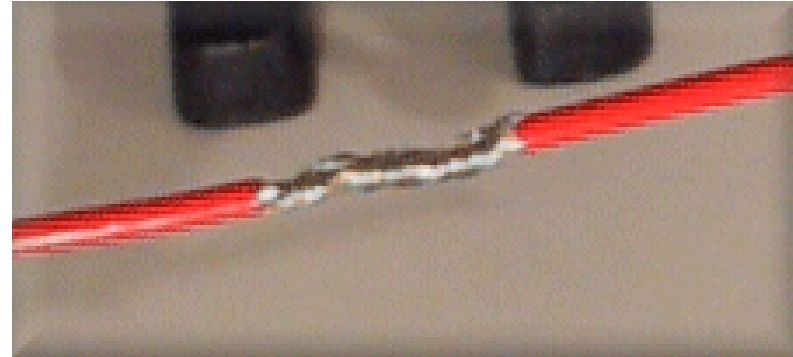

Heat Shrink Vinyl Sleeve




- With heat will shrink 50 %

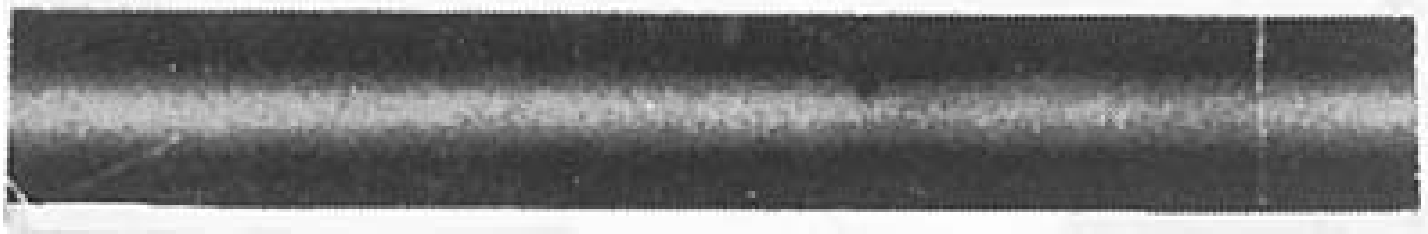

How to Solder



How to Solder

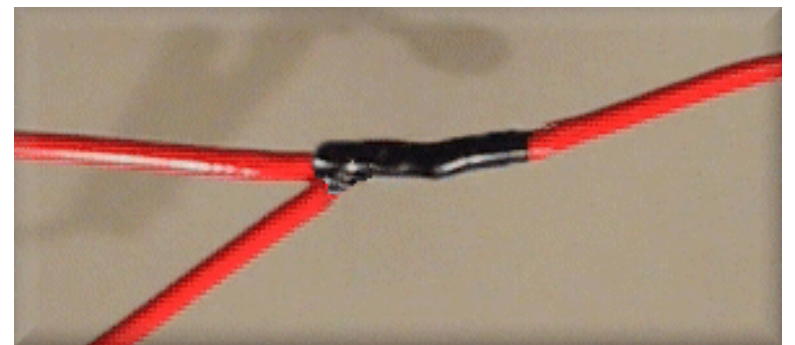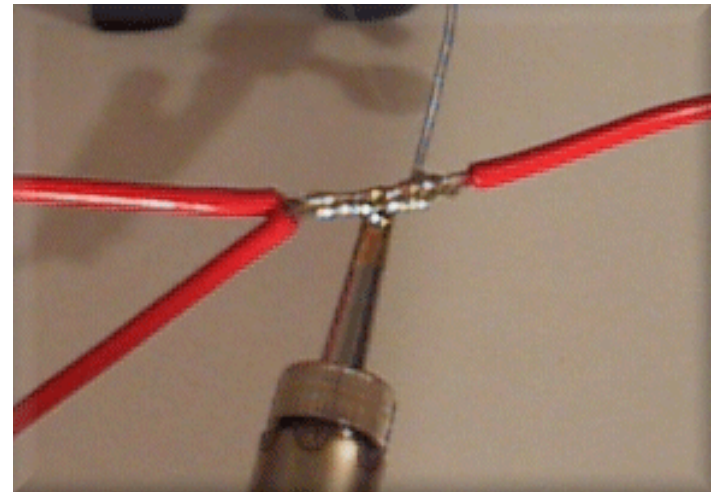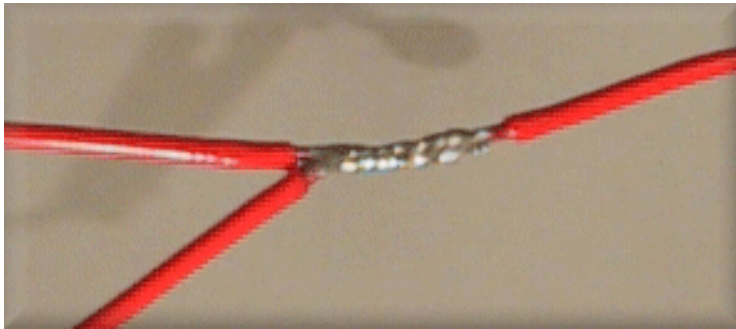

Interactive Toy for Special Need Students

