

# 16.311 Electronics Lab. I

## Experiment 2

### Junction – Diode Characteristics

#### Objective:

1. Become familiar with the basic properties of junction diodes.
2. Measure and plot the forward and reverse-biases I.V. characteristics of a diode

#### Materials Needed:

1. One Signal Diode 1N914
2. One Rectifier Diode 1N4004.
3. One Zenner Diode 1N751 (5.1volts)
4. Resistors; 330 Ohm, 1 meg.Ohm.

Note:DMM - Digital Multimeter.

#### Procedure:

1. Diode measurement with a DMM ,1N914 (signal diode)
  - a. Initially your DMM should be set to it's highest range.
  - b. Measure it's forward resistance  $R_f$  as shown in fig. 1a
  - c. Measure the reverse resistance  $R_r$  as shown in fig. 1b
  - d. Place the DMM on the Diode range, repeat steps b & c
  - e. Record the data in your notebook.
2. Diode measurement with a DMM ,1N4004 (rectifier diode)
  - a. Initially your DMM should be set to it's highest range.
  - b. Measure it's forward resistance  $R_f$  as shown in fig. 1a
  - c. Measure the reverse resistance  $R_r$  as shown in fig. 1b
  - d. Place the DMM on the Diode range, repeat steps b & c
  - e. Record the data in your notebook.
3. Diode measurement with a DMM ,1N751 (zenner diode)
  - a. Initially your DMM should be set to it's highest range.
  - b. Measure it's forward resistance  $R_f$  as shown in fig. 1a
  - c. Measure the reverse resistance  $R_r$  as shown in fig. 1b
  - d. Place the DMM on the Diode range, repeat steps b & c
  - e. Record the data in your notebook.


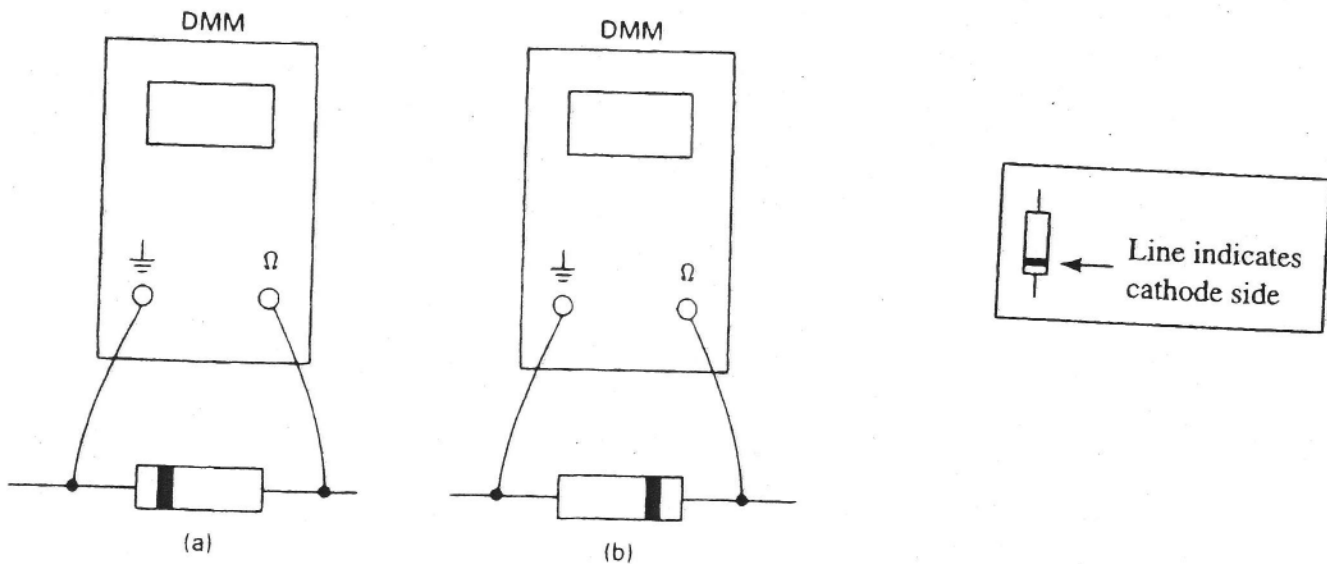


Figure 1

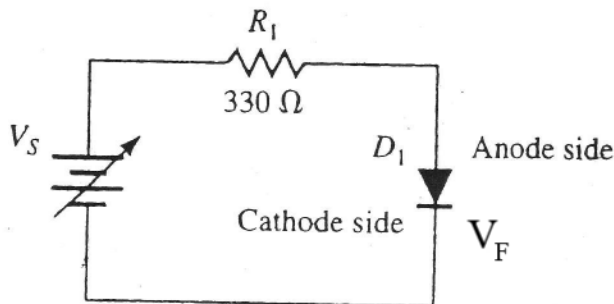4. **Diode Conduction – The Forward Drop, 1N914**
- Construct the forward-bias circuit shown in fig. 2, set P.S. to zero volts
  - Monitor the forward voltage drop  $V_f$  across the diode, slowly increase  $V_s$  (P.S.) to establish 0.45 Volts across the diode.
  - Measure the voltage across the resistor  $R_1$  and record it in data table
  - The diode forward current  $I_f$  can be found by applying Ohm's Law Compute and enter in the table.
  - Repeat steps c and d for each voltage listed in table.



$V_F$ (measured)	$V_{R1}$ (measured)	$I_F$ (computed)
0.45 V		
0.50 V		
0.55 V		
0.60 V		
0.65 V		
0.70 V		
0.75 V		


Figure 2

Data Table

5. **Diode Conduction – The Forward Drop, 1N4004.**
- Construct the forward-bias circuit shown in fig. 2, set P.S. to zero volts
  - Monitor the forward voltage drop  $V_f$  across the diode, slowly increase  $V_s$  (P.S.) to establish 0.45 Volts across the diode.
  - Measure the voltage across the resistor  $R_1$  and record it in data table
  - The diode forward current  $I_f$  can be found by applying Ohm's Law Compute and enter in the table.
  - Repeat steps c and d for each voltage listed in table.
6. **Diode Conduction – The Forward Drop, 1N751**
- Construct the forward-bias circuit shown in fig. 2, set P.S. to zero volts
  - Monitor the forward voltage drop  $V_f$  across the diode, slowly increase  $V_s$  (P.S.) to establish 0.45 Volts across the diode.
  - Measure the voltage across the resistor  $R_1$  and record it in data table
  - The diode forward current  $I_f$  can be found by applying Ohm's Law Compute and enter in the table.
  - Repeat steps c and d for each voltage listed in table.

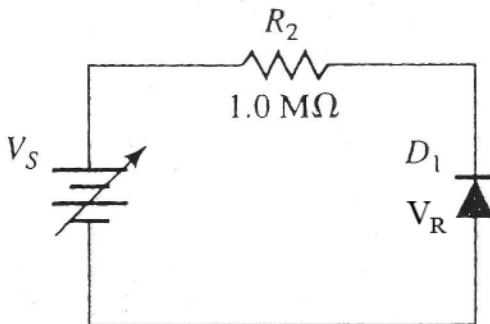**7. Reverse-Bias Current and Break-down Voltage**

- Connect a reverse-bias circuit as shown below
- Set the power supply to voltages as in the table below.
- Measure and record the voltage across  $R_2$  , compute the reverse current.
- Note that the Fluke meter has input resistance of 10 meg. Ohms  
( adjust your calculations to allow for meter loading )
- Repeat for each diode and record the results.



$V_S$	$V_R$ (measured)	$V_{R2}$ (measured)	$I_R$ (computed)
5V	<input type="text"/>	<input type="text"/>	<input type="text"/>
10V	<input type="text"/>	<input type="text"/>	<input type="text"/>
15V	<input type="text"/>	<input type="text"/>	<input type="text"/>
20V	<input type="text"/>	<input type="text"/>	<input type="text"/>