# $16.312 \hspace{0.1 cm} (\text{Formal Report})$

# LM-555

# Project

 Design a 50% Duty Cycle Oscillator at a frequency of 1 KHz.

#### Solderless Prototyping Board top half for LM555 **devices** bottom half for **trigger source** jacks for **power connections**



## LM555 Timer

The LM555 is a highly stable device for generating accurate time delays or oscillation. Additional terminals are provided for triggering or resetting if desired.

#### LM 555 Timer

Dual-In-Line, Small Outline and Molded Mini Small Outline Packages



#### Astable operation

- Pins 2 & 6 connected
- Trigger itself and free run as a multivibrator



#### Astable operation



#### **Astable** Operation



Charge time (output high): t1 = 0.693 (Ra + Rb) CDischarge time (output low): t2 = 0.693 (Rb) CTotal period: T = t1 + t2 = 0.693 (Ra + 2Rb) CDuty cycle: D = W/T = t1/T = (Ra+Rb)/(Ra + 2Rb)

# Grading

- Preparation:
  - circuit design schematic diagram: 30%
- Final design schematics: 10%
- Circuit description (how it works): 15%
- Neat circuit wiring on board: 10%
- Scope pictures: 10%
- Bench quiz: 15%
- Clean up the space:

10%

# Being late?

- Please be on time to your lab session.
  This will be good for you to finish your experiment on time.
- As a penalty, you will lose 5% of that experiment if you are >15 minutes late; lose 10% if you are 30 minutes late.

#### Leave early?

- Bad attitude:
  - Leave early without finishing the experiment;
  - and do not report to the TA with a reasonable excuse;
  - As a penalty, you will lose 5% of that experiment if you leave >15 minutes earlier; lose 10% if you leave >30 minutes earlier.
- The TA will need to allocate additional time to help you with the make-up session.

#### Penalty for Plagiarism

- Don't copy others in reports. Plagiarism
- = Failure in reports
- = F in this class!