

EMag I. Prof. Xingwei Wang

Homework #2_solution

Due day: Sept. 24(Monday) before class.

Problem 2.1 A transmission line of length l connects a load to a sinusoidal voltage source with an oscillation frequency f . Assuming the velocity of wave propagation on the line is c , for which of the following situations is it reasonable to ignore the presence of the transmission line in the solution of the circuit:

- (a) $l = 20$ cm, $f = 20$ kHz,
- (b) $l = 50$ km, $f = 60$ Hz,
- (c) $l = 20$ cm, $f = 600$ MHz,
- (d) $l = 1$ mm, $f = 100$ GHz.

Solution: A transmission line is negligible when $l/\lambda \leq 0.01$.

- (a) $\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{(20 \times 10^{-2} \text{ m}) \times (20 \times 10^3 \text{ Hz})}{3 \times 10^8 \text{ m/s}} = 1.33 \times 10^{-5}$ (negligible).
- (b) $\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{(50 \times 10^3 \text{ m}) \times (60 \times 10^0 \text{ Hz})}{3 \times 10^8 \text{ m/s}} = 0.01$ (borderline).
- (c) $\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{(20 \times 10^{-2} \text{ m}) \times (600 \times 10^6 \text{ Hz})}{3 \times 10^8 \text{ m/s}} = 0.40$ (nonnegligible).
- (d) $\frac{l}{\lambda} = \frac{lf}{u_p} = \frac{(1 \times 10^{-3} \text{ m}) \times (100 \times 10^9 \text{ Hz})}{3 \times 10^8 \text{ m/s}} = 0.33$ (nonnegligible).

Problem 2.2 A two-wire copper transmission line is embedded in a dielectric material with $\epsilon_r = 2.6$ and $\sigma = 2 \times 10^{-6}$ S/m. Its wires are separated by 3 cm and their radii are 1 mm each.

(a) Calculate the line parameters R' , L' , G' , and C' at 2 GHz.

Solution:

(a) Given:

$$\begin{aligned} f &= 2 \times 10^9 \text{ Hz,} \\ d &= 2 \times 10^{-3} \text{ m,} \\ D &= 3 \times 10^{-2} \text{ m,} \\ \sigma_c &= 5.8 \times 10^7 \text{ S/m (copper),} \\ \epsilon_r &= 2.6, \\ \sigma &= 2 \times 10^{-6} \text{ S/m,} \\ \mu &= \mu_c = \mu_0. \end{aligned}$$

Problem 2.4 A 1-GHz parallel-plate transmission line consists of 1.2-cm-wide copper strips separated by a 0.15-cm-thick layer of polystyrene. Appendix B gives $\mu_c = \mu_0 = 4\pi \times 10^{-7}$ (H/m) and $\sigma_c = 5.8 \times 10^7$ (S/m) for copper, and $\epsilon_r = 2.6$ for polystyrene. Use Table 2-1 to determine the line parameters of the transmission line. Assume $\mu = \mu_0$ and $\sigma \simeq 0$ for polystyrene.

Solution:

$$\begin{aligned} R' &= \frac{2R_s}{w} = \frac{2}{w} \sqrt{\frac{\pi f \mu_c}{\sigma_c}} = \frac{2}{1.2 \times 10^{-2}} \left(\frac{\pi \times 10^9 \times 4\pi \times 10^{-7}}{5.8 \times 10^7} \right)^{1/2} = 1.38 \text{ } (\Omega/\text{m}), \\ L' &= \frac{\mu d}{w} = \frac{4\pi \times 10^{-7} \times 1.5 \times 10^{-3}}{1.2 \times 10^{-2}} = 1.57 \times 10^{-7} \text{ (H/m),} \\ G' &= 0 \quad \text{because } \sigma = 0, \\ C' &= \frac{\epsilon w}{d} = \epsilon_0 \epsilon_r \frac{w}{d} = \frac{10^{-9}}{36\pi} \times 2.6 \times \frac{1.2 \times 10^{-2}}{1.5 \times 10^{-3}} = 1.84 \times 10^{-10} \text{ (F/m).} \end{aligned}$$