

Due day: Oct. 10(Wednesday) before class.

Problem 2.47 Use the Smith chart to find the reflection coefficient corresponding to a load impedance of

- (a) $Z_L = 3Z_0$
- (b) $Z_L = (2 - j2)Z_0$
- (c) $Z_L = -j2Z_0$
- (d) $Z_L = 0$ (short circuit)

Solution: Refer to Fig. P2.47.

- (a) Point A is $z_L = 3 + j0$. $\Gamma = 0.5e^{0^\circ}$
- (b) Point B is $z_L = 2 - j2$. $\Gamma = 0.62e^{-29.7^\circ}$
- (c) Point C is $z_L = 0 - j2$. $\Gamma = 1.0e^{-53.1^\circ}$
- (d) Point D is $z_L = 0 + j0$. $\Gamma = 1.0e^{180.0^\circ}$

Problem 2.49 Use the Smith chart to find the normalized load impedance corresponding to a reflection coefficient of

- (a) $\Gamma = 0.5$
- (b) $\Gamma = 0.5 \angle 60^\circ$
- (c) $\Gamma = -1$
- (d) $\Gamma = 0.3 \angle -30^\circ$
- (e) $\Gamma = 0$
- (f) $\Gamma = j$

- (a) Point A' is $\Gamma = 0.5$ at $z_L = 3 + j0$.
- (b) Point B' is $\Gamma = 0.5e^{j60^\circ}$ at $z_L = 1 + j1.15$.
- (c) Point C' is $\Gamma = -1$ at $z_L = 0 + j0$.
- (d) Point D' is $\Gamma = 0.3e^{-j30^\circ}$ at $z_L = 1.60 - j0.53$.
- (e) Point E' is $\Gamma = 0$ at $z_L = 1 + j0$.
- (f) Point F' is $\Gamma = j$ at $z_L = 0 + j1$.

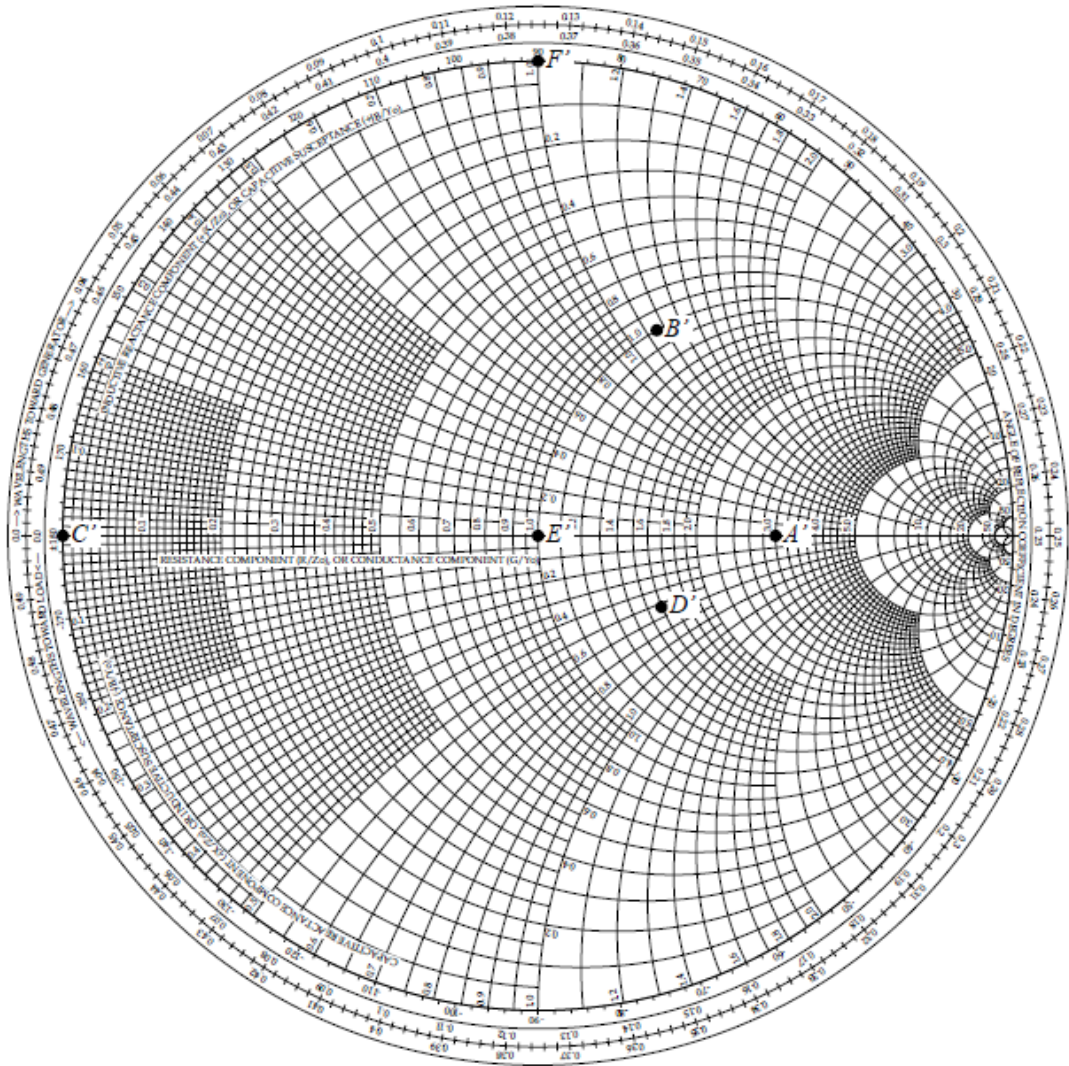


Figure P2.49: Solution of Problem 2.49.

Solution: Refer to Fig. P2.49.