

EMag I. Prof. Xingwei Wang

Homework #5

Due day: Oct. 15(Mon) before class.

Problem 2.53 A lossless $50\text{-}\Omega$ transmission line is terminated in a load with $Z_L = (50 + j25)\ \Omega$. Use the Smith chart to find the following:

- (a) The reflection coefficient Γ .
- (b) The standing-wave ratio.
- (c) The input impedance at 0.35λ from the load.
- (d) The input admittance at 0.35λ from the load.
- (e) The shortest line length for which the input impedance is purely resistive.
- (f) The position of the first voltage maximum from the load.

Problem 2.66 A $200\text{-}\Omega$ transmission line is to be matched to a computer terminal with $Z_L = (50 - j25)\ \Omega$ by inserting an appropriate reactance in parallel with the line. If $f = 800\text{ MHz}$ and $\epsilon_r = 4$, determine the location nearest to the load at which inserting:

- (a) A capacitor can achieve the required matching, and the value of the capacitor.
- (b) An inductor can achieve the required matching, and the value of the inductor.

Problem 2.68 A $50\text{-}\Omega$ lossless line is to be matched to an antenna with $Z_L = (75 - j20)\ \Omega$ using a shorted stub. Use the Smith chart to determine the stub length and distance between the antenna and stub.