



Chapter 9


Memory Devices, Circuits, and Subsystem Design

Introduction

- 9.1 Program and Data Storage Memory—✓
- 9.2 Read-Only Memory—✓
- 9.3 Random Access Read/Write Memories—✓
- 9.4 Parity, Parity Bit, and Parity-Checker/Generator Circuit
- 9.5 FLASH Memory
- 9.6 Wait-State Circuitry—✓
- 9.7 8088/8086 Microcomputer System Memory Interface Circuitry—✓

 9.1 Program and Data Storage Memory— The Memory Unit

- Memory—provides the ability to store and retrieve digital information
 - Instructions of a program
 - Data to be processed
 - Results produced by processing
- Organization of the Microcomputer memory unit




- **Secondary storage—stores information that is not currently in use**
 - Slow-speed
 - Very large storage capacity
 - Implemented with magnetic/optical storage devices—in PC
 - Hard disk drive
 - Floppy disk drive
 - Zip drive
- **Primary storage—stores programs and data that are currently active**
 - High-speed
 - Smaller storage capacity
 - Implemented with semiconductor memory
- **Partitioning of Primary Storage**
 - **Program storage memory—holds instructions of the program and constant information such as look-up tables**
 - EPROM (BIOS in PC)
 - FLASH memory
 - DRAM (volatile code storage in a PC)
 - **Data storage memory—holds data that frequently changes such as the information to be processed by a program**
 - SRAM
 - DRAM (PC)

9.2 Read-Only Memory– Types

- Read-only memory (ROM)
 - Used for storage of machine code of program
 - Stored information can only be read by the MPU
 - Information is nonvolatile—not lost when power turned off
 - Types:
 - ROM—mask-programmable read only memory
 - Programmed as part of manufacturing process
 - Lowest cost
 - High volume applications
 - PROM—one-time programmable read-only memory
 - Permanently programmed with a programming instrument
 - EPROM—erasable programmable read-only memory
 - Programmed like a PROM
 - Erasable by Ultraviolet light
 - Electrically alterable ROM-like devices
 - FLASH memory
 - EEROM (E²ROM)

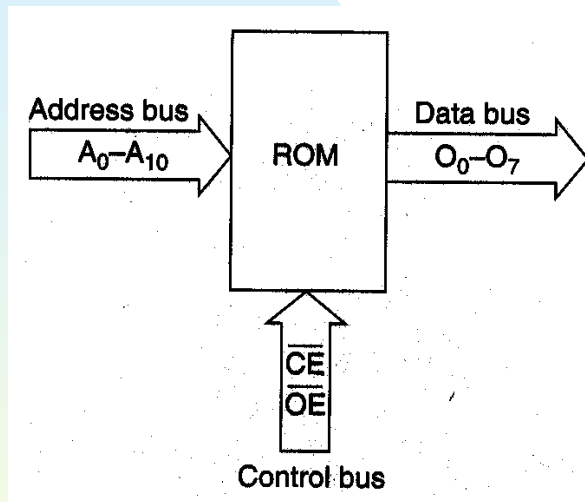9.2 Read-Only Memory– Block Diagram

- Block diagram of the ROM, PROM, and EPROM are essentially the same
- Signal interfaces
 - Address bus (A10-A0)—MPU inputs address information that selects the storage location to be accessed
 - Data Bus (D7-D0)—information from the accessed storage location output to be read by MPU
 - Control bus—enables device and/or enables output from device
 - CE* = chip enable—active 0; 1 low-power stand by mode
 - OE* = output enable—active 0; 1 high-Z state
- Byte capacity– number of bytes a device can store
 - Calculated from number of address bits
 - EX: Address = 11-bit address
Storage capacity = $2^{11} = 2048$ bytes
- Organization—how the size of a ROM is described
 - Formed from capacity and data bus width
 - EX: 2048 X 8 or just 2K X 8
- Storage density—number of bits of storage in a ROM
 - Calculated from byte capacity and data width
 - EX: Storage density = $2048 \times 8 = 16384$ bits (16K bits)



The 8088 and 8086 ROMs provide 16K bits of storage

9.2 Read-Only Memory– Organization and Capacity

- Example:

A ROM device has 15 address lines and 8 data lines. What are the address range, byte capacity, organization, and storage density?

- Solution:

- Address range

$$\begin{aligned} A_{14}-A_0 &= 000\ 0000\ 0000\ 0000_2 \rightarrow 111\ 1111\ 1111\ 1111_2 \\ &= 0000H \rightarrow 7FFFH \end{aligned}$$

- Byte capacity

$$2^{15} = 32,768 \text{ bytes} = 32K \text{ bytes}$$

- Organization

$$32768 \times 8 \text{ bit}$$


- Storage density

$$32768 \times 8 = 262144 \text{ bits} = 256K \text{ bits}$$

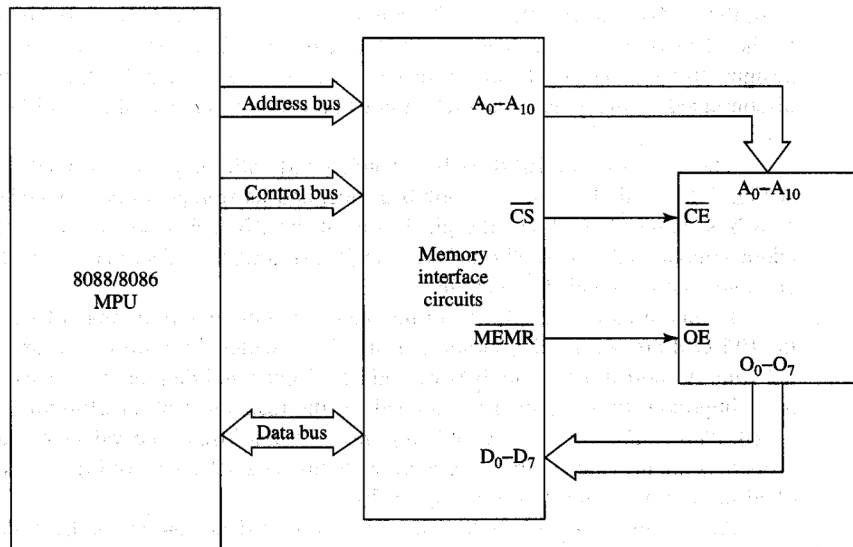9.2 Read-Only Memory– Operation

■ Read operation

- MPU outputs address and control information on its bus.
- Interface circuit applies Address A10-A0 to the address inputs of the ROM to select a specific byte wide storage location
- Interface circuits decode additional address bits to produce a chip select output
- Logic 0 at CS* applied to the CE* input of the ROM to enable it for operation
- Memory interface circuitry produces appropriately timed MEMR* output
- MEMR* applied to OE* input of the ROM to enable the information at the addressed storage location onto the output bus D7-D0
- Memory interface supplies the byte of data from the ROM to the MPUs data bus
- MPU reads the byte of data from the ROM from its data bus




9.2 Read-Only Memory– **Standard EPROM ICs**

- EPROM part numbers formed by adding the prefix “27” to the device total Kbytes of storage capacity
 - Examples:
 - 16K bit EPROM → 2716
 - 32K bit EPROM → 2732
 - 1M bit EPROM → 27C010
 - Most EPROM available in byte wide organization
 - Examples:
 - 2764 → 8K X 8
 - 27C020 → 256K X8
 - NMOS versus CMOS process
 - Manufacturing processes used to make EPROMs
 - NMOS=N-channel metal-oxide semiconductor
 - CMOS= complementary symmetry metal-oxide semiconductor
 - “CMOS” designated by “C” in part number
 - NMOS—older devices such as 2716 and 2732
 - CMOS—all newer devices 27C64 and up

EPROM	Density (bits)	Capacity (bytes)
2716	16K	2K × 8
2732	32K	4K × 8
27C64	64K	8K × 8
27C128	128K	16K × 8
27C256	256K	32K × 8
27C512	512K	64K × 8
27C010	1M	128K × 8
27C020	2M	256K × 8
27C040	4M	512K × 8

9.2 Read-Only Memory– Pin Layouts

27C512	27C128	27C64	2732A	2716	Pin
A ₁₅	V _{PP}	V _{PP}			1
A ₁₂	A ₁₂	A ₁₂			2
A ₇	A ₇	A ₇	A ₇	A ₇	3
A ₆	A ₆	A ₆	A ₆	A ₆	4
A ₅	A ₅	A ₅	A ₅	A ₅	5
A ₄	A ₄	A ₄	A ₄	A ₄	6
A ₃	A ₃	A ₃	A ₃	A ₃	7
A ₂	A ₂	A ₂	A ₂	A ₂	8
A ₁	A ₁	A ₁	A ₁	A ₁	9
A ₀	A ₀	A ₀	A ₀	A ₀	10
O ₀	O ₀	O ₀	O ₀	O ₀	11
O ₁	O ₁	O ₁	O ₁	O ₁	12
O ₂	O ₂	O ₂	O ₂	O ₂	13
Gnd	Gnd	Gnd	Gnd	Gnd	14

 


Pin	2716	2732A	27C64	27C128	27C512
28			V _{CC}	V _{CC}	V _{CC}
27			$\overline{\text{PGM}}$	$\overline{\text{PGM}}$	A ₁₄
26	V _{CC}	V _{CC}	N.C.	A ₁₃	A ₁₃
25	A ₈	A ₈	A ₈	A ₈	A ₈
24	A ₉	A ₉	A ₉	A ₉	A ₉
23	V _{PP}	A ₁₁	A ₁₁	A ₁₁	A ₁₁
22	$\overline{\text{OE}}$	$\overline{\text{OE}}/\text{V}_{\text{PP}}$	$\overline{\text{OE}}$	$\overline{\text{OE}}$	$\overline{\text{OE}}/\text{V}_{\text{PP}}$
21	A ₁₀	A ₁₀	A ₁₀	A ₁₀	A ₁₀
20	$\overline{\text{CE}}$	$\overline{\text{CE}}$	$\overline{\text{CE}}$	$\overline{\text{CE}}$	$\overline{\text{CE}}$
19	O ₇	O ₇	O ₇	O ₇	O ₇
18	O ₆	O ₆	O ₆	O ₆	O ₆
17	O ₅	O ₅	O ₅	O ₅	O ₅
16	O ₄	O ₄	O ₄	O ₄	O ₄
15	O ₃	O ₃	O ₃	O ₃	O ₃

- EPROM pin layouts are designed for compatibility
 - Permit easy upgrade from lower to higher density
 - Publish pin layouts of future densities
 - Allows design of circuit boards to support drop in upgrade to higher densities
- Most pins are independent and serve a common function for all densities
 - Examples:
 - pin 10– A0
 - pin 11--O0
 - pin 14– Gnd
- Some have one multi-function pin
 - OE*/Vpp
 - Vpp mode during programming only

9.2 Read-Only Memory– EPROM Switching Waveforms

■ Timing of the read operation

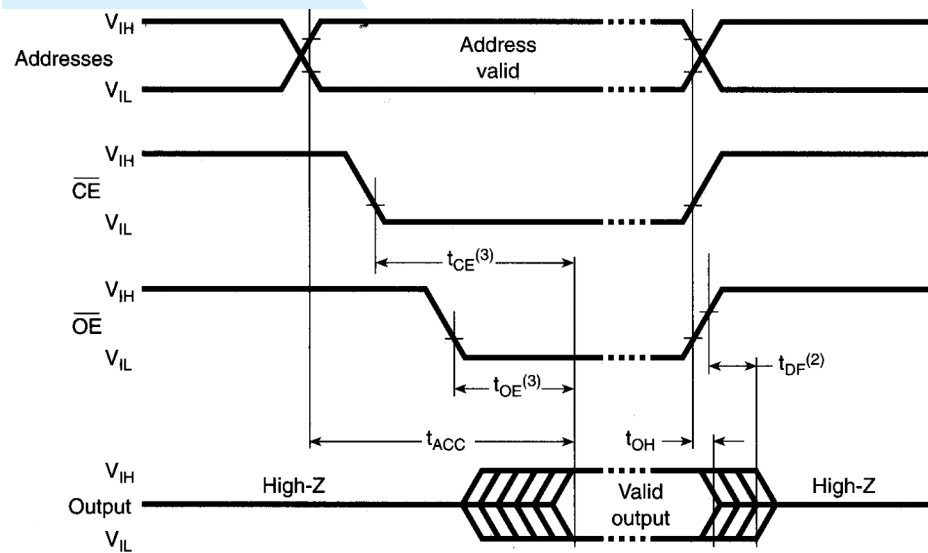

- Output data is not immediately available at the outputs
 - Delays exist between the application of the address, CE^* and OE^* signals and the occurrence of a valid output
 - t_{acc} = access time—address to valid output delay time
 - t_{CE} = chip-enable time—chip enable to valid output delay
 - t_{OE} = output-enable time—output enable to valid data delay
- To assure that the MPU reads valid data, these inputs must be applied at the appropriate times
 - Responsibility of the memory interface circuitry
- Another delay occurs at the removal of OE^* before the outputs lines are returned to the high-Z state
 - t_{DF} = chip-deselect time—time for the outputs to recover

9.2 Read-Only Memory– 27C256 Read Cycle Timing Characteristics

- EPROM part numbers include access time and power supply tolerance information

Versions		V _{CC} ± 5%		27C256-120V05		27C256-135V05		27C256-150V05		27C256-1 P27C256-1 N27C256-1		27C256-2 P27C256-2 N27C256-2		27C256 P27C256 N27C256		Unit
		V _{CC} ± 10%		27C256-135V10		27C256-150V10				27C256-20 P27C256-20 N27C256-20		27C256-25 P27C256-25 N27C256-25				
Symbol	Parameter	Min	Max	Min	Max	Min	Max	Min	Max	Min	Max	Min	Max	Min	Max	
t _{ACC}	Address to output delay		120		135		150		170		200		250		250	ns
t _{CE}	CE to output delay		120		135		150		170		200		250		250	ns
t _{OE}	OE to output delay		60		65		70		75		75		100		100	ns
t _{DF} ⁽²⁾	OE high to output high-Z		30		35		45		55		55		60		60	ns
t _{OH} ⁽²⁾	Output hold from addresses, CE or OE change—whichever is first	0		0		0		0		0		0		0		ns

Notes:

- A.C. characteristics tested at V_{IH} = 2.4 V and V_{IL} = 0.45 V. Timing measurements made at V_{OL} = 0.8 V and V_{OH} = 2.0 V.
- Guaranteed and sampled.
- Package Prefixes: No Prefix = CERDIP; N = PLCC; P = Plastic DIP.

- **27C256120V05**
t_{ACC} = 120ns
V_{CC} = ± 5%
- **27C256-1**
t_{ACC} = 170ns
V_{CC} = ± 10% (standard—unmarked)
- **Maximum access times of the 27C256-120V05**
 - t_{acc}=120ns
 - t_{CE}= 120ns
 - t_{OE}= 60ns
 - t_{DF}= 30ns
 - Note that t_{acc} and t_{CE} should be applied at the same time
 - More delays in t_{CE} path!

9.2 Read-Only Memory– DC Electrical Characteristics


Symbol	Parameter	Notes	Min	Typ ⁽³⁾	Max	Unit	Test Conditions
I_{LI}	Input load current			0.01	1.0	μA	$V_{IN} = 0\text{V to } V_{CC}$
I_{LO}	Output leakage current				± 10	μA	$V_{OUT} = 0\text{V to } V_{CC}$
I_{PP1}	V_{PP} read current	5			200	μA	$V_{PP} = V_{CC}$
I_{SB1}	V_{CC} current standby	TTL			1.0	mA	$\overline{CE} = V_{IH}$
I_{SB2}		CMOS			100	μA	$\overline{CE} = V_{CC}$
I_{CC1}	V_{CC} current active	5, 8			30	mA	$\overline{CE} = V_{IL}$ $f = 5\text{ MHz}$
V_{IL}	Input low voltage ($\pm 10\%$ supply) (TTL)		-0.5		0.8	V	
	Input low voltage (CMOS)		-0.2		0.8		
V_{IH}	Input high voltage ($\pm 10\%$ supply) (TTL)		2.0		$V_{CC} + 0.5$	V	
	Input high voltage (CMOS)		$0.7 V_{CC}$		$V_{CC} + 0.2$		
V_{OL}	Output low voltage				0.45	V	$I_{OL} = 2.1\text{ mA}$
V_{OH}	Output high voltage		3.5			V	$I_{OH} = -2.5\text{ mA}$
I_{OS}	Output short circuit current	6			100	mA	
V_{PP}	V_{PP} read voltage	7	$V_{CC} - 0.7$		V_{CC}	V	

Notes:

- Minimum D.C. input voltage is -0.5V . During transitions, the inputs may undershoot to -2.0V for periods less than 20 ns . Maximum D.C. voltage on output pins is $V_{CC} + 0.5\text{V}$ which may overshoot to $V_{CC} + 2\text{V}$ for periods less than 20 ns .
- Operating temperature is for commercial product defined by this specification. Extended temperature options are available in EXPRESS and Military version.
- Typical limits are at $V_{CC} = 5\text{V}$, $T_A = +25^\circ\text{C}$.
- \overline{CE} is $V_{CC} \pm 0.2\text{V}$. All other inputs can have any value within spec.
- Maximum Active power usage is the sum $I_{PP} + I_{CC}$. The maximum current value is with outputs O_0 to O_7 unloaded.
- Output shorted for no more than one second. No more than one output shorted at a time. I_{OS} is sampled but not 100% tested.
- V_{PP} may be one diode voltage drop below V_{CC} . It may be connected directly to V_{CC} . Also, V_{CC} must be applied simultaneously or before V_{PP} and removed simultaneously or after V_{PP} .
- V_{IL} , V_{IH} levels at TTL inputs.


- Some important operating DC voltage and current ratings
 - V_{CC} is $\pm 5\%$ or $\pm 10\%$
 - High and low output voltages
 - V_{OL} max = 0.45V
 - V_{OH} min = 3.5V
 - High and low input voltages
 - V_{IL} max = $.8\text{V}$ (TTL)
 - V_{IH} min = 2V (TTL)
 - V_{CC} current—active
 - $I_{CC1} = 30\text{ ma}$ (TTL)
 - V_{CC} current—standby
 - $I_{SS1} = 1\text{ ma}$ (TTL)

 9.2 Read-Only Memory– Expanding Byte Capacity




- Many applications require more ROM capacity than is available in a single device
 - Need more bytes of storage
 - Connects to a wider data bus
- Expanding byte capacity with 2 EPROMS
 - Connect address bus lines in parallel
 - Connect output lines in parallel
 - Connect OE* in parallel
 - Enable chips with separate chip selects
 - Address bit A15 decoded to produce CS₀* and CS₁*
 - A15=0 → CS₀*
 - A15=1 → CS₁*
 - Implemented with inverting buffer
 - Byte capacity
 - $2^{16} = 64\text{K bytes}$
 - Organization
 - 64K X 8 bit
 - Storage density
 - $2 \times 32\text{K} \times 8 = 512\text{K bits}$

 9.2 Read-Only Memory– Expanding Word Length




- Expanding word length with 2 EPROM
 - Connecting to 8086 16-bit data bus
 - Connect address bus lines in parallel
 - Connect CE* in parallel
 - Connect OE* in parallel
 - 8 data outputs of EPROM 0 used to supply the lower data bus lines D₀-D₇
 - 8 data outputs of EPROM 1 used to supply the upper 8 data bus lines D₈-D₁₅
 - Byte capacity
 $2 \times 2^{15} = 64\text{K byte}$
 - Organization
 $32\text{K} \times 16 \text{ bit}$
 - Storage density
 $32\text{K} \times 16 = 512\text{K bits}$

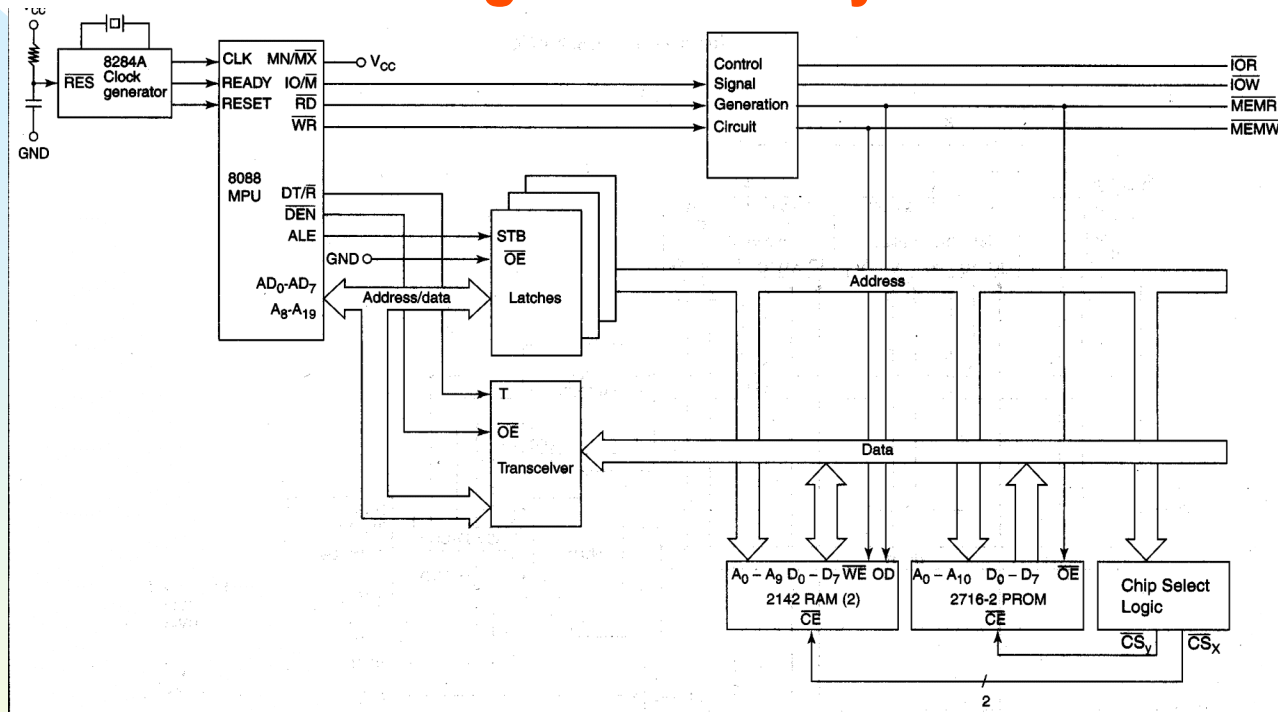9.7 8088/8086 Microcomputer System Memory Circuitry– Minimum-Mode 8088 System Program Memory Interface*



- Program memory
 - Implemented with a single 2716 EPROM—2K X 8-bit
 - Program memory address range
 $A_{10}-A_0 = 0000H - 007FFH$
 - $CS_Y^* = 0$ produced by decoding additional address bit
 ie. $A_{11}-A_{19} = 0 \rightarrow CS_Y^*$
 $A_{11}-A_{19} = 10000000 \rightarrow CS_X^*$
 - $MEMR^* \rightarrow OE^*$

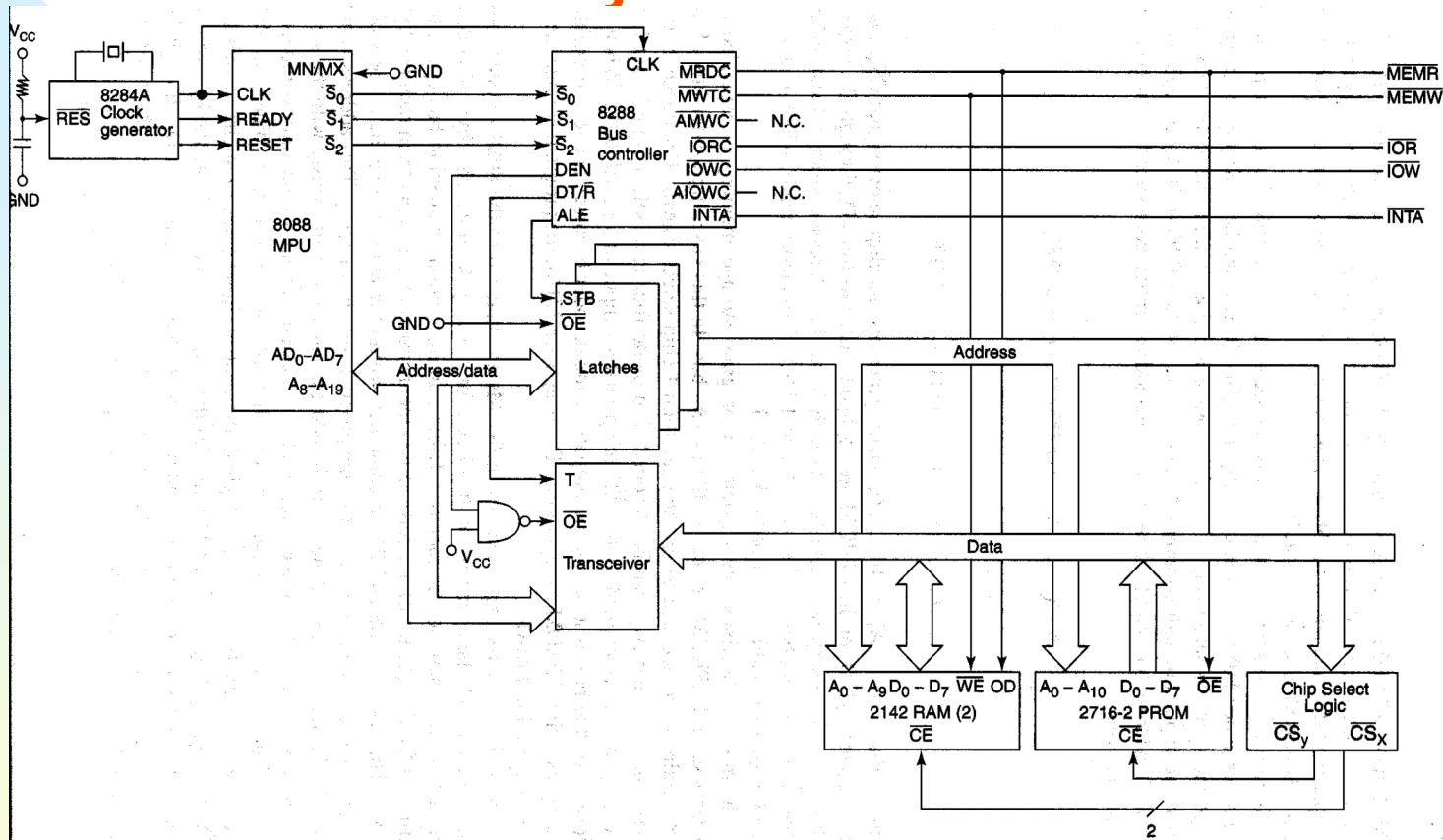9.7 8088/8086 Microcomputer System Memory Circuitry– Maximum-Mode 8088 System Memory Interface*




- Enable signals for address latches, data bus transceivers, RAM, and PROM produced by bus controller

9.3 Random Access Read/Write Memories— Types of RAMs

- Random Access Read/Write Memory (RAM)
 - Used for temporary storage of data and program information
 - Stored information can be altered by MPU—read or written
 - Information read from RAM
 - Modified by processing
 - Written back to RAM for reuse at a later time
 - Information normally more frequently randomly accessed than ROM
 - Information is volatile— lost when power turns off
 - Types:
 - Static RAM (SRAM)— data once entered remains valid as long as power supply is not turned off
 - Lower densities
 - Higher cost
 - Higher speeds
 - DRAM—data once entered requires both the power to be maintained and a periodic refresh
 - Higher densities
 - Lower cost
 - Lower speeds
 - Refresh requires additional circuitry

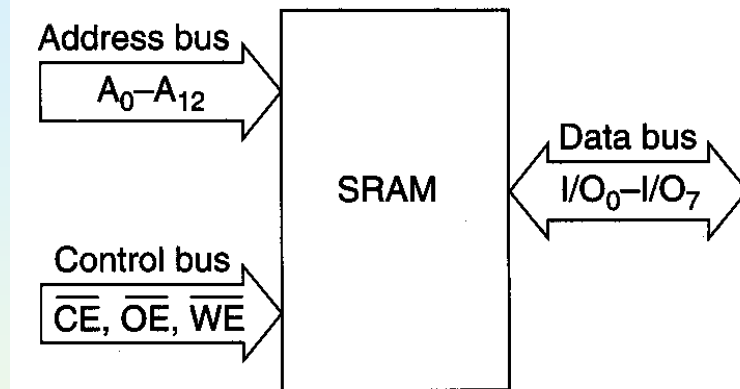9.3 Random Access Read/Write Memories— SRAM Block Diagram




- **Signal interfaces**
 - **Address bus (A₁₂-A₀)**—MPU inputs address information that selects the storage location to be accessed
 - **Data Bus (I/O₇-I/O₀)**—input/output of information for the accessed storage location from/to MPU
 - **Control bus**—enables device, enables output from device, and selects read/write operation
 - **CE*** = chip enable—active 0
 - **OE*** = output enable—active 0
 - **WE*** = write enable
 - 0 = write to RAM
 - 1 = read from RAM

9.3 Random Access Read/Write Memories— Standard SRAM ICs


SRAM	Density (bits)	Organization
4361	64K	64K × 1
4363	64K	16K × 4
4364	64K	8K × 8
43254	256K	64K × 4
43256A	256K	32K × 8
431000A	1M	128K × 8

- Part numbers vary widely by manufacturer—Hitachi/NEC use “43xxx
- SRAMs are available in a variety of densities and organization
 - Typical SRAM densities
 - 64K bit
 - 256K bit
 - 1M bit
 - Typical organizations of the 64K bit SRAM
 - 64K X 1 bit
 - 16K X 4 bit
 - 8K X 8 bit

 9.3 Random Access Read/Write Memories– Pin Layout of SRAMs




(a)

 

(b)

- 4364 and 43256A pin layouts are designed for compatibility
- 4364 pin configuration (Fig a)
 - A₁₂-A₀ → 13-bit address
 $2^{13} = 8K$ bytes
 - I/O₇-I/O₀ → byte wide
 - Pin 1 NC = no connect
 - Pin 27 WE*
 - Pin 20 CE1* → active 0
 - Pin 26 CE2 → active 1
 - Pin 22 → OE*
 - Pin 28 V_{cc}
 - Pin 14 GND
- 43256A differences (Fig b)
 - Pin 1 → A₁₄
 - Pin 26 → A₁₃
 - Pin 20 called CS* (function unchanged)

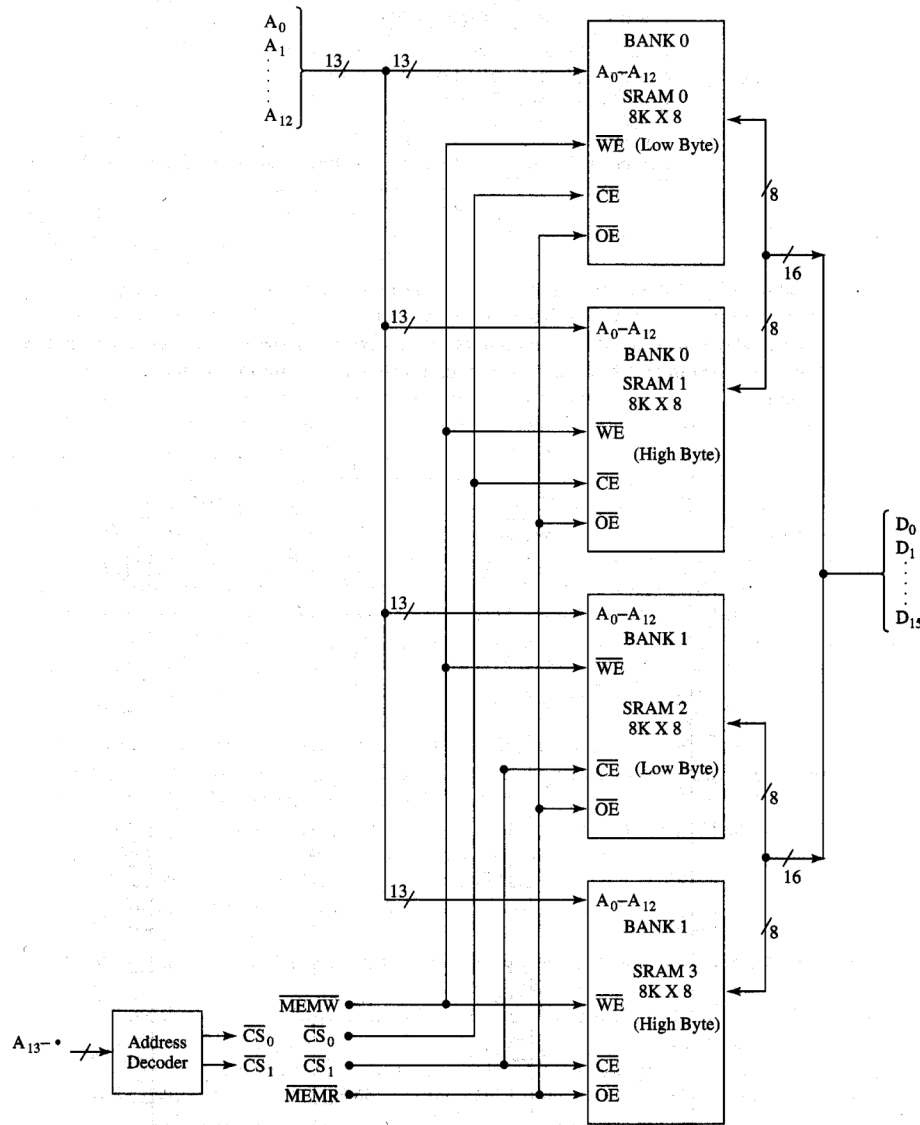9.3 Random Access Read/Write Memories— Expanding Word-Width and Capacity



Most SRAM subsystems

- Require both word-width and bit capacity expansion
- Require the ability to write on byte-wide or word wide basis— design only supports words
- Expansions performed in a similar way as for EPROMs
- 16K X 16-bit SRAM circuit
 - A₀-A₁₂ in parallel
 - A₁₃ decoded to form CS₀* and CS₁*
 - CS₀* → enable Bank 0
 - CS₁* → enable Bank 1
 - SRAMs 0 & 2—input/outputs connected in parallel and supply low byte of data bus
 - SRAMs 1 & 3—input/ outputs connected in parallel and supply high byte of data bus
 - MEMW* and MEMR* produces independent write and read enables

MEMW* MEMR* Data Transfer

MEMW*	MEMR*	Data Transfer
0	0	Invalid
0	1	Word write
1	0	Word read
1	1	Inactive

The 8088 and 8086 Microprocessors Triebel and Singh

How can the circuit be modified to support byte wide write?

9.3 Random Access Read/Write Memories— Standard Read/Write Cycle Times

Part number	Read/write cycle time
4364-10	100 ns
4364-12	120 ns
4364-15	150 ns
4364-20	200 ns

- Speed of a SRAM identified as read/write cycle time
 - Variety of speeds available—4364 available in speeds ranging from 100ns to 200ns
 - Shorter the cycle time the better
- Designated by a dash speed indicator following the part number
 - 10 = 100ns
 - 12 = 120ns

9.3 Random Access Read/Write Memories– DC Electrical Characteristics

Parameter	Symbol	Limits			Unit	Test Conditions
		Min	Typ	Max		
Input leakage current	I_{LI}			1	μA	$V_{IN} = 0\text{ V to }V_{CC}$
Output leakage current	I_{LO}			1	μA	$V_{IO} = 0\text{ V to }V_{CC}$ $\overline{CE}_1 = V_{IH}$ or $\overline{CE}_2 = V_{IL}$ or $\overline{OE} = V_{IH}$ or $\overline{WE} = V_{IL}$
Operating supply current	I_{CCA1}			(1)	mA	$\overline{CE}_1 = V_{IL}$, $\overline{CE}_2 = V_{IH}$, $I_{IO} = 0$, Min cycle
	I_{CCA2}		5	10	mA	$\overline{CE}_1 = V_{IL}$, $\overline{CE}_2 = V_{IH}$, $I_{IO} = 0$, DC current
	I_{CCA3}		3	5	mA	$\overline{CE}_1 \leq 0.2\text{ V}$, $\overline{CE}_2 \geq V_{CC} - 0.2\text{ V}$, $V_{IL} \leq 0.2\text{ V}$, $V_{IH} \geq V_{CC} - 0.2\text{ V}$, $f = 1\text{ MHz}$, $I_{IO} = 0$
Standby supply current	I_{SB}			(2)	mA	$\overline{CE}_1 \geq V_{IH}$ or $\overline{CE}_2 = V_{IL}$
	I_{SB1}			(3)	mA	$\overline{CE}_1 \geq V_{CC} - 0.2\text{ V}$ $\overline{CE}_2 \geq V_{CC} - 0.2\text{ V}$
	I_{SB2}			(3)	mA	$\overline{CE}_2 \leq 0.2\text{ V}$
Output voltage, low	V_{OL}			0.4	V	$I_{OL} = 2.1\text{ mA}$
Output voltage, high	V_{OH}	2.4			V	$I_{OH} = -1.0\text{ mA}$


Notes:

(1) $\mu\text{PD4364-10/10L}$: 45 mA max
 $\mu\text{PD4364-12/12L/12LL}$: 40 mA max
 $\mu\text{PD4364-15/15L/15LL}$: 40 mA max
 $\mu\text{PD4364-20/20L/20LL}$: 35 mA max

(2) $\mu\text{PD4364-xx}$: 5 mA max (3) $\mu\text{PD4364-xx}$: 2 mA max
 $\mu\text{PD4364-xxL}$: 3 mA max $\mu\text{PD4364-xxL}$: 100 μA max
 $\mu\text{PD4364-xxLL}$: 3 mA max $\mu\text{PD4364-xxLL}$: 50 μA max

- Some important operating DC voltage and current ratings
 - $V_{CC} = 5\text{V} \pm 10\%$
 - High and low output voltages
 - $V_{OL} \text{ max} = 0.4\text{V}$
 - $V_{OH} \text{ min} = 2.4\text{V}$
 - I_{CC} —operating current
 - Varies based on frequency of repeated read/write cycles
 - I_{CCA1} —repeatedly performing fastest R/W cycle
 - $I_{CCA1} \text{ max} = 45\text{mA @ } -100\text{ns}$
 - $I_{CCA1} \text{ max} = 35\text{mA @ } -200\text{ns}$
 - I_{CCA1} increases with frequency
 - Fastest read cycle of -20 is $\frac{1}{2}$ the frequency of the fastest -10 cycle
 - I_{CCA2} —no R/W taking place (DC)
 - $I_{CCA2} \text{ max} = 10\text{mA}$

 9.3 Random Access Read/Write Memories– Write Cycle and Timing



Notes:

1. A write occurs during the overlap of a low \overline{CE}_1 and a high CE_2 and a low \overline{WE}
2. \overline{CE}_1 or \overline{WE} [or CE_2] must be high [low] during any address transaction.
3. If \overline{OE} is high the I/O pins remain in a high-impedance state.

■ Timing is referenced to valid address

- t_{WC} = write cycle time—address must remain valid for this period
4364-10 $t_{WC} = 100\text{ns}$
- Other important timing characteristics
 - t_{CW1} = \overline{CE}_1^* to end of write time—minimum amount of time between \overline{CE}_1^* becoming active and completion of write cycle
4364-10 $t_{CW1} = 80\text{ns}$
 - t_{CW2} = CE_2 to end of write time—minimum amount of time between CE_2 becoming active and completion of write cycle
4364-10 $t_{CW2} = 80\text{ns}$
 - t_{AS} = address set-up time—minimum amount of time the address must be stable before \overline{WE}^* becomes active
4364-10 $t_{AS} = 0\text{ns}$
 - t_{WP} = write pulse width—minimum duration of the write
4364-10 $t_{WP} = 60\text{ns}$
 - t_{DW} = data valid to end of write pulse—minimum time that input data must be maintained valid after the leading edge of \overline{WE}^*
4364-10 $t_{DW} = 60\text{ns}$
 - t_{DH} = data hold time—minimum time that input data must be maintained valid after the trailing edge of \overline{WE}^*
4364-10 $t_{DH} = 0\text{ns}$
 - t_{WR} = write recovery hold time—minimum time that must elapse from trailing edge of \overline{WE}^* before another write can be initiated
4364-10 $t_{WR} = 5\text{ns}$

9.6 Wait-State Circuitry— Extending the Bus Cycle

- If the memory or I/O device is slow for the bus cycle of the MPU, read/write access cycles must be extended with wait states

- Recall—bus cycle duration


- 5MHz 8088/8086 = 800ns
- 8MHz 8088/8086 = 500ns
- 10MHz 8086 = 400ns

- Memory device speed not a problem with these older processor


- 100MHz 80486—10ns clock
- 2 clocks/bus cycle—20ns bus cycle duration

- Slow I/O devices are a potential problem
- Solution is wait-state generator circuit

 - Accepts CLK and bus cycle control signals as inputs
- Circuit detects when bus cycle is in progress and delays active READY for an appropriate number of clock cycles



(a)

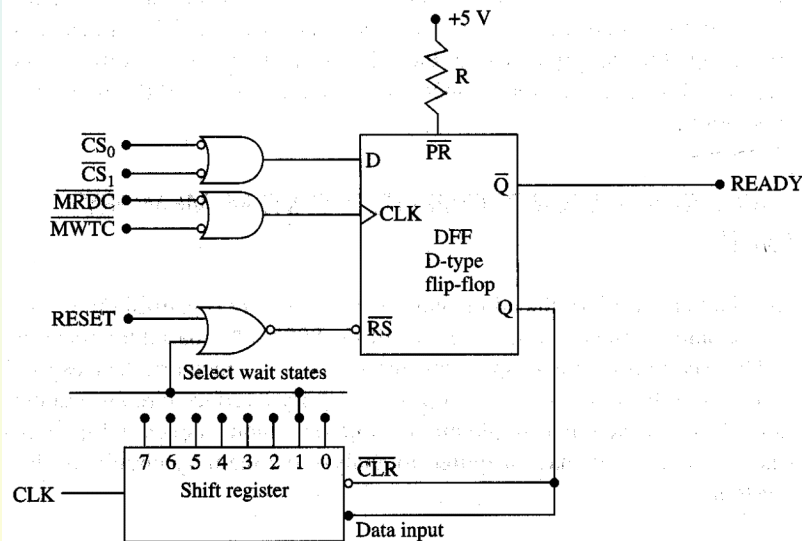

(b)


9.6 Wait-State Circuitry– Wait-State Generator Circuit Inputs and Outputs

■ Input of FF


- CS0* and CS1* represents chip selects for the program and data storage memory
- MRDC* and MWTC* correspond to read or write commands that occur during a memory access cycle
- RESET is hardware reset of the MPU
- Strapped output of the shift register is another input
- CLK is MPU clock and drives shift register

● Output of FF

 - Q* output goes to the READY input of the MPU
 - 0 = extend the bus cycle with wait states
 - 1 = complete the current bus cycle



(a)


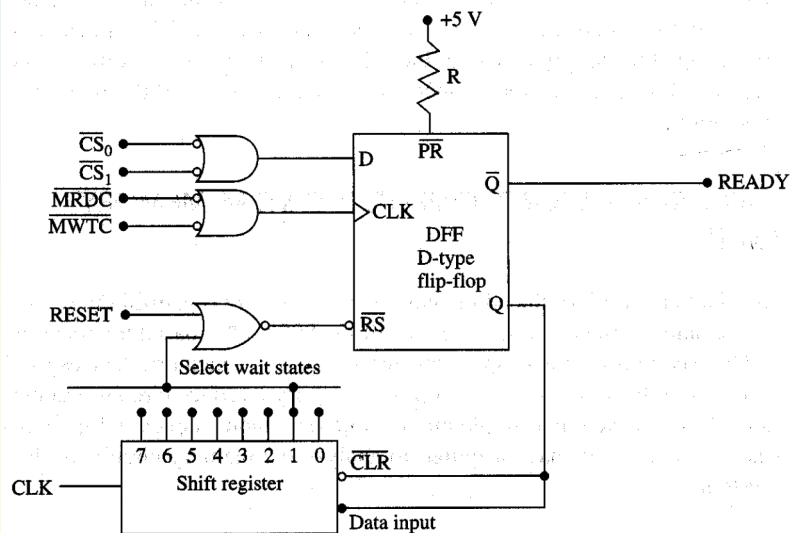


(b)

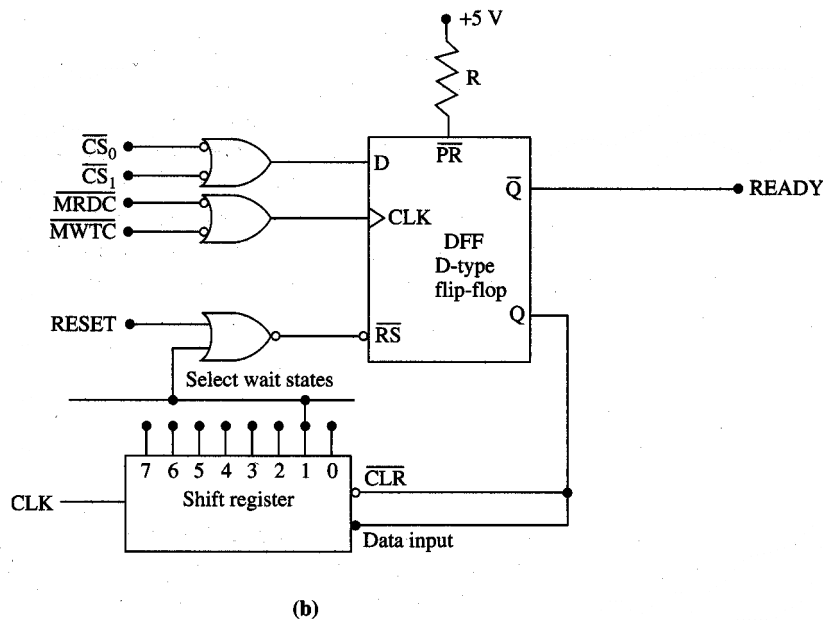 
9.6 Wait-State Circuitry– Wait-State Generator Circuit Operation

■ Operation

- Initial state after pulse at RESET is FF reset
 - $Q^* = 1 \rightarrow \text{READY}$
 - $Q \rightarrow \text{CLR}$ of shift register and makes SR outputs = 0
- Bus cycle initiated
 - $\overline{CS_0}^*$ or $\overline{CS_1}^*$ becomes active = 0 making $D=1$
 - Pulse to 0 at either \overline{MRDC}^* or \overline{MWTC}^* clocks FF
 - FF sets making $Q^* = 0$ and $Q = 1$
 - $Q^* = 0 \rightarrow \text{READY}$ inactive insert wait states
 - $Q = 1$ applied as data input of SR
 - SR no longer held in clear state
 - CLK shifts logic 1 applied at Data input up through the SR
- Bus cycle completes
 - When selected SR output (1) become 1, \overline{RS}^* input of FF made 0 and it resets
 - $Q = 0 \rightarrow$ clears SR
 - $Q^* = 1 \rightarrow \text{READY}$ active and bus cycle completes
- **Bus cycle extended by how many clocks?**




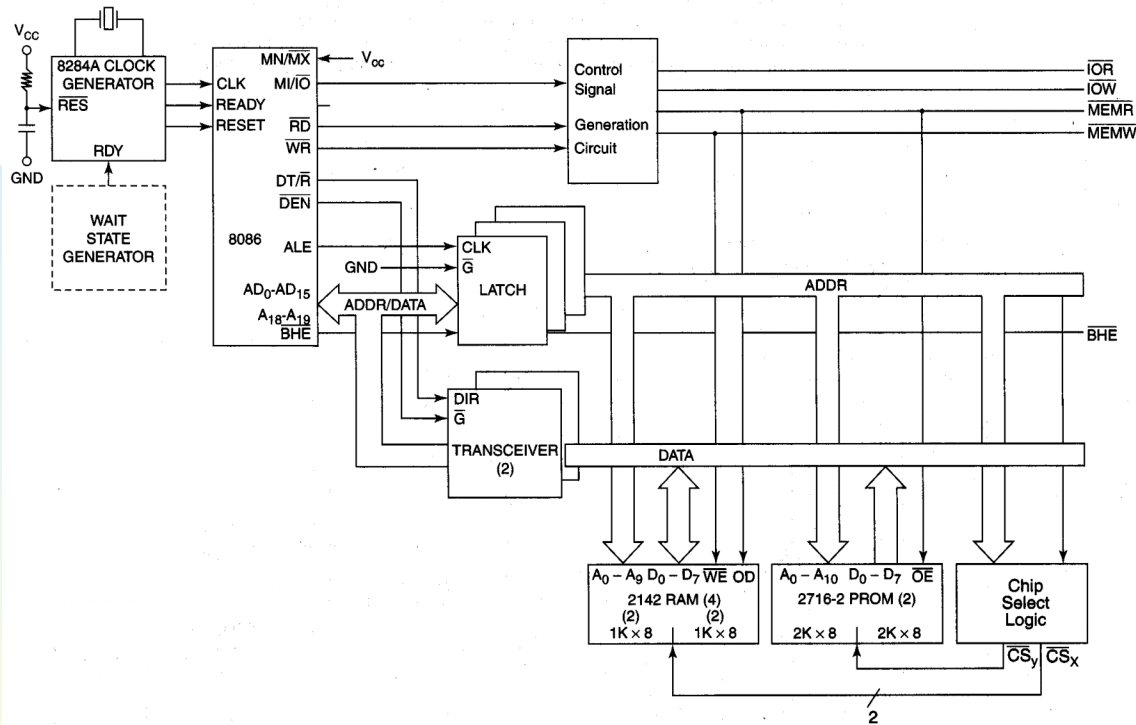9.7 8088/8086 Microcomputer System Memory Circuitry— Minimum-Mode 8086 System Data Memory Interface



- Data memory
 - Implemented with 4 2142 1K X 4-bit SRAMs—1K X 16-bit
 - Assume: A11-A19 = 100000000 → CS_x*
 - SRAM memory address range
 $A_{11}-A_0 = 1000\ 0000\ 0000_2 - 1011\ 1111\ 1111_2$
 $= 00800H - 00BFFH$
 - MEMW* → WE*
 - MEMR* → OD

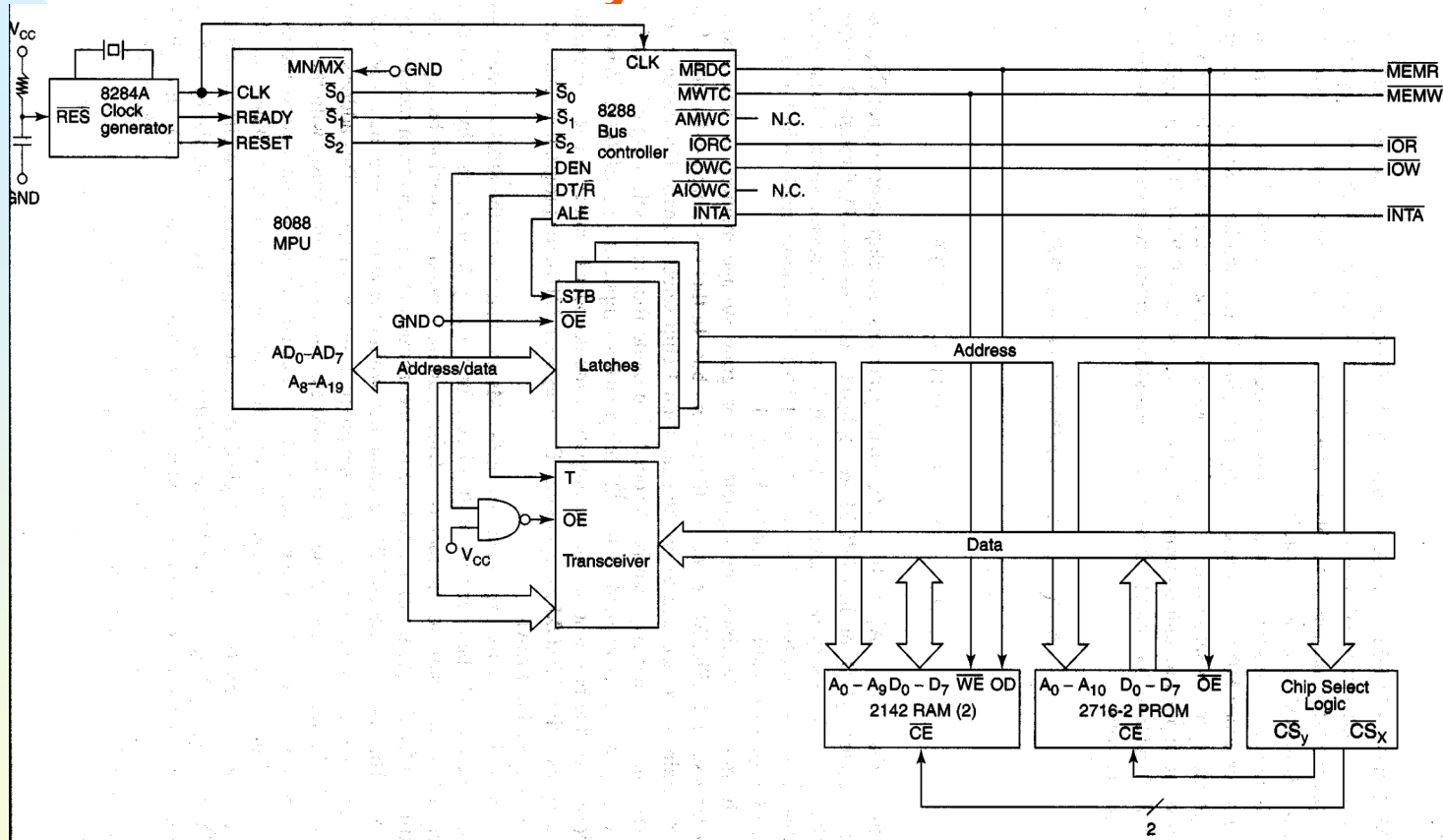9.7 8088/8086 Microcomputer System Memory Circuitry– Maximum-Mode 8088 System Memory Interface




- Enable signals for address latches, data bus transceivers, RAM, and PROM produced by bus controller

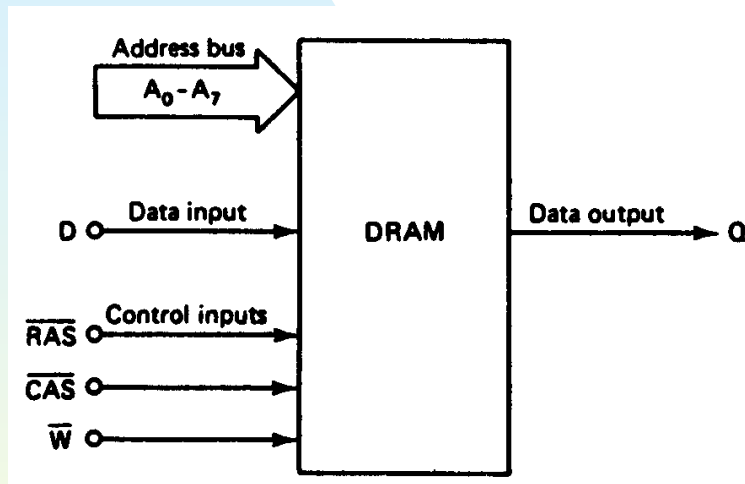9.3 Random Access Read/Write Memories– DRAM Block Diagram

- DRAM signal interfaces

- ◆ Address multiplexed in external circuitry into a separate row and column address
 - ✦ Row address = A_7-A_0
 - ✦ Column address = $A_{15}-A_8$
- ◆ Special RAS* and CAS* inputs used to strobe address into DRAM
- ◆ Row and column addresses applied at different times to address inputs A_0 through A_7
 - ✦ Row address first
 - ✦ Column address second
 - ✦ Known as “RAS before CAS”
 - ✦ Address reassembled into 16-bit address inside DRAM
- ◆ Frequently data organizations are X1, X2, and X4
 - ✦ Separate data inputs and outputs
 - ✦ Data input labeled D
 - ✦ Data output labeled Q
- ◆ Read/write (W) input signals read or write operation




9.3 Random Access Read/Write Memories– Standard DRAM ICs

- DRAMs are available in a variety of densities and organization
 - Typical DRAM densities
 - 64K bit
 - 256K bit
 - 1M bit, Etc.
 - Modern DRAMS as large as 1G bit
 - Typical organizations of the 4M bit DRAM
 - 4M X 1 bit
 - 1M X 4 bit
 - Modern higher density devices also available in X8, X16, and X32 organizations


DRAM	Density (bits)	Organization
2164B	64K	64K × 1
21256	256K	256K × 1
21464	256K	64K × 4
421000	1M	1M × 1
424256	1M	256K × 4
44100	4M	4M × 1
44400	4M	1M × 4
44160	4M	256K × 16
416800	16M	8M × 2
416400	16M	4M × 4
416160	16M	1M × 16

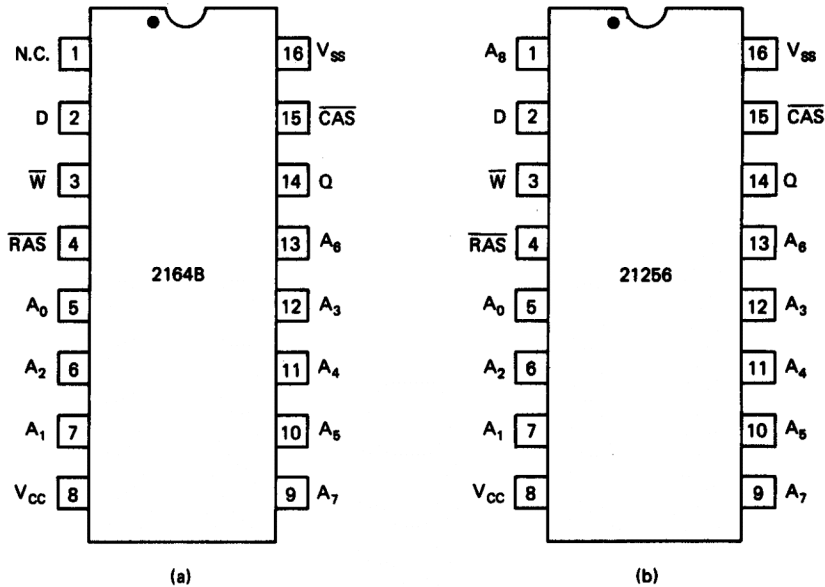9.3 Random Access Read/Write Memories— DRAM IC Packaging




■ Packaging

- Multiplexed address permits device to be built in a package with less pins
 - Typically 16 pin DIP or 18 pin DIP
- Modern devices available in a circuit card format—called a “module”
 - SIMM—single in-line memory module—30 pin and 72 pin versions
 - DIMM—dual in-line memory module—168 pins and 184 pins
 - SIMM and DIMM differ in size, pin layout, and signal distribution
 - Permits easier upgrade of systems with more DRAM memory by simply inserting another module

 

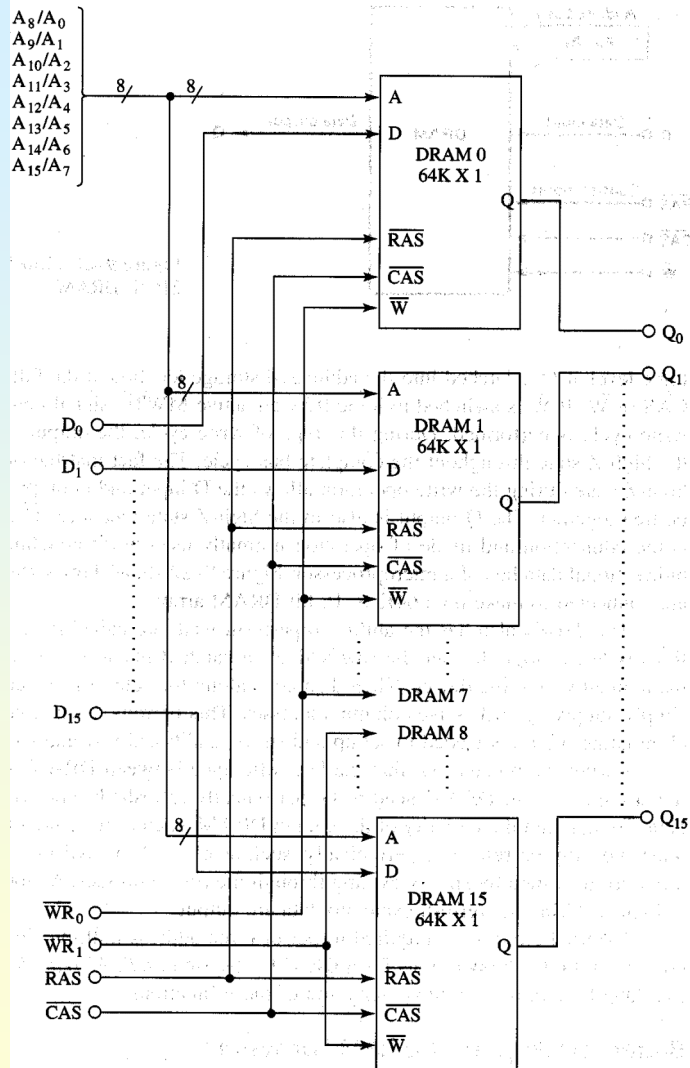9.3 Random Access Read/Write Memories— Circuit Design using DRAMS




Sixteen 64KX1-bit DRAMs interconnected to form a 64K word memory subsystem—1M-bits of memory

◆ Circuit connections

- 8 multiplexed address inputs of all devices connected in parallel
- RAS and CAS lines of all devices connected in parallel
- Data input and output lines
 - Independent data lines arranged to form a 16-bit wide output bus
 - Independent input lines arranged to form a 16-bit wide input bus
 - In most microprocessor applications input and output lines are connected together
- Read/write lines
 - W inputs of upper 8 DRAMs connected together and driven by WR0*
 - W inputs of lower 8 DRAMs connected together and driven by WR1*
 - Permits byte-wide or word-wide reads and writes

 9.3 Random Access Read/Write Memories— Circuitry of a DIMM Module



- 256M byte DIMM circuit
 - ◆ Organized 32MX64-bit or 64MX32-bit
 - ✦ Designed with 256M bit SDRAMs
 - Data transfer operations synchronized using clock (CKE) input
 - ✦ Permits connection to 32-bit or 64 bit buses
 - Connect CS_0^* and CS_2^* together for 64-bit-wide operation
 - Multiplexed input/outputs DQ_0 - DQ_{63}
 - Input/output mask (DQM_{0-7}) inputs used to put outputs into Hi-Z state
 - ◆ Other versions available
 - ✦ With extra parity SDRMS—72 data lines

9.4 Parity, The Parity Bit, and Parity-Checker/Generator Circuit– Parity and the Parity Bit

- Data exchange between the MPU and data memory subsystem in a microcomputer must be done without error

- ◆ Sources of errors


- ✦ Emissions that affect data on the data bus line
- ✦ Electrical noise signals—spikes or transients that affect data on data lines
- ✦ Defective bit in a DRAM
- ✦ Soft errors of DRAM

- ◆ Solutions for improving data integrity


- ✦ Parity
- ✦ Error correction code (ECC)
- ✦ Parity most frequently used

- ◆ Parity

- ✦ Add an additional bit of data to each byte or word of data so that all elements of data have the same parity
- ✦ Extra bit is known as the “parity bit”
 - Even parity—element of data has an even number of bits at the 1 logic level
 - Odd parity—element of data has an odd number of bit that are logic 1
- ✦ Circuitry added to the DRAM memory interface to generate an appropriate parity bit on writes to memory
- ✦ Extra DRAM required to store the parity bit
- ✦ Circuitry checks element of data from correct parity during read operations
- ✦ Parity errors (PE) reported to MPU usually as an interrupt

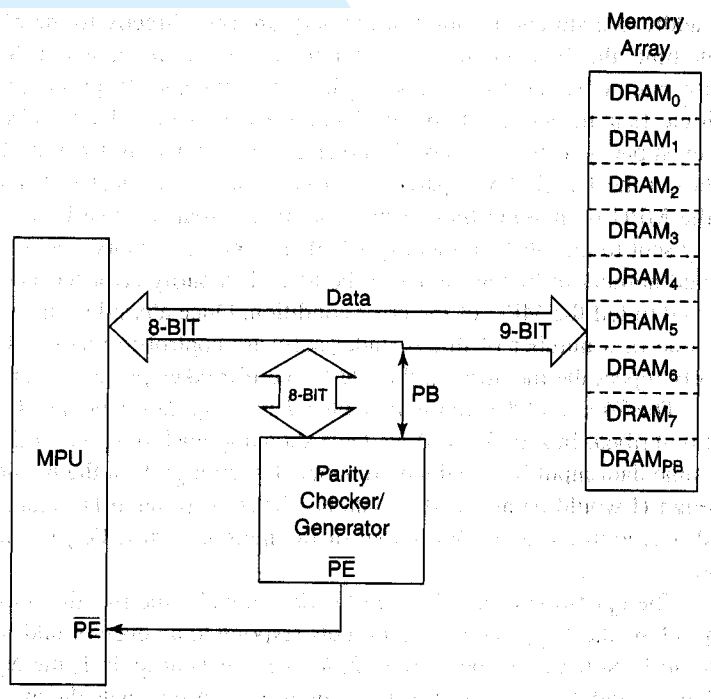

 9.4 Parity, The Parity Bit, and Parity-Checker/Generator Circuit– Parity Generator/Checker Circuitry




NUMBER OF INPUTS A THRU I THAT ARE HIGH	OUTPUTS	
	Σ EVEN	Σ ODD
0,2,4,6,8	H	L
1,3,5,7,9	L	H

(b)

- Parity generator/checker circuit—circuit added to the data memory interface to implement parity
 - ◆ May be implemented with a 74AS280 parity generator/checker IC
 - ✦ 9 inputs A through I
 - ✦ Two outputs Σ_{odd} and Σ_{even}
 - ✦ Operation
 - Even number of inputs are logic 1 →
 - $\Sigma_{\text{even}} = 1$ and $\Sigma_{\text{odd}} = 0$
 - Signals that input has even parity
 - Odd number of inputs are logic 1 →
 - $\Sigma_{\text{even}} = 0$ and $\Sigma_{\text{odd}} = 1$
 - Signals that input has odd parity

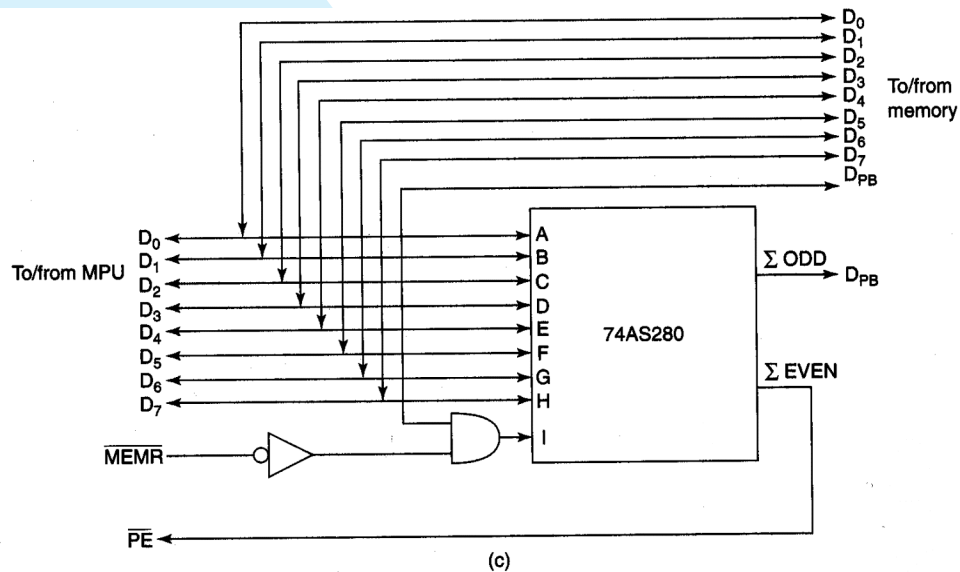9.4 Parity, The Parity Bit, and Parity-Checker/Generator Circuit– Parity Generator/Checker Circuitry

- Even parity generator circuit
 - ◆ Circuit configuration




- ◆ Inputs A through H attach in parallel to data bus lines D0 through D7
- ◆ Input I is attached to the data output of the parity DRAM
 - Only activated during reads
- ◆ Σ odd output is attached to the data input of parity DRAM
- ◆ MPU write operation
 - ◆ Accepts byte of data to be written to memory as input from the data bus
 - ◆ Data also applied in parallel to the input of the DRAMs for data lines D0 through D7
 - ◆ Circuit checks parity and generates Σ odd and Σ even outputs
 - ◆ Σ odd output supplied to input of parity DRAM for storage along with the byte in memory
 - ◆ If parity is even— Σ odd = 0 and 9-bit value saved in memory still has even parity
 - ◆ If parity is odd— Σ odd = 1 and parity of 9-bit value changed to even and saved in memory

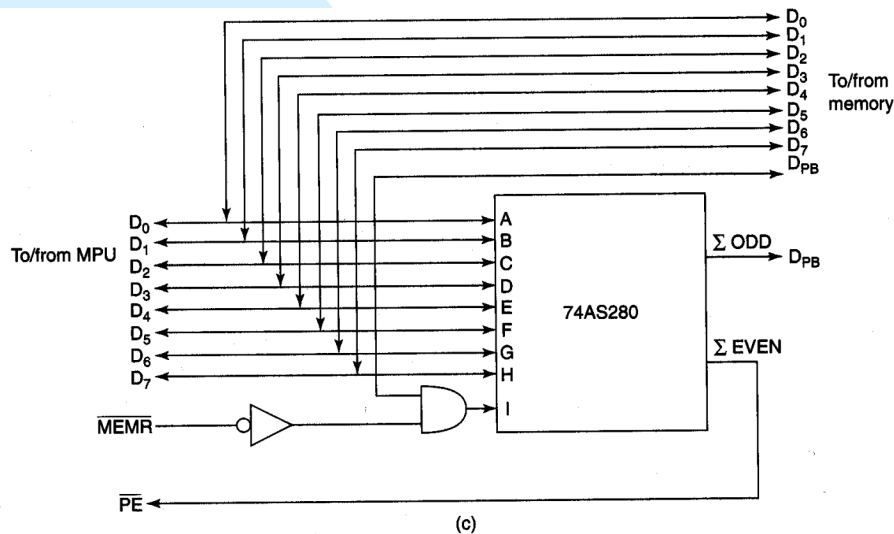9.4 Parity, The Parity Bit, and Parity-Checker/Generator Circuit— Parity Generator/Checker Circuitry

- Read operation:

- ◆ Accepts 9-bit wide input from data outputs of the DRAM subsystem
- ◆ Checks the number of bits that are at the 1 logic level
- ◆ Produces appropriate logic level signals at odd parity and even parity outputs



- ◆ If parity is even— Σ even = 1 and parity is correct
 - Memory operation completes normally
- ◆ If parity is odd— Σ even = 0 and a parity error is detected
 - Error condition signaled to MPU by logic 0 at PE*
 - Usually applied as NMI input to the MPU
 - Must get serviced before executing next instruction
 - MPU may
 - Reattempt memory access
 - Initiate an orderly shut down of application



Chapter 8


The 8088 and 8086 Microprocessors—Their I/O Interface

Introduction

- 8.14 Types of Input/Output—✓
- 8.15 Isolated Input/Output—✓
- 8.16 Input/Output Data Transfers—✓
- 8.17 Input/Output Instructions—✓
- 8.18 Input/Output Bus Cycles—✓

 
8.14 Types of Input/Output- Role and Types of Input/Output

- 8088/8086 architecture implements independent memory and input/output address spaces
 - Memory address space- 1,048,576 bytes long (1M-byte)—00000H-FFFFFH
 - Input/output address space- 65,536 bytes long (64K-bytes)—0000H-FFFFH
 - Input/output can be implemented in either the memory or I/O address space
- Role of I/O
 - Allows I/O devices such as peripheral ICs to input data or receive results
 - Each input/output address is called a port
 - An I/O device may be assigned a range of I/O ports
- Types of Input/Output
 - Isolated I/O— ports implemented in the I/O address space
 - Memory mapped I/O—ports implemented in the memory address space
 - Microcomputer systems can employ both types




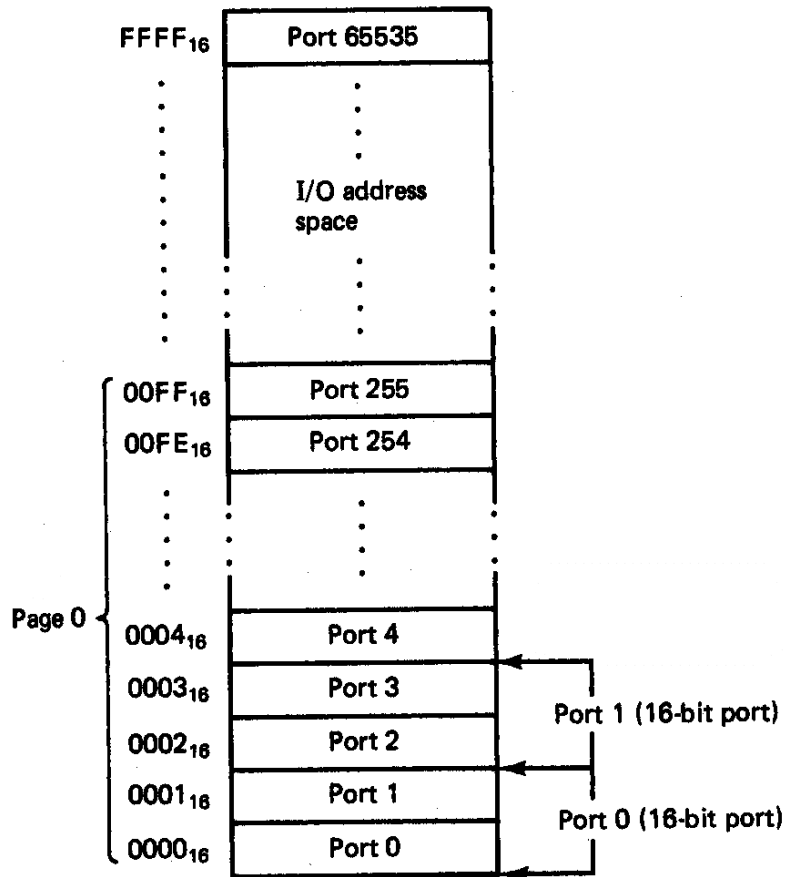8.14 Real-Mode Input-Output Address Space- Isolated I/O

- Input/output data organization
 - Supports byte and word I/O ports
 - 64K independent byte-wide I/O ports
 - 32K independent aligned word-wide I/O ports
 - Word ports may also be misaligned
 - Examples:
 - Byte ports 0,1,2 → addresses 0000H, 0001H, and 0002H
 - Word ports 0,1,2 → addresses 0000H, 0002H, 0004H
- Advantages of isolated I/O
 - Complete memory address space available for use by memory
 - I/O instructions tailored to maximize performance
- Disadvantage of Isolated I/O
 - All inputs/outputs must take place between an I/O port and accumulator register




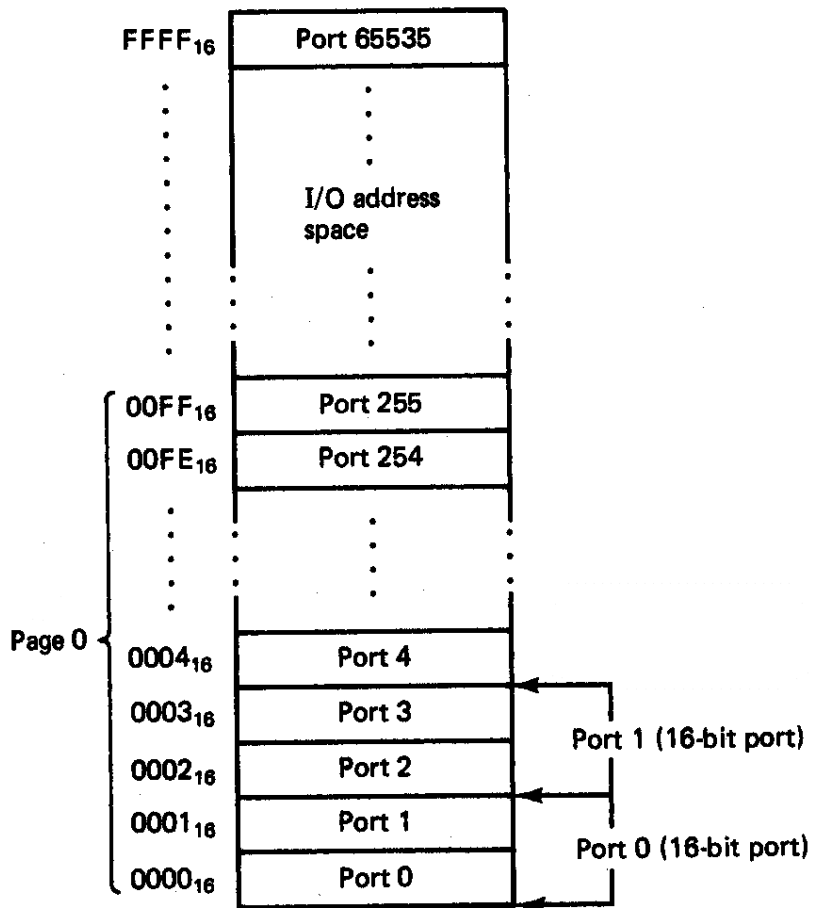8.14 Real-Mode Input-Output Address Space- Isolated I/O (Continued)



- All I/O accesses take either one or two bus cycles
 - Byte input/output= 1 bus cycle
 - Aligned word input/output= 1 bus cycle—on 8086
 - Misaligned word input/output = 2 bus cycles
- Page 0
 - First 256 byte addresses → 0000H - 00FFH
 - Can be accessed with direct or variable I/O instructions
 - Ports F8H through FFH reserved

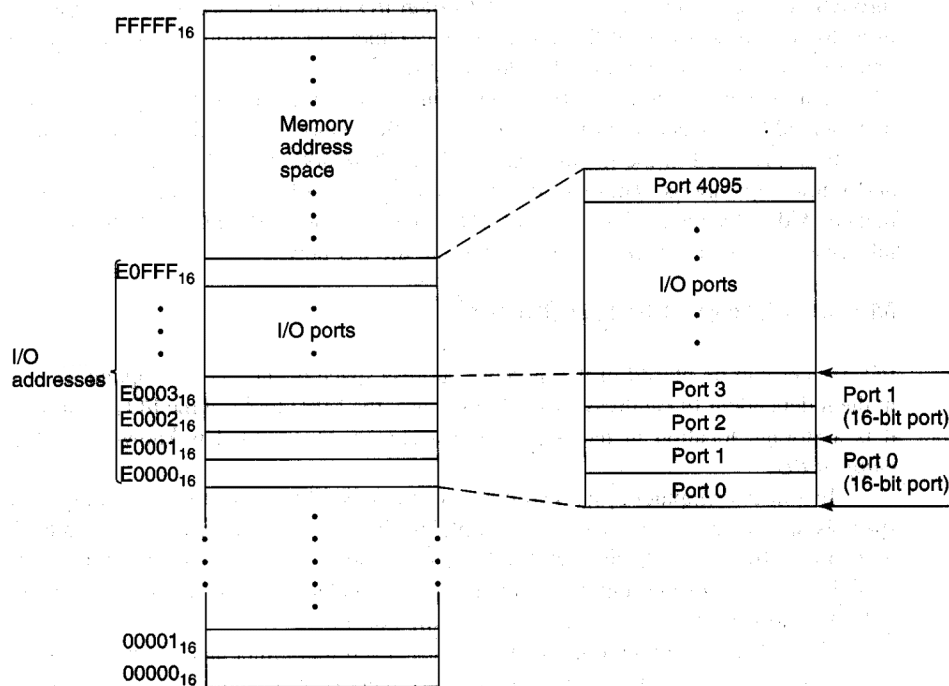8.14 Input-Output Address Space- **Memory Mapped I/O**



- **Memory mapped I/O**—a part of the memory address space is dedicated to I/O devices
 - **Example:**
 - $E0000H-E0FFFH \rightarrow 4096$ memory addresses assigned to I/O ports
 - $E0000H$, $E0001H$, and $E0002H$ correspond to byte-wide ports 0, 1, and 2
 - $E0000H$ and $E0001H$ correspond to word-wide port 0 at address $E0000H$
- **Advantages of memory mapped I/O**
 - Instructions that affect data in memory (MOV, ADD, AND, etc.) can be used to perform I/O operations
 - I/O transfers can take place between and I/O port and any of the registers
- **Disadvantage of memory mapped I/O**
 - Memory instructions perform slower
 - Part of the memory address space cannot be used to implement memory

8.15 Isolated Input/Output Interface– 8088 Minimum-Mode Interface


- Similar in structure and operation to memory interface
- I/O devices—can represent LEDs, switches, keyboard, serial communication port, printer port, etc.
- I/O data transfers take place between I/O devices and MPU over the multiplexed-address data bus

AD0-AD7


A8-A15

Control signal review

- ALE = pulse to logic 1 tells bus interface circuitry to latch I/O address
- RD* = logic 0 tells the I/O interface circuitry that an input (read) is in progress
- WR* = logic 0 tells the I/O interface circuitry that an output (write) is in progress
- IO/M* = logic 1 tells I/O interface circuits that the data transfer operation is for the IO subsystem
- DT/R* = sets the direction of the data bus for input (read) or output (write) operation
- DEN* = enables the interface between the I/O subsystem and MPU data bus


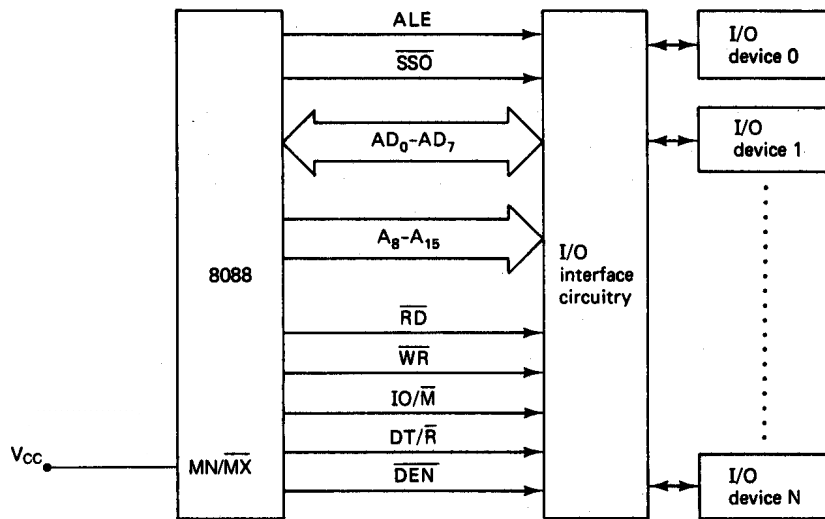


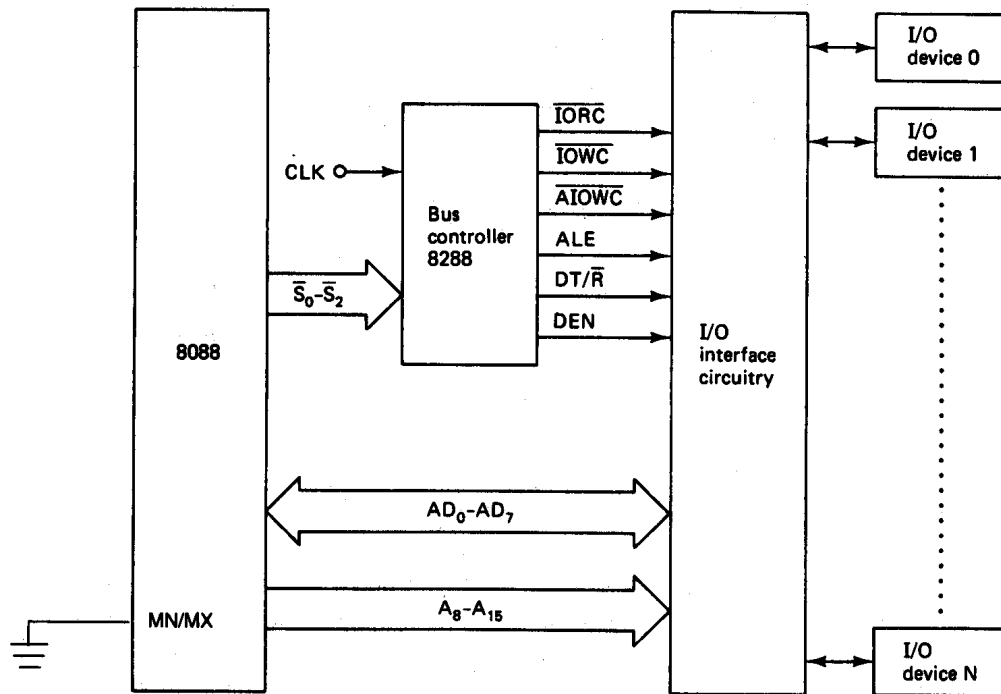8.15 Isolated Input/Output Interface– 8088 Maximum-Mode Interface



- Maximum-mode interface differences review
 - 8288 bus controller produces the control signals
 - Signal changes
 - \overline{IORC}^* replaces RD^*
 - \overline{IOWC}^* and \overline{AIOWC}^* replace WR^*
 - DEN is complement of DEN^*
 - IO/M^* no longer needed (bus controller creates separate IO read/write controls)
 - SSO^* no longer part of interface

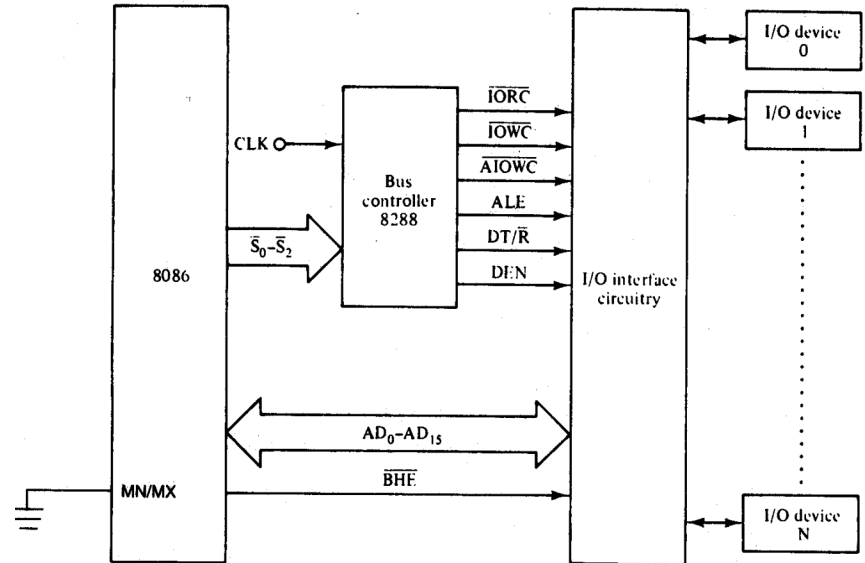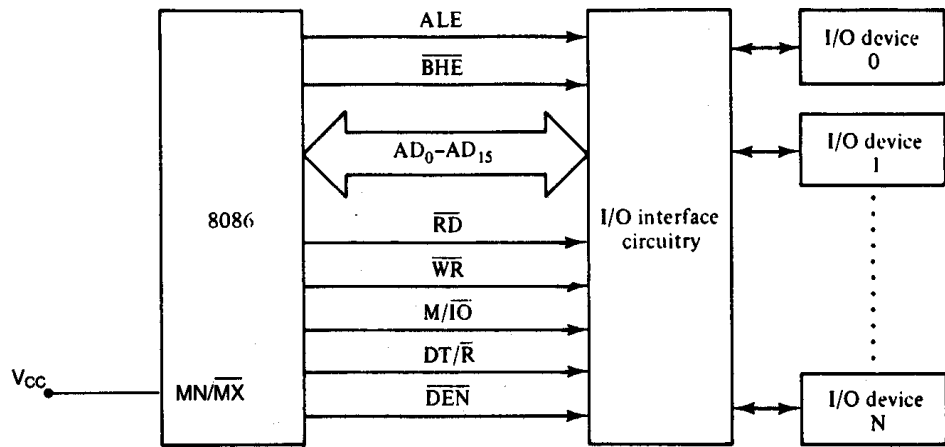8.15 Isolated Input/Output Interface– 8086 Minimum and Maximum-Mode Interfaces



8.15 I/O Control Signals– 8088/8086 Maximum-Mode Bus Status Codes

Status inputs			CPU cycle	8288 command
\bar{S}_2	\bar{S}_1	\bar{S}_0		
0	0	0	Interrupt acknowledge	\overline{INTA}
0	0	1	Read I/O port	\overline{IORC}
0	1	0	Write I/O port	$\overline{IOWC}, \overline{AIOWC}$
0	1	1	Halt	None
1	0	0	Instruction fetch	\overline{MRDC}
1	0	1	Read memory	\overline{MRDC}
1	1	0	Write memory	$\overline{MWTC}, \overline{AMWC}$
1	1	1	Passive	None

- Bus status code review
 - During all I/O accesses one of two bus cycle status code are output by the MPU
 - Read I/O port
 - Write I/O port
 - 8288 decodes to produce appropriate control command signals
 - $\overline{IORC}^* \rightarrow$ input (read I/O)
 - $\overline{IOWC}^* \rightarrow$ output (write I/O)
 - $\overline{AIOWC}^* \rightarrow$ output (write I/O)

8.17 Input/Output Instructions— Direct I/O Instructions

- Types of instructions
 - Direct I/O instructions—only allow access to ports at page 0 addresses
 - Variable I/O instructions—allows access of ports anywhere in the I/O address space
- Direct I/O instructions
 - IN Acc,Port
 - OUT Port,Acc
 - Port = 8-bit direct address—limited to 0H through FFH (page 0)
 - Acc = accumulator register AX (word transfer); AH or AL (byte transfer)
 - Example:
 - IN AL, 0FEH
 - (FE) → AL (byte input operation)
- Also known as accumulator I/O—because source or destination must always be in accumulator (A) register

Mnemonic	Meaning	Format	Operation
IN	Input direct	IN Acc,Port	(Acc) ← (Port) Acc = AL or AX
	Input indirect (variable)	IN Acc,DX	(Acc) ← ((DX))
OUT	Output direct	OUT Port,Acc	(Port) ← (Acc)
	Output indirect (variable)	OUT DX,Acc	((DX)) ← (Acc)

8.17 Input/Output Instructions— Variable I/O Instructions

- Variable I/O instructions

IN Acc,DX

OUT DX,Acc

- DX = 16-bit indirect address—allows access to full I/O address space
- Acc = accumulator register AX (word transfer); AH or AL (byte transfer)

- Example:

MOV DX,0A000H ;load I/O address

IN AL,DX ;input value to AL

MOV BL,AL ;copy value to BL

(A000H) → BL (byte input operation)

Mnemonic	Meaning	Format	Operation
IN	Input direct	IN Acc,Port	(Acc) ← (Port) Acc = AL or AX
	Input indirect (variable)	IN Acc,DX	(Acc) ← ((DX))
OUT	Output direct	OUT Port,Acc	(Port) ← (Acc)
	Output indirect (variable)	OUT DX,Acc	((DX)) ← (Acc)

8.17 Input/Output Instructions– Examples

- Write instructions to output the value FFH to the byte wide port at I/O address ABH
- Solution:
MOV AL, 0FFH ;load data into AL
OUT 0ABH,AL ;output to port ABH

- Write instructions to output the value FFH to the byte wide port at I/O address B000H
- Solution:
MOV DX,0B000H ; load address into DX
MOV AL, 0FFH ; load data into AL
OUT DX,AL ; output to port B000H

8.17 Input/Output Instructions– Examples (Continued)


- Read data from byte-wide ports at addresses AAH and A9H. Output as a word to the word-wide port at address B000H.

- Solution:

```
IN  AL,0AAH      ; input first byte
MOV AH, AL       ; load data into AL
IN  AL,0A9H      ; input 2nd byte
MOV DX,0B000H    ; load address into DX
OUT DX,AX        ; output word to port B000H
```

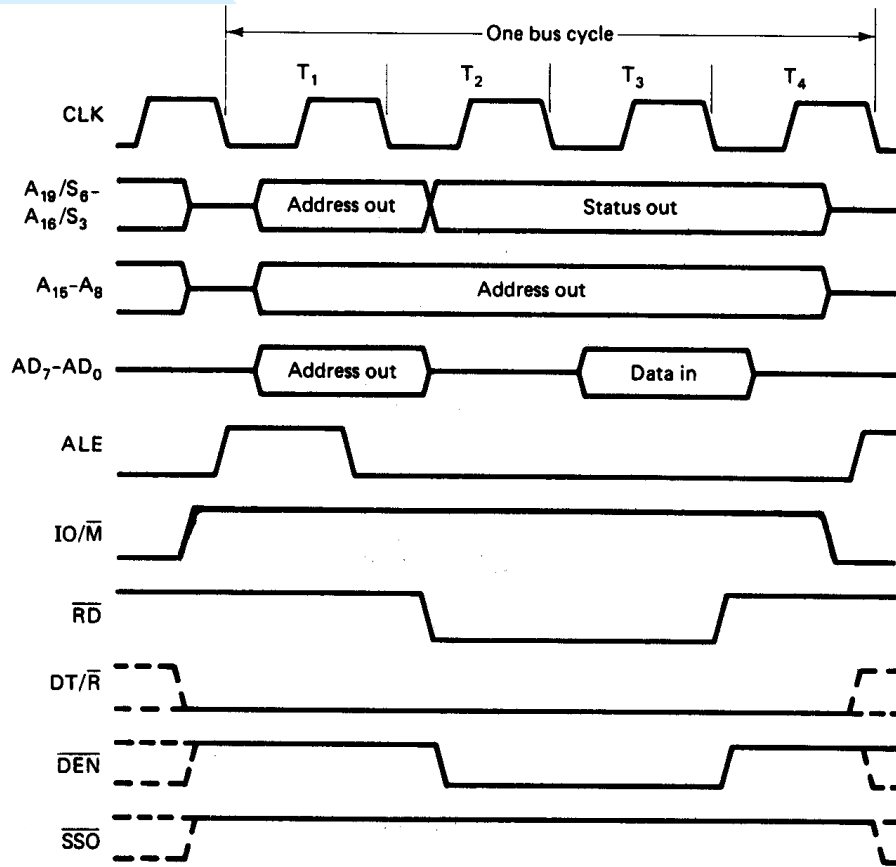8.18 Input and Output Bus Cycles— 8088 Minimum Mode Input Bus Cycle

Input (I/O read) bus cycle timing diagram—shows relationship between signals relative to time states




- **T1 state—input cycle begins**
 - Address output on A0-A15
 - Pulse produced at ALE--address should be latched in external circuitry on trailing edge of ALE
 - IO/M* set to 1 → I/O bus cycle
 - DT/R* set to 0 → set external data bus control circuitry for receive mode (input)
- **T2 state**
 - Status code output on S3-S6
 - AD0 through AD7 tri-stated in preparation for data bus operation
 - RD* set to 0 → input cycle
 - DEN* set to 0 → enable external data bus control circuitry
- **T3 state**
 - Data on D0-D7 input (read) by the MPU
- **T4 state—input cycle finishes**
 - RD* returns to 1 → inactive level
 - Complete address/data bus tri-stated
 - IO/M* returned to 0 → memory bus cycle
 - DEN* returned to 1 → inactive level
 - DT/R* returns to 1 → transmit level

 8.18 Input and Output Bus Cycles– 8088 Minimum Mode Output Bus Cycle

- Output (I/O write) bus cycle timing diagram

- T1 state—output cycle begins
 - Address output on A0-A15
 - Pulse produced at ALE and address latched in external circuitry on trailing edge of ALE
 - IO/M* set to 1 → I/O bus cycle
 - DT/R* set to 1 → external data bus control circuitry for transmit mode (output)
- T2 state
 - Status code output on S3-S6
 - AD0 through AD7 transitioned to data bus and output data placed on bus
 - DEN* set to 0 → enable external data bus control circuitry
 - WR* set to 0 → output cycle
- T3 or T4 state
 - Data on D0-D7 output (write) into I/O port (I/O device decides when!)
- T4 state—output cycle finishes
 - WR* returns to 1 → inactive level
 - Complete address/data bus tri-stated
 - IO/M* returned to 0 → memory bus cycle
 - DEN* returned to 1 → inactive level



8.18 Input and Output Bus Cycles– 8086 Minimum Mode Read and Write Bus Cycles

