

# Chapter 12: Sinusoids and Phasors

**Instructor:** Jean-François MILLITHALER

[http://faculty.uml.edu/JeanFrancois\\_Millithaler/FunElec/Spring2017](http://faculty.uml.edu/JeanFrancois_Millithaler/FunElec/Spring2017)

# Sinusoids

- ▶ Consider the sinusoidal voltage



$$v(t) = V_m \sin \omega t$$

- ▶ Where

- $V_m$  = the amplitude of the sinusoid
- $\omega$  = the angular frequency in radians/s
- $\omega t$  = the argument of the sinusoid

- ▶ The period is


$$T = \frac{2\pi}{\omega}$$

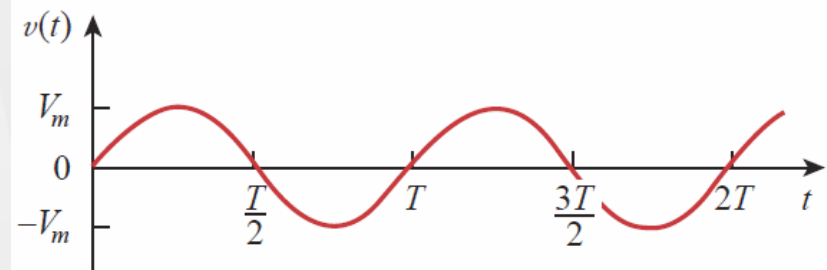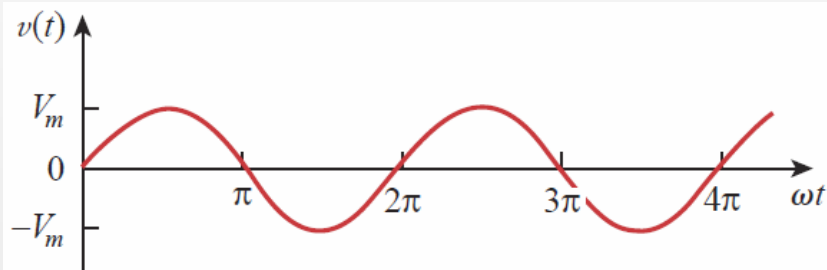

# Sinusoids

- ▶ The more general expression is

$$v(t) = V_m \sin(\omega t + \phi)$$

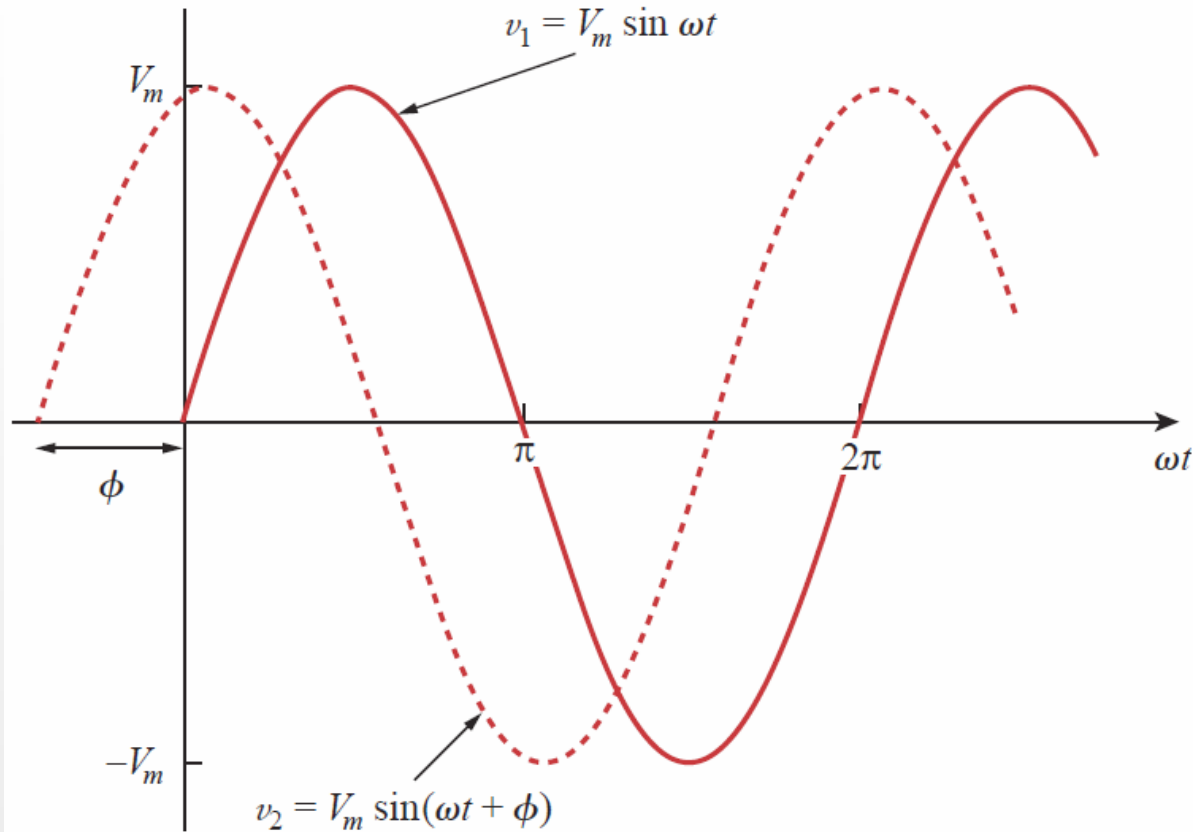

# Phasors

- ▶ A **phasor** is a complex number that represents the amplitude and phase of a sinusoid

# Complex Numbers

- ▶ A complex number  $z$  can be written in rectangular form as:

$$z = x + jy$$

- ▶ Where  $j = \sqrt{-1}$ ;  $x$  is the real part of  $z$ ;  
 $y$  is the imaginary part of  $z$


- ▶  $z$  can also be written in exponential form as:

$$z = r e^{j\phi}$$

- ▶ The relationship between the rectangular and the exponential form is:

$$r = \sqrt{x^2 + y^2}, \quad \phi = \tan^{-1} \frac{y}{x}$$
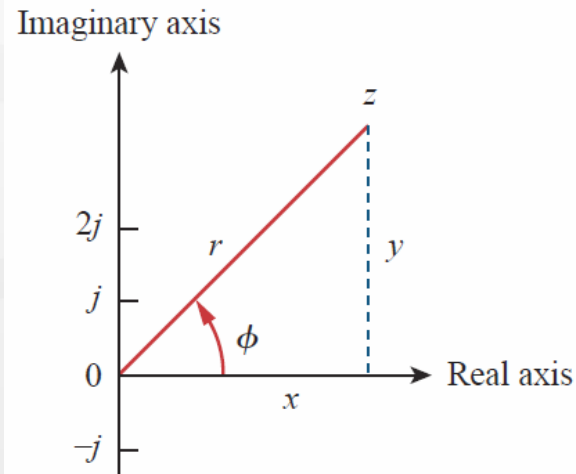
$$x = r \cos \phi, \quad y = r \sin \phi$$



# Phasors

- ▶ A **phasor** is a complex number that represents the amplitude and phase of a sinusoid
- ▶ Let's see the phasor relationship for circuit elements

# phasor relationship for circuit elements



## Resistor

- ▶ If the current through a resistor  $R$  is  $i = I_m \cos(\omega t + \phi)$ , the voltage across it is given by Ohm's law as

$$v = iR = RI_m \cos(\omega t + \phi)$$

- ▶ The phasor representation in frequency domain is

$$\mathbf{V} = R\mathbf{I}$$

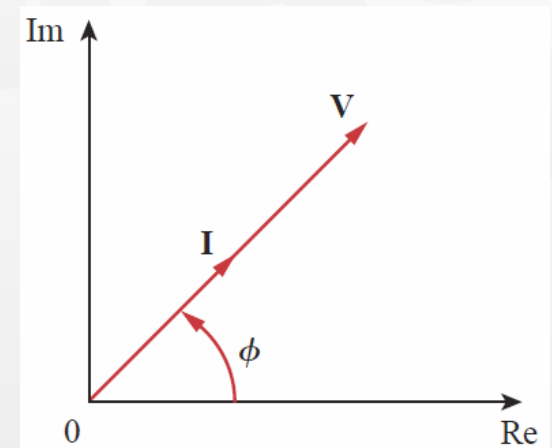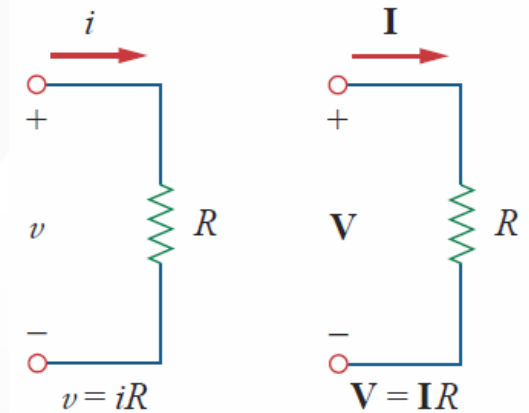

# phasor relationship for circuit elements

## Inductor

- ▶ If the current through an inductor  $L$  is  $i = I_m \cos(\omega t + \phi)$ , the voltage across it is

$$v = L \frac{di}{dt} = -\omega L I_m \sin(\omega t + \phi)$$

- ▶ With  $-\sin A = \cos(A + 90^\circ)$ , we got



$$v = \omega L I_m \cos(\omega t + \phi + 90^\circ)$$

- ▶ Which transform to the phasor

$$\mathbf{V} = \omega L I_m e^{j(\phi + 90^\circ)}$$

- ▶ Thus

$$\mathbf{V} = j\omega L \mathbf{I}$$

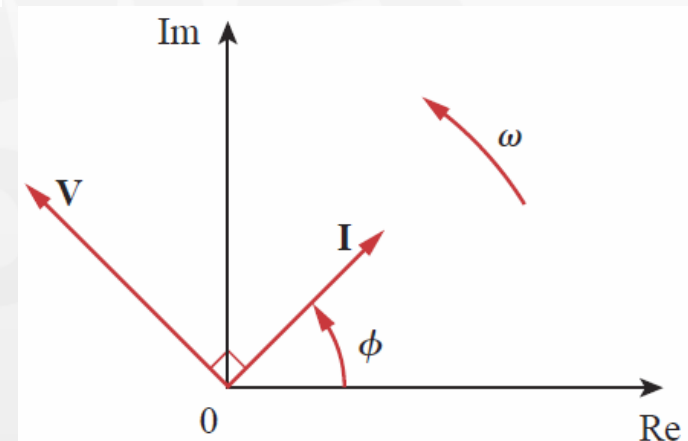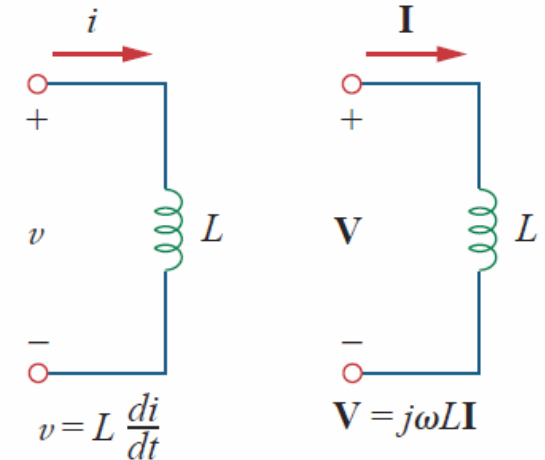




# phasor relationship for circuit elements

## Capacitor


- ▶ For the Capacitor  $C$ , assume the voltage across it is  $v = V_m \cos(\omega t + \phi)$ . The current through the capacitor is

$$i = C \frac{dv}{dt}$$

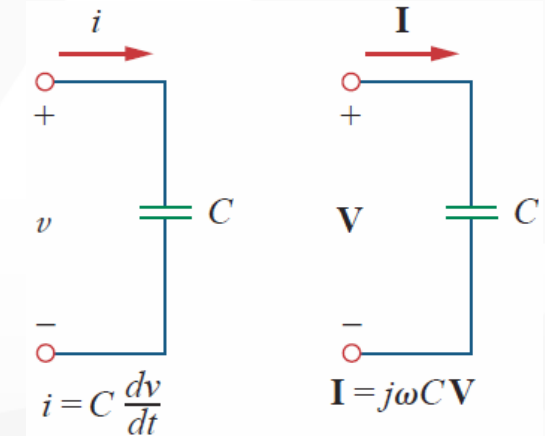

- ▶ In frequency we obtain
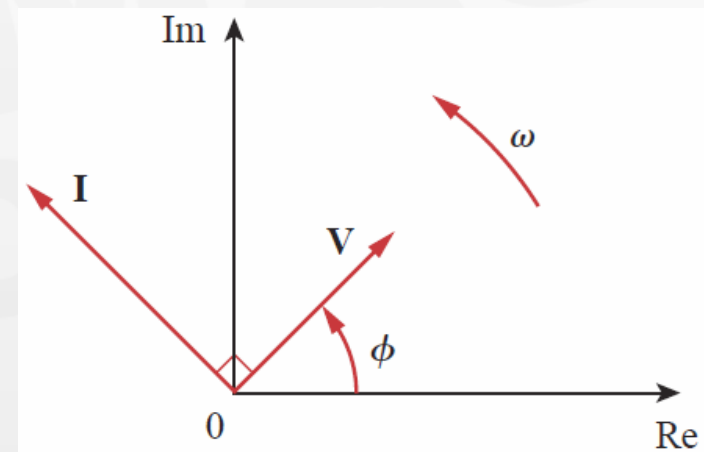
$$I = j\omega CV \quad \Rightarrow \quad V = \frac{I}{j\omega C}$$



# Impedance and Admittance

- ▶ From the table we can write the ratio of the phasor voltage and the phasor current as

$$\frac{V}{I} = R, \quad \frac{V}{I} = j\omega L, \quad \frac{V}{I} = \frac{1}{j\omega C}$$

- ▶ The **impedance**  $\mathbf{Z}$  of a circuit is the ratio of the phasor voltage  $\mathbf{V}$  to the phasor current  $\mathbf{I}$ , measured in ohms ( $\Omega$ )

$$\mathbf{Z} = \frac{V}{I}, \quad \mathbf{V} = \mathbf{Z}\mathbf{I}$$

- ▶ As a complex quantity, the impedance may be expressed as

$$\mathbf{Z} = R + jX = |\mathbf{Z}|e^{\theta}$$

$$|\mathbf{Z}| = \sqrt{R^2 + X^2}, \quad \theta = \tan^{-1} \frac{X}{R}$$

$$R = |\mathbf{Z}|\cos\theta, \quad X = |\mathbf{Z}|\sin\theta$$


# Summary

Element	Time domain	Frequency domain
$R$	$v = Ri$	$\mathbf{V} = R\mathbf{I}$
$L$	$v = L \frac{di}{dt}$	$\mathbf{V} = j\omega L\mathbf{I}$
$C$	$i = C \frac{dv}{dt}$	$\mathbf{V} = \frac{\mathbf{I}}{j\omega C}$

Element	Impedance	Admittance
$R$	$\mathbf{Z} = R$	$\mathbf{Y} = \frac{1}{R}$
$L$	$\mathbf{Z} = j\omega L$	$\mathbf{Y} = \frac{1}{j\omega L}$
$C$	$\mathbf{Z} = \frac{1}{j\omega C}$	$\mathbf{Y} = j\omega C$

# Impedance Combination

$N$  impedance in series

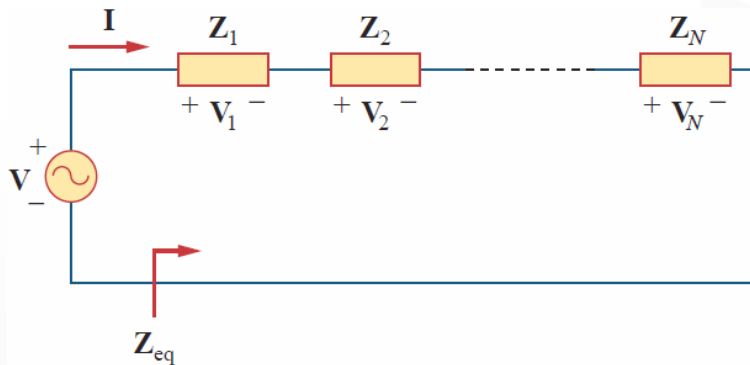


$$V = V_1 + V_2 + \cdots + V_N = I(Z_1 + Z_2 + \cdots + Z_N)$$

$$Z_{eq} = \frac{V}{I} = Z_1 + Z_2 + \cdots + Z_N$$

$$Z_{eq} = Z_1 + Z_2 + \cdots + Z_N$$

$N$  impedance in parallel

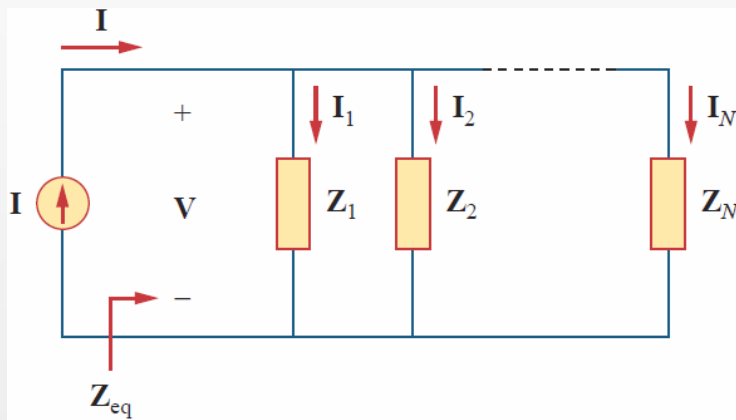

$$I = I_1 + I_2 + \cdots + I_N = V \left( \frac{1}{Z_1} + \frac{1}{Z_2} + \cdots + \frac{1}{Z_N} \right)$$

$$\frac{1}{Z_{eq}} = \frac{I}{V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \cdots + \frac{1}{Z_N}$$

$$Y_{eq} = Y_1 + Y_2 + \cdots + Y_N$$


# Impedance Combination

If  $N=2$ , the current through the series impedances is

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}_1 + \mathbf{Z}_2}$$

Since  $\mathbf{V}_1 = \mathbf{Z}_1 \mathbf{I}$  and  $\mathbf{V}_2 = \mathbf{Z}_2 \mathbf{I}$

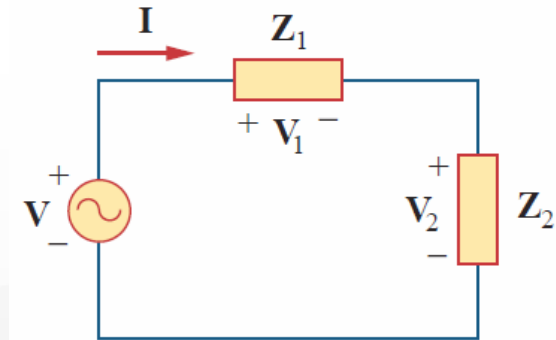
$$\mathbf{V}_1 = \frac{\mathbf{Z}_1}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{V}, \quad \mathbf{V}_2 = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{V}$$




If  $N=2$ , the current through the parallel impedances is

$$\mathbf{Z}_{\text{eq}} = \frac{1}{\mathbf{Y}_{\text{eq}}} = \frac{1}{\mathbf{Y}_1 + \mathbf{Y}_2} = \frac{1}{1/\mathbf{Z}_1 + 1/\mathbf{Z}_2} = \frac{\mathbf{Z}_1 \mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2}$$
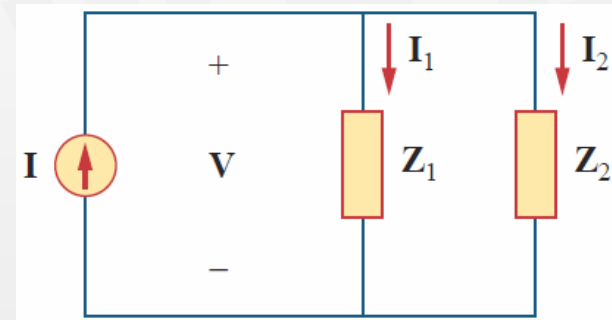
$$\mathbf{I}_1 = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{I}, \quad \mathbf{I}_2 = \frac{\mathbf{Z}_1}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{I}$$




# Exercice

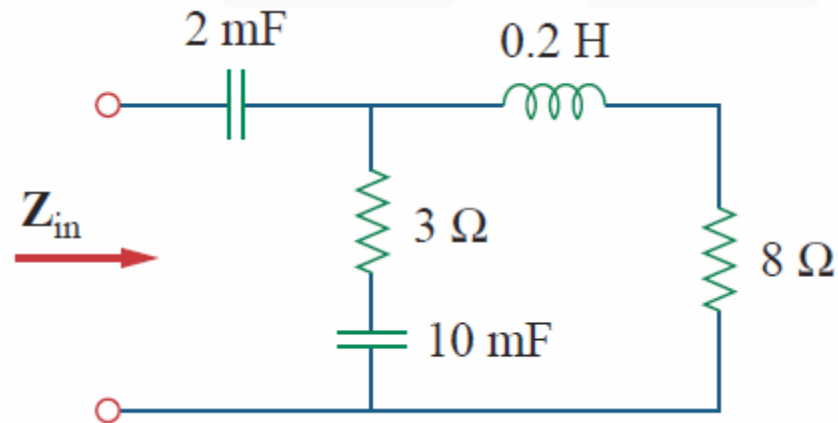

- Find the input impedance of the circuit. Assume that the circuit operates at  $\omega = 50\text{ rad/s}$
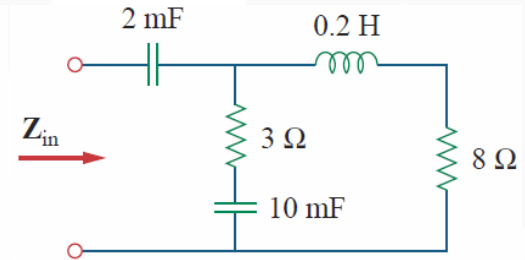
# Solution

- Let  $Z_1$  = Impedance of the 2-mF capacitor  
 $Z_2$  = Impedance of the 3- $\Omega$  resistor in series with the 10-mF capacitor  
 $Z_3$  = Impedance of the 0.2-H inductor in series with the 8- $\Omega$  resistor



Then

$$Z_1 = \frac{1}{j\omega C} = \frac{1}{j50 \times 2 \times 10^{-3}} = -j10 \Omega$$

$$Z_2 = 3 + \frac{1}{j\omega C} = 3 + \frac{1}{j50 \times 10 \times 10^{-3}} = (3 - j2) \Omega$$

$$Z_3 = 8 + j\omega L = 8 + j50 \times 0.2 = (8 + j10) \Omega$$

The input impedance is

$$\begin{aligned} Z_{in} &= Z_1 + Z_2 \parallel Z_3 = -j10 + \frac{(3 - j2)(8 + j10)}{11 + j8} \\ &= -j10 + \frac{(44 + j14)(11 - j8)}{11^2 + 8^2} = -j10 + 3.22 - j1.07 \Omega \end{aligned}$$

Thus

$$Z_{in} = 3.22 - j11.07 \Omega$$