

Chapter 13: RC & RL Circuits

Instructor: Jean-François MILLITHALER


http://faculty.uml.edu/JeanFrancois_Millithaler/FunElec/Spring2017

Impedance & Admittance


Element	Impedance	Admittance
R	$\mathbf{Z} = R$	$\mathbf{Y} = \frac{1}{R}$
L	$\mathbf{Z} = j\omega L$	$\mathbf{Y} = \frac{1}{j\omega L}$
C	$\mathbf{Z} = \frac{1}{j\omega C}$	$\mathbf{Y} = j\omega C$

RC Circuit

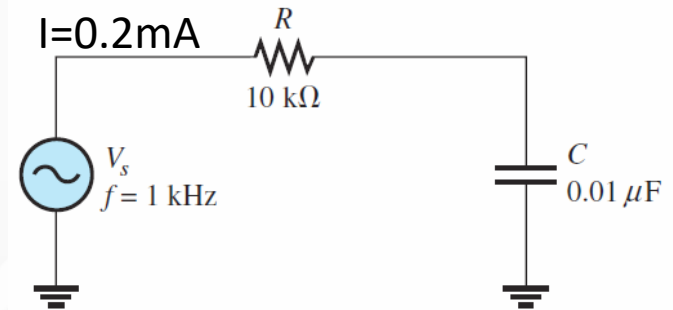- Determine the source voltage and the phase angle.
- Draw the impedance triangle.




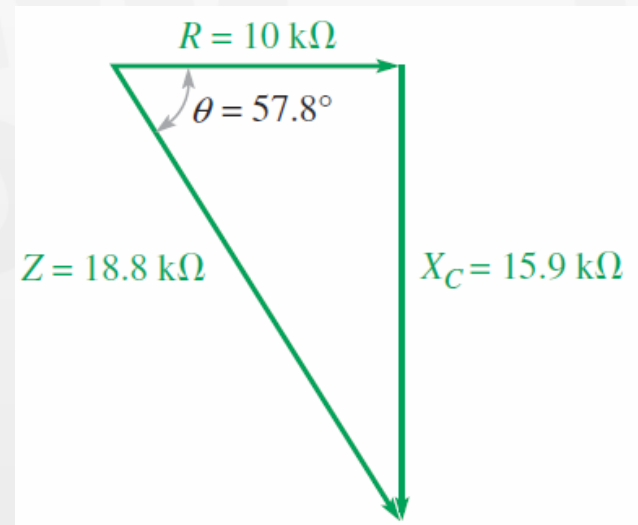- $Z = R + \frac{1}{j\omega C} = R - j\frac{1}{\omega C} = 10^4 - j\frac{1}{2\pi \cdot 10^3 \cdot 10^{-8}} = 10^4 - j(15.9 \cdot 10^3)$
- $Z = A + jB$ $A = 10\text{k}\Omega$ $B = 15.9\text{k}\Omega$
- $Z = \sqrt{A^2 + B^2} = 18.8\text{k}\Omega$
- $\theta = \tan^{-1}\left(\frac{-15.9\text{k}\Omega}{10\text{k}\Omega}\right) = 57.8^\circ$
- $V_S = IZ = 0.2 \cdot 18.8 = 3.76\text{ V}$







Variation of phase angle with frequency

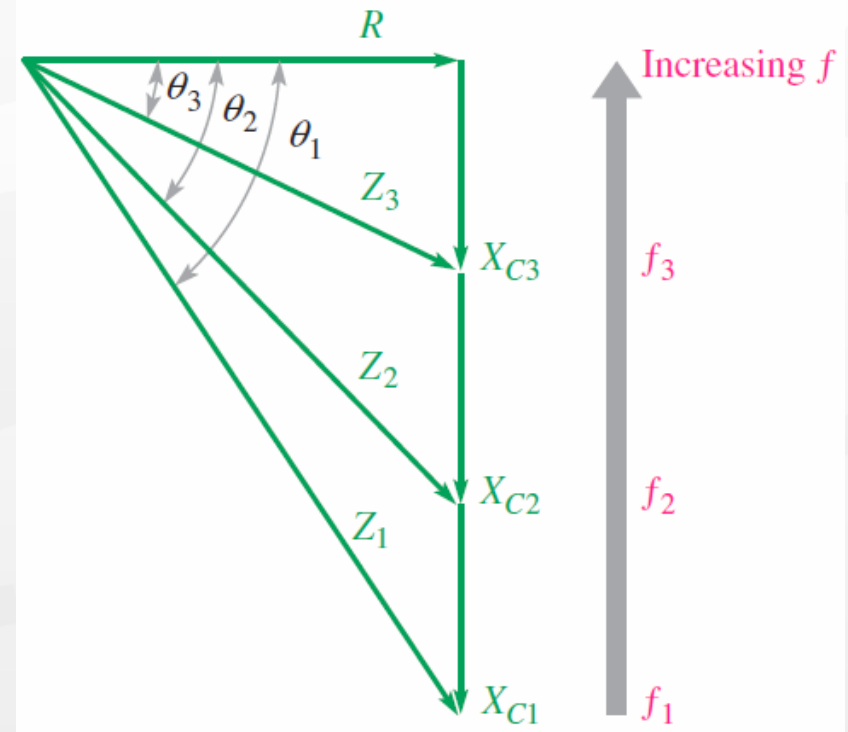- ▶ Phasor diagrams that have reactance phasors can only be drawn for a single frequency because $X_C = \frac{1}{\omega C}$ is a function of frequency.
- ▶ As frequency changes, the impedance triangle for an RC circuit changes as illustrated here because X_C decreases with increasing f . This determines the *frequency response* of RC circuits.




Frequency response

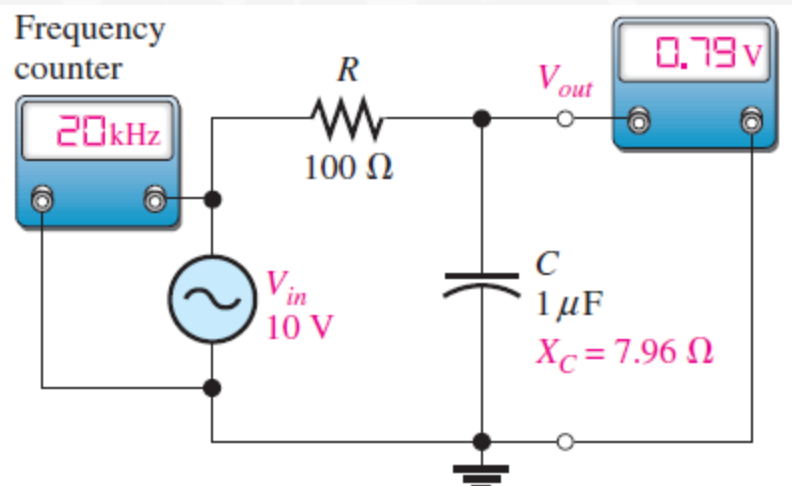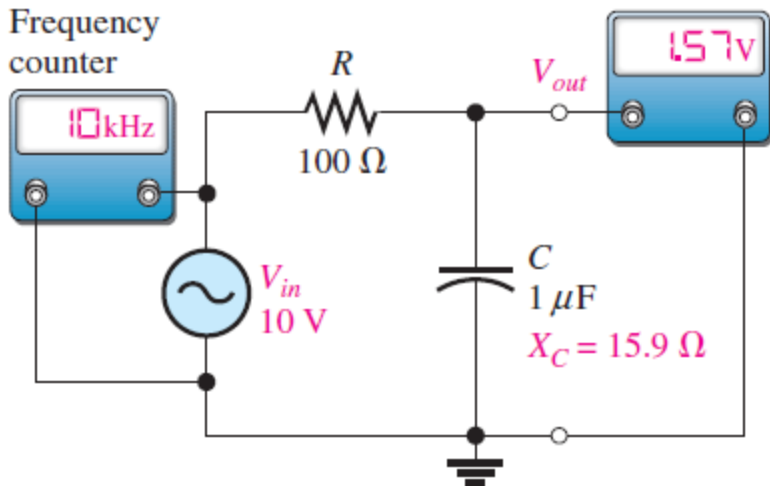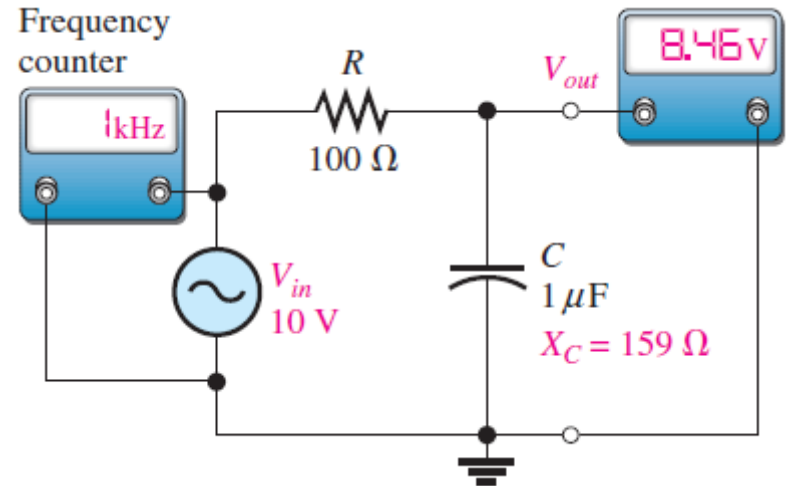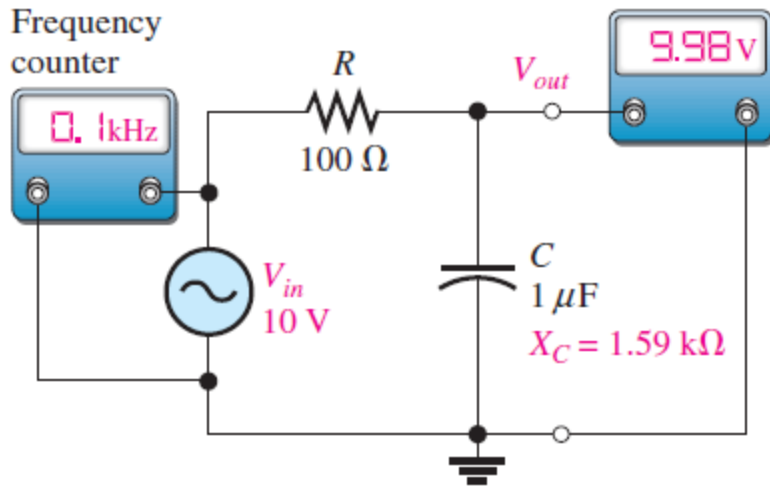

Frequency response

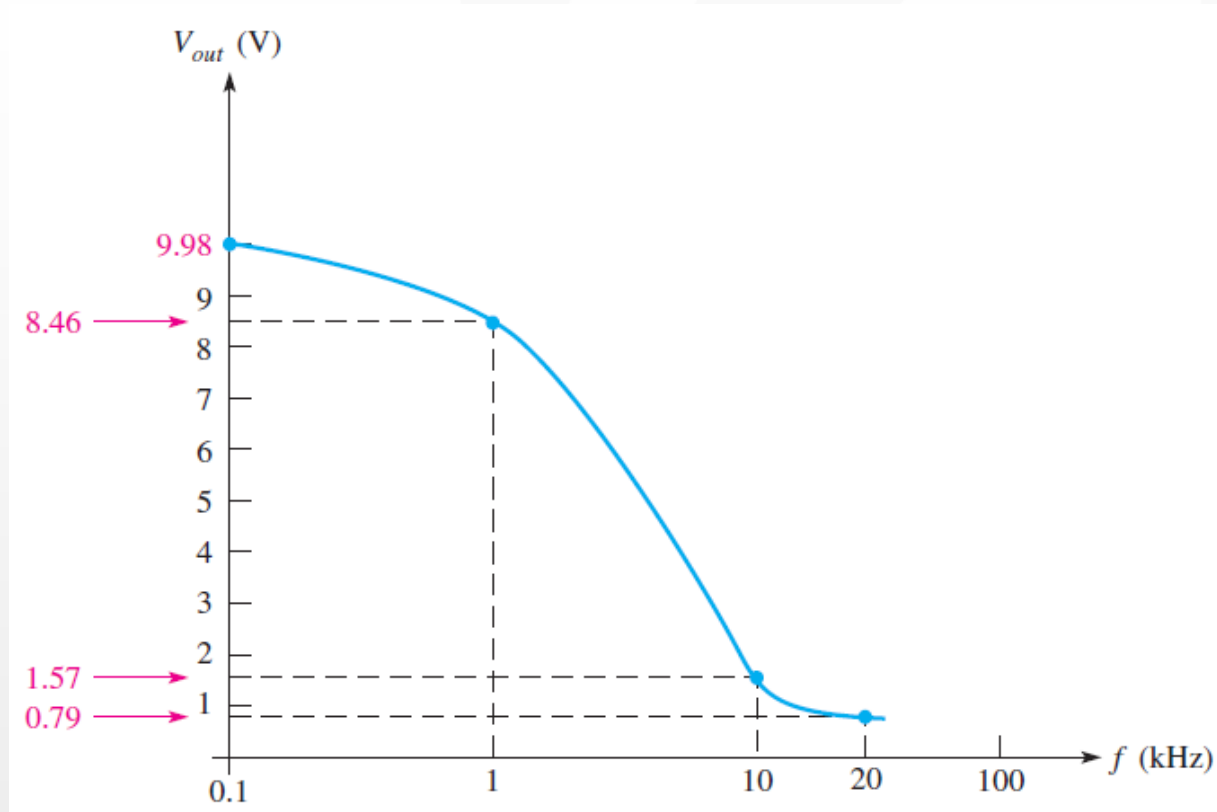
- **Frequency response** of the low-pass RC circuit



Frequency response




Cutoff Frequency

$$f_c = \frac{1}{2\pi RC}$$

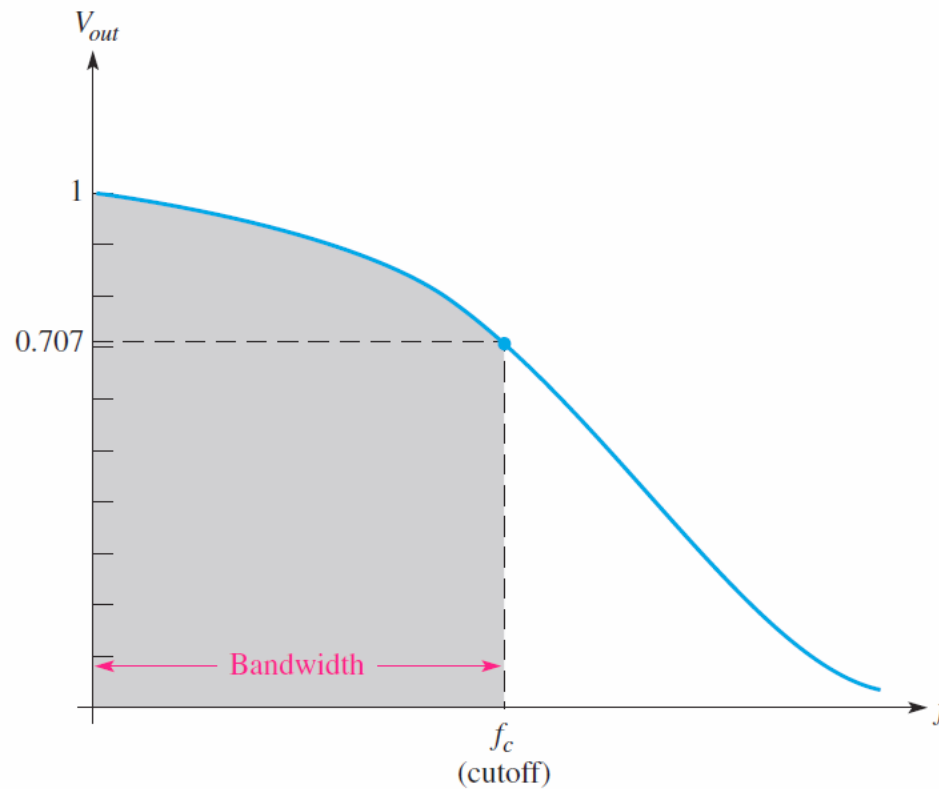


Applications

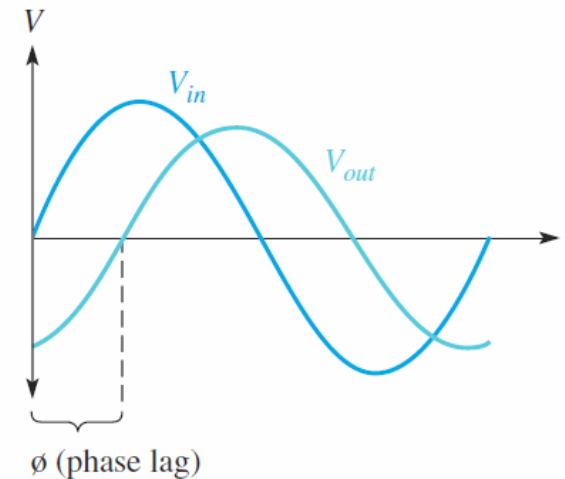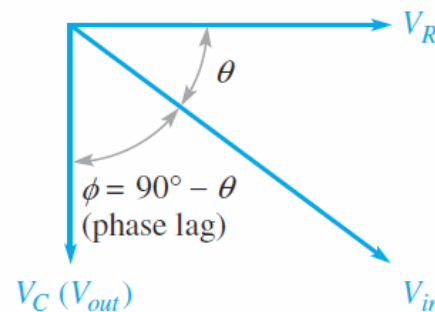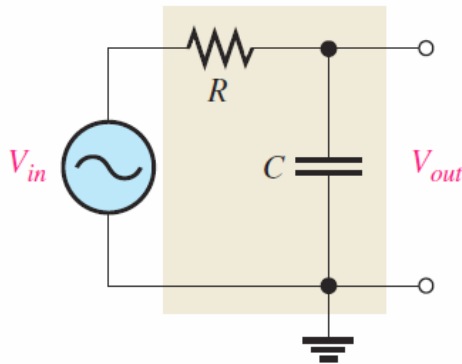
- ▶ For a given frequency, a series RC circuit can be used to produce a phase lag by a specific amount between an input voltage and an output by taking the output across the capacitor. This circuit is also a basic *low-pass filter*, a circuit that passes low frequencies and rejects all others.



Applications

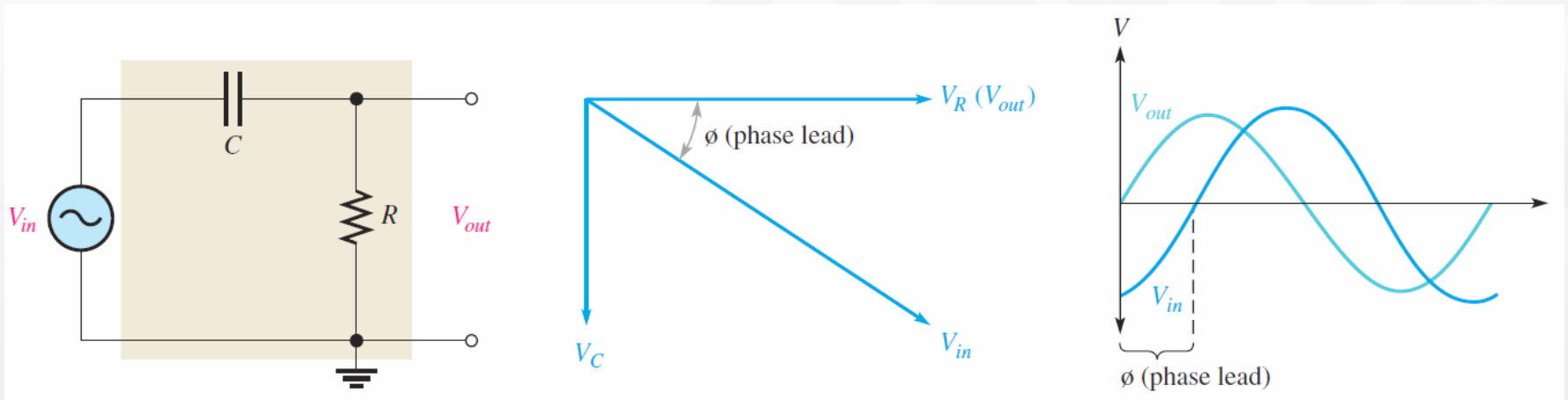- ▶ Reversing the components in the previous circuit produces a circuit that is a basic lead network. This circuit is also a basic *high-pass filter*, a circuit that passes high frequencies and rejects all others. This filter passes high frequencies down to a frequency called the *cutoff* frequency.




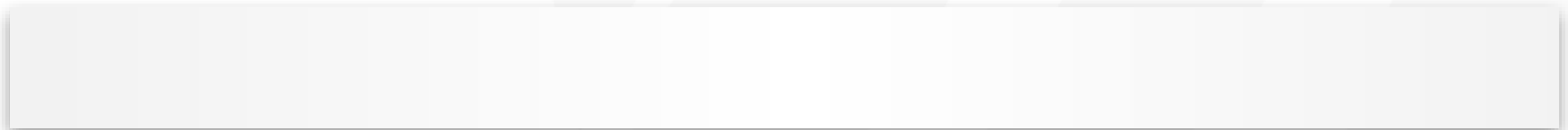

UMASS
LOWELL

RL Circuit

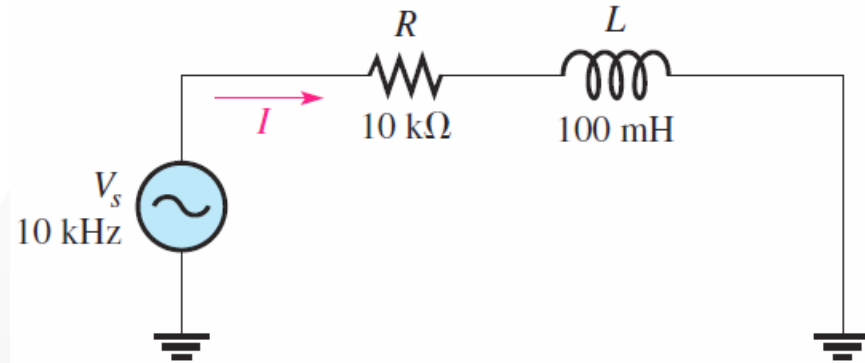- ▶ The current is $200\ \mu\text{A}$.
Determine the source voltage.




- ▶ $2\pi fL = 2\pi(10\ \text{kHz})(100\ \text{mH}) = 6.28\ \text{k}\Omega$
- ▶ The impedance is
- ▶ $|Z| = \sqrt{(10\ \text{k}\Omega)^2 + (6.28\ \text{k}\Omega)^2} = 11.8\ \text{k}\Omega$
- ▶ $\theta = \tan^{-1}\left(\frac{6.28\ \text{k}\Omega}{10\ \text{k}\Omega}\right) = 32.1^\circ$
- ▶ Applying Ohm's law yields
- ▶ $V_S = IZ = (200\ \mu\text{A})(11.8\ \text{k}\Omega) = 2.36\ \text{V}$

Phase Relationships of the Current and Voltages

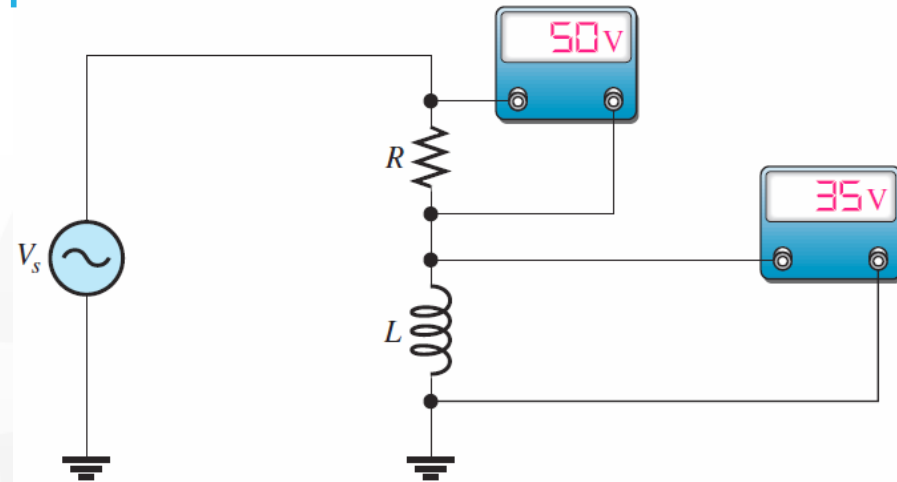
Example

- Determine the source voltage and the phase angle



- The source voltage is the phasor sum of V_R and V_L .
- $V_S = \sqrt{V_R^2 + V_L^2} = \sqrt{50^2 + 35^2} = 61 \text{ V}$
- The phase angle between the resistor voltage and the source voltage is
- $\theta = \tan^{-1} \left(\frac{V_L}{V_R} \right) = \tan^{-1} \left(\frac{35}{50} \right) = 35^\circ$

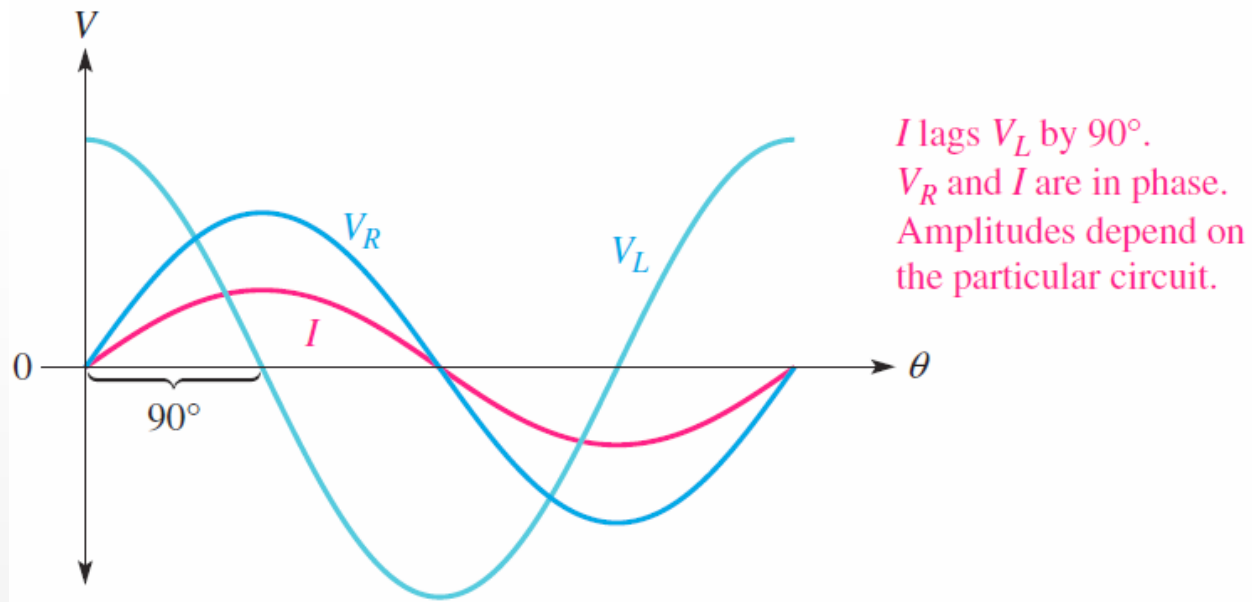Phase Relationships of the Current and Voltages



$$V_S = \sqrt{V_R^2 + V_L^2} \quad \theta = \tan^{-1} \left(\frac{V_L}{V_R} \right)$$

Variation of Impedance and Phase Angle with Frequency

- ▶ Phasor diagrams that have reactance phasors can only be drawn for a single frequency because X is a function of frequency.
- ▶ As frequency changes, the impedance triangle for an RL circuit changes as illustrated here because $j\omega L$ increases with increasing f .
- ▶ This determines the *frequency response* of RL circuits.

