

Chapter 4: Series circuits

Instructor: Jean-François MILLITHALER


http://faculty.uml.edu/JeanFrancois_Millithaler/FunElec/Spring2017

Resistors in series

Attributes

► Three common attributes

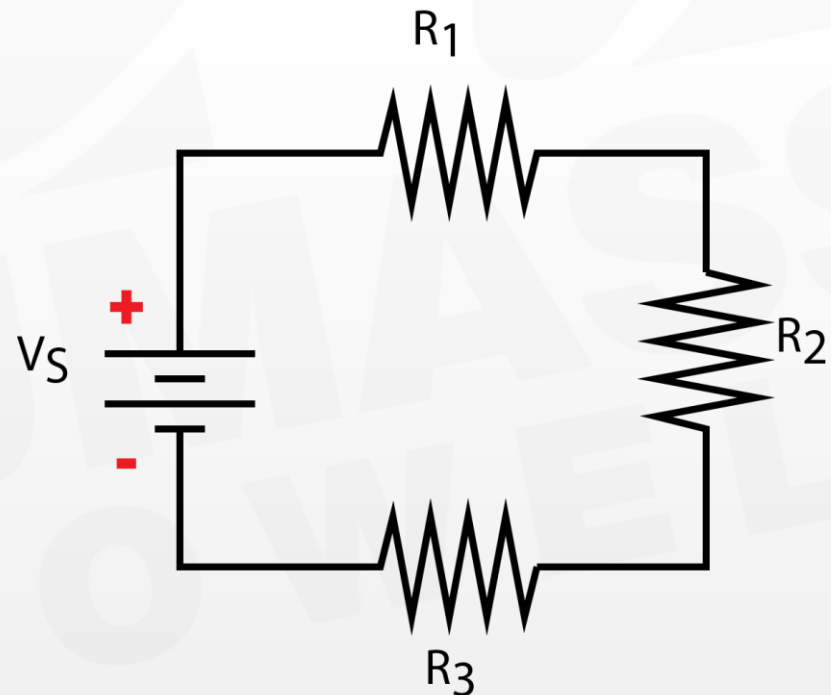
1. A source of voltage
2. A load
3. A complete path



Resistors in series

One path

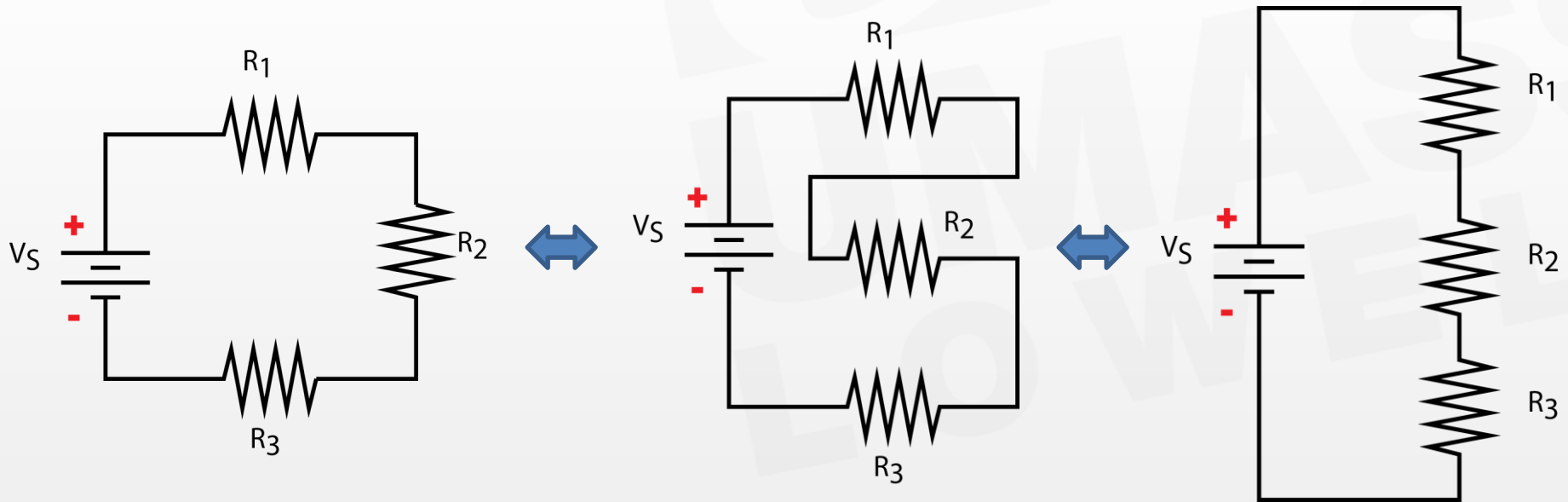- ▶ A **series circuit** is one that has **only one current path**




Resistors in series

Rule for current

Because there is only one path, the current everywhere is **the same**

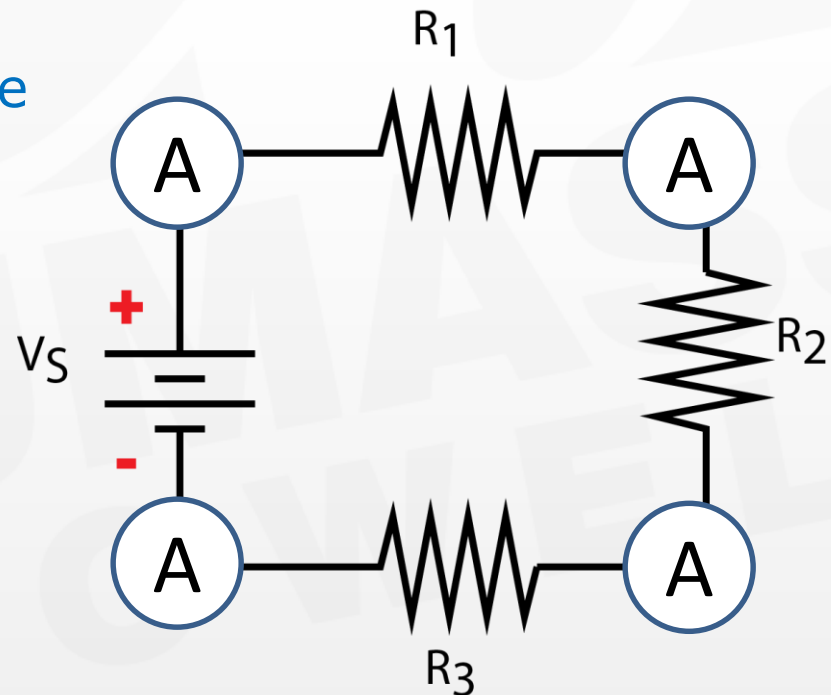An ammeter placed anywhere will give the **same value**




Resistors in series

Total resistance

The total resistance of resistors in series is **the sum of the individual resistors**


$$R_T = \sum_i R_i$$

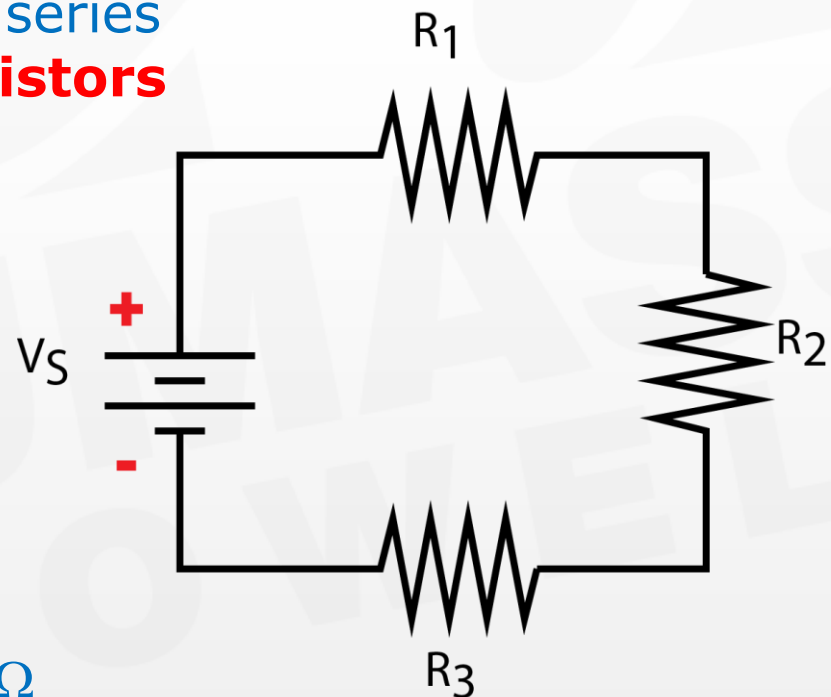

Ex: $R_1 = 550\Omega$, $R_2 = 1.5\text{k}\Omega$, $R_3 = 2.2\text{k}\Omega$

$R_T = ?$


Resistors in series

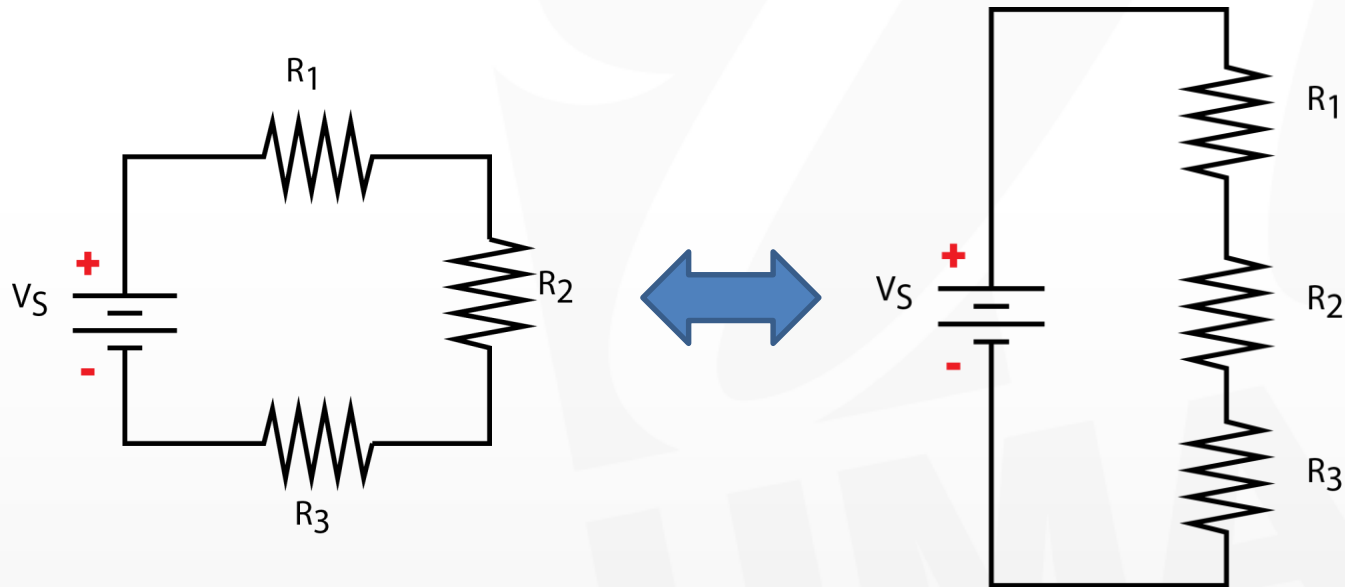

These two circuits are exactly the same

The 2nd can be easier for visualization and to make calculations

Resistors in series

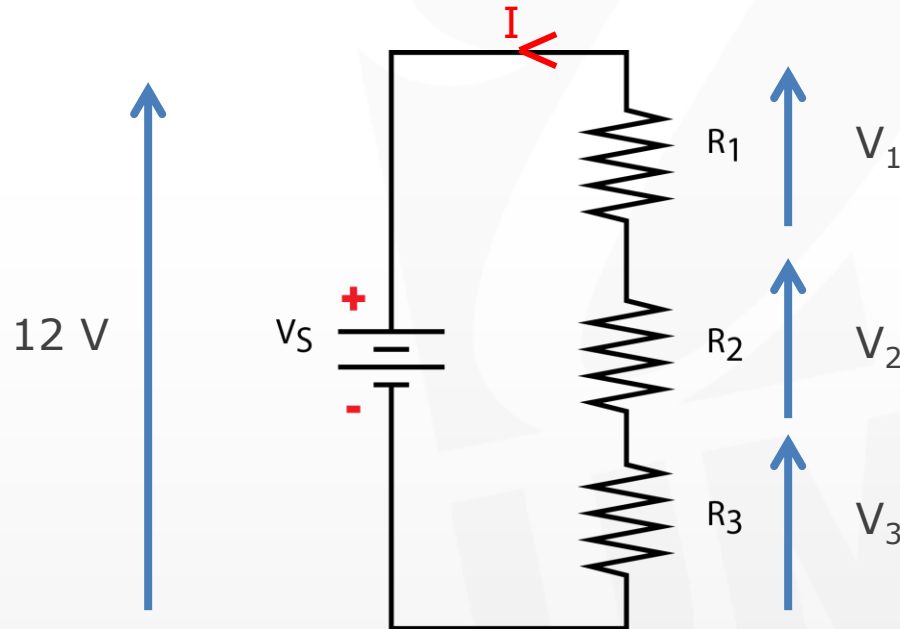

$$R_1 = 500\Omega, R_2 = 1.3\text{k}\Omega, R_3 = 2.2\text{k}\Omega$$

$$R_T =$$


Using Ohm's law, the current is:

$$I =$$

What are V_1 , V_2 and V_3 ?

Resistors in series

Current	Resistance	Voltage	Power
$I =$	$R_1 = 500 \Omega$	$V_1 =$	$P_1 =$
$I =$	$R_2 = 1.3 \text{ k}\Omega$	$V_2 =$	$P_1 =$
$I =$	$R_3 = 2.2 \text{ k}\Omega$	$V_3 =$	$P_1 =$
$I = 3 \text{ mA}$	$R_T =$	$V_T = 12 \text{ V}$	$P_T =$

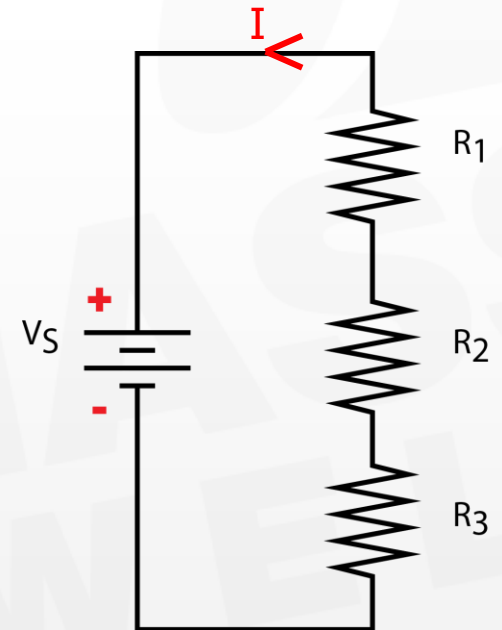

Kirchhoff's voltage law

Kirchhoff's voltage law (KVL):




The sum of all voltage drops around a single closed path in a circuit is equal to the total source voltage in that closed path.

KVL applies to all circuits, but you must apply it to only one closed path. In a series circuit, this is (of course) the entire circuit

A mathematical shorthand way of writing KVL is


$$\sum_{i=1}^n V_i = 0$$

Voltage sources in series

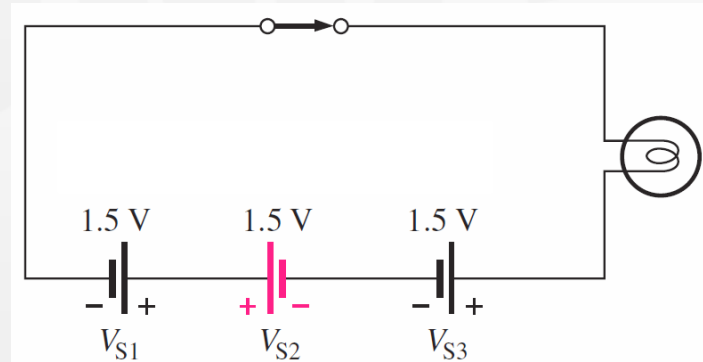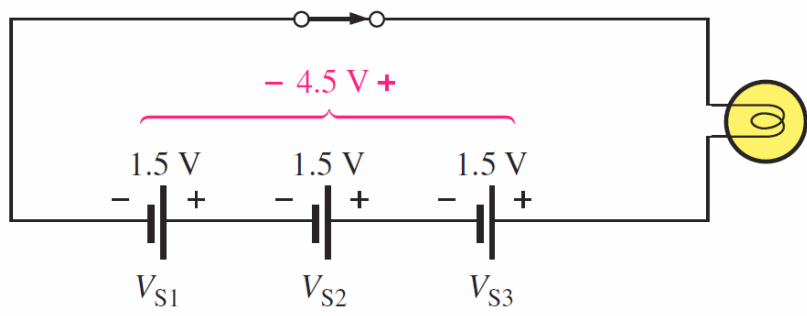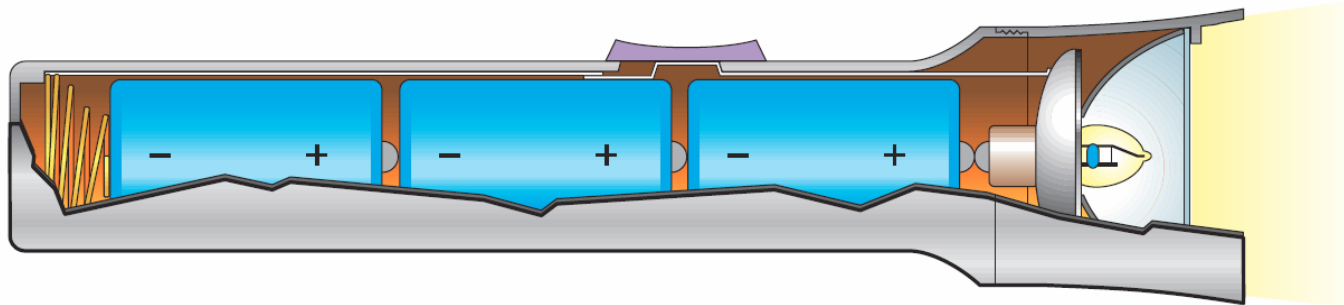

Kirchhoff's voltage law

Current	Resistance	Voltage	Power
$I = 3 \text{ mA}$	$R_1 = 500 \ \Omega$	$V_1 = 1.5 \text{ V}$	$P_1 = 4.5 \text{ mW}$
$I = 3 \text{ mA}$	$R_2 = 1.3 \text{ k}\Omega$	$V_2 = 3.9 \text{ V}$	$P_1 = 11.7 \text{ mW}$
$I = 3 \text{ mA}$	$R_3 = 2.2 \text{ k}\Omega$	$V_3 = 6.6 \text{ V}$	$P_1 = 19.8 \text{ mW}$
$I = 3 \text{ mA}$	$R_T = 4 \text{ k}\Omega$	$V_T = 12 \text{ V}$	$P_T = 36 \text{ mW}$

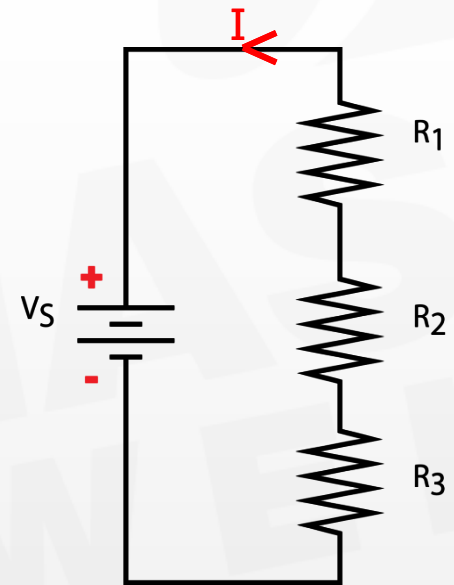

The sum of all resistor voltages is equal to the source voltage

$$\sum_{i=1}^n V_i = V_1 + V_2 + V_3 - V_T = 0$$

Voltage divider rule


The voltage drop across any given resistor in a series circuit is equal to the ratio of that resistor to the total resistance, multiplied by source voltage

$$V_i = \frac{R_i}{R_T} V_S$$

Q 1: If R_1 is twice R_2 ,
What is the voltage across R_2 ?

Q2: If $R_1 = R_2$,
What is the voltage across R_2 ?

What is the power dissipated ?

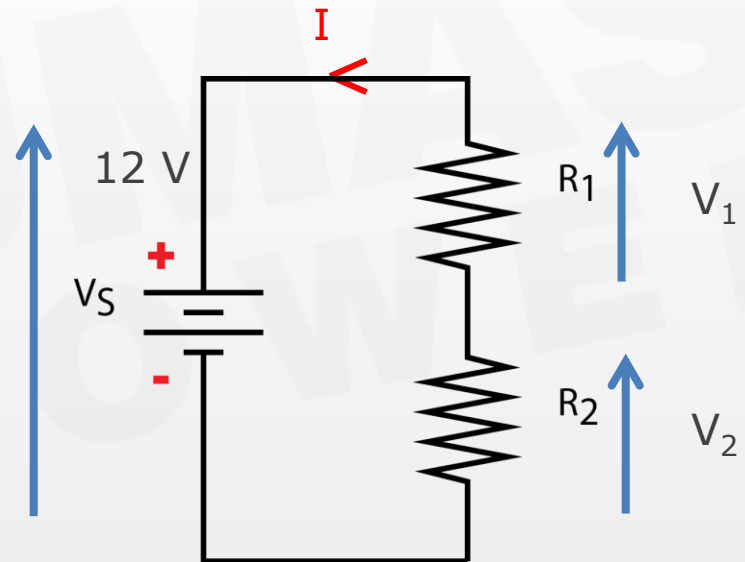

Voltage measurements

Voltage is relative and is measured with respect to another point in the circuit.

Voltages that are given with respect to ground are shown with a single subscript.

V_A means the voltage at point A with respect to ground (reference ground)

V_B means the voltage at point B with respect to ground


V_{AB} means the voltage between points A and B

With $V_S=12V$, $R_1=5k\Omega$ and $R_2=10k\Omega$

$V_A =$

$V_B =$

$V_{AB} =$

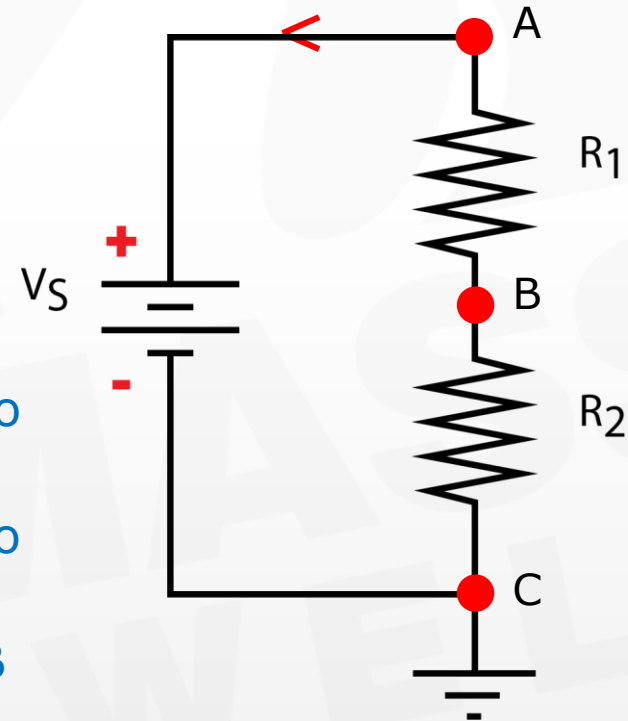

Voltage measurements

Ground reference is not always at the lowest point in a circuit. Assume the ground is moved to B as shown.

With $V_S=12V$, $R_1=5k\Omega$ and $R_2=10k\Omega$

$V_A =$

$V_B =$

$V_C =$

Did V_{AB} changed from previous circuit ?

