


Chapter 5: Parallel circuits

Instructor: Jean-François MILLITHALER

http://faculty.uml.edu/JeanFrancois_Millithaler/FunElec/Spring2017


Resistors in parallel

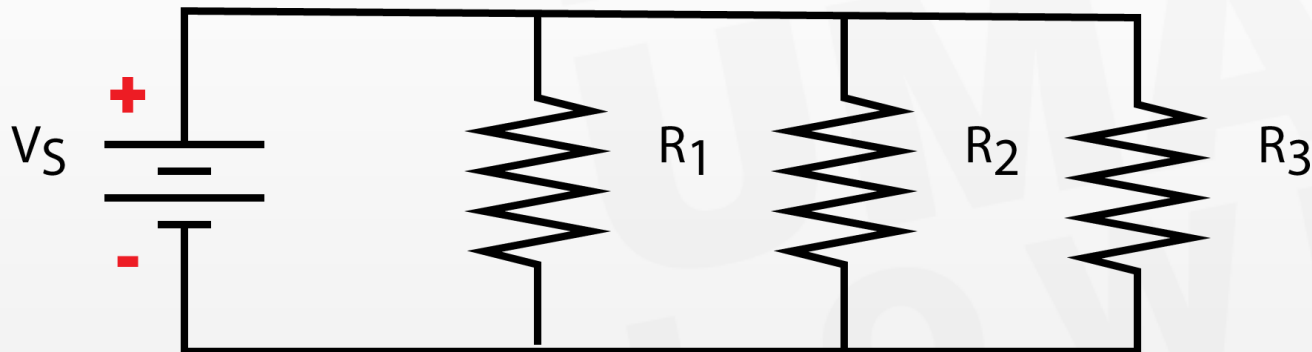- ▶ Resistors that are connected to the same two points are said to be in **parallel**.




Resistors in parallel

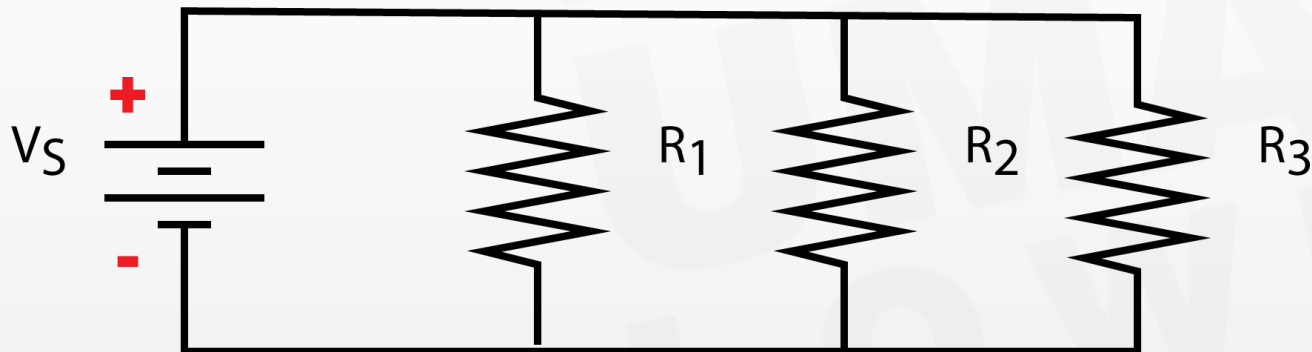- ▶ A **parallel circuit** is identified by the fact that it has more than one current path (branch) connected to a common voltage source.




Resistors in parallel

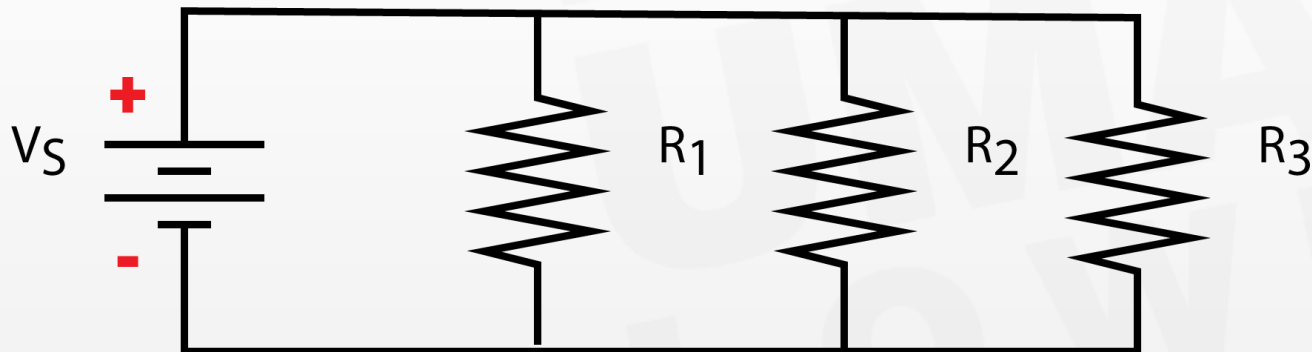- ▶ Because all components are connected across the same voltage source, the voltage across each is **the same**.




Parallel circuit

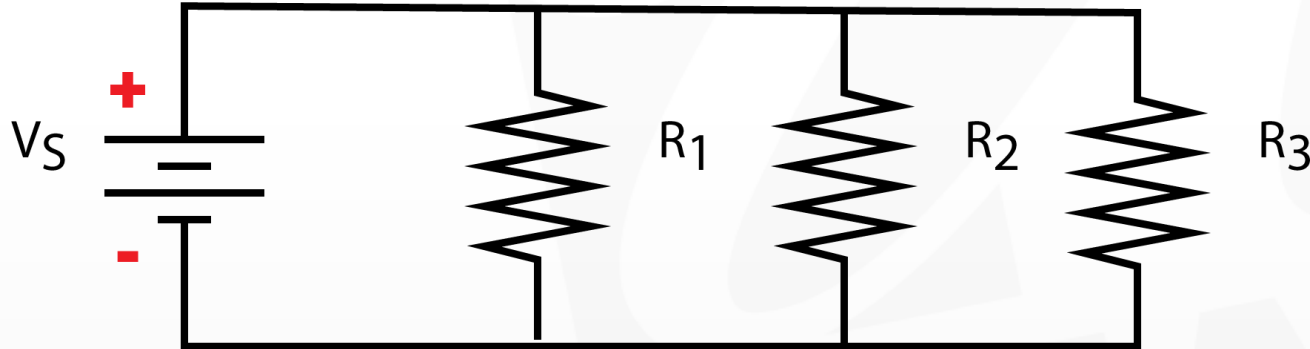


Voltage	Resistance	Current	Power
$V_1=5.0\text{ V}$	$R_1=680\ \Omega$	$I_1=$	$P_1=$
$V_2=5.0\text{ V}$	$R_2=1.5\text{ k}\Omega$	$I_2=$	$P_2=$
$V_3=5.0\text{ V}$	$R_3=2.2\text{ k}\Omega$	$I_3=$	$P_3=$
$V_T=5.0\text{ V}$	$R_T=$	$I_T=$	$P_T=$

Is there a problem?

Rule for resistances

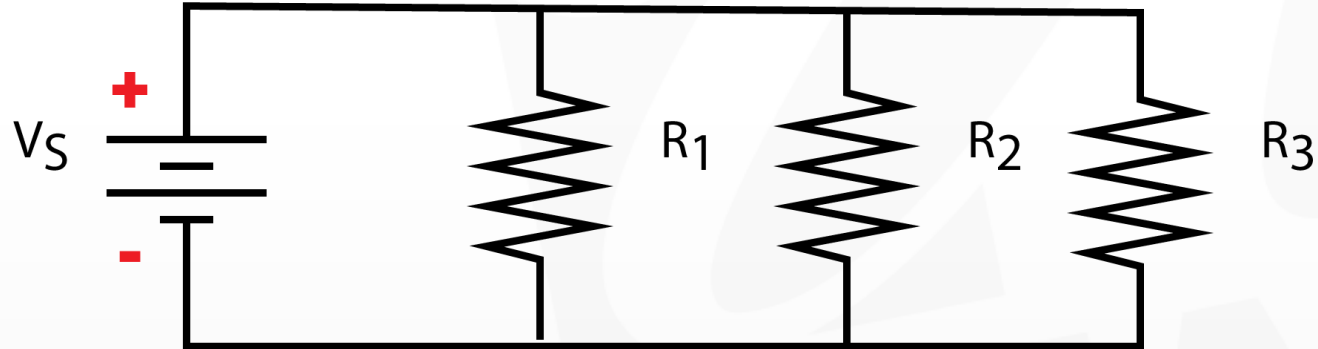


► Equivalent system

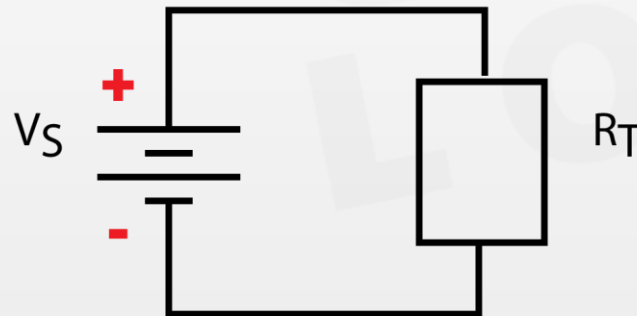

Rule for resistances

- ▶ 2 resistance in parallel
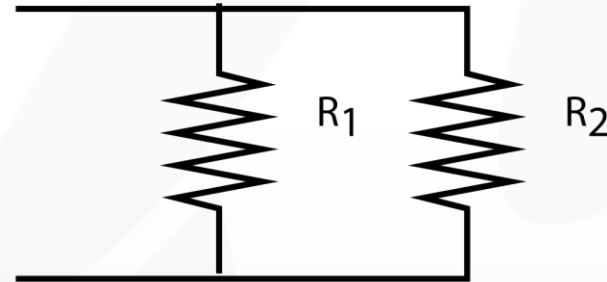
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$



$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

General equation

$$\frac{1}{R_T} = \sum_I \frac{1}{R_I}$$

- ▶ What is the total resistance if $R_1=27\text{k}\Omega$ and $R_2=56\text{ k}\Omega$?


Kirchhoff's current law

Gustav Robert Kirchhoff, German physicist, 1824-1887

- ▶ Kirchhoff's current law (KCL) is generally stated as:
- ▶ The sum of the currents entering a node is equal to the sum of the currents leaving the node.

Voltage	Resistance	Current	Power
$V_1 = 5.0 \text{ V}$	$R_1 = 680 \Omega$	$I_1 = 7.4 \text{ mA}$	$P_1 = 36.8 \text{ mW}$
$V_2 = 5.0 \text{ V}$	$R_2 = 1.5 \text{ k}\Omega$	$I_2 = 3.3 \text{ mA}$	$P_2 = 16.7 \text{ mW}$
$V_3 = 5.0 \text{ V}$	$R_3 = 2.2 \text{ k}\Omega$	$I_3 = 2.3 \text{ mA}$	$P_3 = 11.4 \text{ mW}$
$V_T = 5.0 \text{ V}$	$R_T = 386 \Omega$	$I_T = 13.0 \text{ mA}$	$P_T = 64.8 \text{ mW}$

Kirchhoff's current law

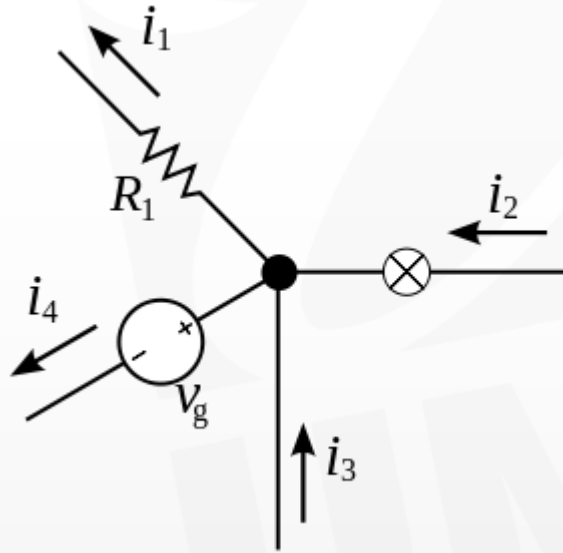

- ▶ The current entering any junction is equal to the current leaving that junction. $i_2 + i_3 = i_1 + i_4$

$$\sum_{k=1}^n I_k = 0$$

Current divider

- ▶ When current enters a node (junction) it divides into currents with values that are inversely proportional to the resistance values.
- ▶ The most widely used formula for the current divider is the two-resistor equation. For resistors R_1 and R_2 ,

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I_T \qquad I_2 = \left(\frac{R_1}{R_1 + R_2} \right) I_T$$

- ▶ Notice the subscripts. The resistor in the numerator is not the same as the one for which current is found.

Current divider

- ▶ Assume that R_1 is a 2.2 k Ω resistor that is in parallel with R_2 , which is 4.7 k Ω . If the total current into the resistors is 8.0 mA, what is the current in each resistor?

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I_T =$$

$$I_2 = \left(\frac{R_1}{R_1 + R_2} \right) I_T =$$

- ▶ Notice that the larger resistor has the smaller current.

Power in parallel circuits

- ▶ Power in each resistor can be calculated with any of the standard power formulas. Most of the time, the voltage is known, so the equation $P = \frac{V^2}{R}$ is most convenient.
- ▶ As in the series case, the total power is the sum of the powers dissipated in each resistor.
- ▶ What is the total power if 10 V is applied to the parallel combination of $R_1 = 270 \Omega$ and $R_2 = 150 \Omega$?

Exercise

- ▶ Assume there are 8 resistive wires that form a rear window defroster for an automobile.
- ▶ If the defroster dissipates 90 W when connected to a 12.6 V source, what power is dissipated by each resistive wire?
- ▶ What is the total resistance of the defroster?