

Chapter 6: Series-Parallel Circuits

Instructor: Jean-François MILLITHALER

http://faculty.uml.edu/JeanFrancois_Millithaler/FunElec/Spring2017





Identifying series-parallel relationships

- ▶ Most practical circuits have combinations of series and parallel components.
- ▶ Components that are connected in series will share a common path.
- ▶ Components that are connected in parallel will be connected across the same two nodes.




Combination circuits

- ▶ Most practical circuits have various combinations of series and parallel components. You can frequently simplify analysis by combining series and parallel components.
- ▶ An important analysis method is to form an **equivalent circuit**.
- ▶ An equivalent circuit is one that **has characteristics that are electrically the same as another circuit but is generally simpler.**

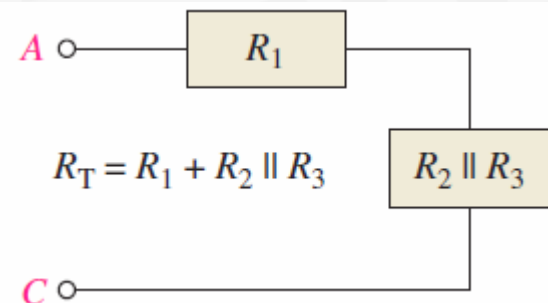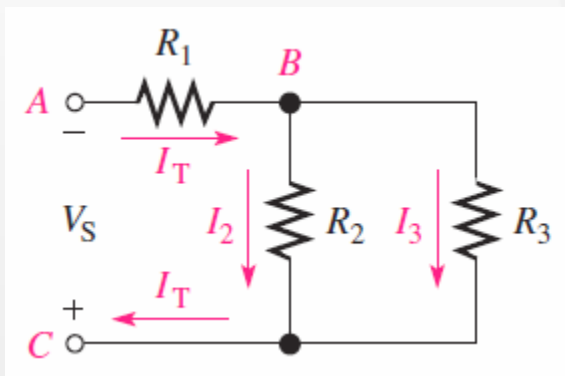
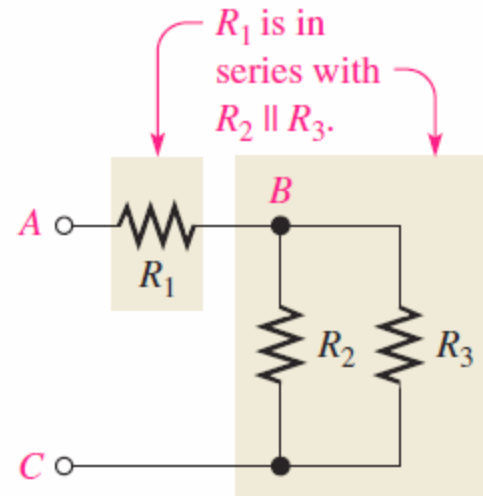
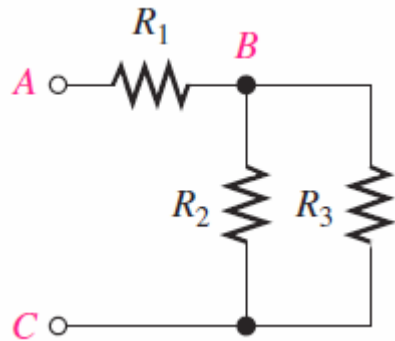
Identifying series-parallel relationships



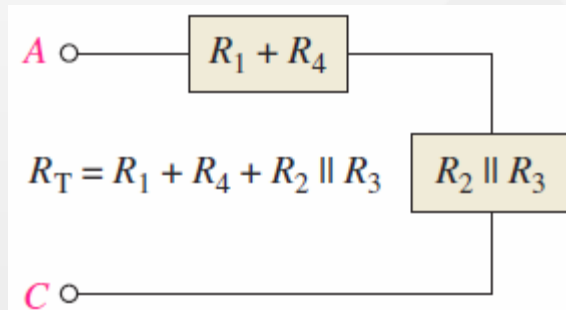
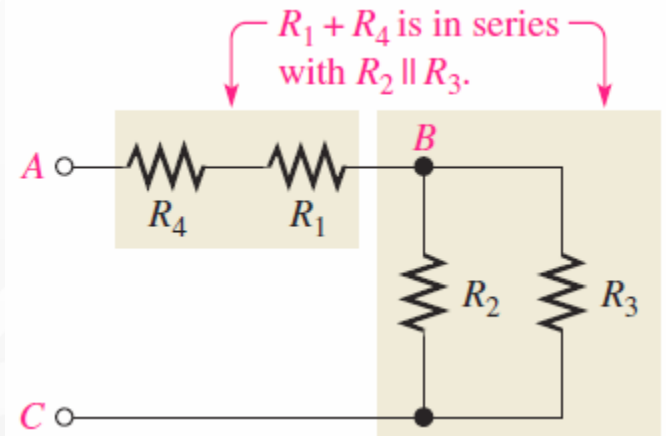
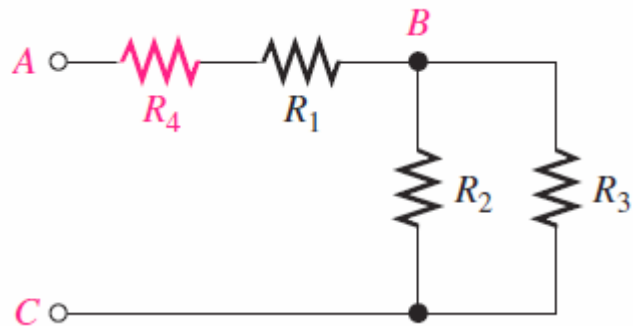
Identifying series-parallel relationships



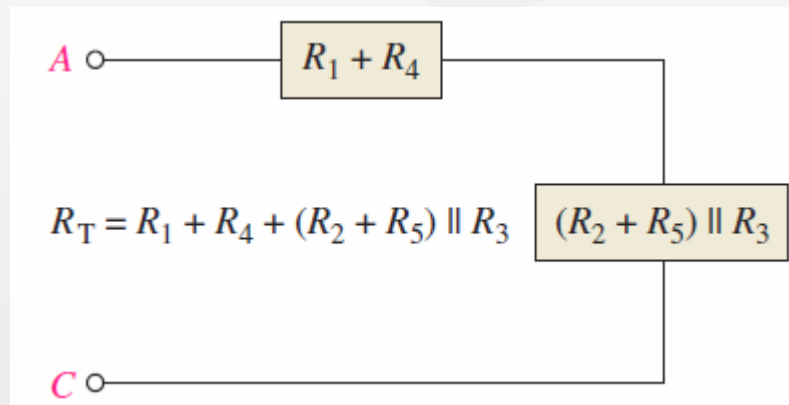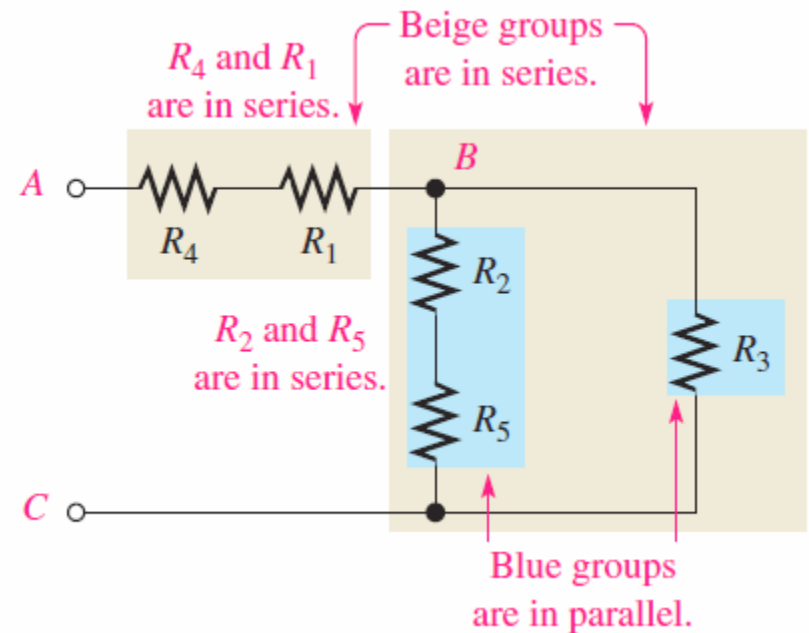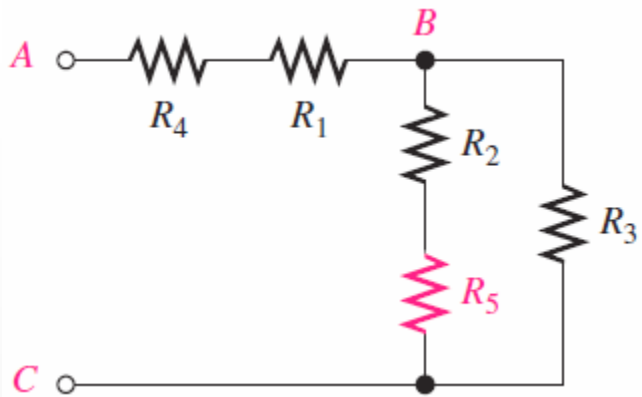
Identifying series-parallel relationships



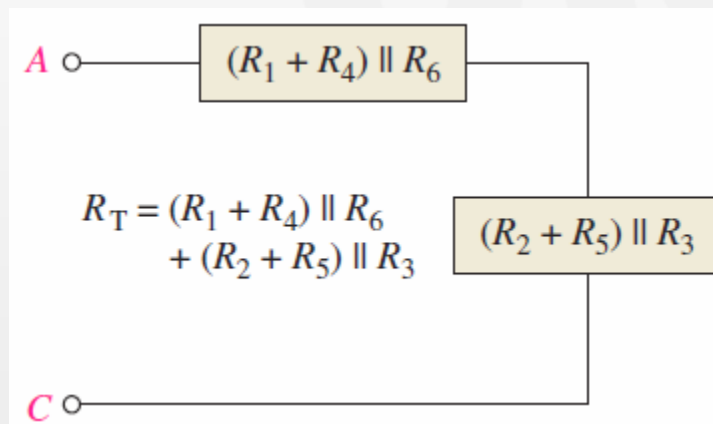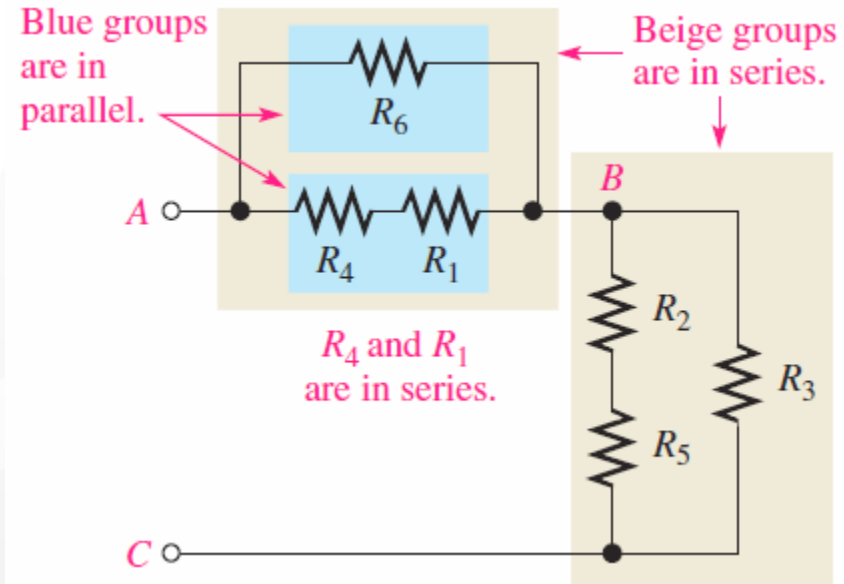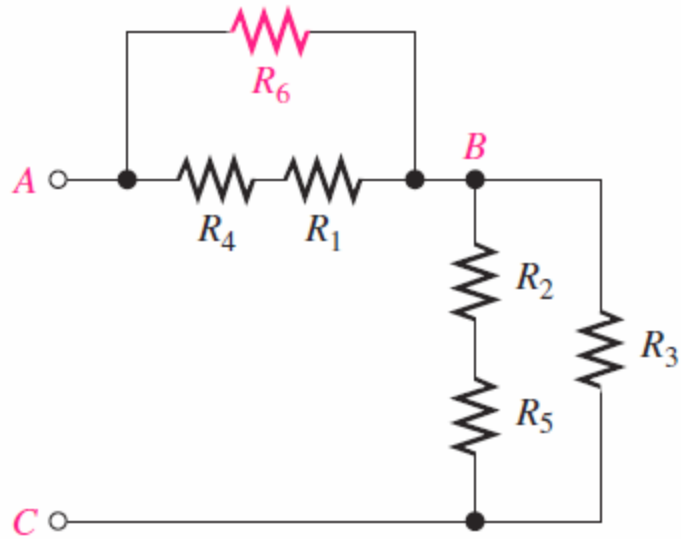
Identifying series-parallel relationships



Examples

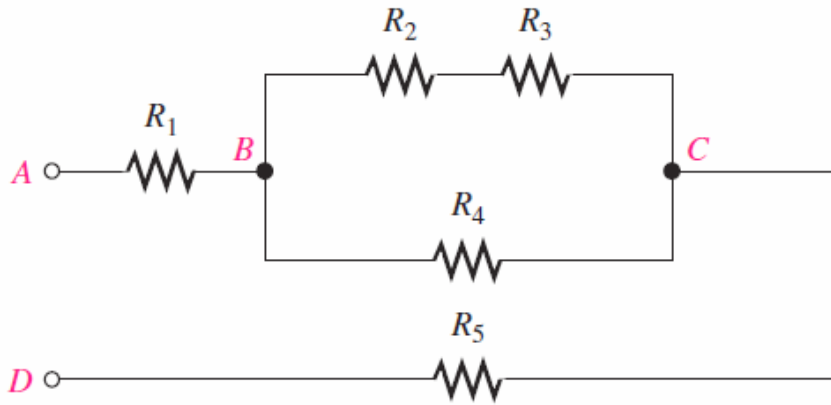

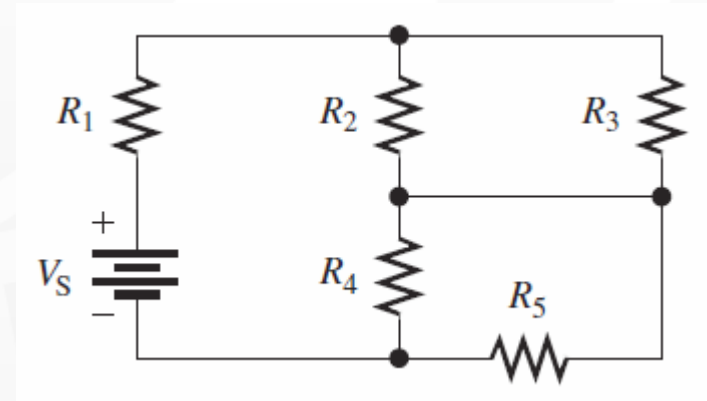
$$R_T = R_1 + R_5 + R_4 \parallel (R_2 + R_3)$$



$$R_T = R_1 + R_2 \parallel R_3 + R_4 \parallel R_5$$


Total resistance

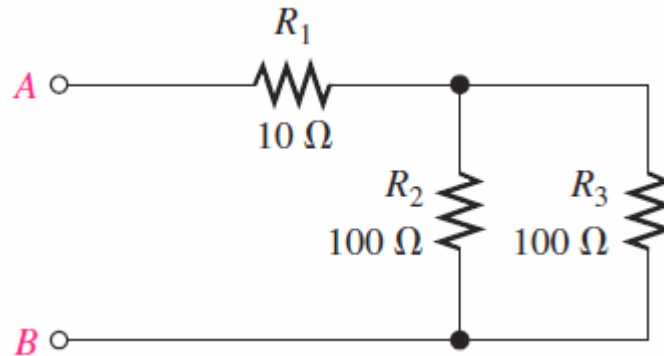

- Identifying the components


- Total resistance $R_T = R_1 + R_2 || R_3 = 10 + 50 = 60 \Omega$

Example

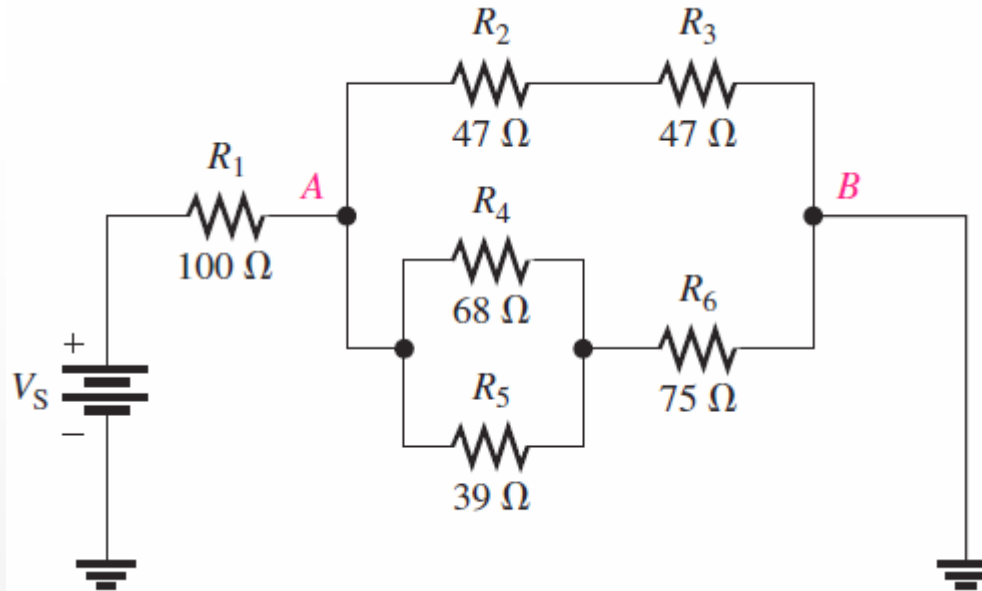


- Find $R_T = 148\ \Omega$

Total Current

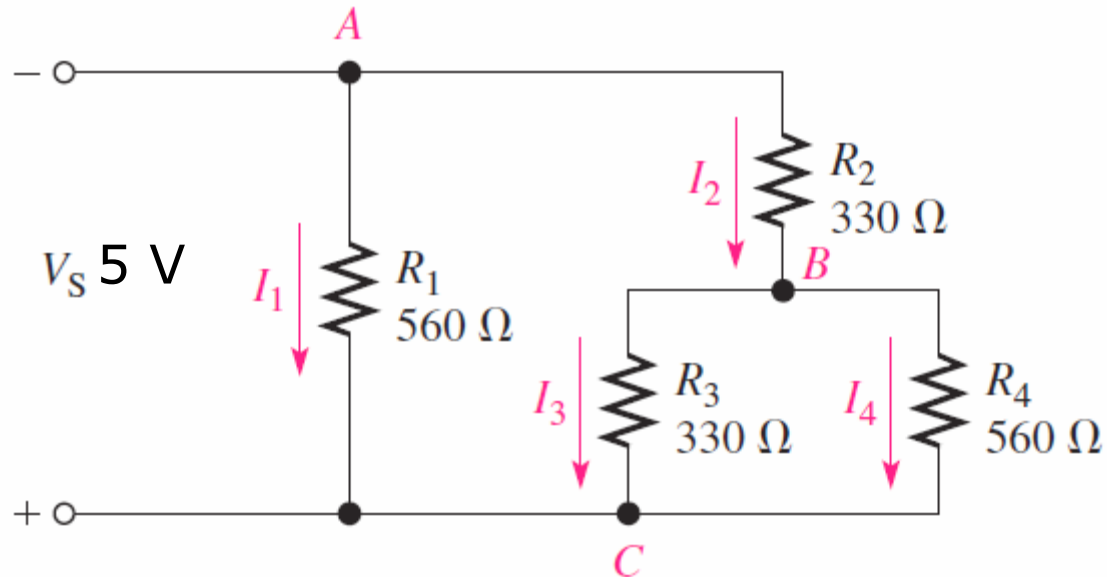

- Ohm's law: $I_T = \frac{V_S}{R_T}$
- Find $I_4 = 3.45 \text{ mA}$ ($I_2 = 9.29 \text{ mA}$)

Voltage Relationships

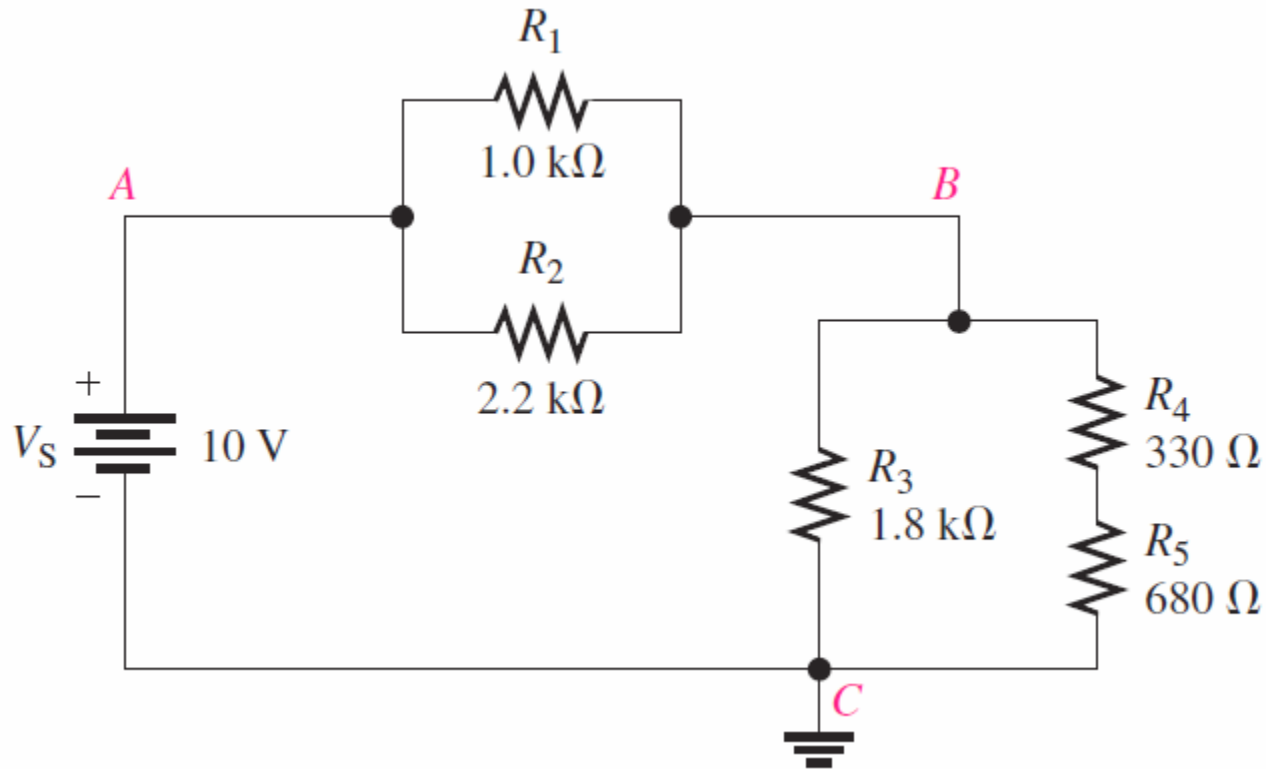

► Find R_{AB} , R_{BC} & R_T


► Find V_1 , V_2 , V_3 , V_4 , and V_5

$$V_1 = V_2 = 5.15 \text{ V}$$

$$V_3 = 4.85 \text{ V}$$

$$V_4 = 1.58 \text{ V}$$


$$V_5 = 3.27 \text{ V}$$

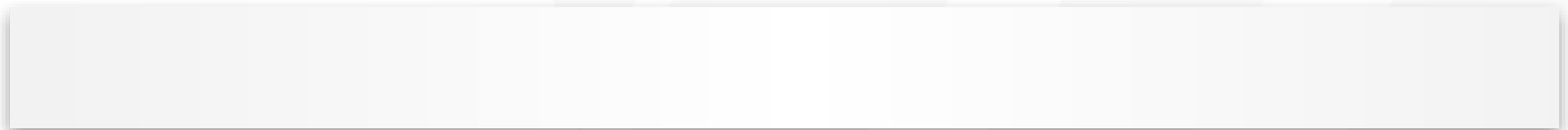

UMASS
LOWELL

THE WHEATSTONE BRIDGE

Sir Charles Wheatstone, 1802-1875

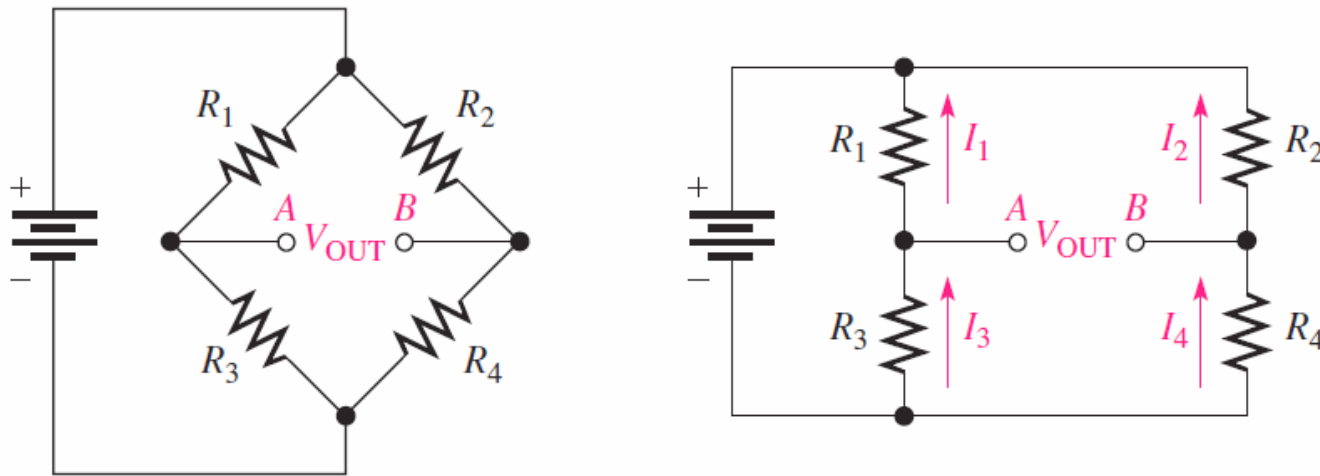

- ▶ Used to precisely measure resistance
- ▶ Used also in conjunction with transducers
- ▶ **Transducer = sensor.**
Change physical parameter in resistance, for example.

THE WHEATSTONE BRIDGE

The balanced bridge

- ▶ Balanced bridge when the output
 $V_{\text{OUT}} = 0\text{V}$


- ▶ We have then $V_1 = V_2$ and $V_3 = V_4$

- ▶ Therefore $\frac{V_1}{V_3} = \frac{V_2}{V_4}$ and $\frac{I_1 R_1}{I_3 R_3} = \frac{I_2 R_2}{I_4 R_4}$

- ▶ Since $I_1 = I_3$ and $I_2 = I_4$

- ▶ We got $\frac{R_1}{R_3} = \frac{R_2}{R_4}$ and finally $R_1 = R_3 \frac{R_2}{R_4}$

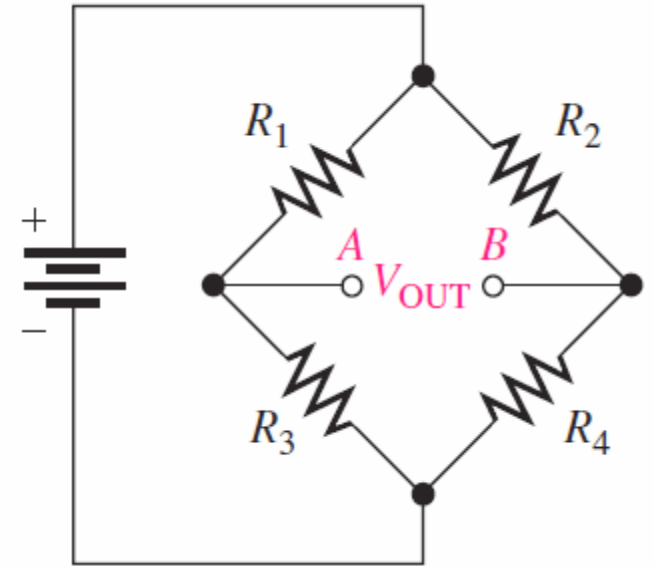- ▶ **Bridge to find an unknown resistance**




THE WHEATSTONE BRIDGE

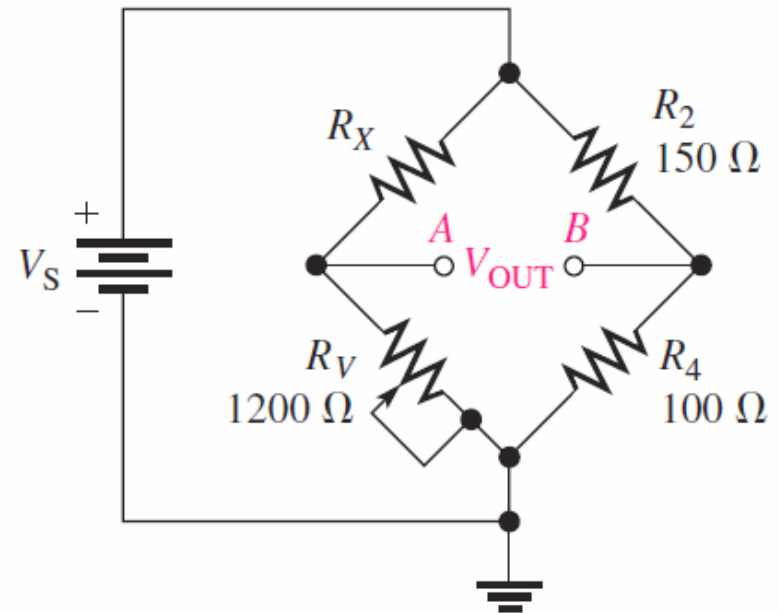Example

Determine the value of R_X .
The bridge is balanced ($V_{OUT} = 0 \text{ V}$)
when R_V is set at 1200Ω


$$R_X = R_V \frac{R_2}{R_4} = 1200 * \frac{150}{100} = 1800 \Omega$$



THE WHEATSTONE BRIDGE

The unbalanced bridge


- ▶ Unbalanced bridge when the output $V_{OUT} \neq 0V$
- ▶ Used to measure several types of physical quantities such as mechanical strain, temperature, or pressure.
- ▶ Connecting the transducer in one leg of the bridge.
- ▶ The resistance of the transducer changes proportionally to the changes in the parameter that it is measuring.
- ▶ If the bridge is balanced at a known point, then the amount of deviation indicates the amount of change in the parameter being measured.
- ▶ Therefore, the value of the parameter being measured can be determined by the amount that the bridge is unbalanced

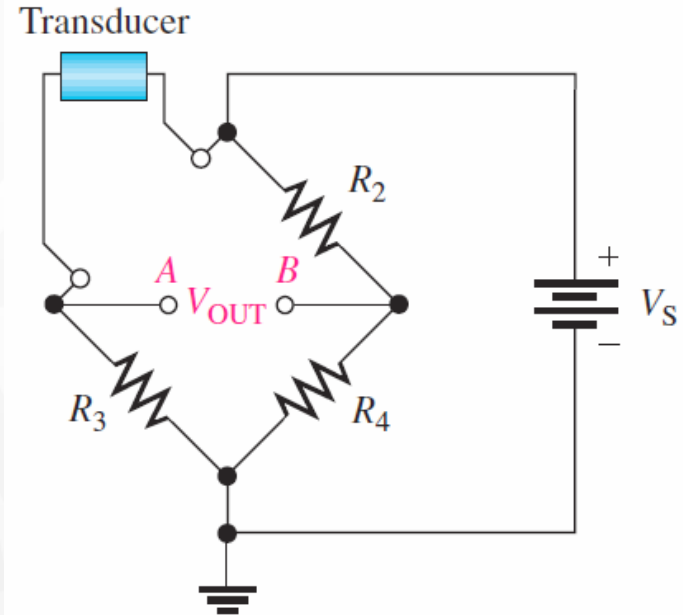


THE WHEATSTONE BRIDGE

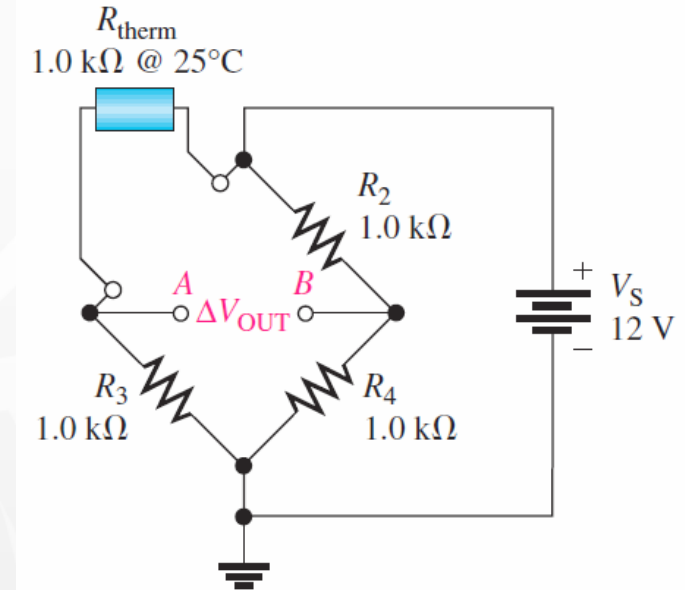Example

- ▶ Determine the output voltage of the temperature-measuring bridge circuit if the thermistor is exposed to a temperature of 50°C and its resistance at 25°C is 1.0 kΩ.
- ▶ Assume the resistance of the thermistor decreases to 900 Ω at 50°C.
- ▶ At 25°C the bridge is balanced.
- ▶ At 50°C the bridge is unbalanced. We can apply the voltage-divider formula to the left and right sides.
- ▶
$$V_A = \left(\frac{R_3}{R_3 + R_{therm}} \right) V_S = \left(\frac{1k\Omega}{1k\Omega + 900\Omega} \right) 12 V = 6.32 V$$
- ▶
$$V_B = \left(\frac{R_4}{R_2 + R_4} \right) V_S = \left(\frac{1k\Omega}{2k\Omega} \right) 12 V = 6. V$$
- ▶
$$V_{OUT} = V_A - V_B = 6.32 - 6 = 0.32 V \text{ at } 50^\circ C$$



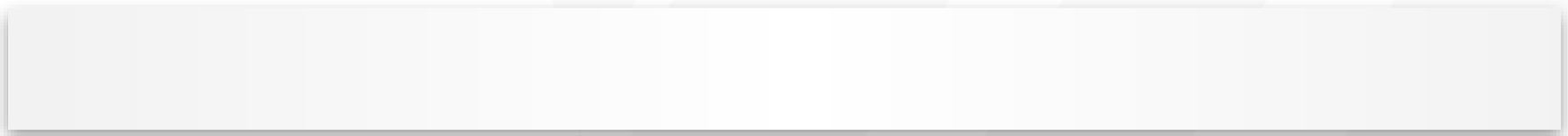


UMASS
LOWELL

THEVENIN's Theorem



Léon Charles Thévenin, French Engineer, 1857-1926

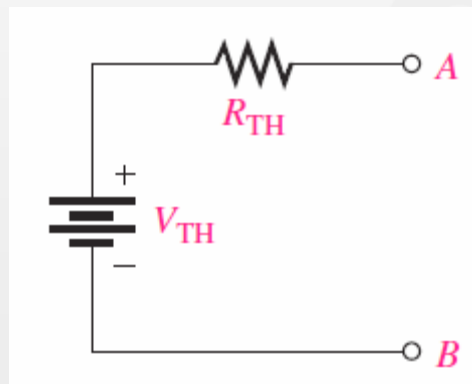- ▶ What for ?
- ▶ To simplify Electric Engineer's Life !!!
- ▶ Simplify a complicate series-parallel circuit into an equivalent circuit
- ▶ Consists of an equivalent voltage source V_{TH}
- ▶ And an equivalent resistance R_{TH}




THEVENIN's Theorem

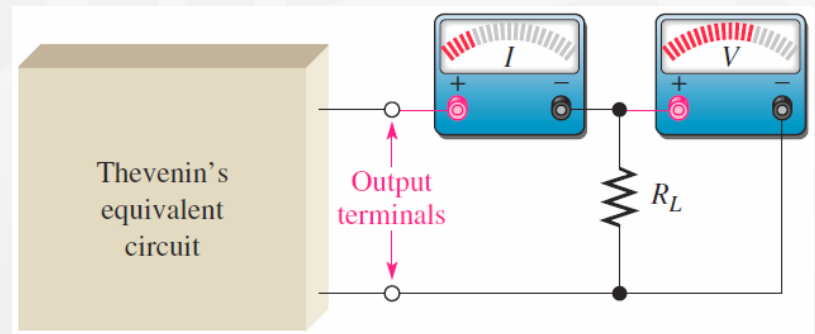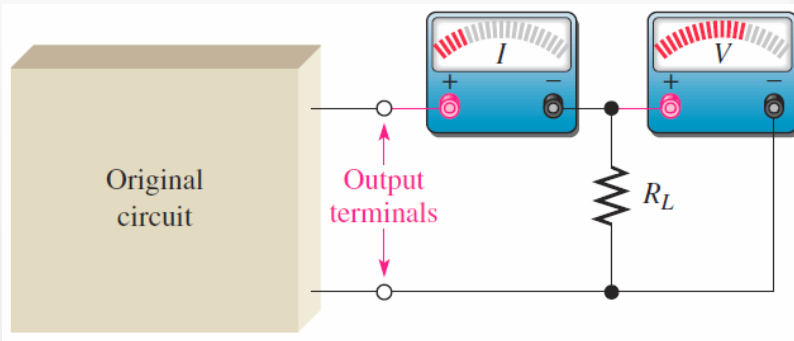- ▶ The Thevenin equivalent voltage V_{TH} is the open circuit (no-load) voltage between two specified output terminals in a circuit.
- ▶ The Thevenin equivalent resistance R_{TH} is the total resistance appearing between two specified output terminals in a circuit with all sources replaced by their internal resistances (which for an ideal voltage source is zero).




Three steps: #1

Circuit “complicate”

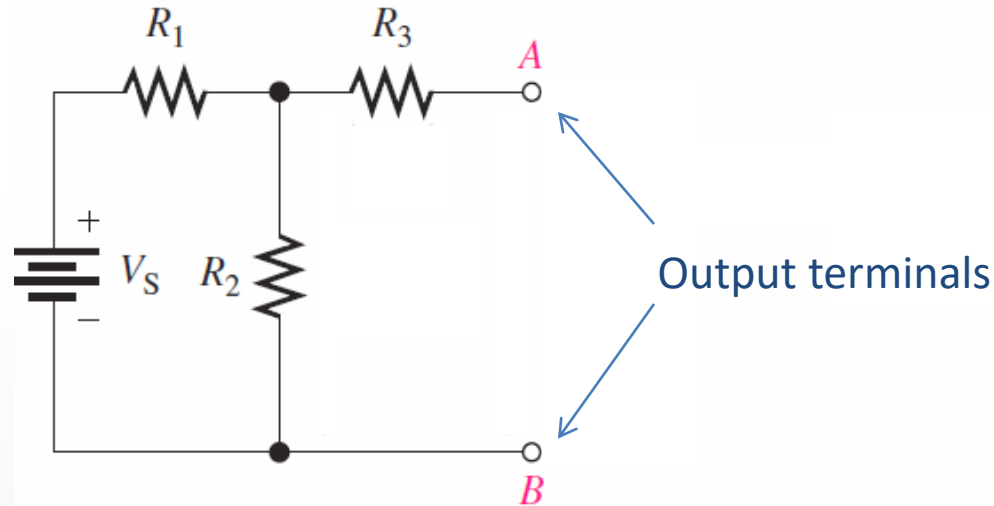


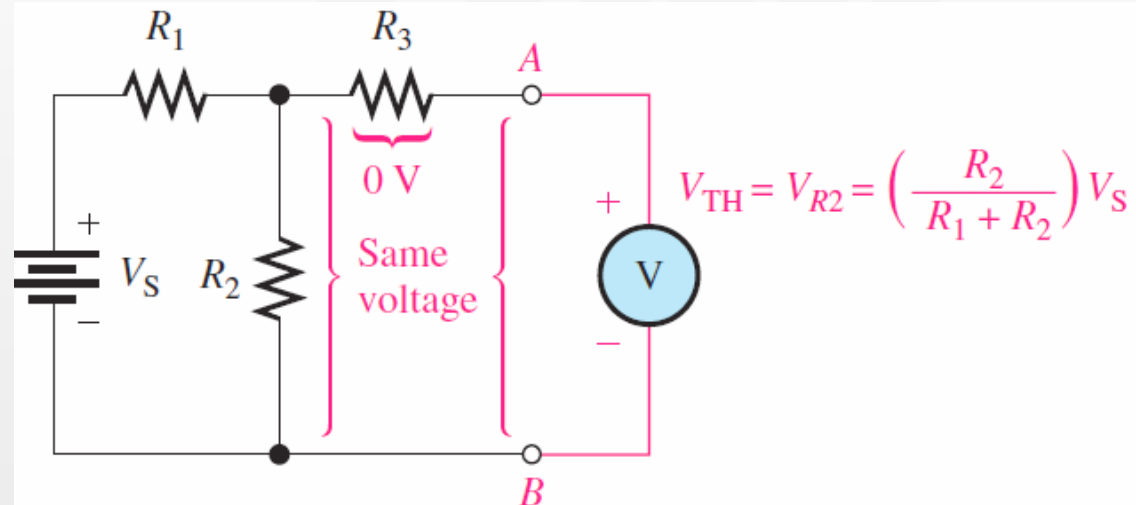- Step 1: Find V_{TH} = Find the voltage between A and B




Three steps: #2

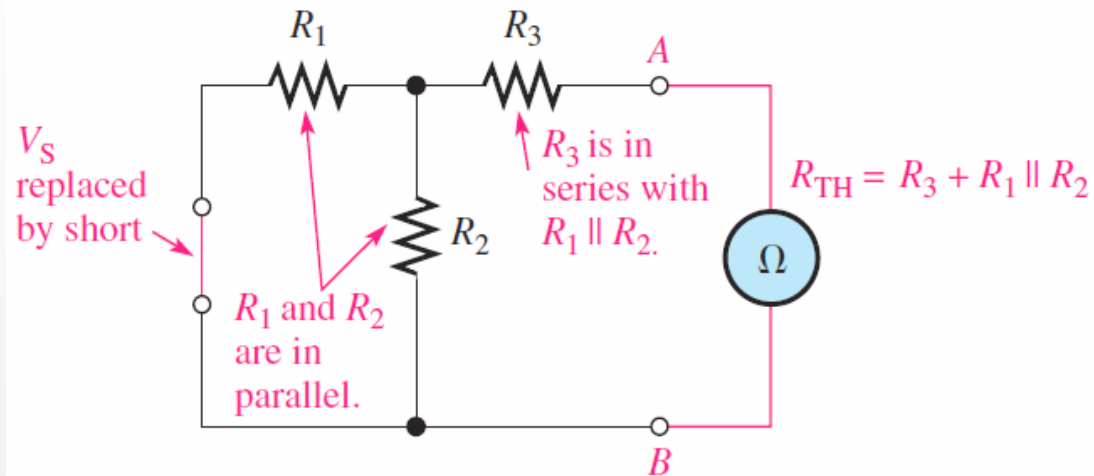- ▶ Step 2: Find R_{TH}
- ▶ Short-circuiting the battery
- ▶ Find the resistance between A and B




Three steps: #3


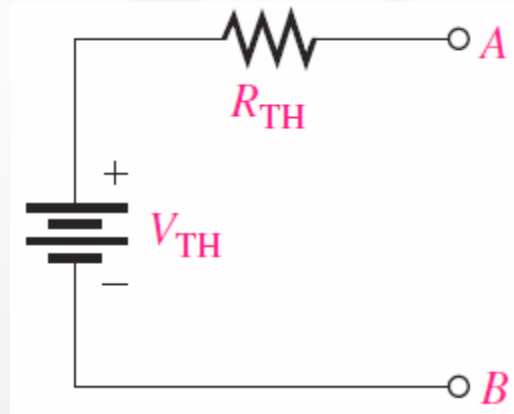
- ▶ Step 3: Combining both V_{TH} and R_{TH}
- ▶ Thevenin equivalent circuit




Depends on the viewpoint

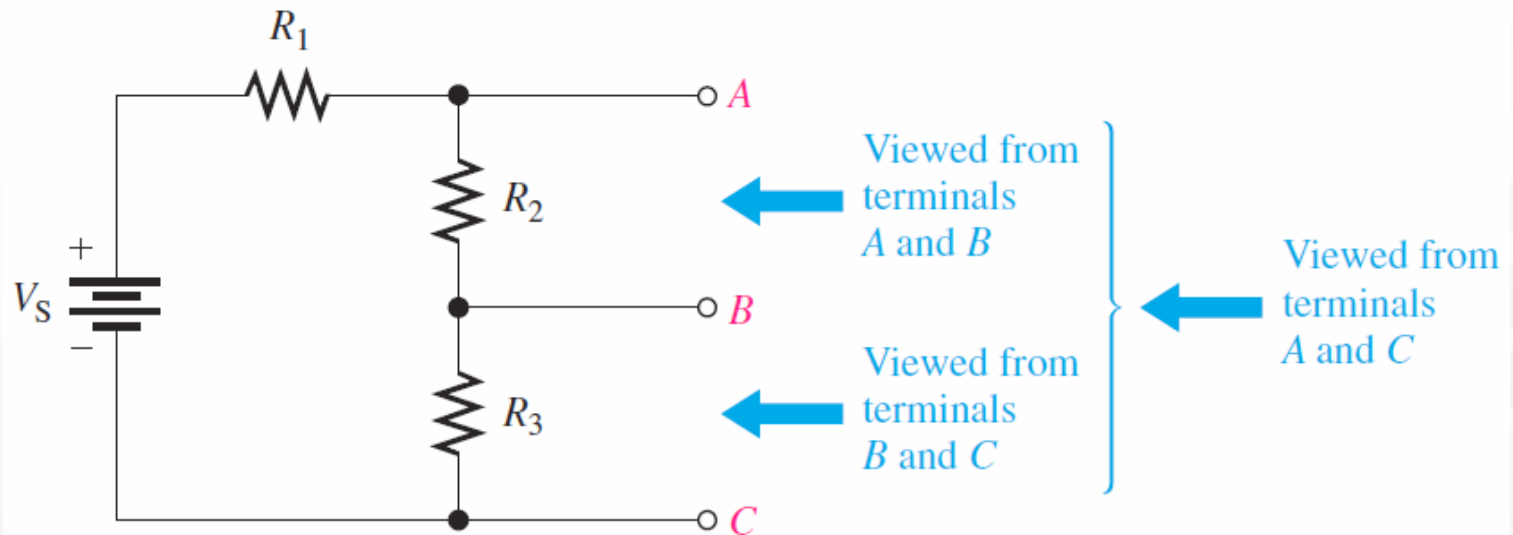



Depends on the viewpoint

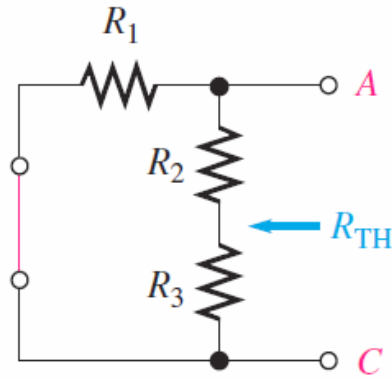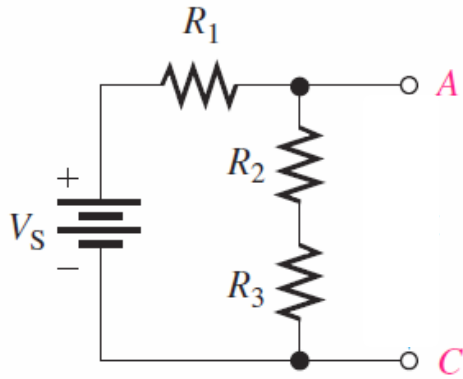

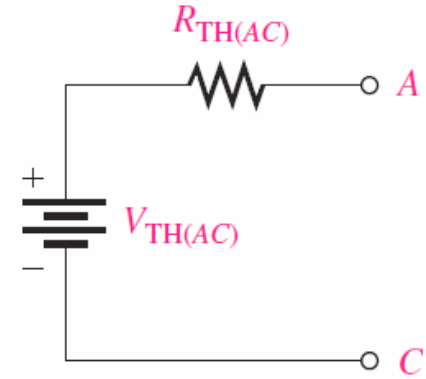
$$R_{TH(AC)} = R_1 \parallel (R_2 + R_3)$$



Thevenin equivalent

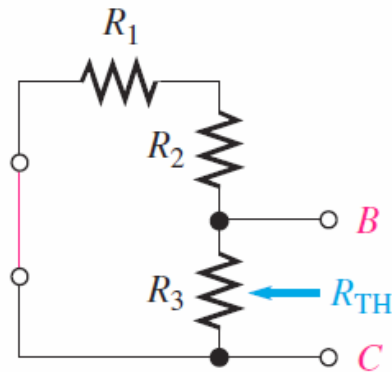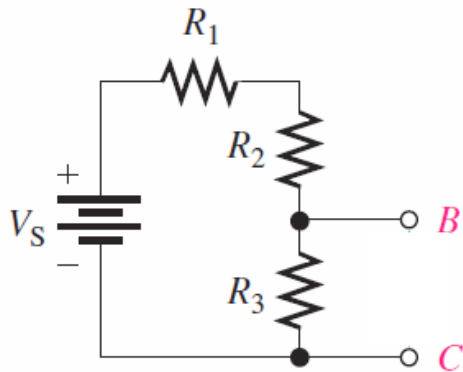


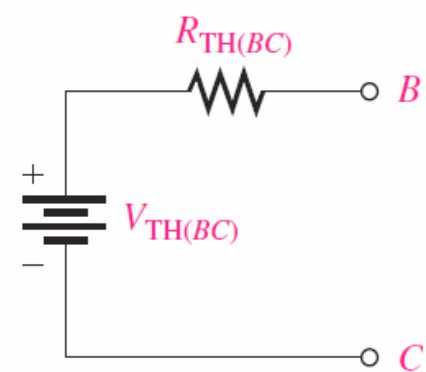
$$R_{TH(BC)} = R_3 \parallel (R_1 + R_2)$$



Thevenin equivalent

Thevenizing a Bridge Circuit

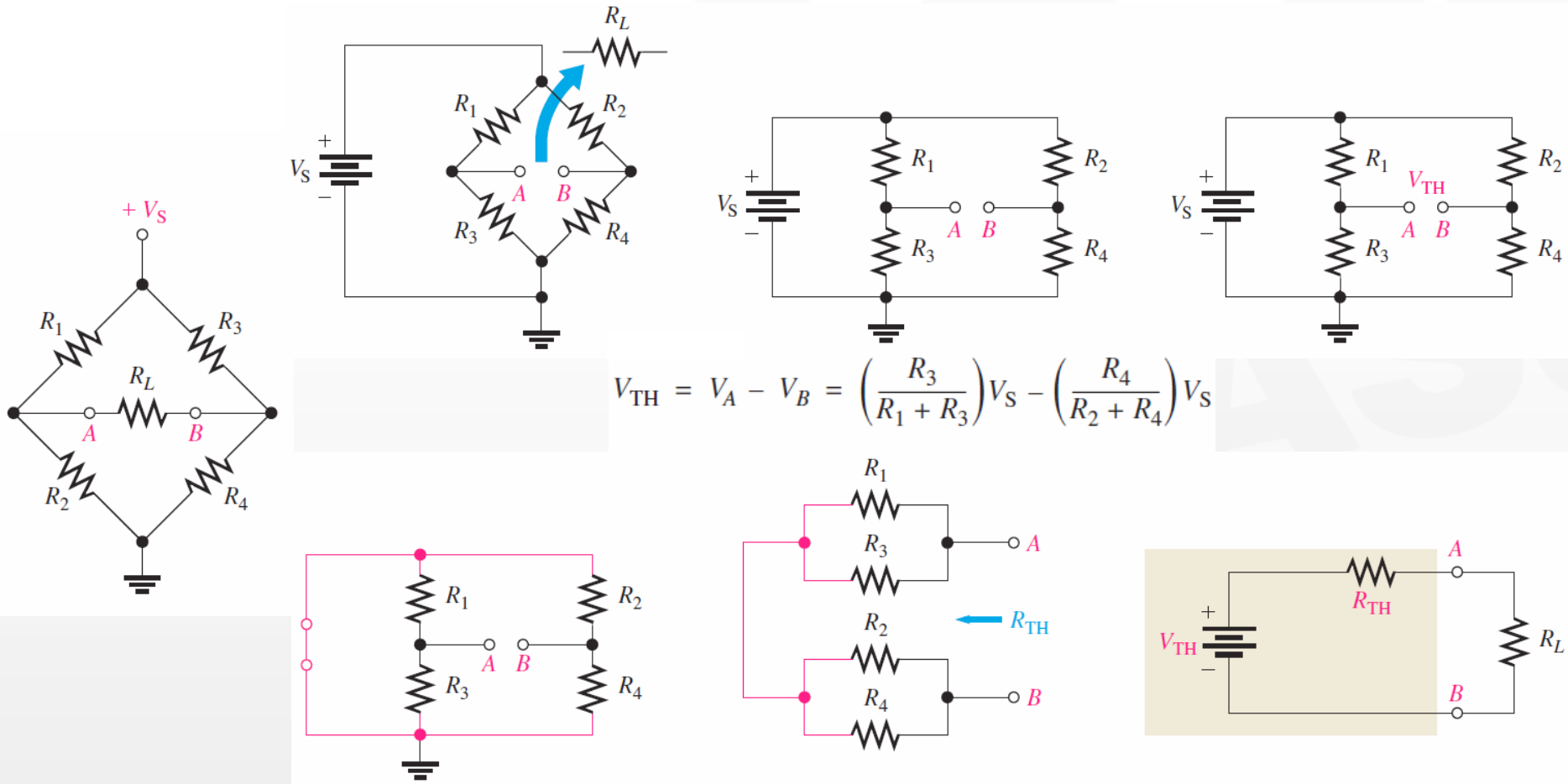


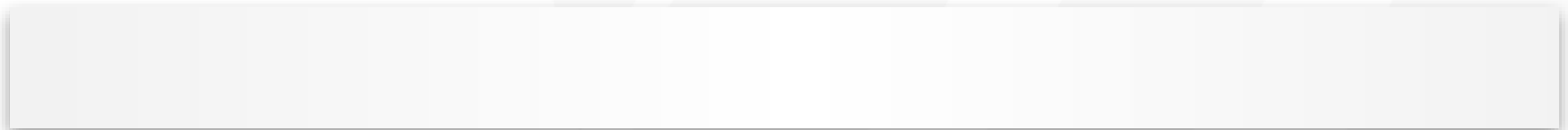


UMASS
LOWELL

Maximum Power Transfer Theorem

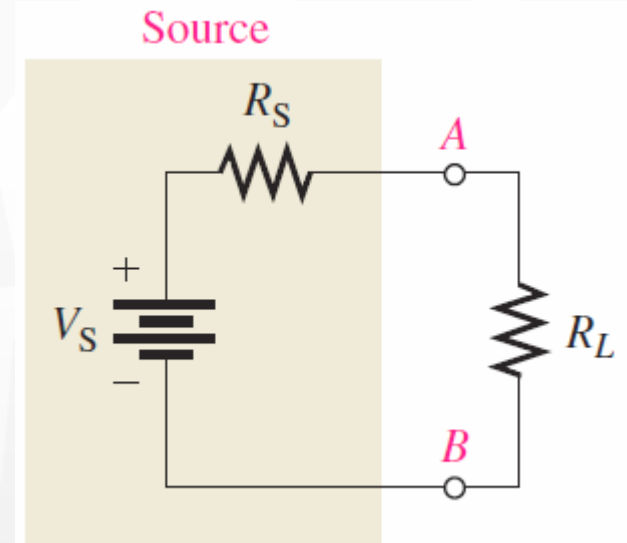- ▶ For a given source voltage, maximum power is transferred from a source to a load when the load resistance is equal to the internal source resistance.
- ▶ Maximum power is transferred to the load when $R_L = R_S$.




Maximum Power Transfer Theorem

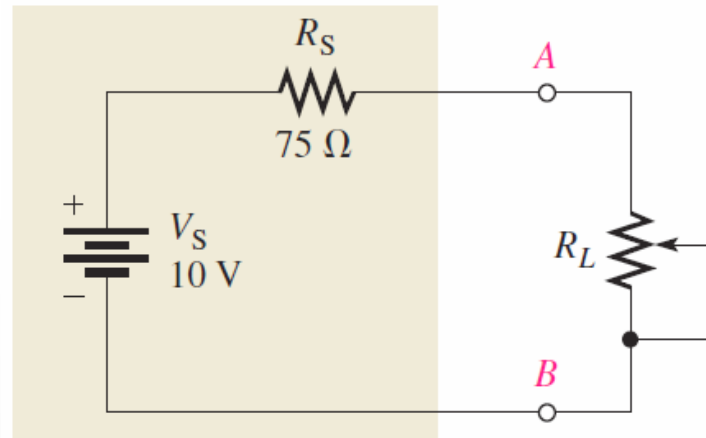

- ▶ Example: Determine the load power for different values of the variable load resistance $[0:125]\ \Omega$
- ▶ Solution: Using Ohm's law and Power Formula
- ▶ For $R_L = 0\ \Omega$

$$I = \frac{V_S}{R_S + R_L} = \frac{10}{75 + 0} = 133\text{ mA}$$
$$P_L = I^2 R_L = 133^2 * 0 = 0\text{ W}$$

Maximum Power Transfer Theorem

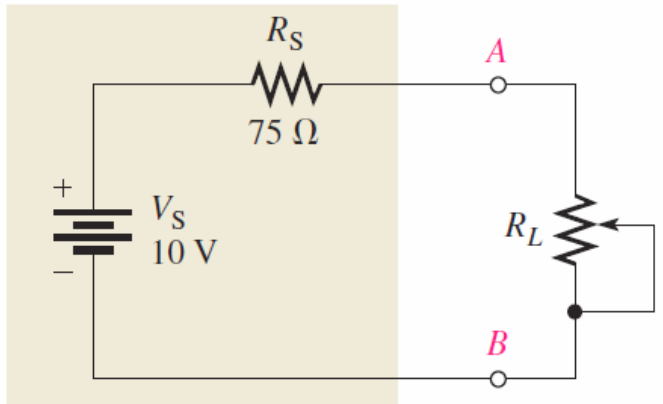

For $R_L = 0\ \Omega$: $P_L = 0\text{ W}$


For $R_L = 25\ \Omega$: $P_L = 250\text{ mW}$

For $R_L = 50\ \Omega$: $P_L = 320\text{ mW}$

For $R_L = 75\ \Omega$: $P_L = 334\text{ mW}$

For $R_L = 100\ \Omega$: $P_L = 326\text{ mW}$

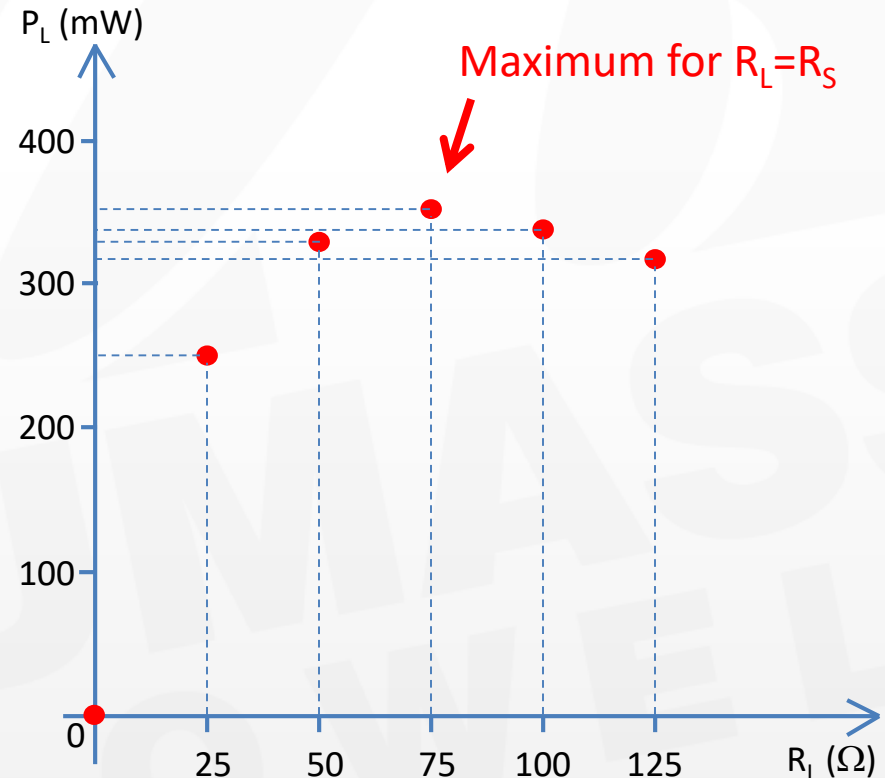
For $R_L = 125\ \Omega$: $P_L = 313\text{ mW}$




► Note that $R_S = R_{TH}$ if we are using the Thevenin's Theorem

Superposition Theorem

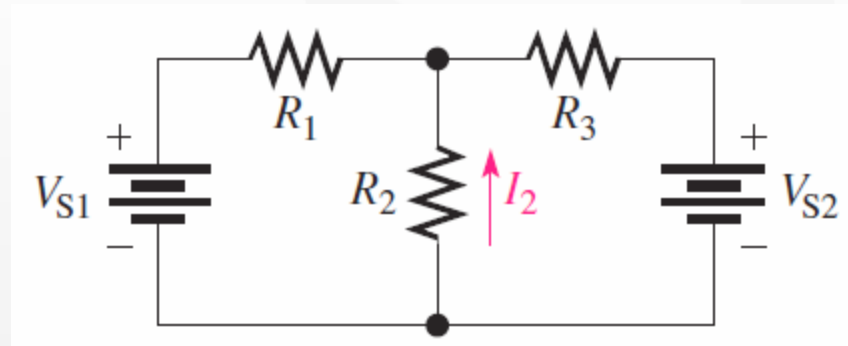
What is happening when there are two or more voltage sources ???
How do we calculate I_2 ???




Superposition Theorem

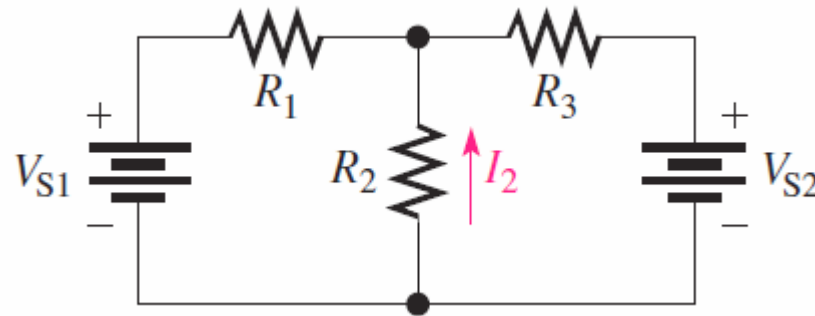

Problem: Find I_2

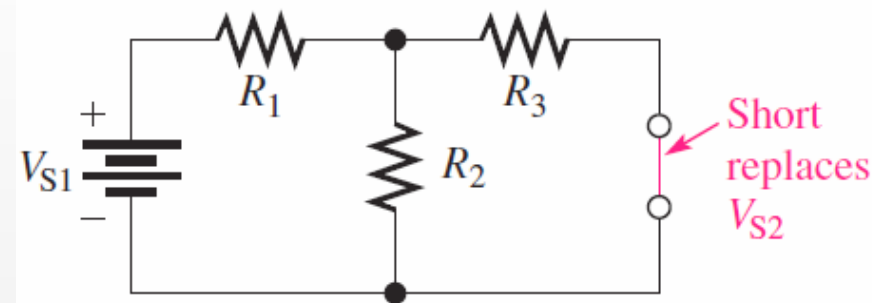

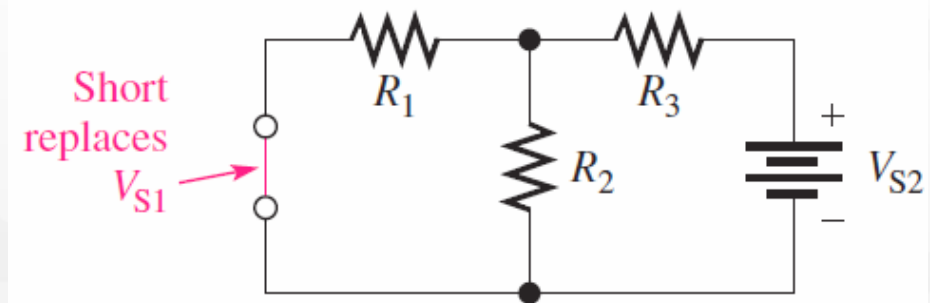Determine R_{T1} and I_{T1}
Then $I_{2(S1)}$




Determine R_{T2} and I_{T2}
Then $I_{2(S2)}$

$$I_2 = I_{2(S1)} + I_{2(S2)}$$

Superposition Theorem

Example

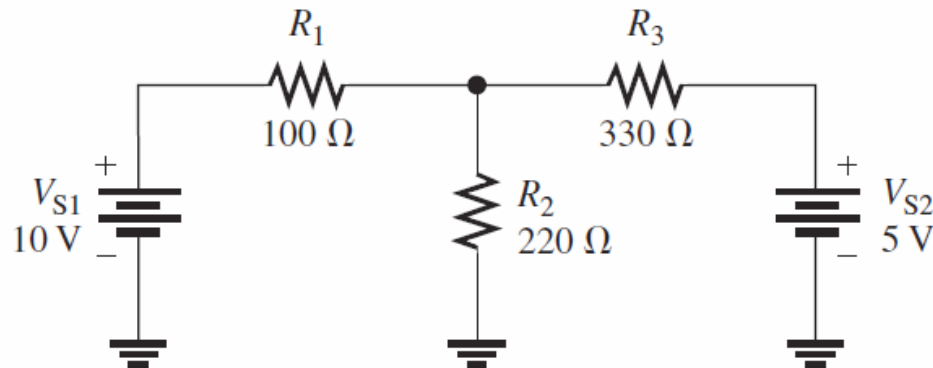

- Find I_2 , the current through R_2
- 1_ short replace V_{S2} , find R_{T1} , then I_{T1} and finally $I_{2(S1)}$
- $R_{T1} = 232\ \Omega$ // $I_{T1} = 43.1\ \text{mA}$ // $I_{2(S1)} = 25.9\ \text{mA}$
- 2_ short replace V_{S1} , find R_{T2} , then I_{T2} and finally $I_{2(S2)}$
- $R_{T2} = 399\ \Omega$ // $I_{T2} = 12.5\ \text{mA}$ // $I_{2(S2)} = 3.9\ \text{mA}$
- $I_2 = I_{2(S1)} + I_{2(S2)} = 25.9 + 3.9 = 29.8\ \text{mA}$