

17.368 Data Conversion and Lab
Lab 2
Fall 2013

Sample and Hold Amplifiers

Lab Report

See separate report form located on the course webpage. This form should be completed during the performance of this lab.

Objectives

- 1) To construct and operate a Sample and Hold circuit using the LF398
- 2) To measure DROOP RATE and GAIN ERROR
- 3) To construct and operate a 1 Bit A/D Converter

Materials

General Material

- | | | |
|--------------------------|---|----------------------------------------------------|
| <input type="checkbox"/> | 1 | Breadboard |
| <input type="checkbox"/> | 2 | Dual Power Supply (+15 V and -15 V) |
| <input type="checkbox"/> | 2 | Oscillator or Function Generator for signal source |
| <input type="checkbox"/> | 1 | Pulse Generator |
| <input type="checkbox"/> | 1 | Voltmeter |
| <input type="checkbox"/> | 1 | Oscilloscope |

Sample and Hold Circuit

- | | | | |
|--------------------------|---|-------------------------------|--------------------------|
| <input type="checkbox"/> | 1 | 741 Linear IC | |
| <input type="checkbox"/> | 1 | LF398 Sample and Hold circuit | |
| <input type="checkbox"/> | 1 | 10 pF Capacitor | (10) |
| <input type="checkbox"/> | 1 | 100 pF Capacitor | (101) |
| <input type="checkbox"/> | 1 | 0.001 μ F Capacitor | (102) |
| <input type="checkbox"/> | 1 | 0.01 μ F Capacitor | (103) |
| <input type="checkbox"/> | 1 | 0.1 μ F Capacitor | (104) |
| <input type="checkbox"/> | 1 | 1.0 μ F Capacitor | (105) |
| <input type="checkbox"/> | 3 | 10 k ohm Resistors | (Brown – Black – Orange) |
| <input type="checkbox"/> | 1 | 10 k ohm Potentiometers | |
- smallest

↓

largest

17.368 Data Conversion and Lab
Lab 2
Fall 2013

WARNINGS AND PRECAUTIONS

- 1) Never install or remove the components from an energized circuit
- 2) Do not construct circuits while energized
- 3) Follow electrical safety precautions

Background Information

The purpose of the Sample-and-Hold amplifier is to freeze an analog voltage of the instant the Hold command is issued and make that analog voltage available for an extended period of time allowing for A/D converter and other applications to utilize the stored voltage.

Pre-Lab Preparation

1. Download Lab # 1 from the course website. Read and understand the lab.
2. Download LF398 Data Sheet from the course Webpage

Procedure

Objective 1. SAMPLE AND HOLD

- a.** Assemble the circuit shown in Figure 1. Values are as follows:

$$\begin{aligned}V_+ &= 15 \text{ volts (Use dual power supply)} \\V_- &= -15 \text{ volts (Use dual power supply)} \\C_h &= 100 \text{ pF}\end{aligned}$$

- b.** Apply a 5 Vpp Sine wave of 10 Hz to the Analog input. Use the Oscillator or Function Generator for the signal source. NOTE: Analog input frequency can range from 10 Hz to 5 KHz. Record the actual value used.
- c.** Apply a 5 Vpp differentiated square wave of 2 KHz to the sample and holding time signal, by using a Pulse Generator.

17.368 Data Conversion and Lab
Lab 2
Fall 2013

- d.** Record the actual sample and holding time duty cycle (frequency). Make note of the output signal. Compare the input signal to that of the output.
- e.** Change the sample and holding time (duty cycle). Make note of the output signal changes as the duty cycle changes.
- f.** Repeat Step 1.d. with an Analog input frequency of 100 Hz.
- g.** Repeat Step 1.d. with an Analog input frequency of 1 KHz.

OBJECTIVE 2. DROOP RATE AND GAIN ERROR

- a.** Assemble the circuit shown in figure 1. Values are as follows:

$V_+ = 15$ volts (Use dual power supply)
 $V_- = -15$ volts (Use dual power supply)
 $C_h = 10$ pF

- b.** Let the analog input = 1 VDC from a DC power supply (be sure to disconnect the function generator).
- c.** Measure the output (V_o) with a DC voltmeter while the 5 Vpp 2 kHz differentiated square wave is clocking the LF398 IC.
- d.** Disconnect the clock input, and observe V_o on a DC voltmeter for 60 seconds. Record V_o at the end of 60 seconds.

17.368 Data Conversion and Lab
Lab 2
Fall 2013

- e. Calculate the droop rate in volts/sec.

TABLE 1					
DROOP RATE					
C _h (Hold Capacitor)		Voltage Start	Voltage Comp		Droop Rate (Calculated)
10 pF					
100 pF					
0.001 μF					
0.01 μF					
0.1 μF					
1.0 μF					

- f. Repeat Steps 2.b. through Step 2.e. by replacing C_h with the different values for the hold capacitor as indicated in TABLE 1. Record the output droop rate for each capacitor used.
- g. Using the same circuit, Figure 1, with C_h= 0.001μF, observe the output transient at start of sample mode. (Sample rate: 8kHz)
- h. Test for Gain Error (input vs output). Compare with data sheet values. Gain error is calculated as follows:

$$GAINERROR = \frac{V_{OUT} - V_{IN}}{V_{IN}} * 100\%$$

17.368 Data Conversion and Lab
Lab 2
Fall 2013

OBJECTIVE 3. 1 BIT A/D CONVERTER

a. Assemble the circuit shown in Figure 2. Values are as follows:

$V_+ =$ 15 volts (Use dual power supply)
 $V_- =$ -15 volts (Use dual power supply)
 $C_h =$ 100 pF

b. Apply a 5 Vpp Sine wave of 1 KHz to the Analog input. Apply a 5 Vpp differentiated square wave of 2 KHz to the sample and holding time signal, by using a Pulse Generator. Set the comparator to 70% of the sampled signal. Output will be high (digital 1) when input signal reaches the reference voltage on the 741 output.

SUMMARY:

This lab provided an introduction to the Sample-and-Hold amplifier. The Sample-and-Hold amplifier freezes an analog voltage at the instant the Hold command is issued and makes that analog voltage available for an extended period of time allowing for A/D converter and other applications to utilize the voltage.

Lab Notebook Requirements:

1. Ensure that you have recorded all the data requested during the lab in your lab notebook as well as your lab report.

Lab Report:

1. Use template provided on the Class Web Site.

Lab Questions:

1. None

17.368 Data Conversion and Lab
Lab 2
Fall 2013

Figure 1 – Sample and Hold Circuit

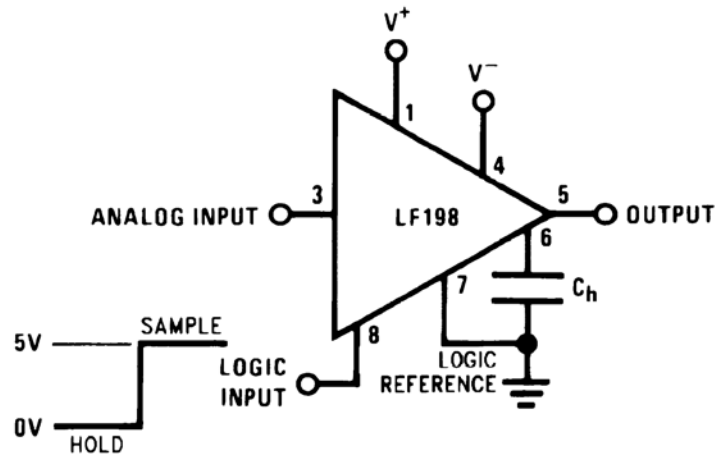


Figure 2 – One (1) Bit A/D Converter

